

4:16 de multiplexer using eSim

THEORY: A de multiplexer (or de mux) is a device that takes a single input line and routes it to one of several digital output lines. A de multiplexer of 2^n outputs has n select lines, which are used to select which output line to send the input. A de multiplexer is also called a data distributor.

De multiplexers can be used to implement general purpose logic. By setting the input to true, the de mux behaves as a decoder.

The reverse of the digital de multiplexer is the digital multiplexer

TRUTH TABLE:

INPUTS				OUTPUTS															
A	B	C	D	X ₀	X ₁	X ₂	X ₃	X ₄	X ₅	X ₆	X ₇	X ₈	X ₉	X ₁₀	X ₁₁	X ₁₂	X ₁₃	X ₁₄	X ₁₅
0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
0	1	0	1	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0
0	1	1	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0
1	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0
1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1

CALCULATION:

Eg: v₀(S₀)=5 v₁(S₁)=5 v₂(S₂)=0 v₃(S₃)=5

5055->1011->11(decimal)

q₀=0, q₁=0, q₂=0, q₃=0, q₄=0, q₅=0, q₆=0, q₇=0, q₈=0, q₉=0, q₁₀=0, q₁₁=5, q₁₂=0, q₁₃=0, q₁₄=0, q₁₅=0

SCHEMATIC DIAGRAM

 


Fig 1: 1 to 16 de multiplexer circuit diagram

 


Fig 2: 1 to 4 de multiplexer circuit diagram(Subcircuit)

 


Fig3:1 to 2 deultiplexer circuit diagram(Subcircuit)

NgSpice Plots:

 


Fig1:q15 output plot

Fig2:q14 output plot


 
 
 
 
 
 


Fig3:q13 output plot

Fig4:q12 output plot

 

 


Fig11:q5 output plot

 


Fig12:q4 output plot

 


Fig13:q3 output plot

 


Fig14:q2 output plot

 


Fig15:q1 output plot

 


Fig16:q0 output plot

PYTHON PLOTS:

 


Fig:q11 output plot

 


Fig:All other ooutput plots

References:

<https://linus5.blogspot.in/2016/02/decoders.html>

https://www.tutorialspoint.com/digital_circuits/digital_circuits_demultiplexers.htm