

# Title Of The Experiment: PULSE WIDTH MODULATOR

## THEORY:

Pulse Width Modulation (PWM) is a digital signal which is most commonly used in control circuitry. This signal is set high (5v) and low (0v) in a predefined time and speed. The time during which the signal stays high is called the “on time” and the time during which the signal stays low is called the “off-time”. There are two important parameters for a PWM as discussed below:

The percentage of time in which the PWM signal remains HIGH (on time) is called a duty cycle. If the signal is always ON it is in 100% duty cycle and if it is always of it is 0% duty cycle.

$$\text{Duty Cycle} = \frac{\text{Turn ON time}}{\text{Turn ON time} + \text{Turn OFF time}}$$

The frequency of a PWM signal determines how fast a PWM completes one period. One Period is complete ON and OFF of a PWM signal as shown in the above figure. In our tutorial, we will set a frequency of 5KHz.

We can notice if LED being OFF for half second and LED being ON for another half-second. But if Frequency of ON and OFF times increased from ‘1 per second’ to ‘50 per second’. The human eye cannot capture this frequency. For a normal eye, the LED will be seen, as glowing with half of the brightness. So with the further reduction of ON time, the LED appears much lighter.

## CIRCUIT DIAGRAM:

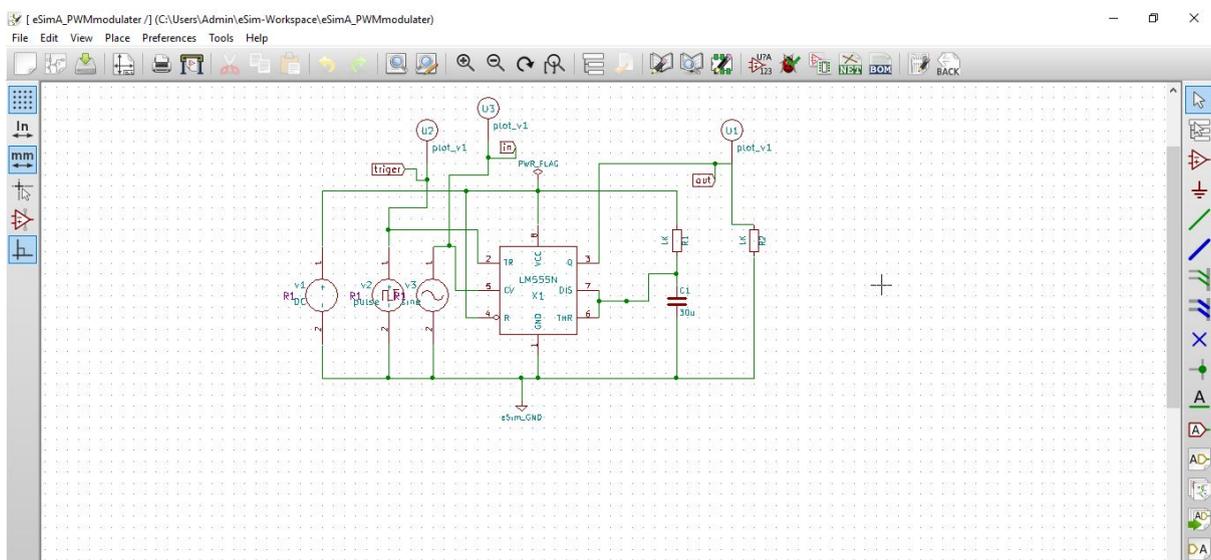


Fig1: Schematic Of Pulse Width Modulator Using IC555

# SIMULATION RESULTS: Ngspice Plots:

## 1.) Input Waveform:

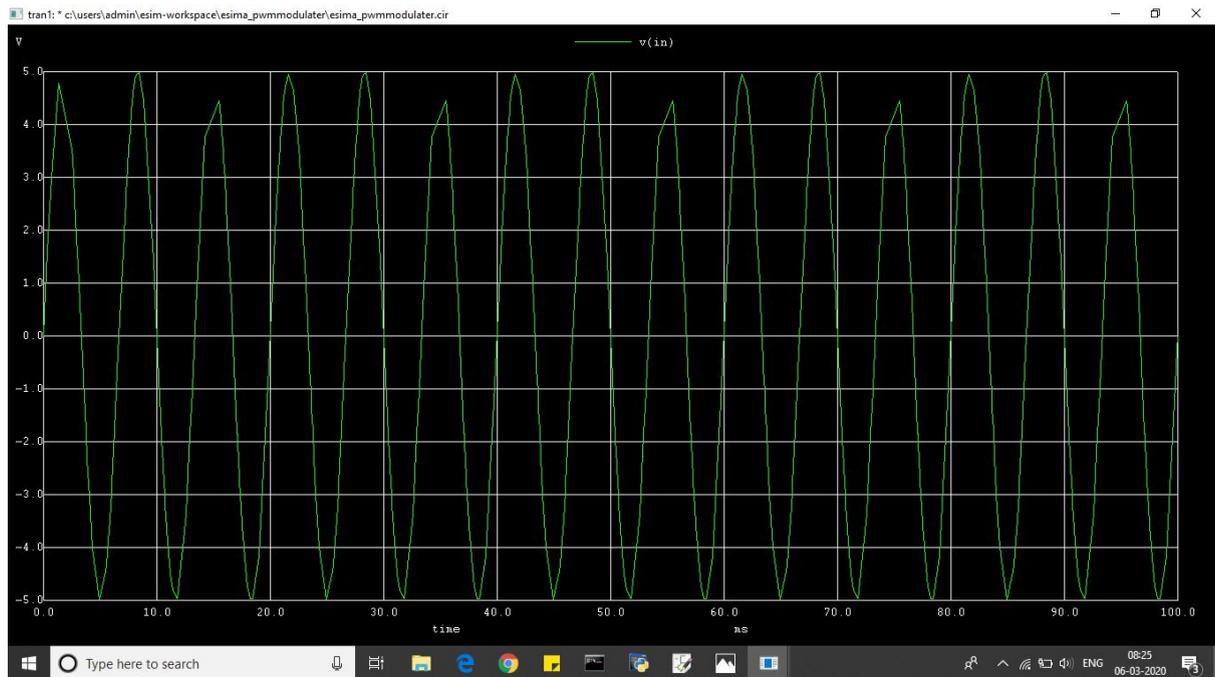


Fig2: Input Sine wave to Pulse Width Modulator

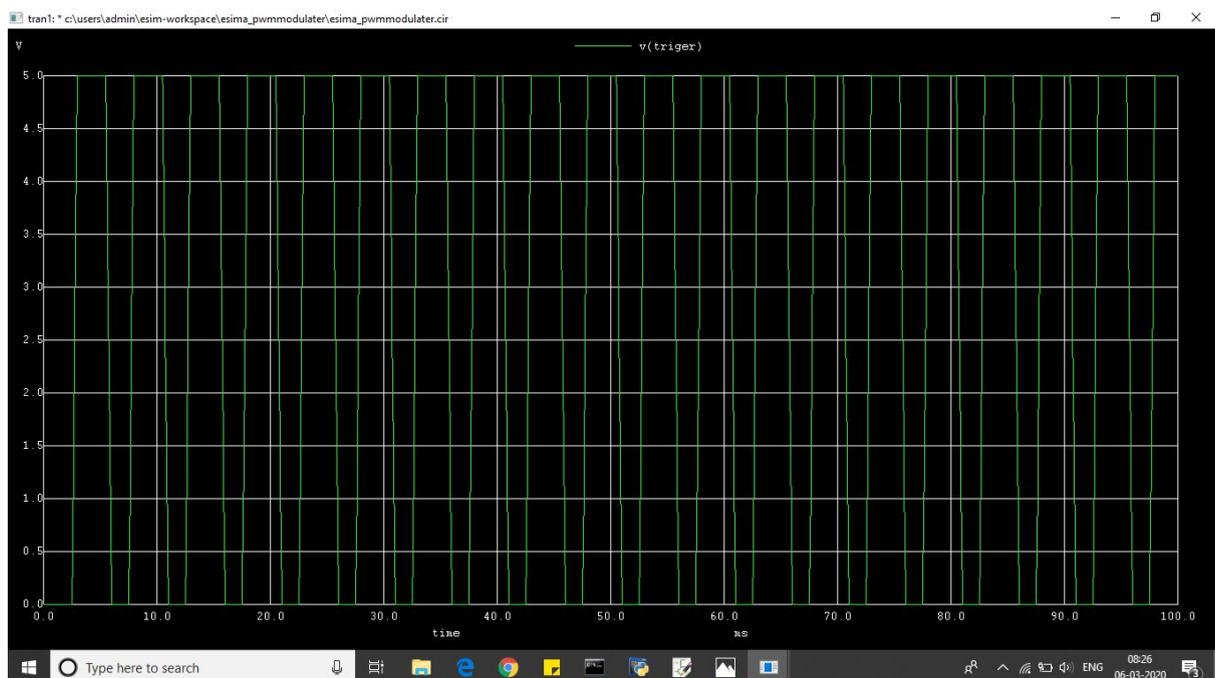


Fig3: Trigger Pulse to Pulse Width Modulator

## 2.) Output Waveform:

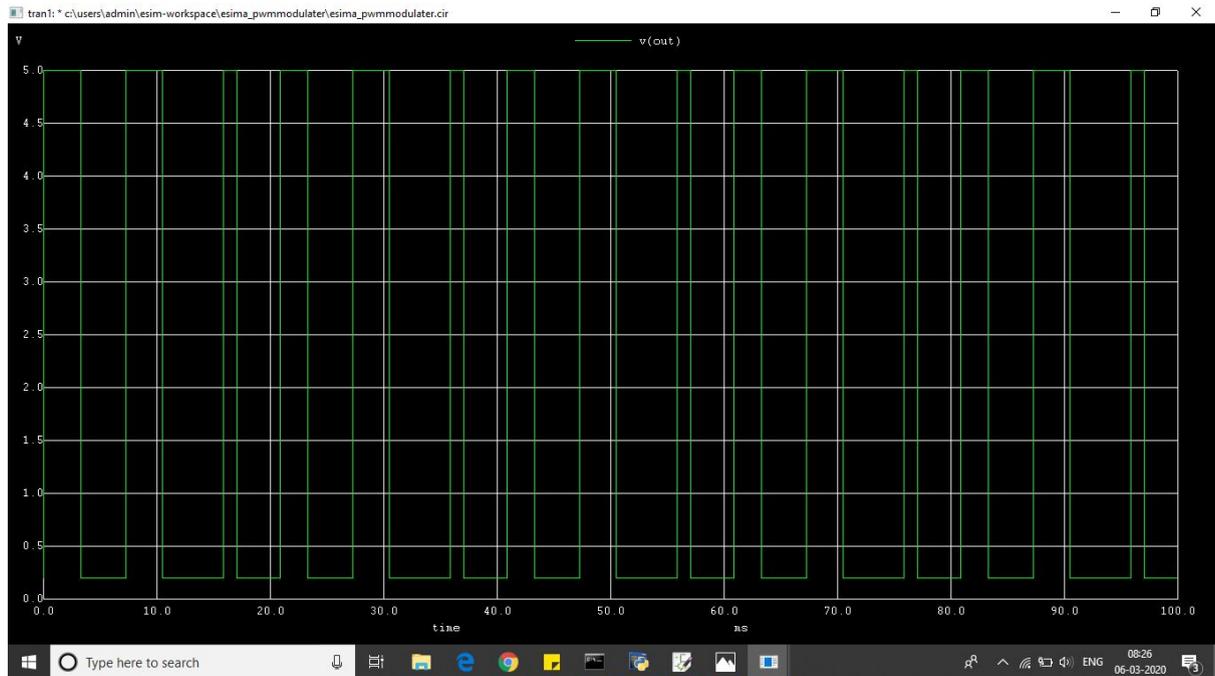


Fig4: Output from Pulse Width Modulator

## Python Plots:

### 1.) Input Waveform

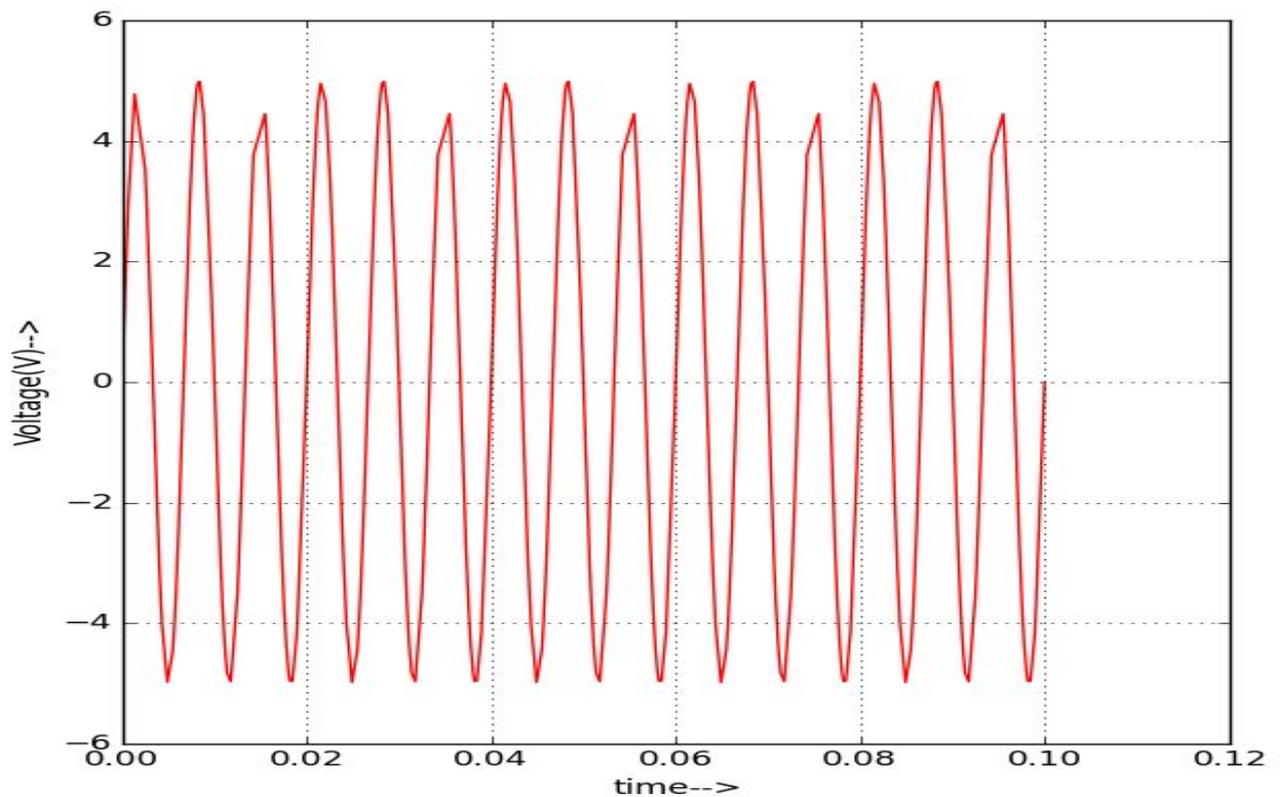


Fig5: Input Sine wave to Pulse Width Modulator

## 2.)Output Waveform

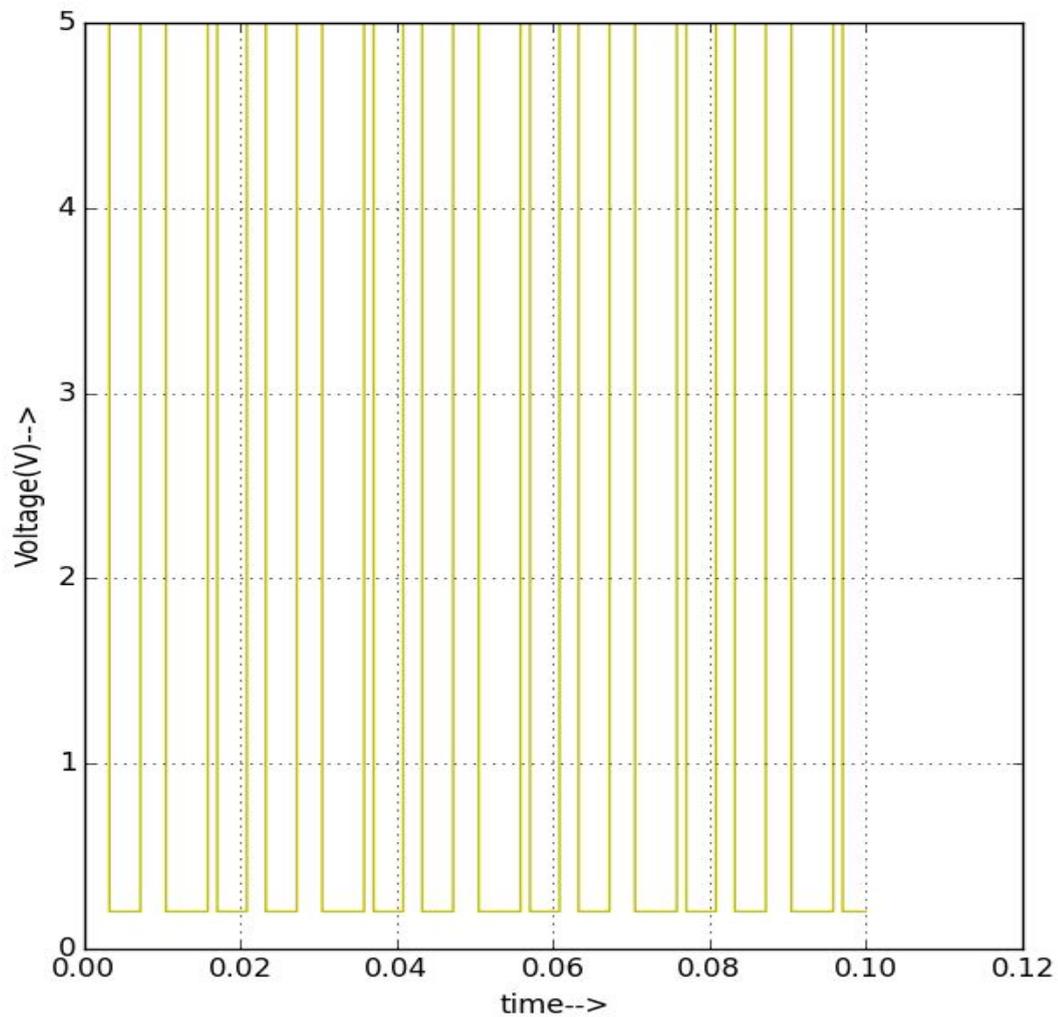


Fig6: Output from Pulse Width Modulator

## CONCLUSION:

Pulse Width Modulator is being studied and simulated in eSim by obtaining Ngspice and Python plots successfully.

## REFERENCES:

<https://www.elprocus.com/fsk-modulation-demodulation-circuit-diagram/>.

