

EXPERIMENT NO. - 9

Aim of the Experiment:


Design, assemble and testing of half adder

Theory:


The half adder adds two single binary digits A and B . It has two outputs, sum (S) and carry (C). The carry signal represents an overflow into the next digit of a multi-digit addition. The simplest half-adder design, pictured on the right, incorporates an [XOR gate](#) for S and an [AND gate](#) for C . With the addition of an OR gate to combine their carry outputs, two half adders can be combined to make a full adder.

The half adder adds two input bits and generates a carry and sum, which are the two outputs of a half adder. The input variables of a half adder are called the augends and addend bits. The output variables are the sum and carry. The truth table for the half adder is:

Inputs		Outputs	
A	B	C	S
0	0	0	0
1	0	0	1
0	1	0	1
1	1	1	0

 


Schematic Circuit:

 


Input Waveform:

a:

 


b:

 


Output Waveform:

Sum(S):

 

Carry(C):

 

Conclusion:

Date:

Signature of the Student

NAME:

ROLL NO.:

GROUP ID:

SUB GROUP NO.:

Experiment Mark: / 20

Instructor's Signature