

Chapter 3

RC FILTERS

AIM

To design and implement circuits for passive RC highpass and lowpass filters.

DESIGN AND CIRCUIT DIAGRAM

Inorder to plot the frequency response of RC highpass and lowpass filters use an AC source whose frequency can be varied during simulation. The AC source of voltage. It is connected across a series connection of resistor and capacitor. The corresponding circuits for RC highpass filter and lowpass filters are shown in figures 3.1 and 3.2 respectively. The cutoff frequency of the filter will be given by

$$f_c = \frac{1}{2\pi RC} \quad (3.1)$$

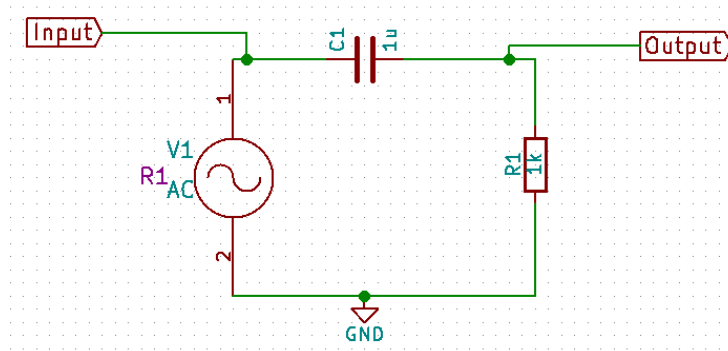


Figure 3.1: Schematic diagram for passive RC high pass filter

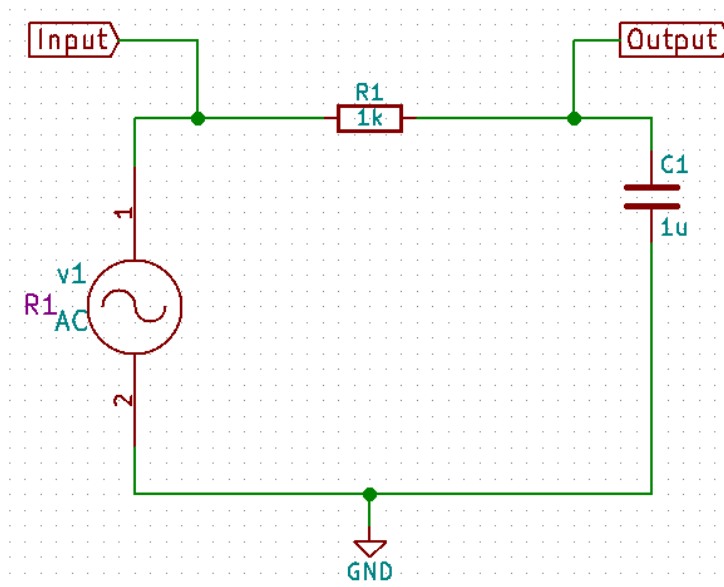


Figure 3.2: Schematic diagram for passive RC low pass filter

PROCEDURE

The steps to plot the characteristics of RC high pass filter are explained below. Follow the same procedure to obtain the response of RC lowpass filter. Note that these are two separate projects.

Launch eSim

Launching eSim will take you to the dialog box which asks for the default workspace. Browse the folders and set the wokspace location. It will finally end up in the eSim window.

Create a New Project

The new project is created by clicking the New icon on the menubar. The name of the project is given in the pop up window as RC_HPF for highpass filter.

Create the Schematic

To create the schematic, click the very first icon of the left toolbar. This will open KiCad Eeschema.

To create a schematic in KiCad, we need to place the required components. After all the required components of the simple RC circuit are placed, wiring

is done using the Place Wire option. The ‘Place Wire’ and ‘Place Component’ tools are available in the left toolbar. Scroll up and down for zooming in and out.

Placing the Components: Normally all the components available in eSim can be chosen by left mouse click in the grid. The components are listed in different libraries.

- Choose AC source from eSim_Sources
- Choose R from eSim_Devices
- Choose C from eSim_Devices
- Choose GND from power

Select the resistor and edit its component value to 1k as shown in Figure 3.3. Also edit the value of capacitor as 1 μ F. You can just type in 1u.

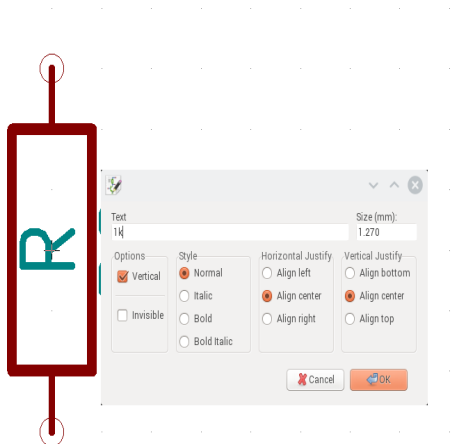


Figure 3.3: Editing the value field of component R

Wire the components to get the circuit. A global label ‘Input’ and ‘Output’ has been added to identify that node whose voltage will be later recorded and plotted. Global label is added from the right toolbar of Eeschema.

Annotating the circuit: Once the schematic diagram is completed, annotate it so that the ‘question marks’ associated with the components are converted to meaningful numbers automatically. For that choose annotate button from the top toolbar. See Figure 3.4 and in the subsequent dialogue boxes appearing click ok and finally close. See Figure 3.5. Now we have the circuit diagram as shown in Figure 3.1.

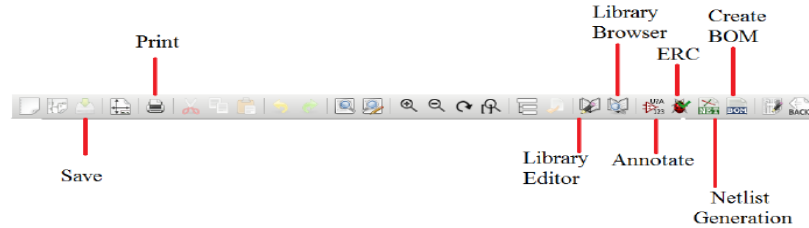


Figure 3.4: Choose annotate from the top tool bar

Note: If some libraries are found missing, you can add them from the ‘Preferences’ menu by following the procedure:

1. Choose ‘Component Libraries’ from Preferences menu.
2. Click on the Add button on the top right side of the window.
3. Choose the required libraries from ‘user/share/kicad/library’ and click OK button

Create Netlist

To simulate the circuit that has been created in the previous section, we need to generate its netlist. Netlist is a list of components in the schematic along with their connection information. To do so, click on the Generate netlist tool from the top toolbar. Click on spice from the window that opens up. Check the option Default Format. Then click on Generate. Save the netlist. This will be a .cir file. Do not change the directory while saving. See Figure 3.6. Now the netlist is ready to be simulated.

KiCad to Ngspice conversion

To convert KiCad netlist of RC circuit to NgSpice compatible netlist click on KiCad to Ngspice icon as shown in Figure 3.7. Now you can choose the type of analysis, source details, device models ngspice models and subcircuit models.

Analysis: Choose AC analysis type and choose Dec scale. Dec scale allows plotting as in a semilog graph sheet. Give the values of AC variables as shown in Figure 3.8. Enter the name of your AC source as on the circuit (here v1) and let its frequency be varied from 1Hz to 10kHz with 10 points chosen in each decade interval of frequency.

Source Details: Set amplitude as 5 and phase shift as 0.

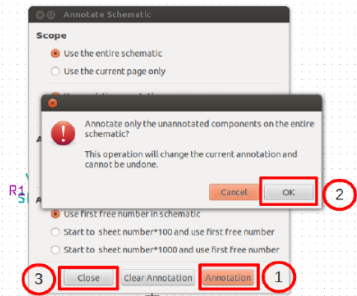


Figure 3.5: Annotation

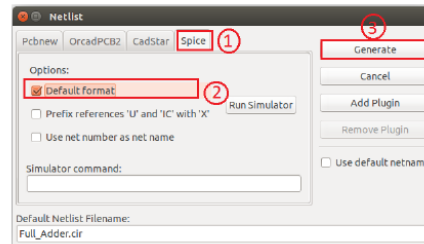


Figure 3.6: Netlist Generation

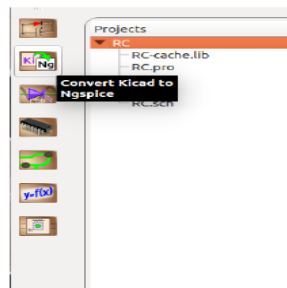


Figure 3.7: Choose Kicad to Ngspice tool

Ngspice Model: No Ngspice model to be given.

Device Model: No Device model to be given.

Subcircuits: No subcircuits to be given.

Once these details are provided click on convert button. Now you are ready to see the simulation results.

Simulate

To run Ngspice simulation click the simulation icon in the left tool bar. It will open up two windows - ngspice plotting window and python plotting window. Inorder to plot the frequency response characteristics let us use the commands in ngspice plotting window.

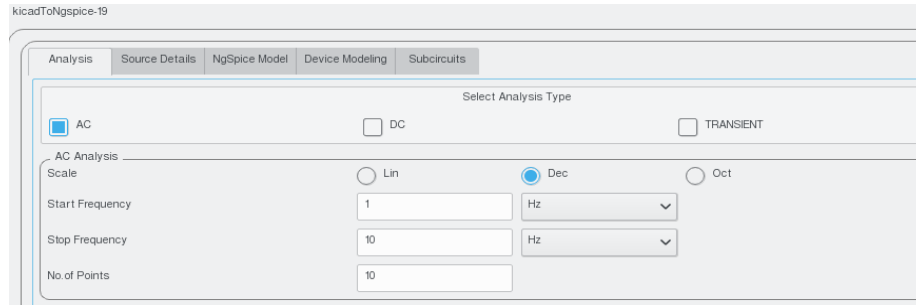


Figure 3.8: Choose AC analysis type and enter the values

We need to plot two graphs.

1. Input voltage value for different frequencies.
2. Output voltage value for different frequencies.

To plot these, let us use the command:

```
plot v(Input), v(Output)
```

This would plot the frequency response characteristics of input and output of the RC high pass filter. The resultant characteristics is shown in the Figure 3.9. The red indicates the Input and the blue indicates the output. The characteristics of RC low pass filter would be as shown in Figure 3.10.

RESULT

The circuit for plotting the frequency response of filter was implemented and simulated.

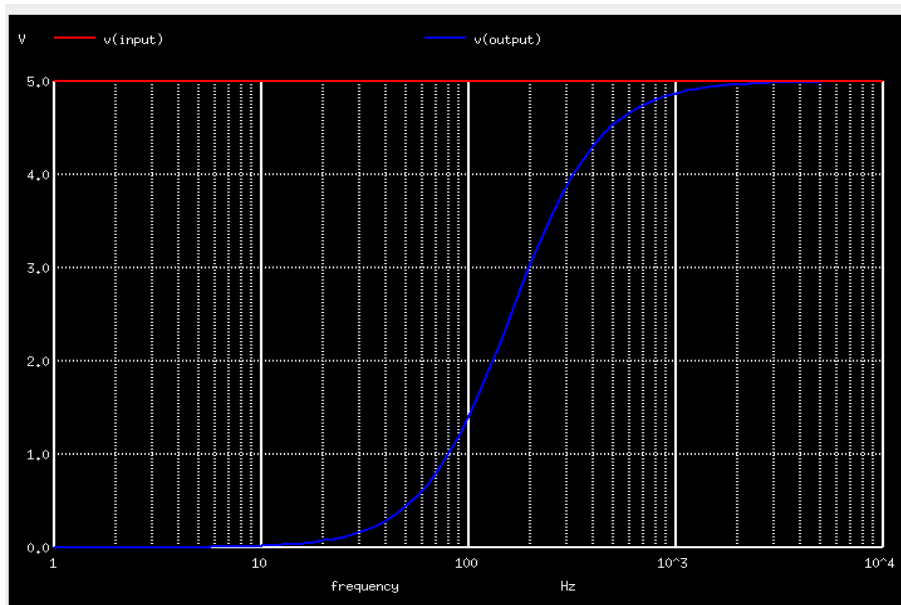


Figure 3.9: The frequency response of RC highpass filter

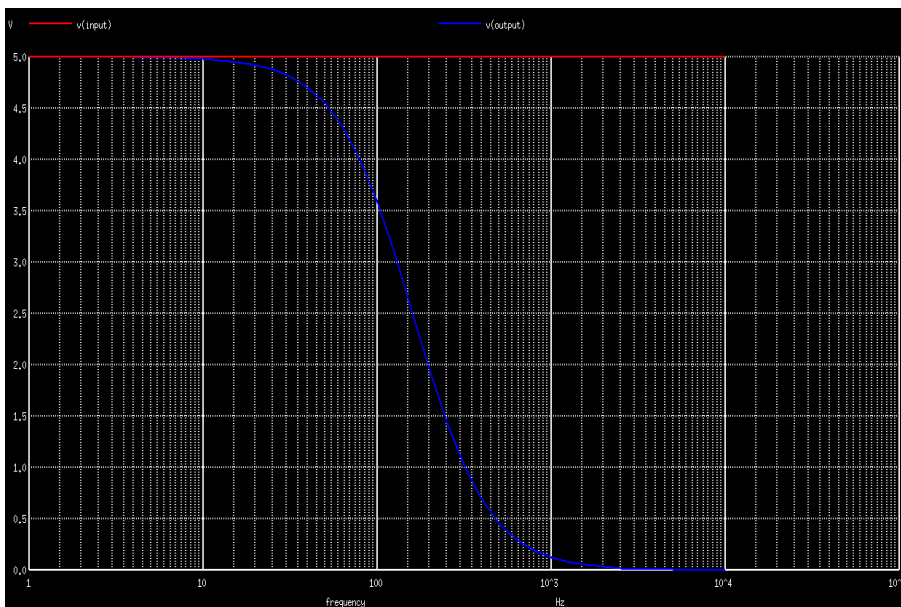


Figure 3.10: The frequency response of RC low pass filter