


## EXPERIMENT-4

---

### IMPEDENCE (Z) -PARAMETER

**PROBLEM STATEMENT:** To study the Z-parameters

**THEORY:**

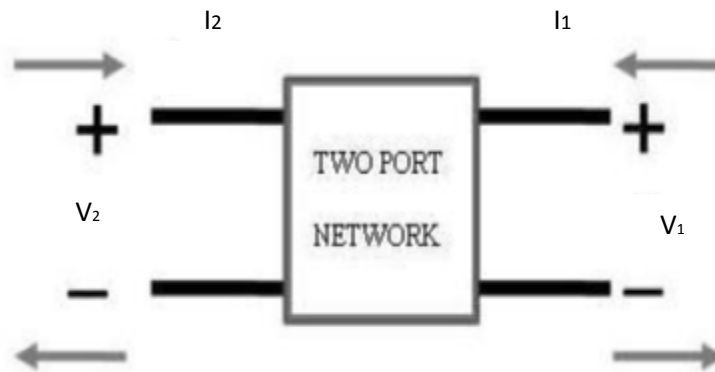

If a network has two pairs of terminals, one pair for connections to a source and one pair for connections to a load, the network is known as a two port network.

In many practical situations, we may not be interested in the internal structure of the network but we are satisfied with its behavior at the given set of terminals

A pair of terminals at which a signal may enter or leave a network is called a port.

If we choose  $I_1$  and  $I_2$  as independent variables and  $V_1$  and  $V_2$  as dependent variables. Then the network can be characterized by following sets of equations.

$$V_1 = Z_{11} * I_1 + Z_{12} * I_2$$

$$V_2 = Z_{21} * I_1 + Z_{22} * I_2$$

Observe that if either  $I_1=0$  or  $I_2=0$  the four parameters may be defined in terms of ratio of a voltage and current.

$$Z_{11} = V_1 / I_1 \text{ when } I_2 = 0$$

$$Z_{12} = V_1 / I_2 \text{ when } I_1 = 0$$

$$Z_{21} = V_2 / I_1 \text{ when } I_2 = 0$$

$$Z_{22} = V_2 / I_2 \text{ when } I_1 = 0$$


In this experiment the focus is on finding the Z- parameters. The individual Z-parameters are added to determine the overall Z- parameters for any number of networks connected in series- series connection.

Two port networks are useful as they form the building block of commonly used electrical systems like filters, attenuators, transmission lines which are inserted between a source and a load. It is easier to design a simple block and then interconnecting them than to design a single complex network.

## SCHEMATIC DIAGRAM:


**For  $I_1=0$**

Refer to "parameters" FOLDER

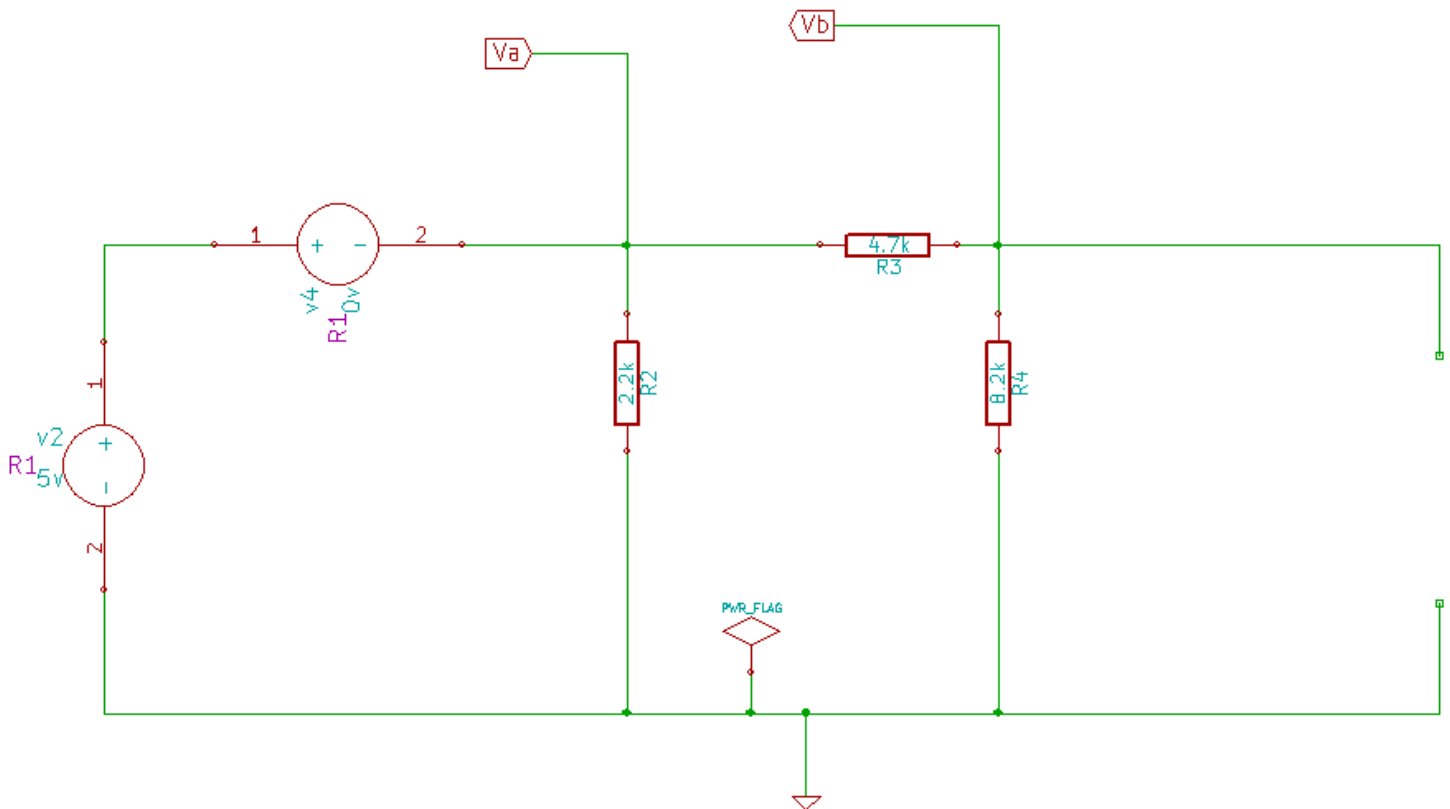


SIMULATION OUTPUT:

Value of  $I_2$

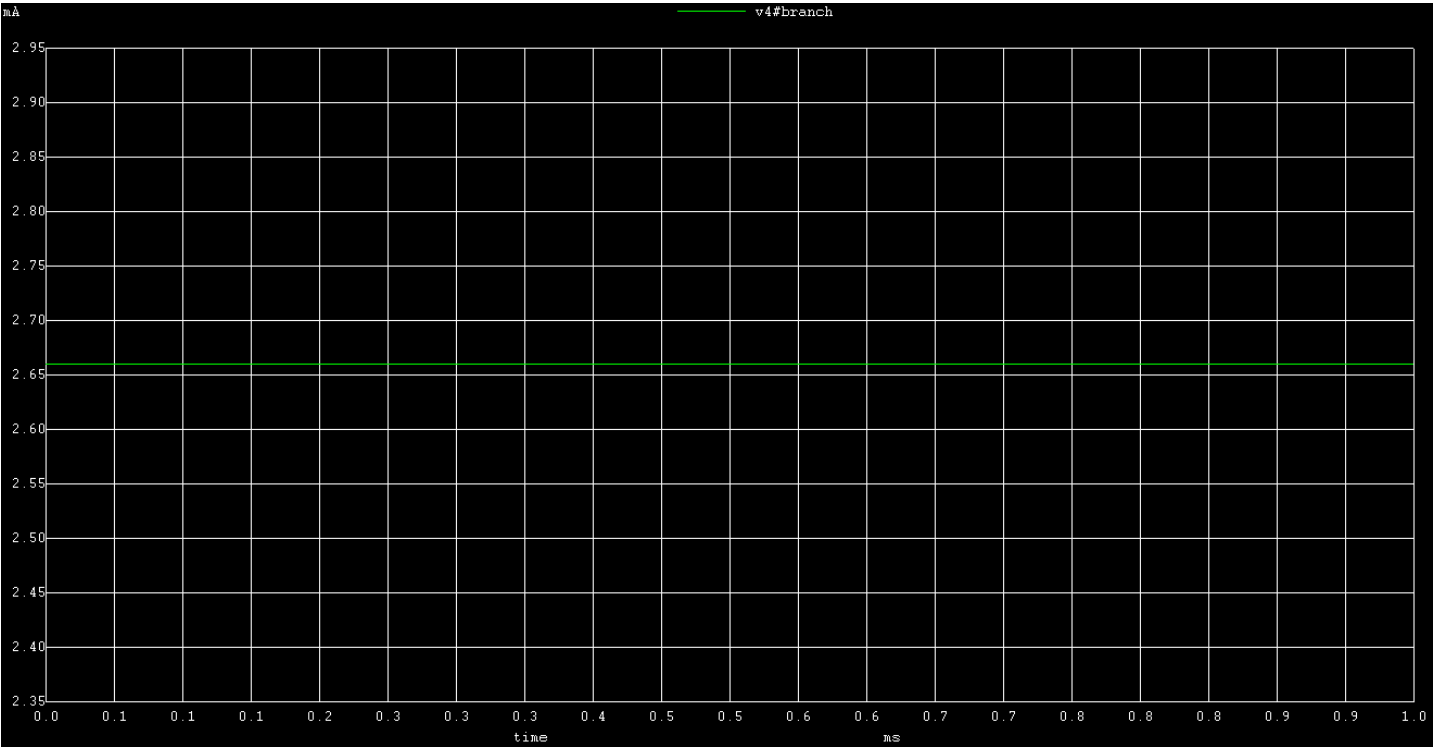




Value of  $V_b$  (V<sub>1</sub>):

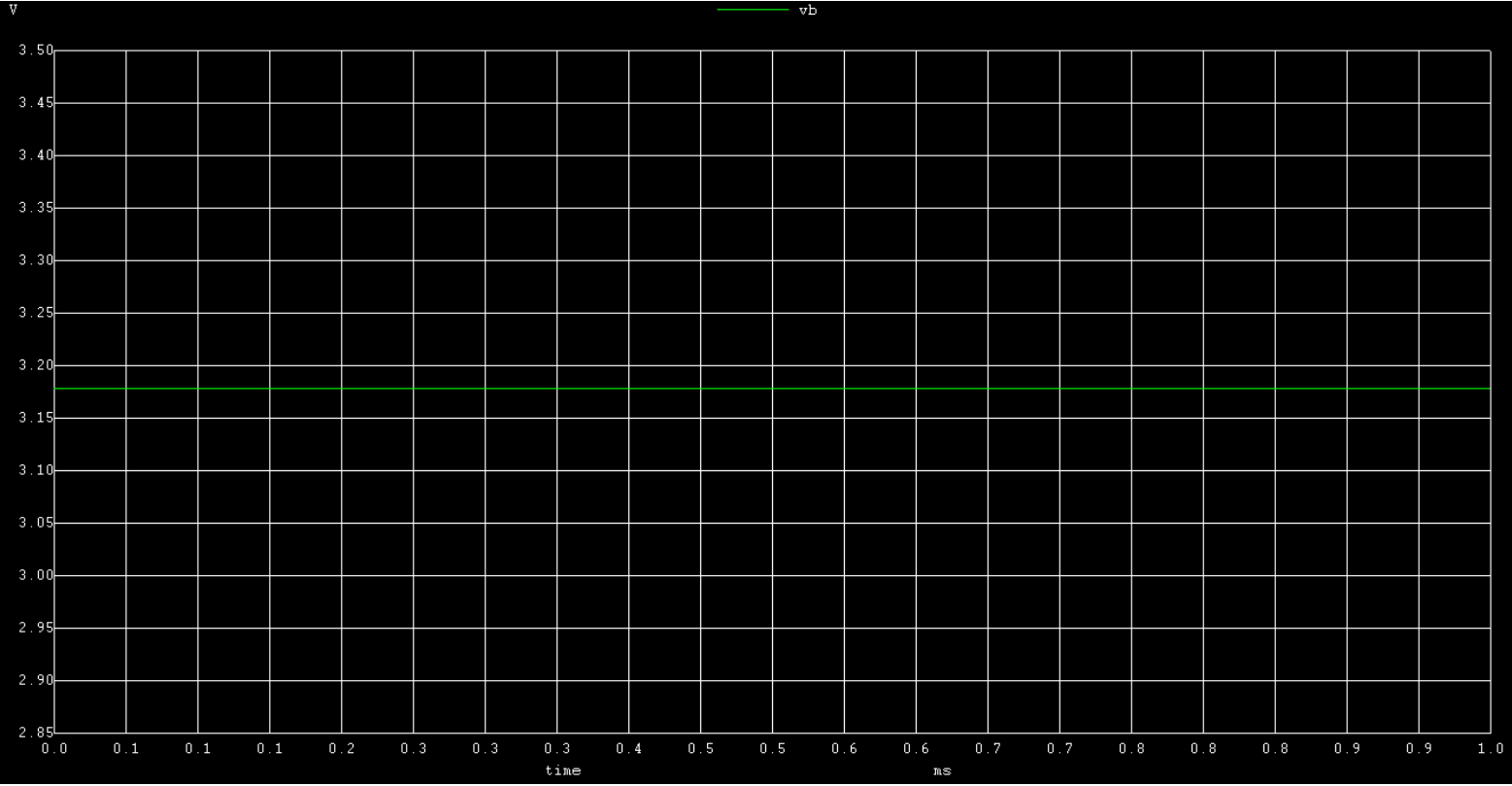


SCHEMATIC DIAGRAM:

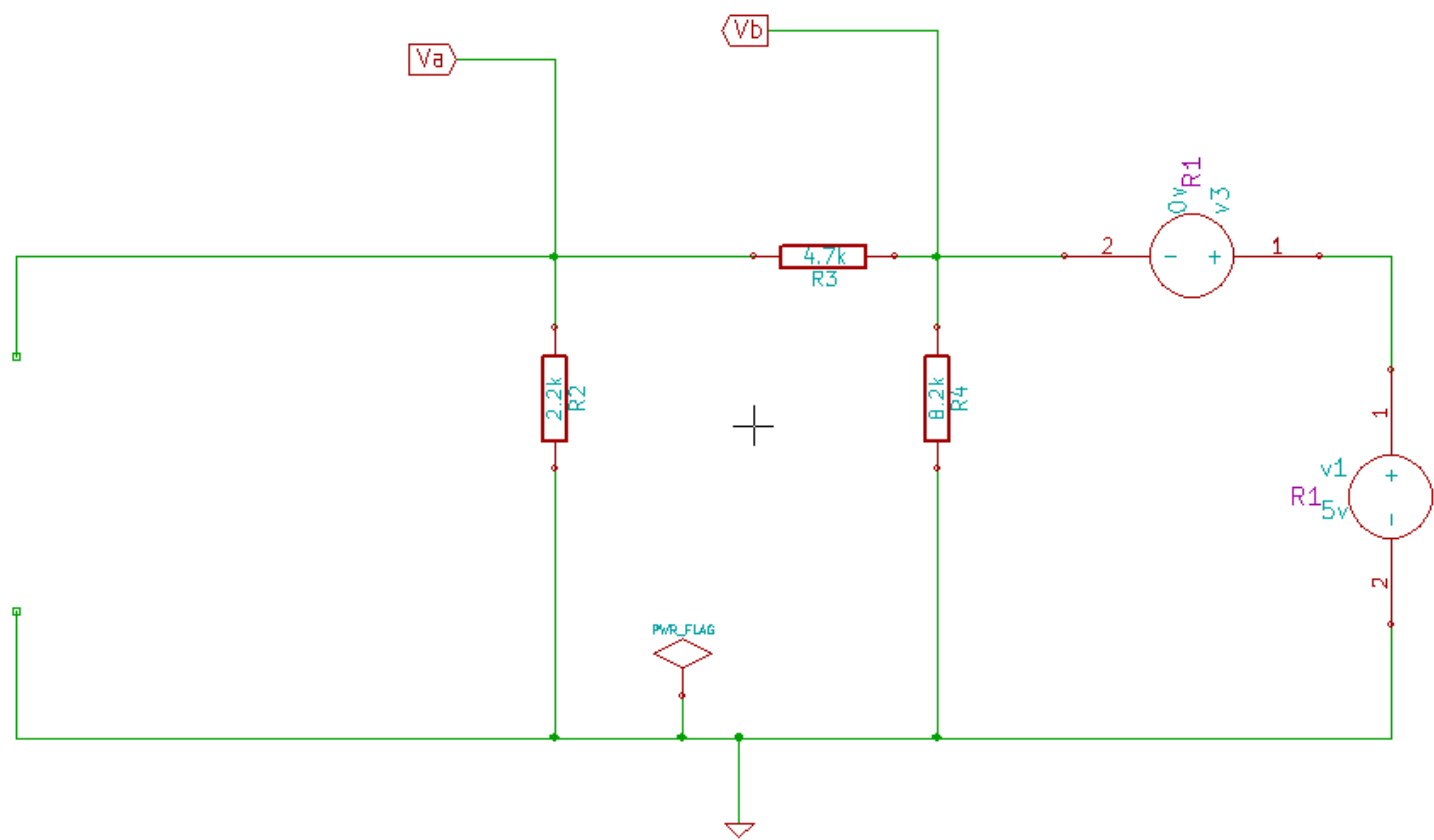For  $I_2=0$  Refer to "parameters1" FOLDER




SIMULATION OUTPUT:

Value of  $I_1$

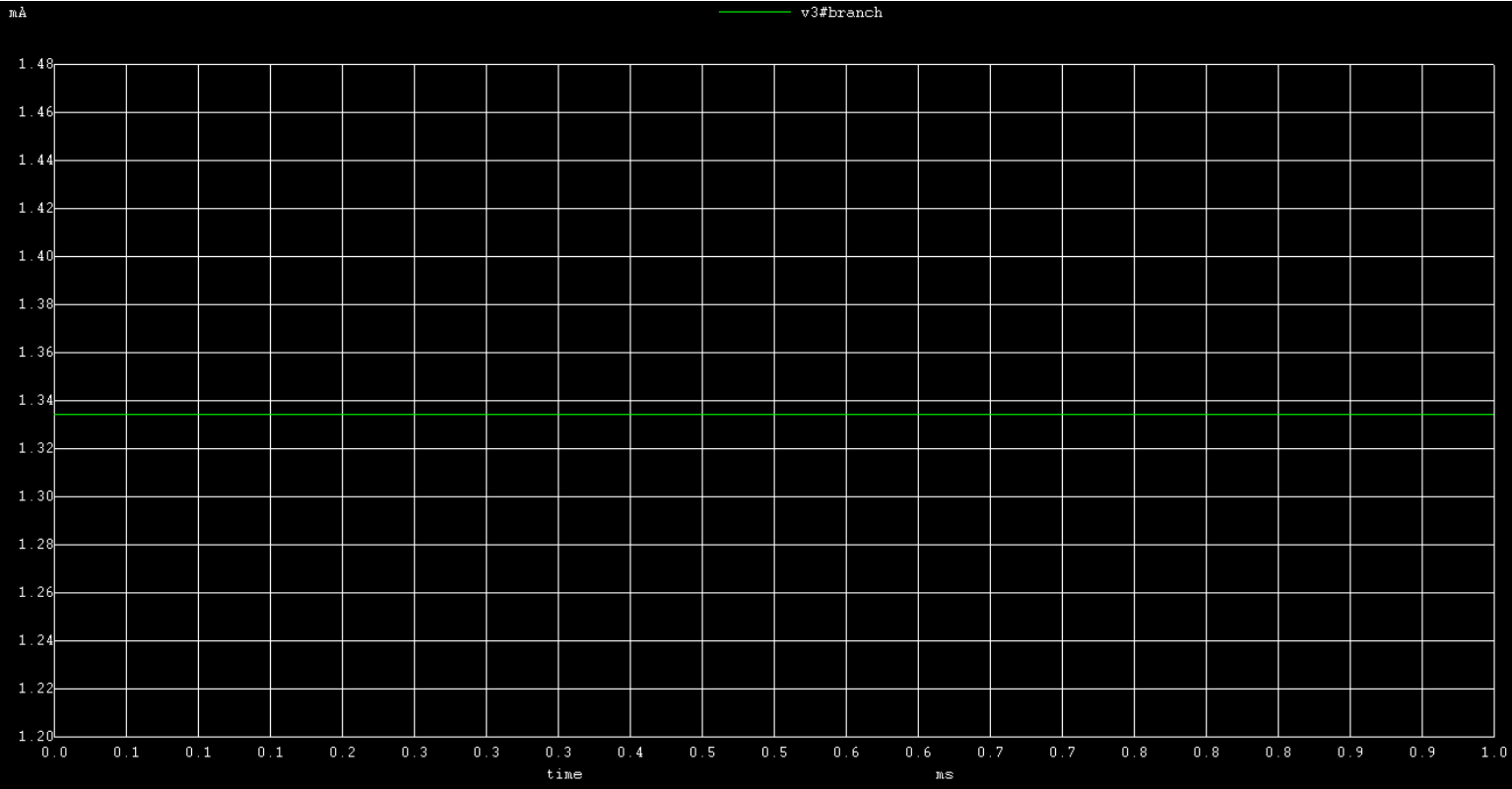

Value of  $V_a$  ( $V_2$ ):

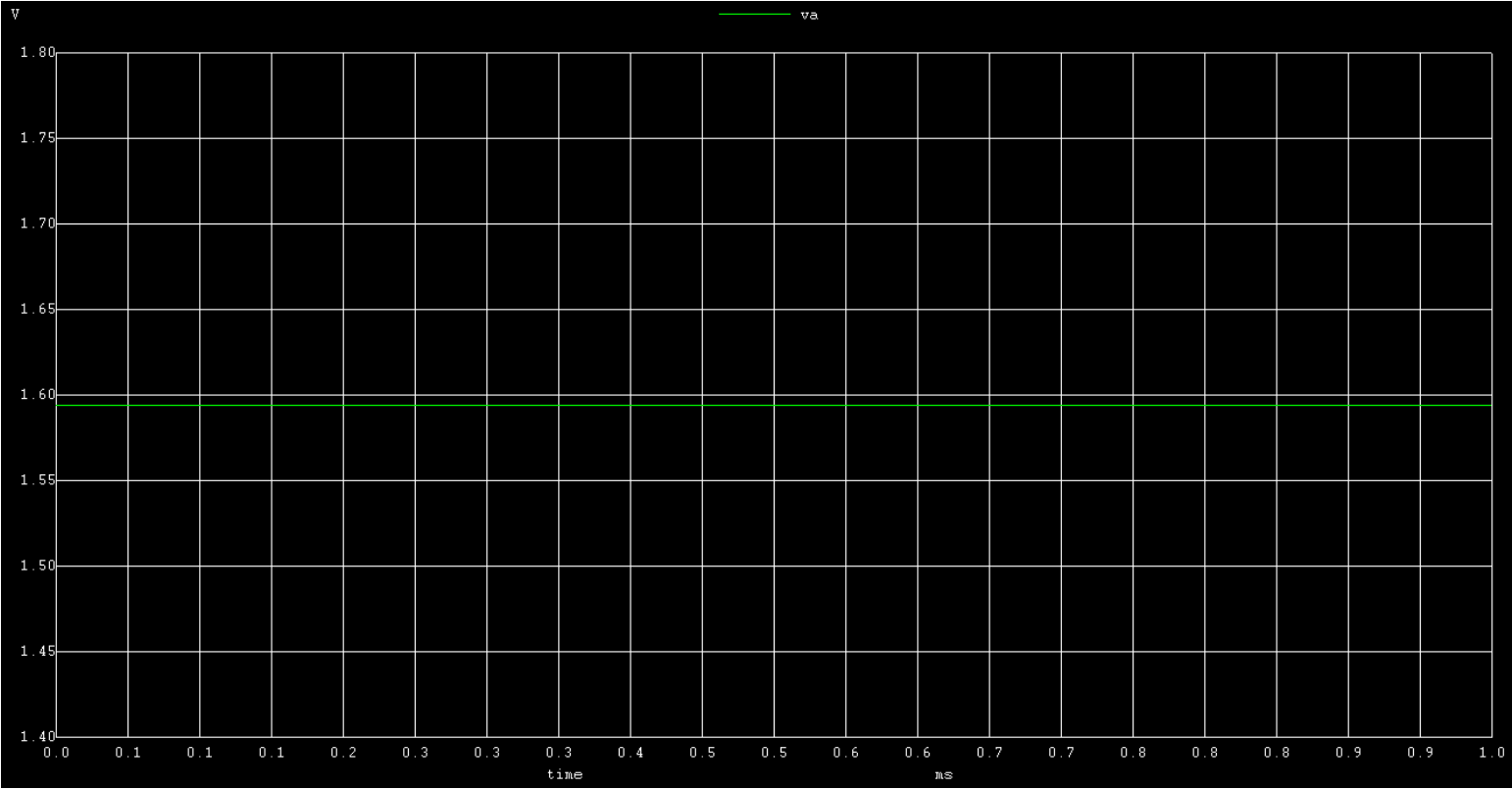

## CALCULATIONS:

$$Z_{11}=V_1/I_1 \text{ when } I_2=0\text{mA}$$

$$I_1=1.337\text{mA}, V_1=5\text{volts}$$

$$\text{So, } Z_{11}= 5/1.337 = 3.74\text{k}\Omega$$

$$Z_{21}=V_2/I_1 \text{ when } I_2=0\text{mA}$$

$$I_1=1.337\text{mA}, V_2=1.556\text{volts}$$

$$\text{So, } Z_{21}= 1.556/1.337 = 1.164\text{k}\Omega$$

$$Z_{22}=V_2/I_2 \text{ when } I_1=0\text{mA}$$

$$I_2=2.64\text{mA}, V_2=5\text{volts}$$

$$\text{So, } Z_{22}= 5/2.64 = 1.89\text{k}\Omega$$

$$Z_{12}=V_1/I_2 \text{ when } I_1=0\text{mA}$$

$$I_2=2.64\text{mA}, V_1=1.556\text{volts}$$

$$\text{So, } Z_{12}= 1.556/2.64 = 0.59\text{k}\Omega$$

<b><math>Z_{11}</math> (k<math>\Omega</math>)</b>	<b><math>Z_{12}</math> (k<math>\Omega</math>)</b>	<b><math>Z_{21}</math> (k<math>\Omega</math>)</b>	<b><math>Z_{22}</math> (k<math>\Omega</math>)</b>
3.74	1.89	1.164	0.59

## CONCLUSION: