

Implementation of Ring counter using Colpitts Oscillator and Multiplexer signal

Narra Hemanth Reddy, JNTUH, College of Engineering

September 28, 2022

Abstract:

An integrator is an op amp circuit, whose output is proportional to the integral of input signal. An integrator is basically an inverting amplifier where we replace feedback resistor with a capacitor of suitable value. A multiplexer (MUX) is a device allowing one or more low-speed analog or digital input signals to be selected, combined and transmitted at a higher speed on a single shared medium or within a single shared device. A Colpitts oscillator looks just like the Hartley oscillator but the inductors and capacitors are replaced with each other in the tank circuit. Schmitt trigger devices are typically used in signal conditioning applications to remove noise from signals used in digital circuits, particularly mechanical contact bounce in switches. A ring counter is a type of counter composed of flip-flops connected into a shift register, with the output of the last flip-flop fed to the input of the first, making a "circular" or "ring" structure.

2. Reference Circuit

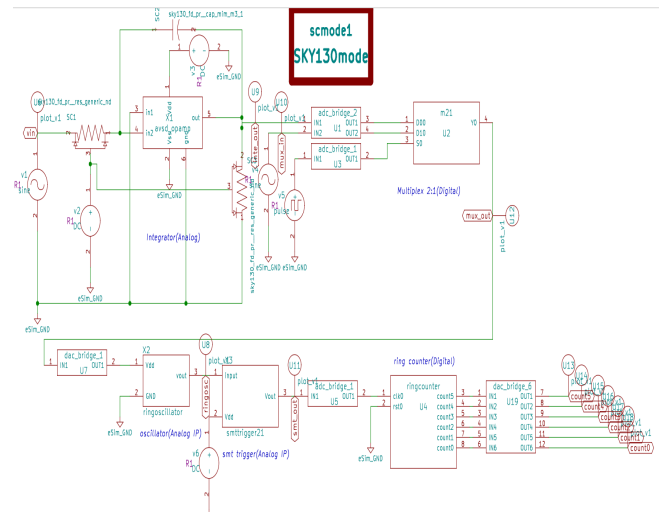


Figure 1

3. Expected Waveform Outputs:

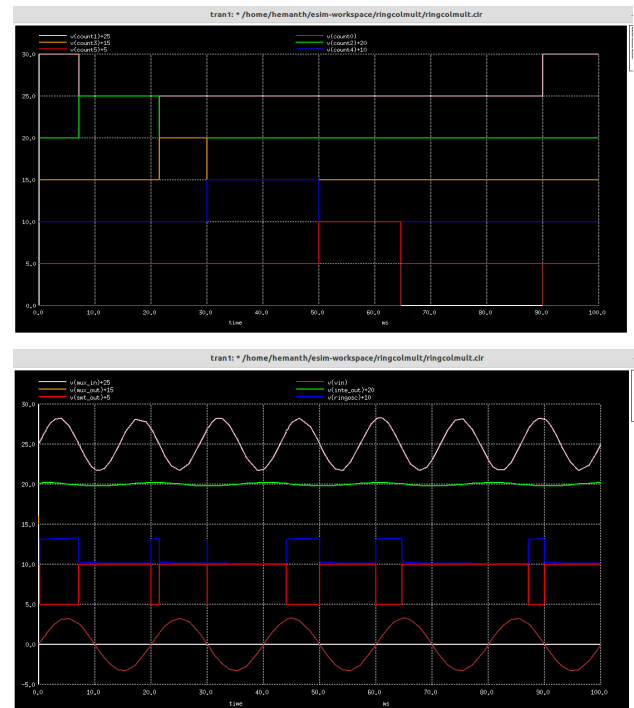


Figure2.

References:

1. Website: "www.allaboutcircuits.com"