

Design of a full adder using eSim

Sowndharya R

Bannari Amman Institute of Technology, Sathyamangalam, Erode

8 October 2022


A Full Adder is a Combinational Logic Circuit. It has three inputs. Full adder consists of 3 inputs and 2 outputs. s. The first two inputs are A and B and the third input is an input carry as Cin. Sum and cout are outputs.

Three DC sources are used as input here. These input sources are passed to the Analog to digital converter. Full adder setup is made using the logic gates. 2 Xor, 2 And and 1 Or gates are used.




$$\text{Sum} = A \oplus B \oplus C_{in}$$

$$\text{Carry} = A \& B | A \& C_{in} | B \& C_{in}$$

Schematic diagram:

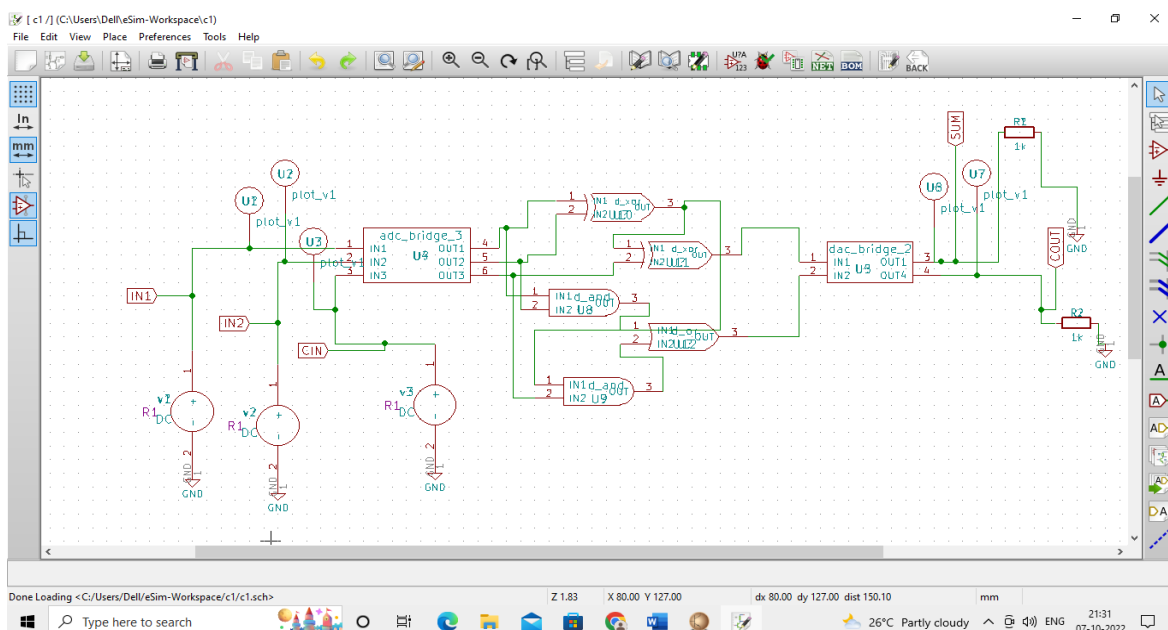

WAVEFORMS:

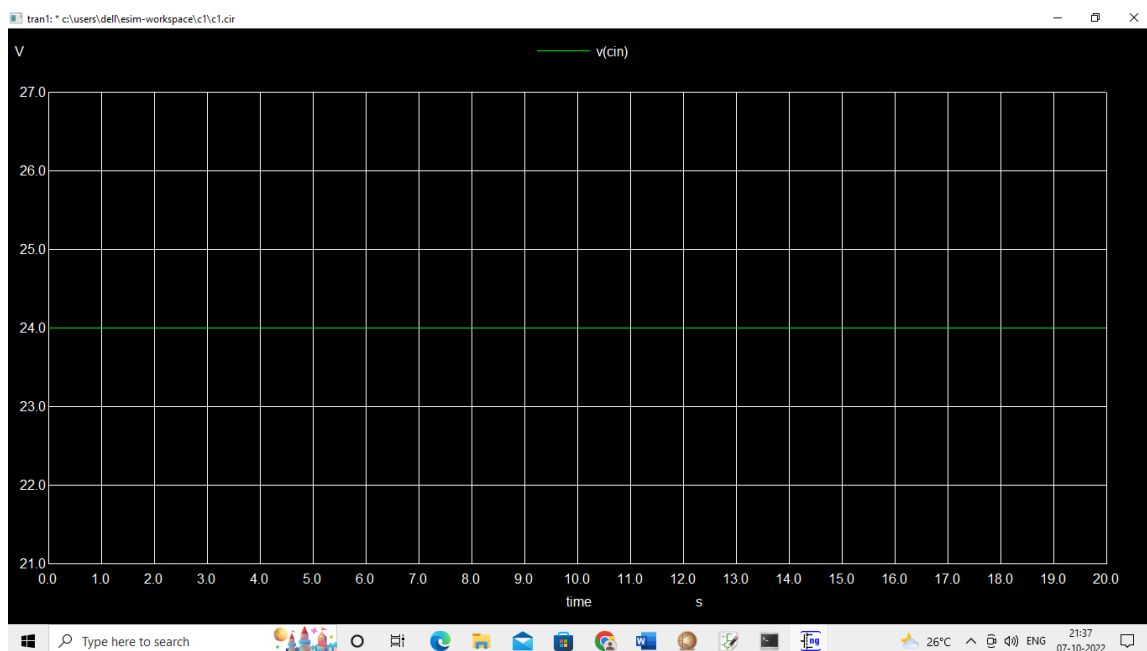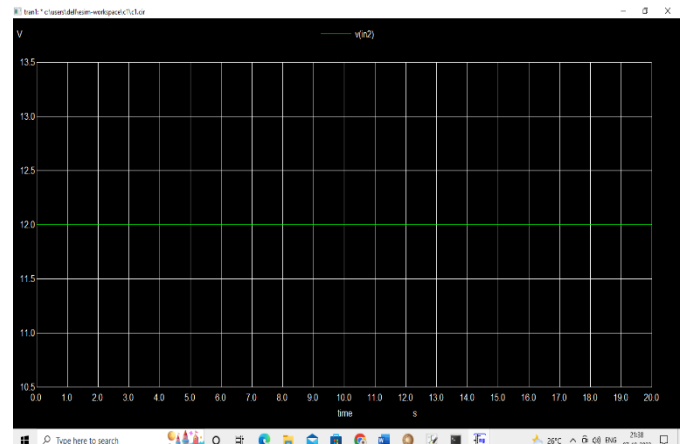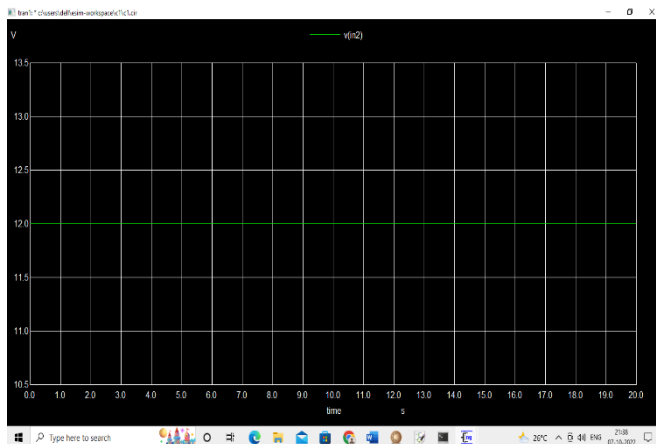

References:

[1]. Design and Analysis of CMOS Full Adder Saurabh J Shewale¹ and Sonal A Shirsath²-International Journal of Advanced Research in Science, Communication and Technology

[2]. Optimized CMOS Design of Full Adder using 45nm Technology, Sheenu Rana M.E.Scholar, Rajesh Mehra Associate Professor-International Journal of Computer applications