

Circuit Simulation Project

Title : Design and Implementation of Instrumentation Amplifier.

Student Name: Ganderla Chaithanya

University Name: Rajiv Gandhi university of knowledge technology.

Problem Statement:

To design, simulate, and validate an Instrumentation Amplifier using the eSim tool ensuring high gain, high input impedance, and low output impedance for accurate low-level signal measurement.

Theory/Description:


An Instrumentation Amplifier (IA or In-Amp) is a type of differential amplifier that is specifically designed for high-precision signal measurement applications. It is widely used in biomedical signal processing (ECG, EEG), industrial sensor interfacing, and low-level signal amplification due to its high gain accuracy, low noise, high input impedance, and excellent common-mode rejection ratio (CMRR).

Theory of Operation


An instrumentation amplifier typically consists of **three operational amplifiers (Op-Amps)** arranged in a **two-stage configuration**:

- The **first stage** consists of **two buffer amplifiers** (Op-Amp 1 and Op-Amp 2) with high input impedance to prevent loading the signal source.
- The **second stage** is a **differential amplifier** (Op-Amp 3) that subtracts the signals from the two inputs and provides the final amplified output.

Circuit Diagram:

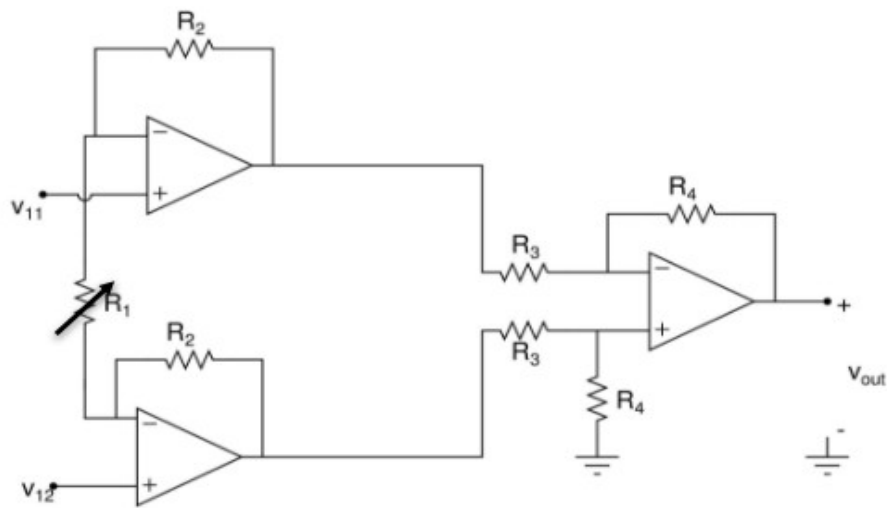

Expected waveforms:

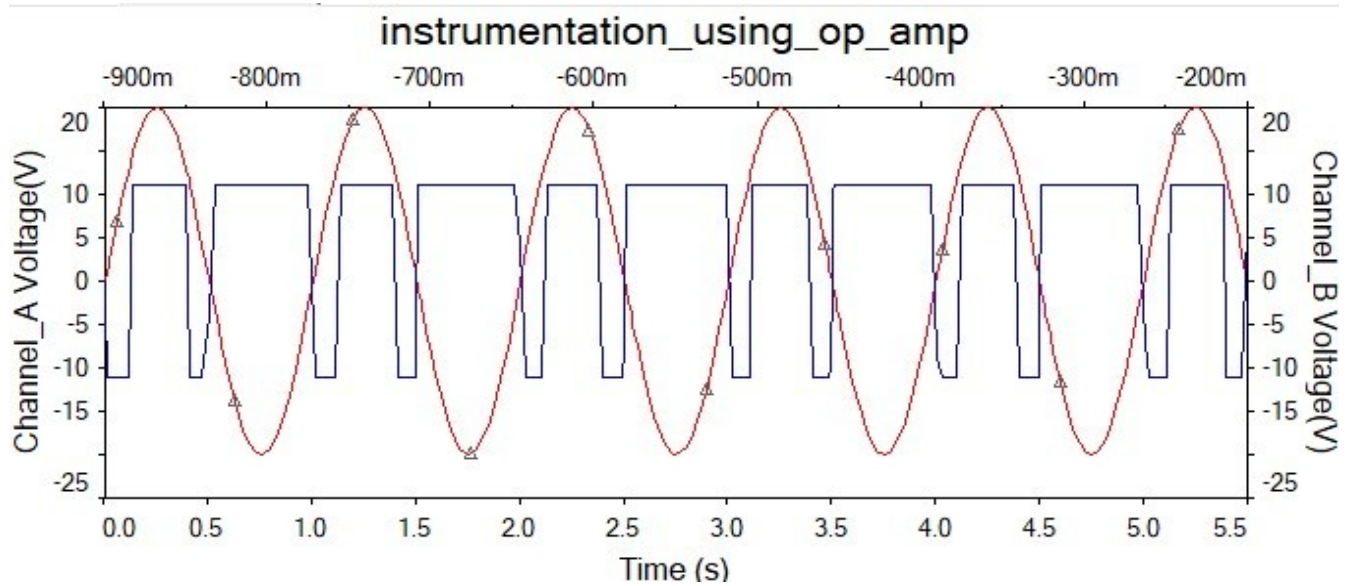

Sources:

Title of the paper: Design and Performance analysis of Instrumentation Amplifier at Nanoscale.

Name of the Journal: International journal of Advance Reasearch ,Ideas And Innovations and technology.

Author: Dr.M.Nizamuddin

Source Link: <https://www.ijariit.com/manuscript/design-performance-analysis-instrumentation-amplifier-nanoscale/>