

TITLE OF THE EXPERIMENT


DESIGN OF TWO BIT MULTIPLIER USING SUBCIRCUIT BUILDER

THEORY


A 2-bit multiplier can be implemented as a straightforward combinational logic circuit using basic logic gates. It consists of 4 inputs and four outputs. The 4 inputs are the two pairs of two bits, call them A and B.

Schematic Diagram


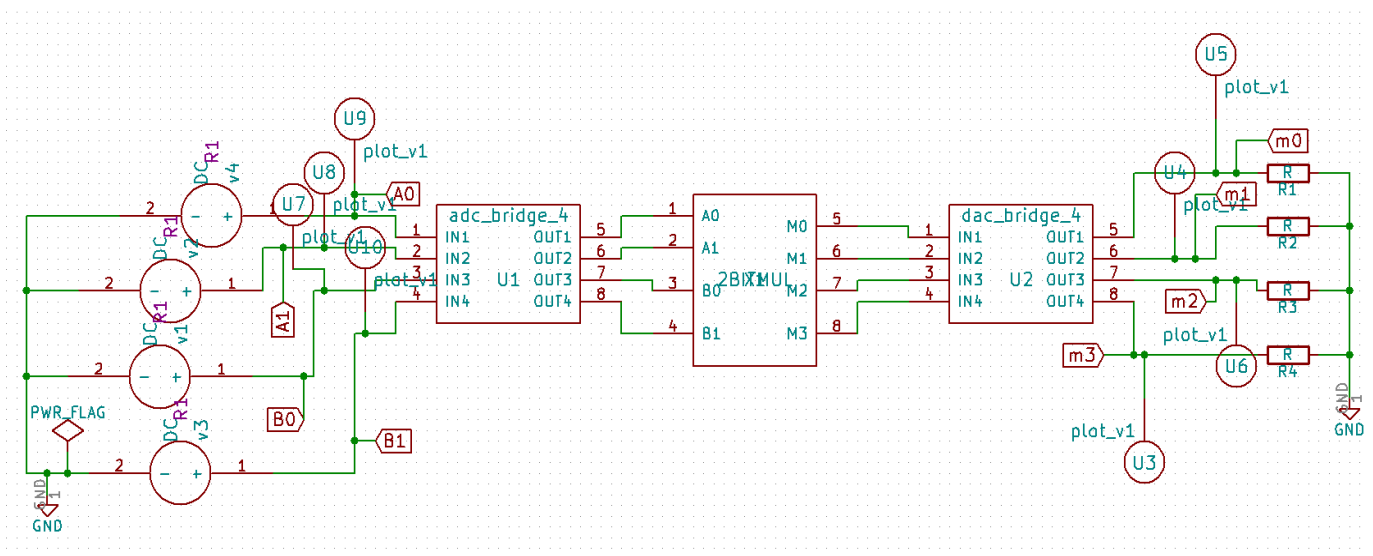
The schematic diagram of two bit multiplier is.





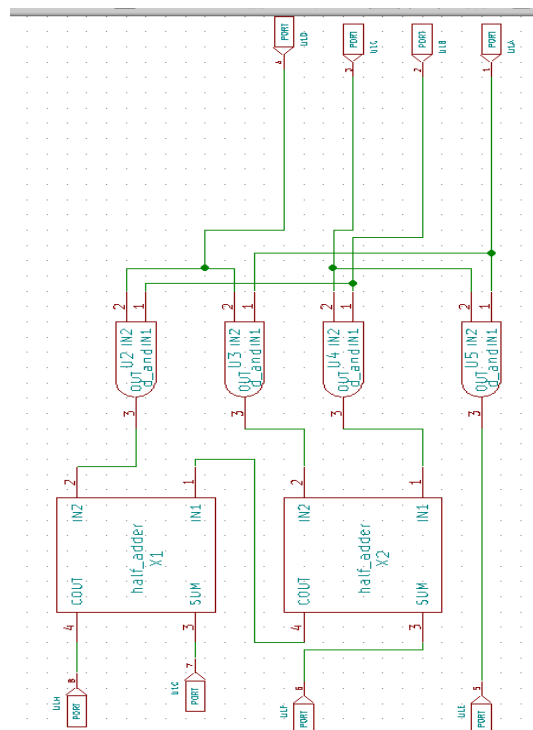Here I used a subcircuit for two bit multiplication. The internal structure of 2 bit multiplier is shown below.







Input Ngspice Plots:

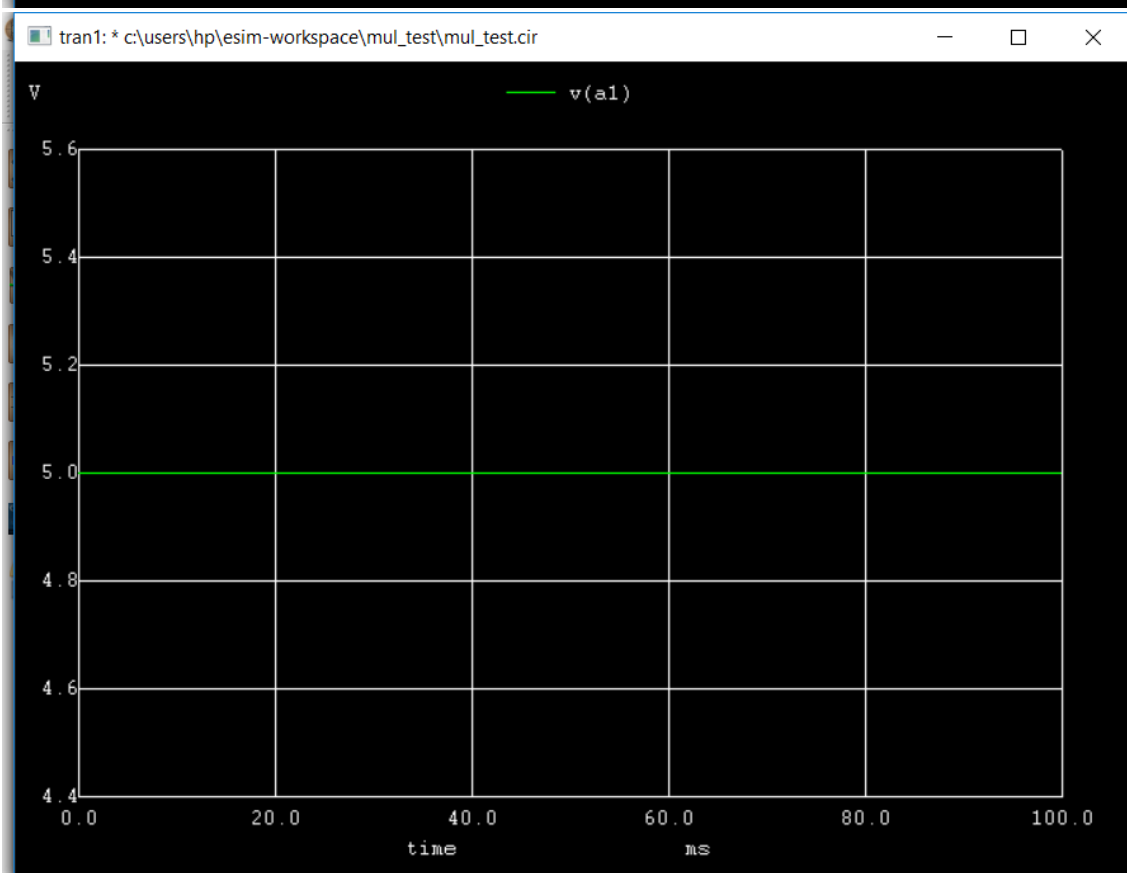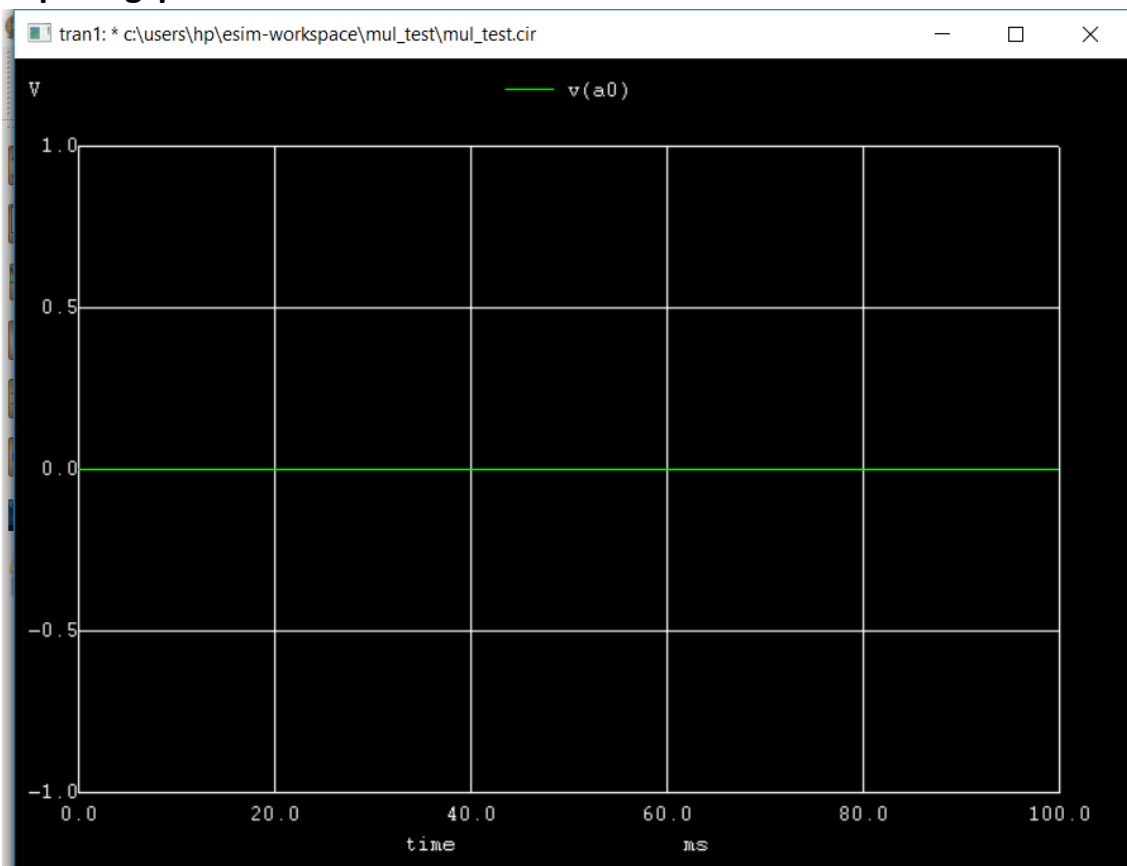

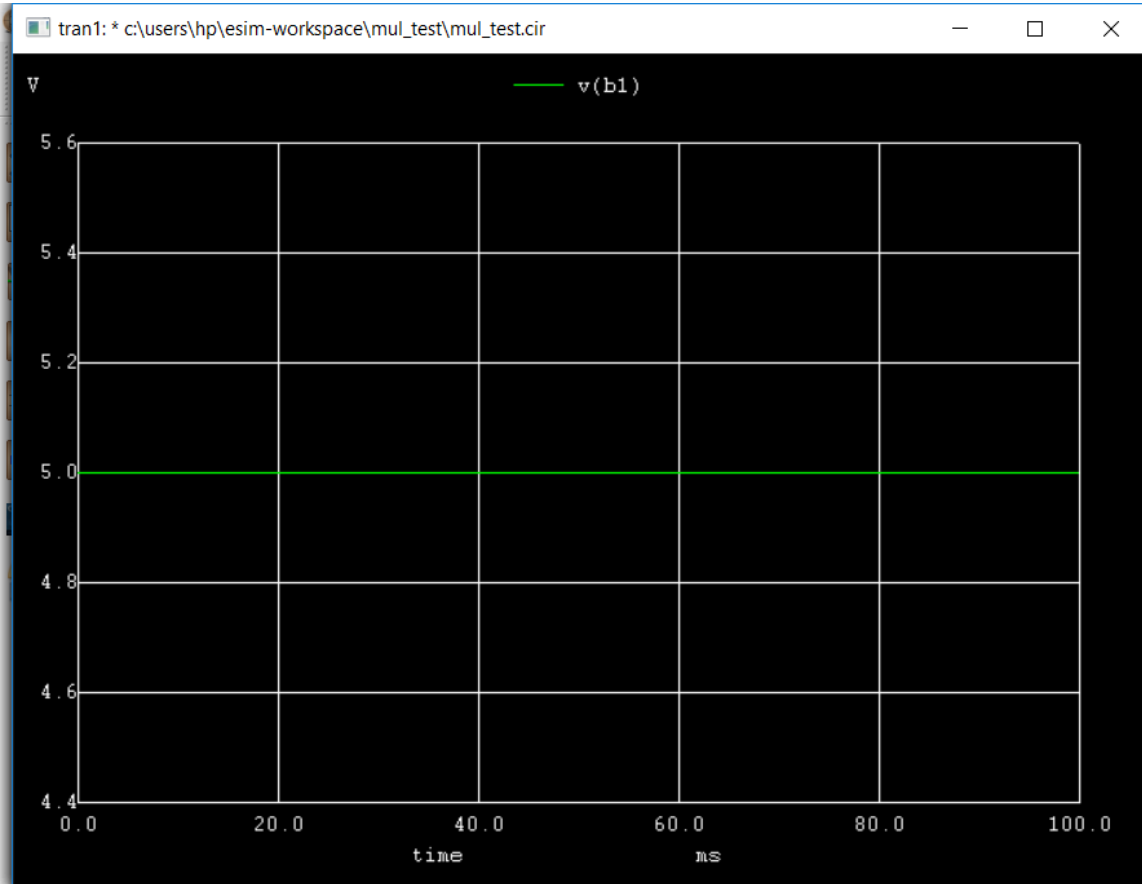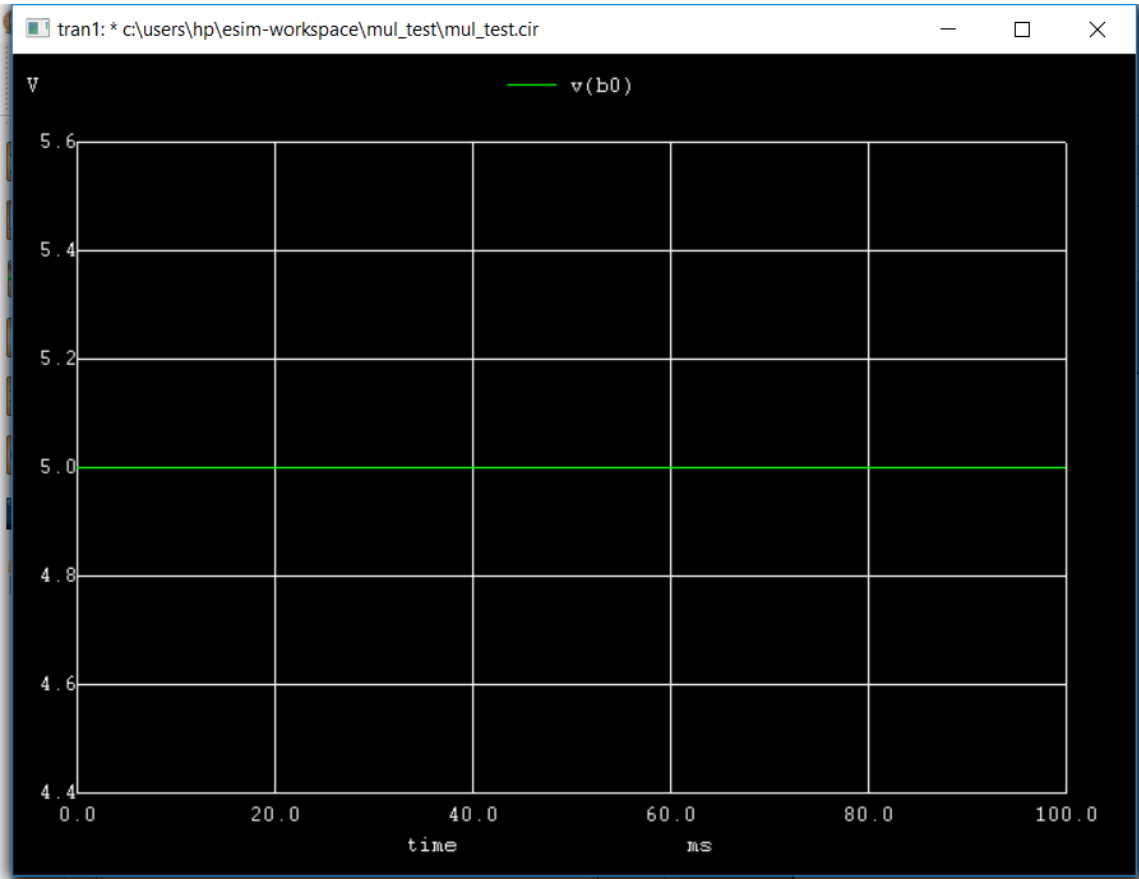


Output Ngspice Plots:

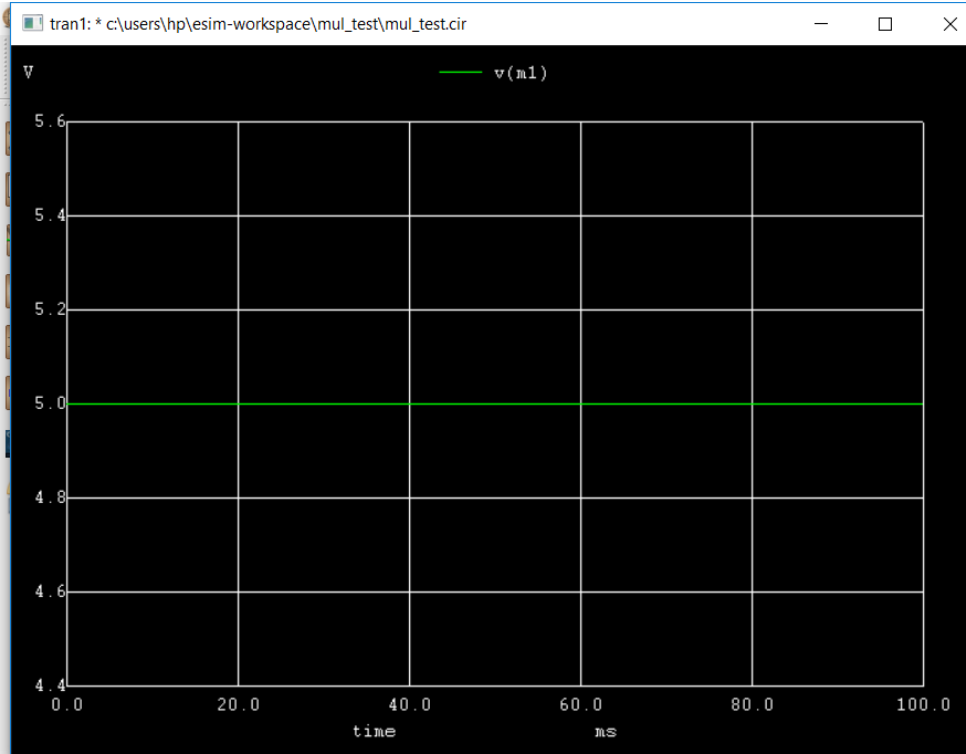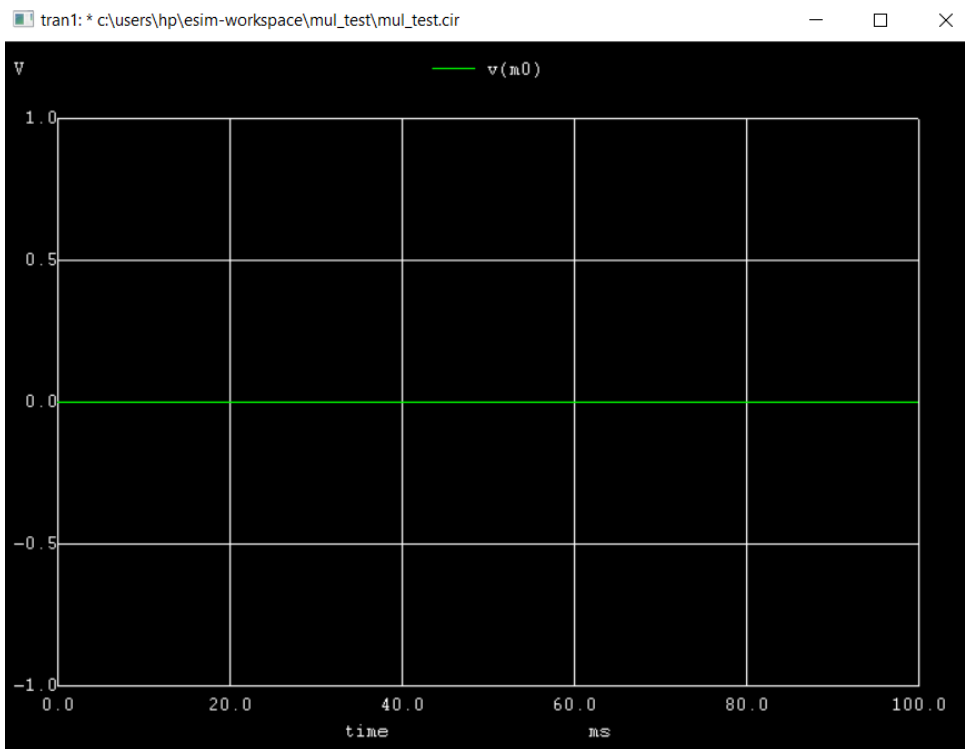

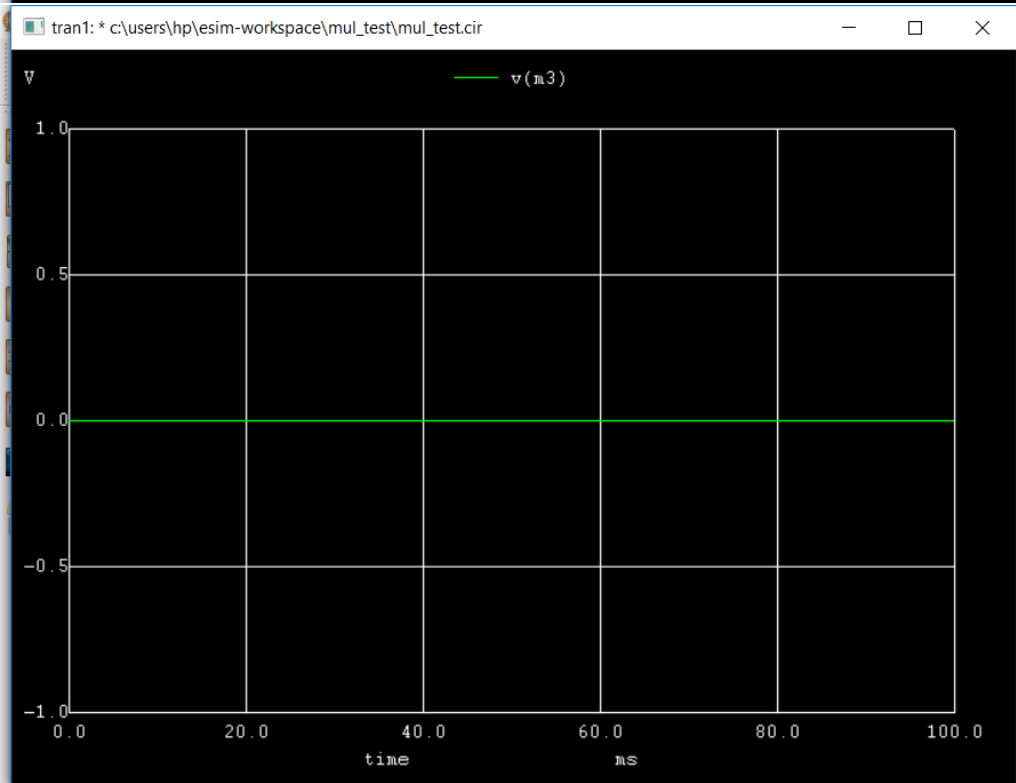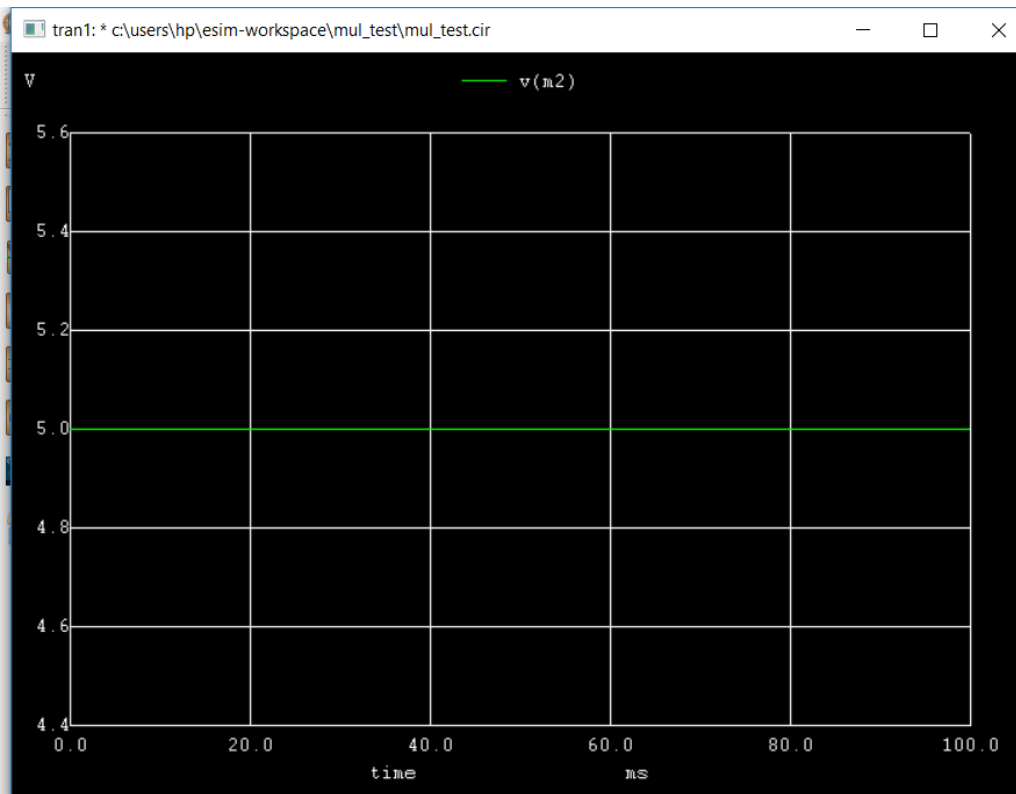

Python Plot:

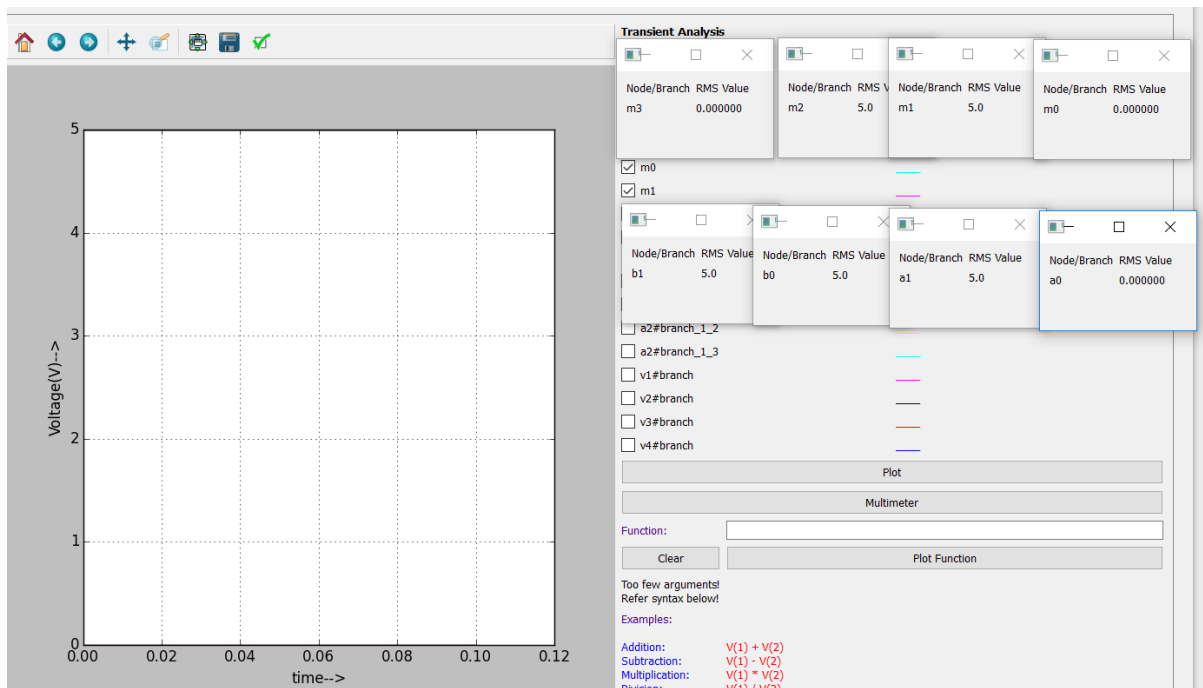

References:

<https://vlsiuniverse.blogspot.com/2013/05/binary-multiplier.html>