

# Circuit Simulation Project

<https://esim.fossee.in/circuit-simulation-project>

**Name of the participant: Monica Singh**

**Project Guide: Dr. R. Maheswari**

**Title of the circuit: Analysis of MOSFET characteristics**


## Theory/Description:

In this project, **MOSFET model NMOS-180um Drain characteristics and Transfer characteristics** is analysed. The metal–oxide–semiconductor field-effect transistor (MOSFET) is a field-effect transistor where the voltage determines the conductivity of the device. It is a four-terminal device with source(S), gate (G), drain (D) and body (B) terminals. These devices can be classified into two types viz., depletion-type and enhancement-type, depending on whether they possess a channel in their default state or no, respectively. Further, each of them can be either p-channel or n-channel devices. The N-Channel MOSFET has an N- channel region located in between the source and drain terminals. In this type of Field Effect Transistor, the drain and source are heavily doped n+ region and the substrate or body are of P-type.

The **drain characteristics** of a MOSFET are drawn between the drain current  $I_D$  and the drain source voltage  $V_{DS}$ . Actually when  $V_{DS}$  is increased, the drain current  $I_D$  should increase, but due to the applied  $V_{GS}$ , the drain current is controlled at certain level. Hence the gate current controls the output drain current.

**Transfer characteristics** define the change in the value of  $V_{DS}$  with the change in  $I_D$  and  $V_{GS}$  in both depletion and enhancement modes.

### Circuit Diagram(s):

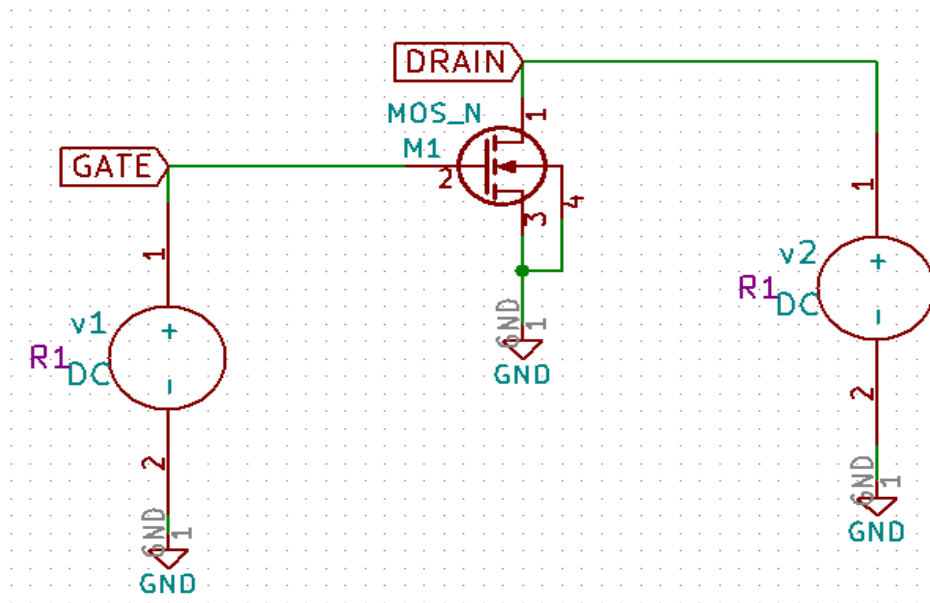


### Results :

#### Ngspice Plots:

##### i) DRAIN CHARACTERISTICS

Plot  $i(v2)$  vs  $V(\text{DRAIN})$

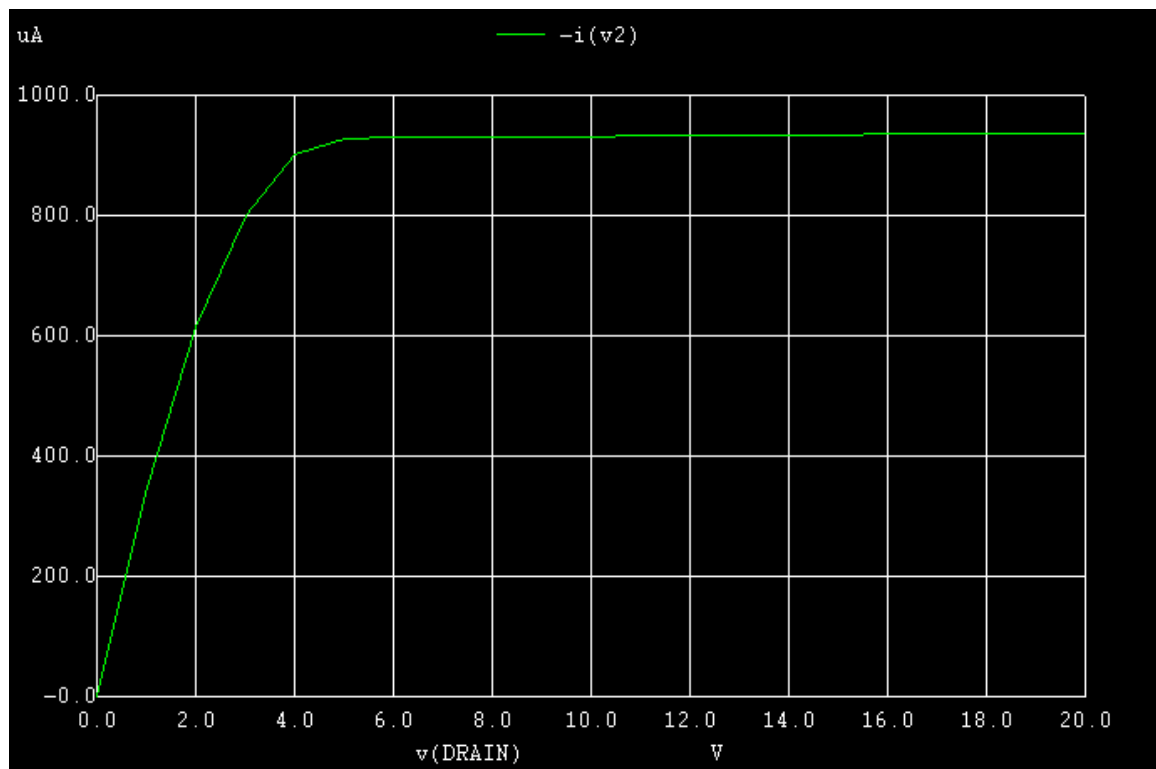

The drain characteristics of NMOS with gate voltage=4v

kicadToNgspice-68

Analysis Source Details NgSpice Model Device Modeling Subcircuits

AC  DC  TRANSIENT

AC Analysis

Scale  Lin  Dec  Oct

Start Frequency  Hz

Stop Frequency  Hz

No. of Points

DC Analysis

Enter Source 1	<input type="text" value="V2"/>	
Start	<input type="text" value="0"/>	<input type="text" value="Volts or Amperes"/>
Increment	<input type="text" value=".1"/>	<input type="text" value="Volts or Amperes"/>
Stop	<input type="text" value="20"/>	<input type="text" value="Volts or Amperes"/>

Convert

Analysis Source Details NgSpice Model Device Modeling Subcircuits

Add parameters for DC source v1


Enter value(Volts/Amps):

Add parameters for DC source v2


Enter value(Volts/Amps):


Convert

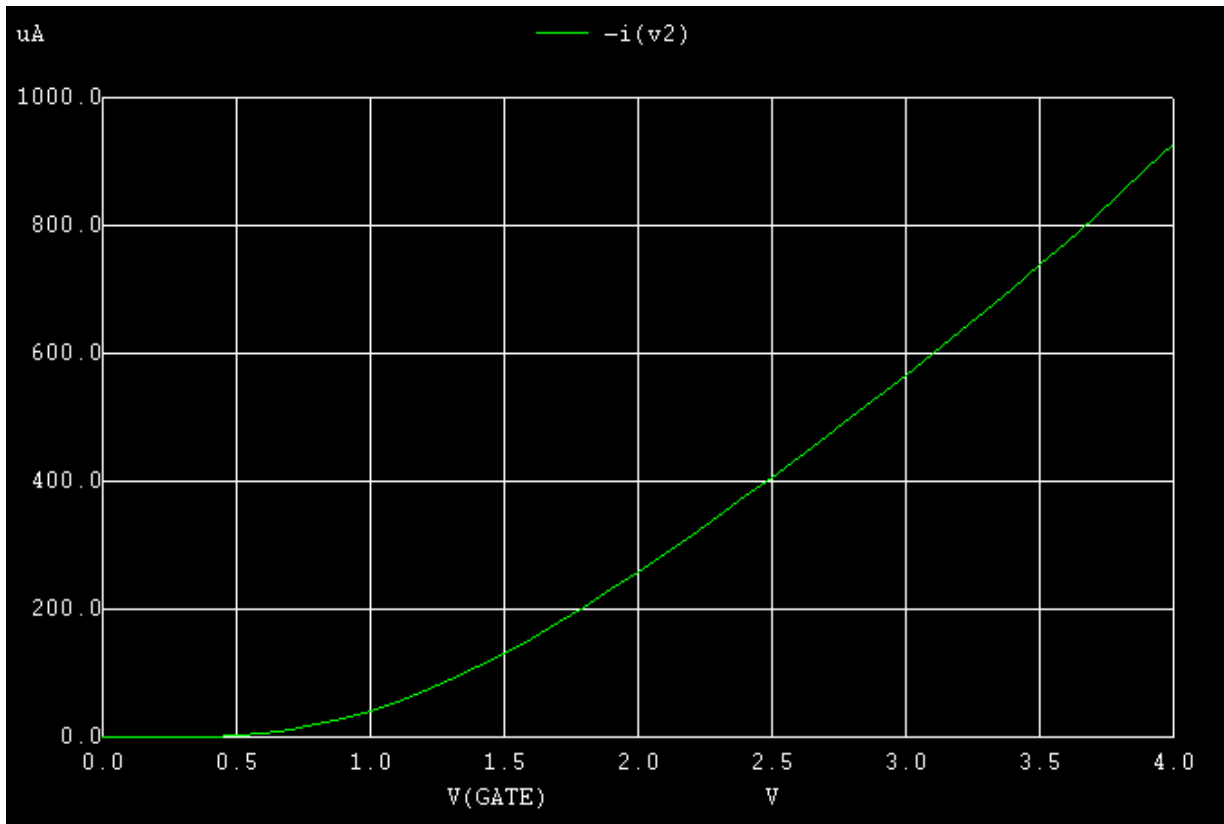**ii) TRANSFER CHRCATERISTICS**  
**Plot i(V2) vs V(GATE)**



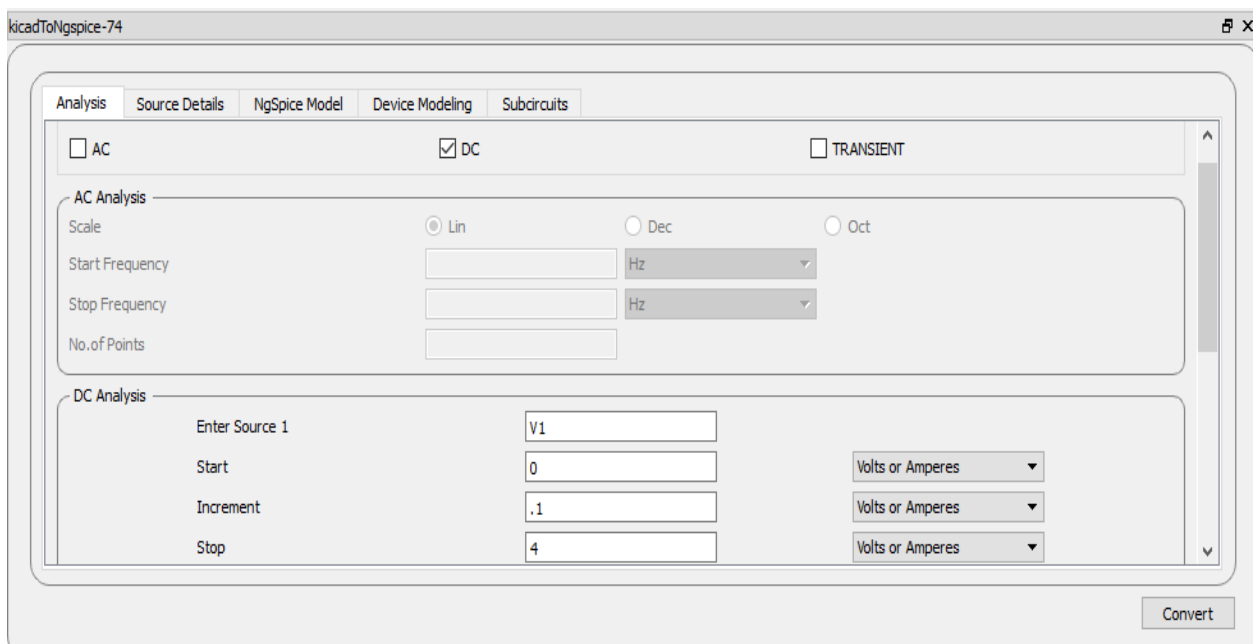**The transfer characteristics of NMOS with drain voltage=5v**



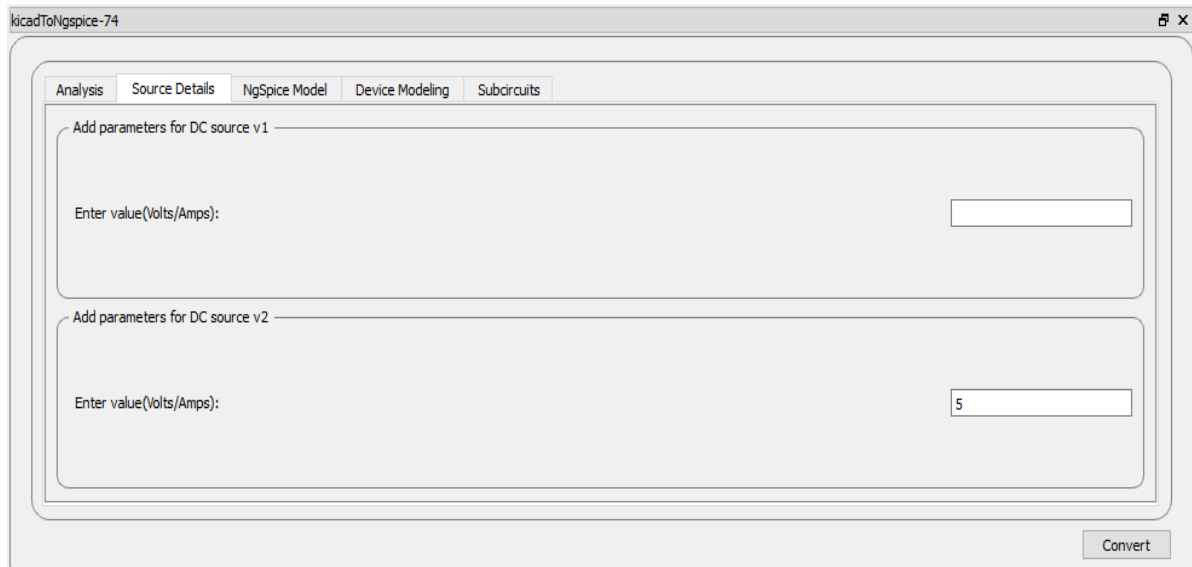

### Conclusion:

Thus, we have studied the drain and transfer characteristics of NMOS using eSim and we got the appropriate waveform.

**Two types of simulation** are there one is for **DRAIN characteristics** and other for **TRANSFER characteristics**

### Source/Reference(s):

<https://en.wikipedia.org/wiki/MOSFET>

<https://vlsi->

[iitg.vlabs.ac.in/MOSFET\\_theory.html](https://vlsi-iitg.vlabs.ac.in/MOSFET_theory.html)