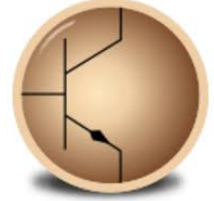




VIT[®]
Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)



Circuit Simulation Project

<https://esim.fossee.in/circuit-simulation-project>

INVERTING SUMMER USING OP-AMP

by

Karthick Srivatsa R


Under the guidance of **Dr.Subhashini N**,SENSE,VIT Chennai

THEORY/DESCRIPTION:

The Inverting summer also known as the adder is an Op-Amp based circuit where multiple input signals of different voltages are added. This is an extended version/example of the Inverting amplifier but with multiple inputs. Here the input voltages are applied the inverting terminal of the. In this Inverting summer the output is sum of the individual inputs and is out of phase by 180° from the sum of the inputs.

DESIGN:

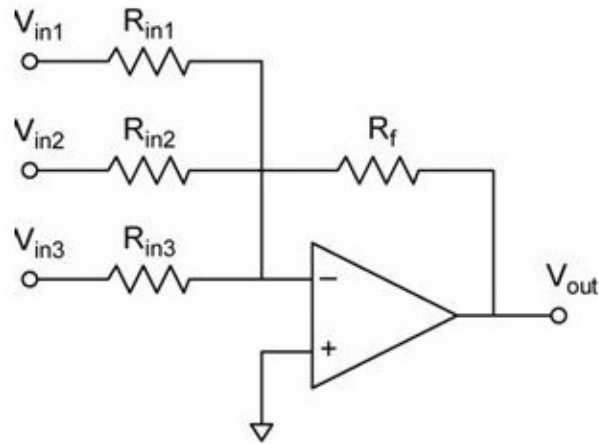A general design of the Inverting summer is shown in the following circuit. Normal Inverting Amplifier circuit has only one voltage / input at its inverting input terminal. If more input voltages are connected to the inverting input terminal as shown, the resulting output will be the sum of all the input voltages applied, but inverted.




The Summing Amplifier Circuit Diagram

$$V_{OUT} = V_1 A_{V1} + V_2 A_{V2} + \dots + V_n A_{Vn}$$

Where V_{out} is the sum of the individual input voltages and $A_v(R_f/R_{in}$ ratio) is the amplification factor which is 1 here. Here for the circuit to act as an summer and not a summing amplifier the $R_{in}, R_{in2}, R_{in3} \dots$ and R_f must be equal. So we will obtain just the sum of the individual inputs.



SCHEMATIC DIAGRAM:

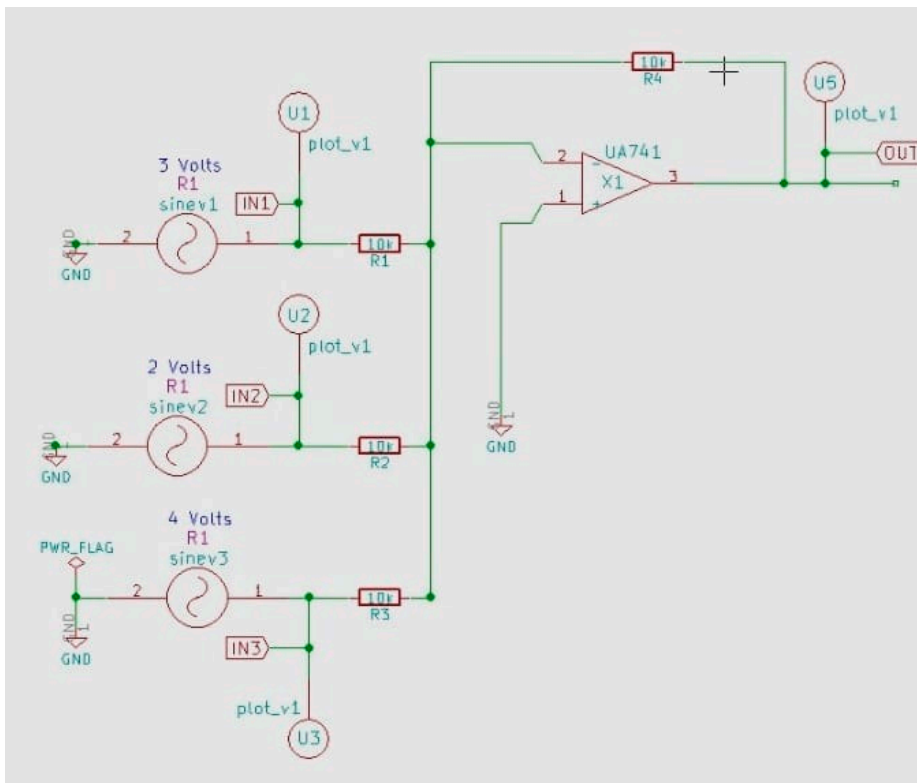


SIMULATION RESULTS:


Ngspice Plots-

Input Voltages

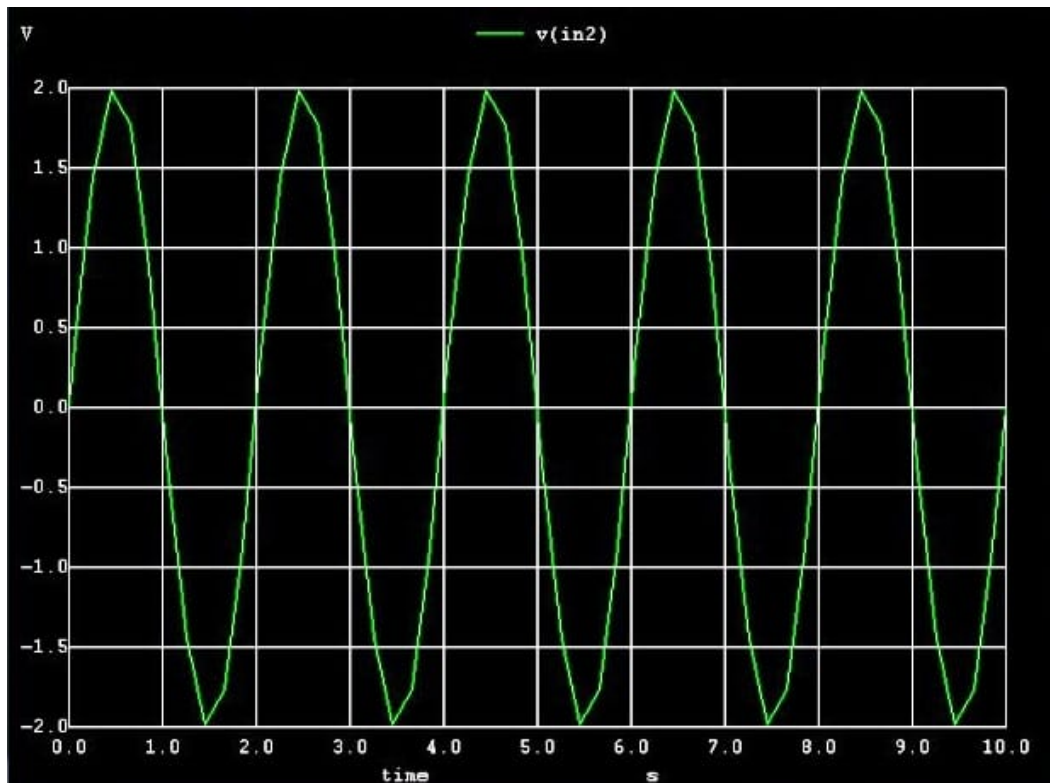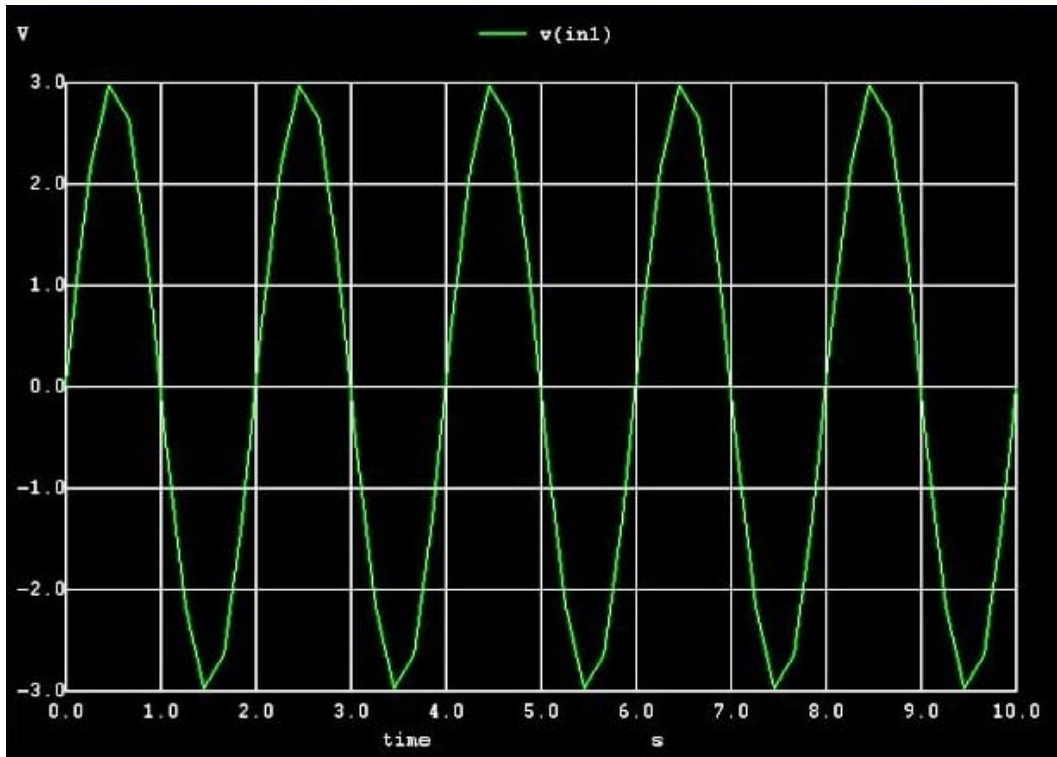


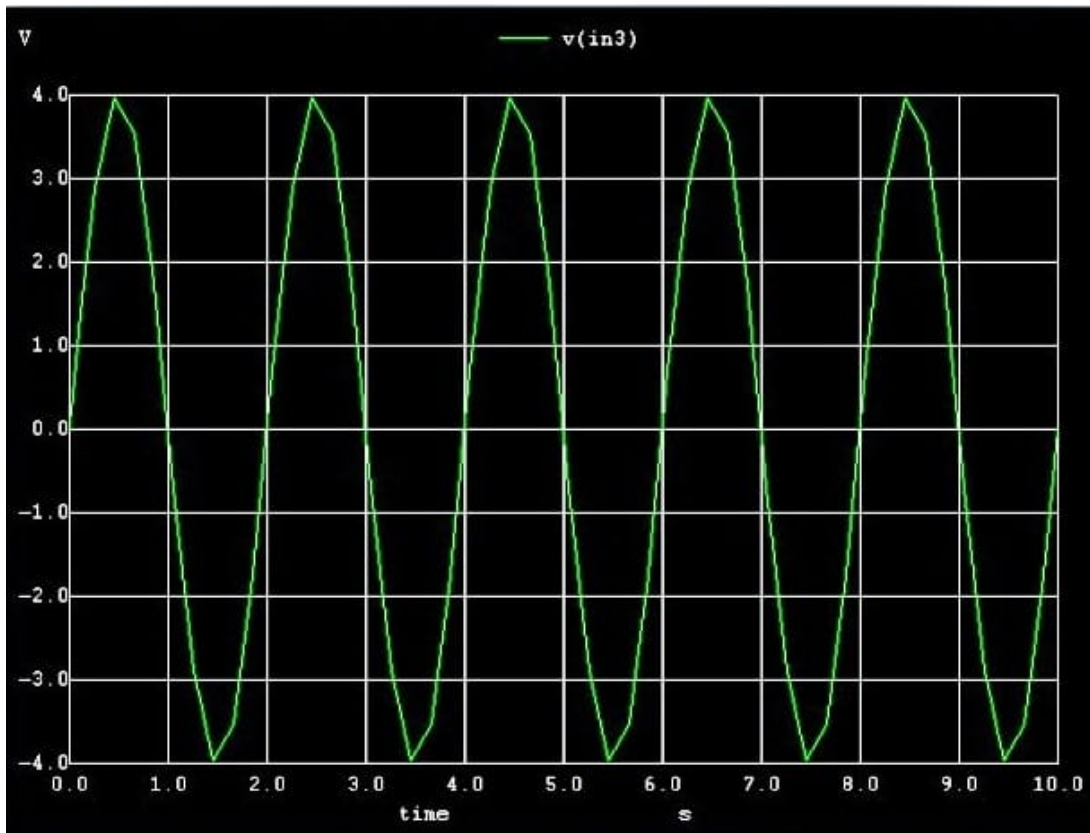



Output Voltage

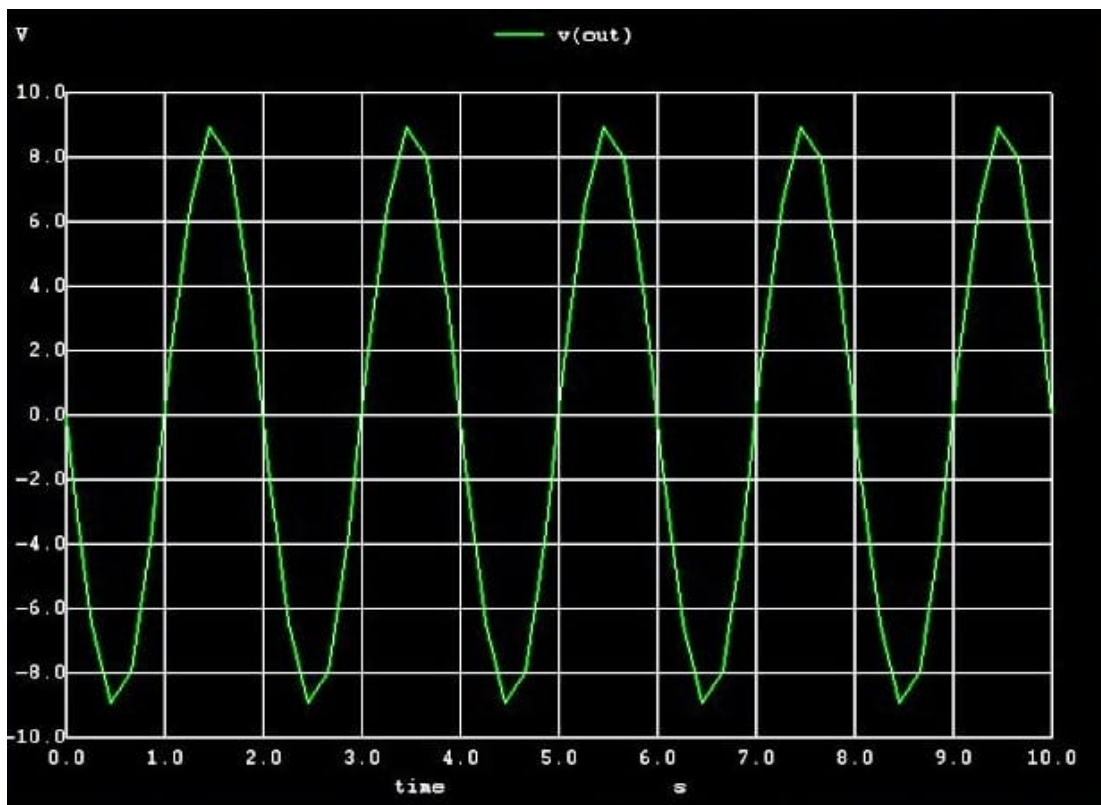


Python plots:

Input plots

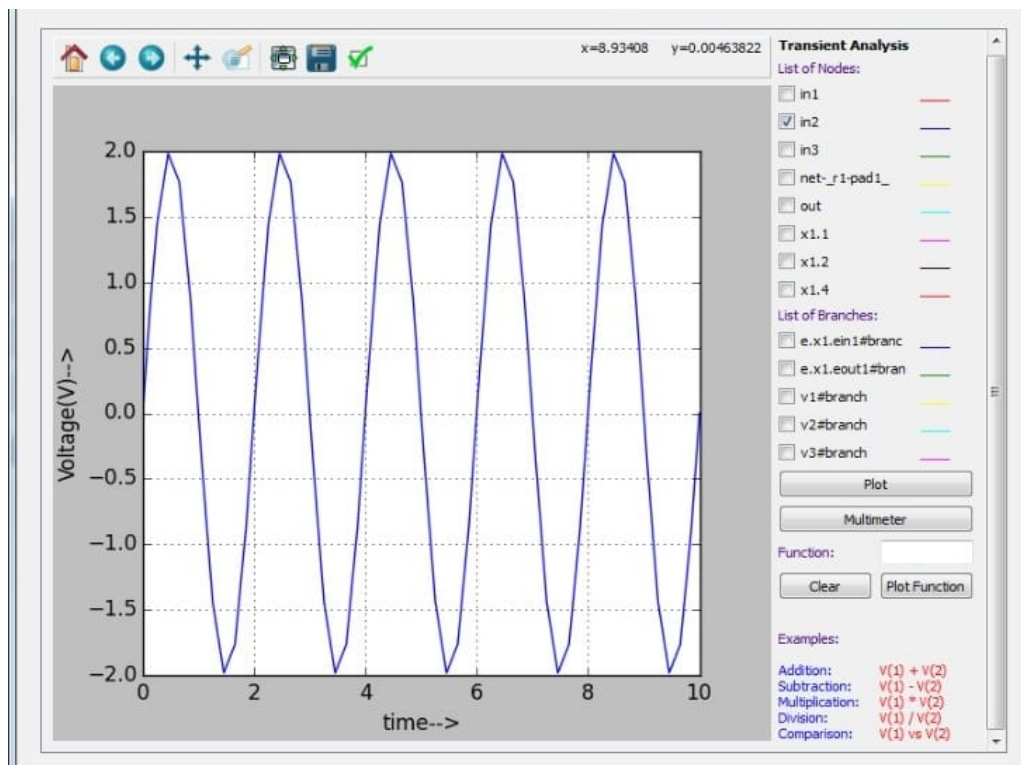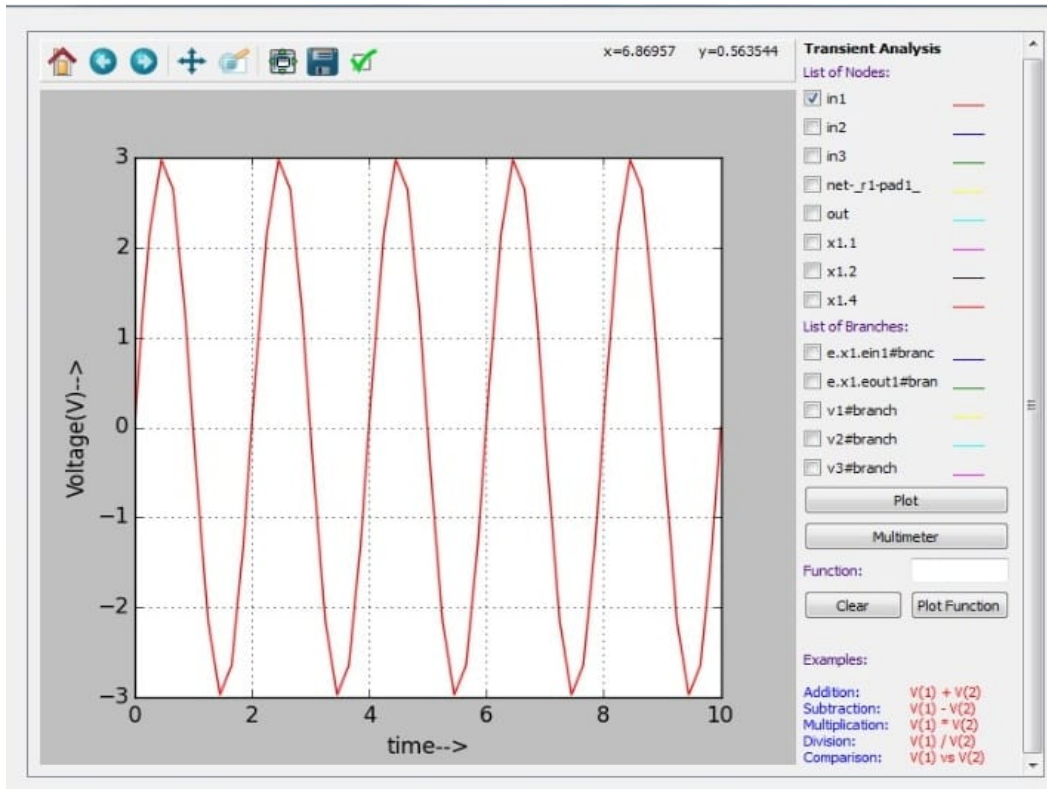


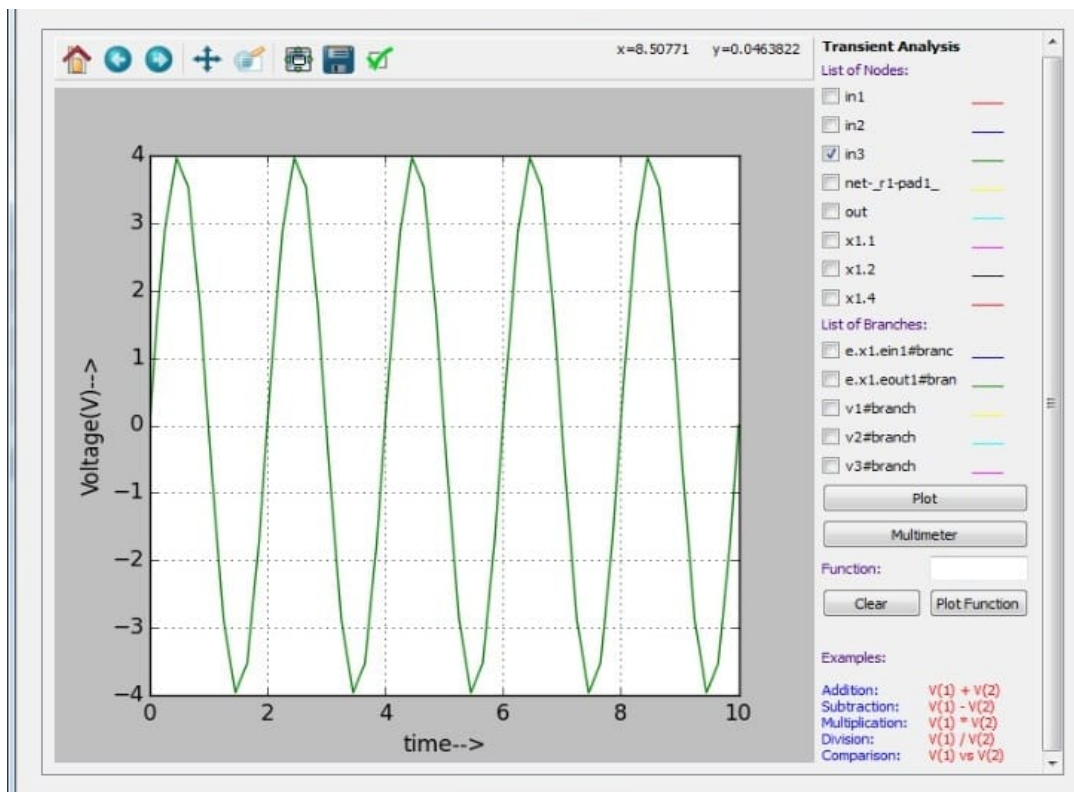

Output plot

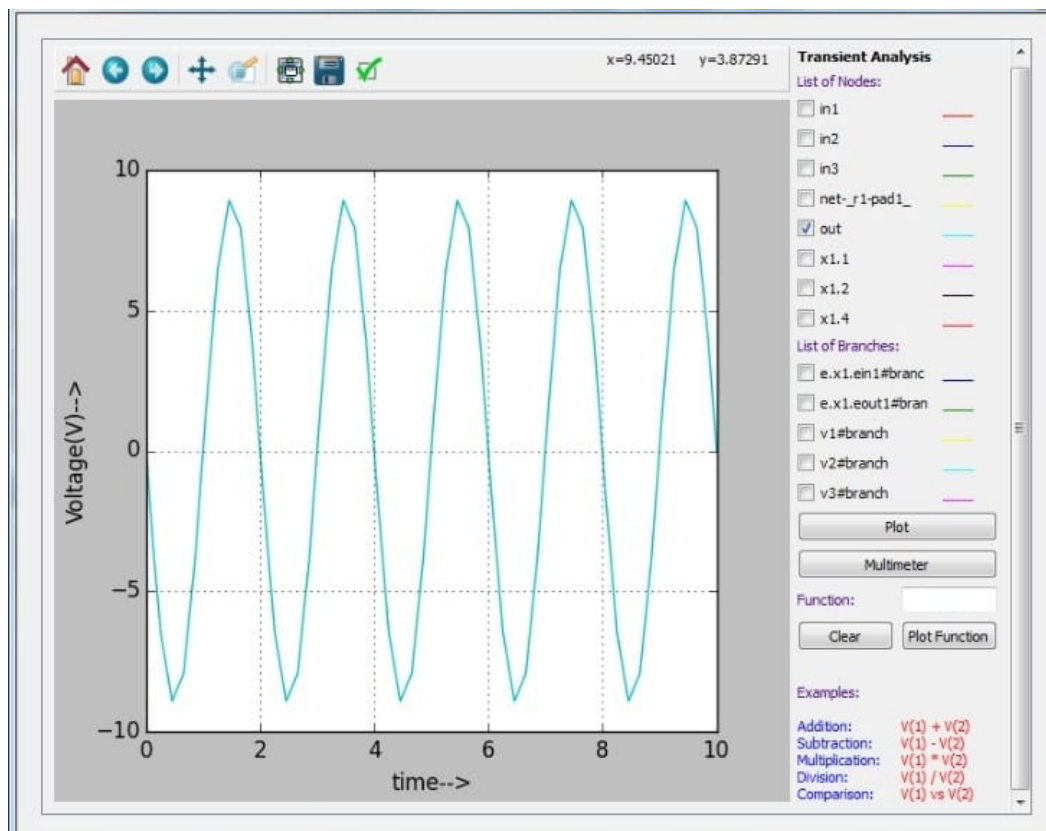

Input and Output voltage Plot

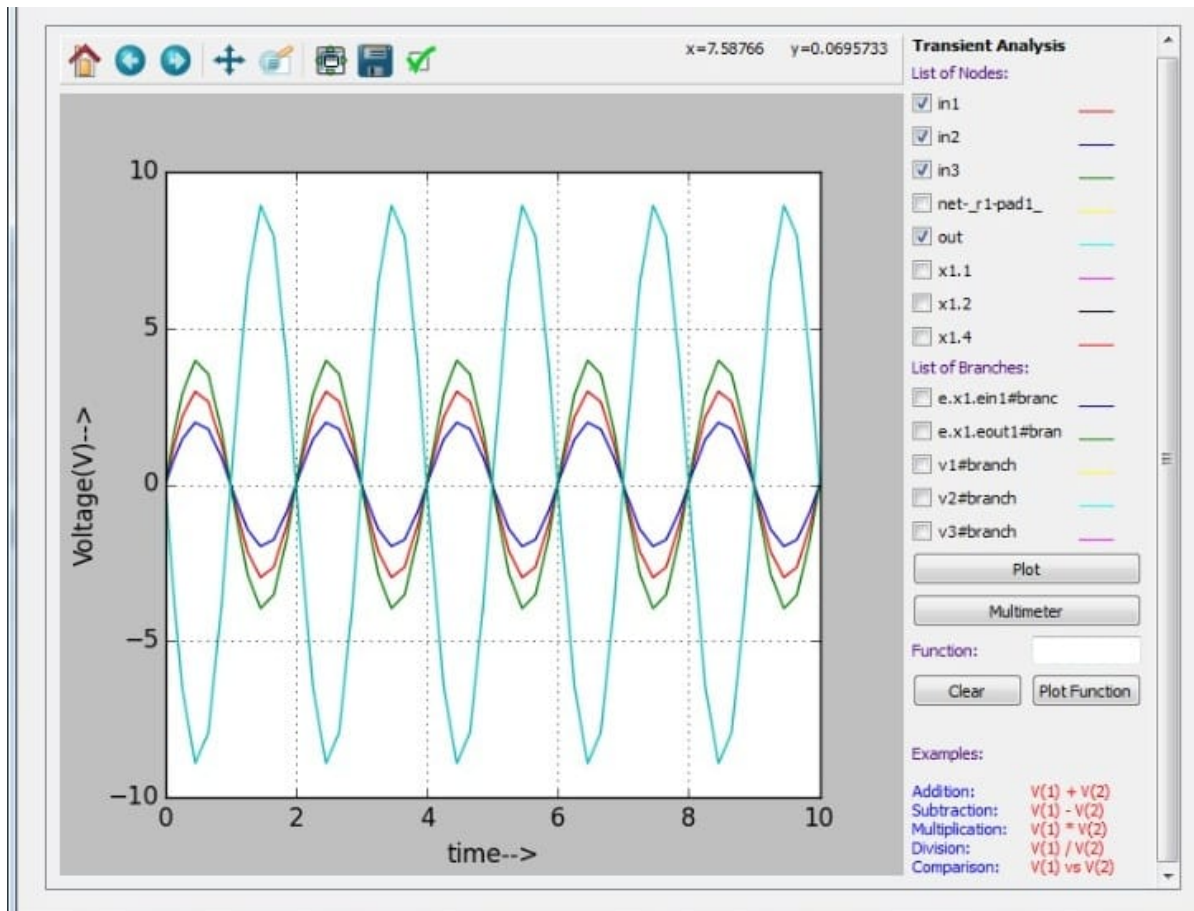

CONCLUSION:

Hence, we have designed an Inverting Summer and plotted the input and output waveforms using esim.

REFERENCES:

<https://www.electronicshub.org/summing-amplifier/>