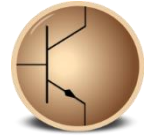




**VIT**<sup>®</sup>  
**Vellore Institute of Technology**  
(Deemed to be University under section 3 of UGC Act, 1956)



## **Circuit Simulation Project**

# **POSITIVE CLAMPER CIRCUIT USING LM741**

**Name of the participant: Ashita Banger**

**Project Guide: Dr. Subhashini N**

**Name of the Institution- Vellore Institute of Technology, Chennai**

**Title of the circuit: Positive Clamper circuit using LM741**

### **Theory/Description:**

A clamper is an electronic circuit that fixes either the positive or the negative peak excursions of a signal to a defined value by shifting its DC value.

The clamper does not restrict the peak-to-peak excursion of the signal; it moves the whole signal up or down so as to place the peaks at the reference level.

In clamper circuits a predetermined dc level is added to the output voltage. (or) The output is clamped to a desired dc level.

- If the clamped dc level is +ve, the clamper is **positive clamper**.
- If the clamped dc level is -ve, the clamper is **negative clamper**.


## Working:

A sinusoidal voltage signal, is applied to the inverting terminal of op-amp through a network that consists of a capacitor and a resistor. That means, AC voltage signal is applied to the inverting terminal of the op-amp.


The DC reference voltage  $V_{ref}$  is applied to the non-inverting terminal of the op-amp. The value of reference voltage  $V_{ref}$  can be chosen by varying the resistor. In this case, we will get a reference voltage  $V_{ref}$  of a positive value.

The circuit produces an output, which is the combination (resultant sum) of the sinusoidal voltage signal  $V_{in}$  and the reference voltage  $V_{ref}$ . That means, the clamper circuit produces an output in such a way that the sinusoidal voltage signal  $V_{in}$  gets shifted vertically upwards by the value of reference voltage  $V_{ref}$ .

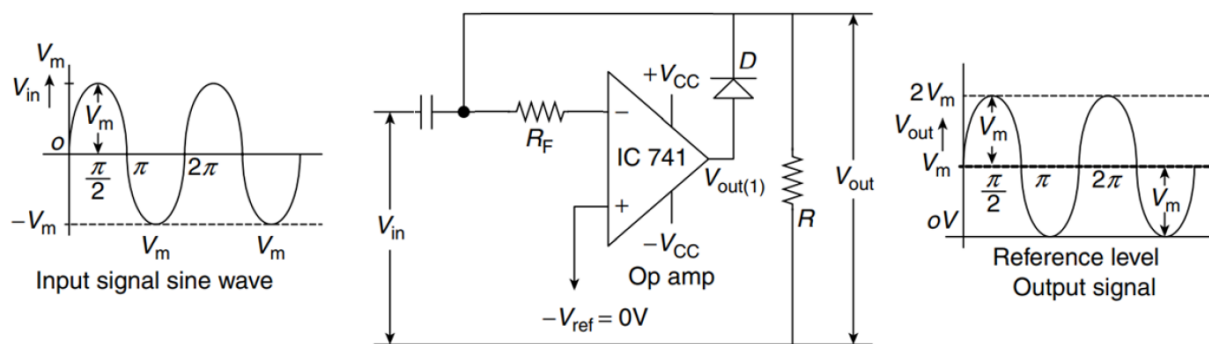
## Positive Clamper circuit with zero reference voltage




## Circuit Diagram:

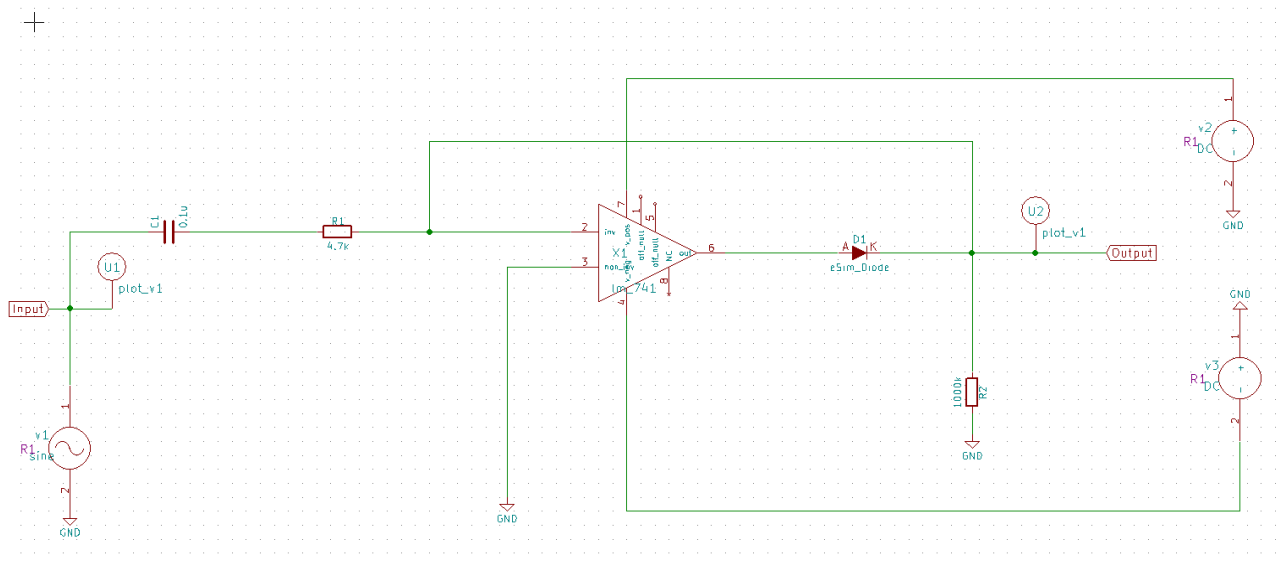


### Input Waveform

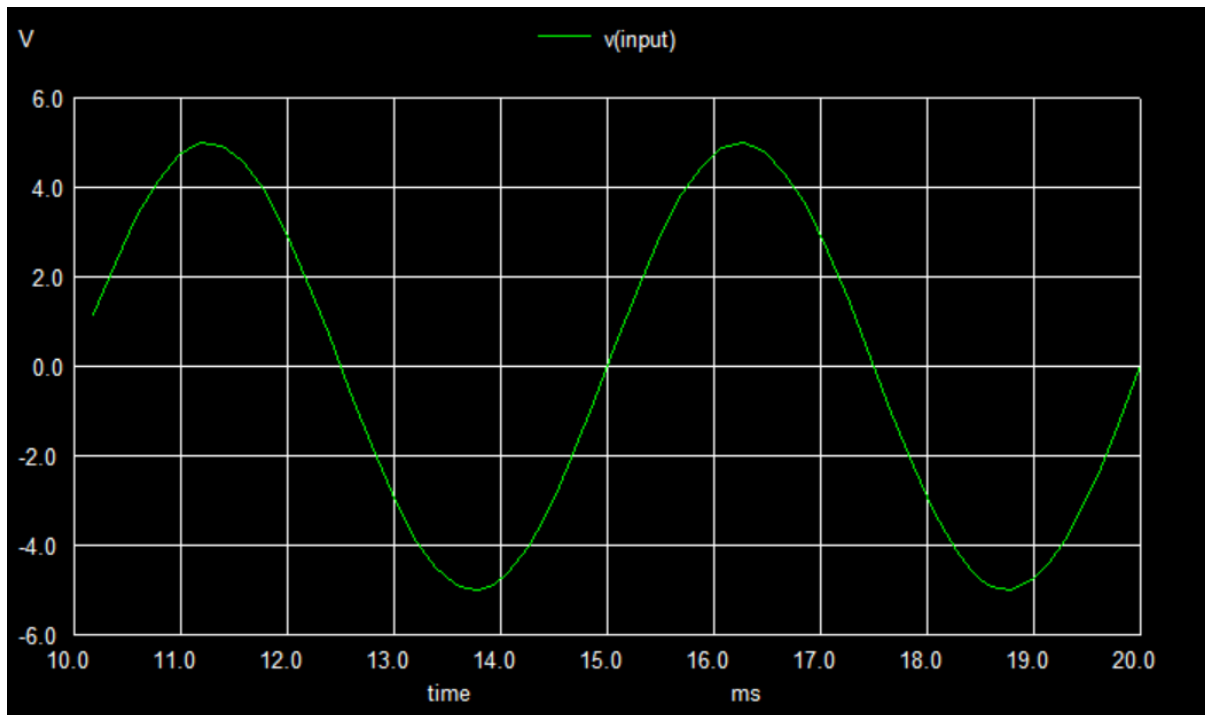

### Output Waveform

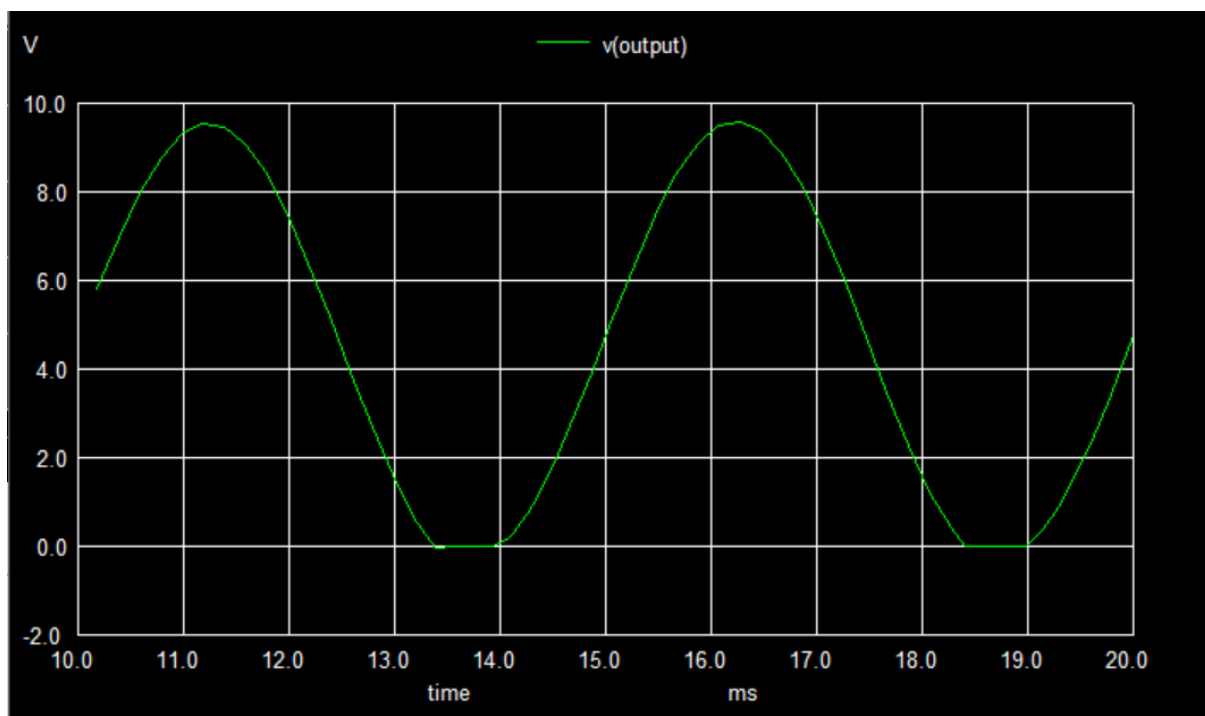

## Python Plot

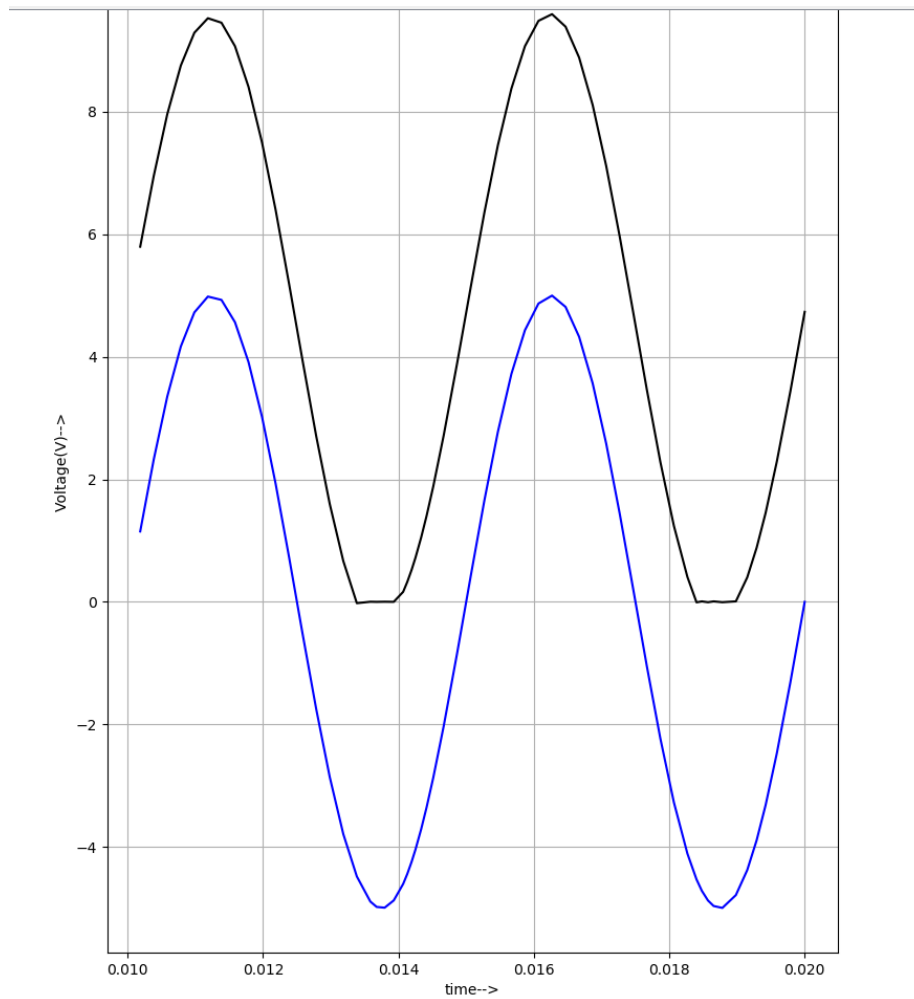

---- Input voltage plot

---- Output voltage plot

**Conclusion:** Hence a positive clamper circuit using LM741 op- amp has been designed and simulated using eSim software.

### References:

[https://www.wikiwand.com/en/Clamper\\_\(electronics\)](https://www.wikiwand.com/en/Clamper_(electronics))

<https://www.electronicshub.org/ic-741-op-amp-basics/>

<https://www.electrical4u.com/clamping-circuit/>