

0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10	1	0	1	0	X	X	X	X
11	1	0	1	1	X	X	X	X
12	1	1	0	0	X	X	X	X
13	1	1	0	1	X	X	X	X
14	1	1	1	0	X	X	X	X
15	1	1	1	1	X	X	X	X

From the above truth table we observe,

$$W = A + BC + BD$$

$$X = B'C + B'D + BC'D'$$

$$Y = CD + C'D'$$

$$Z = D'$$

Circuit Diagram:

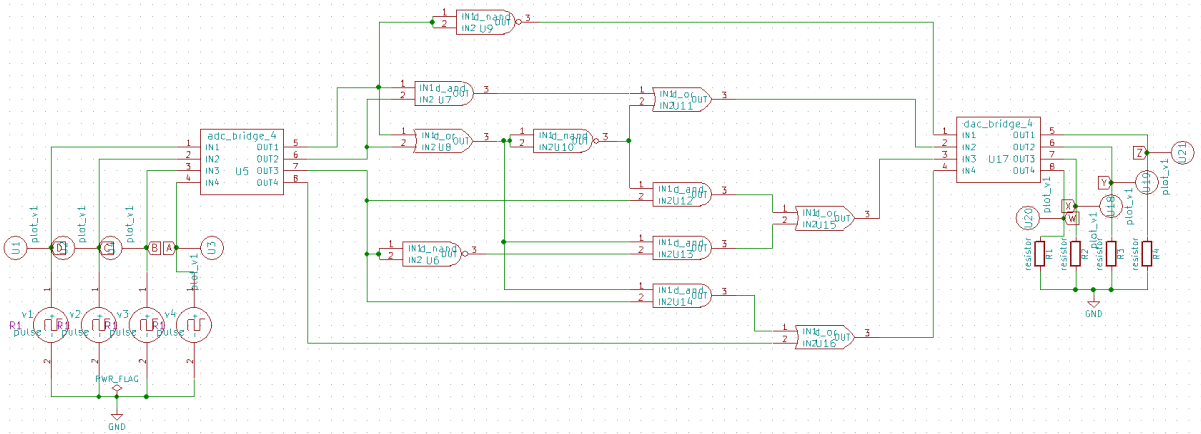


Fig. 1: Main circuit

Fig. 1 represents the schematic for the main circuit. The pulse sources feed the inputs from 0000 to 1111. The ADC bridge is used to convert the analog voltage source inputs into digital bits to be used with the digital gates. The DAC bridge is used to convert the digital signals back to analog so that they can be plotted and viewed as output.

Results (Input, Output waveforms):

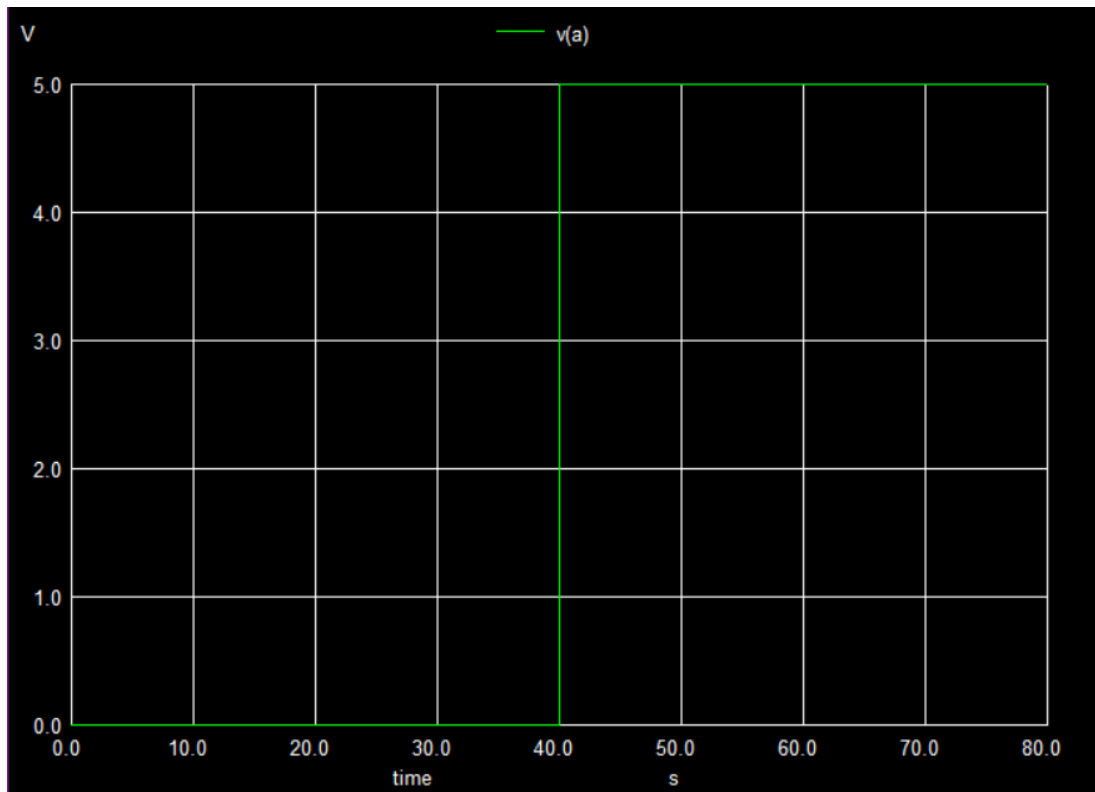


Fig. 2a: Analog signal for A (MSB)

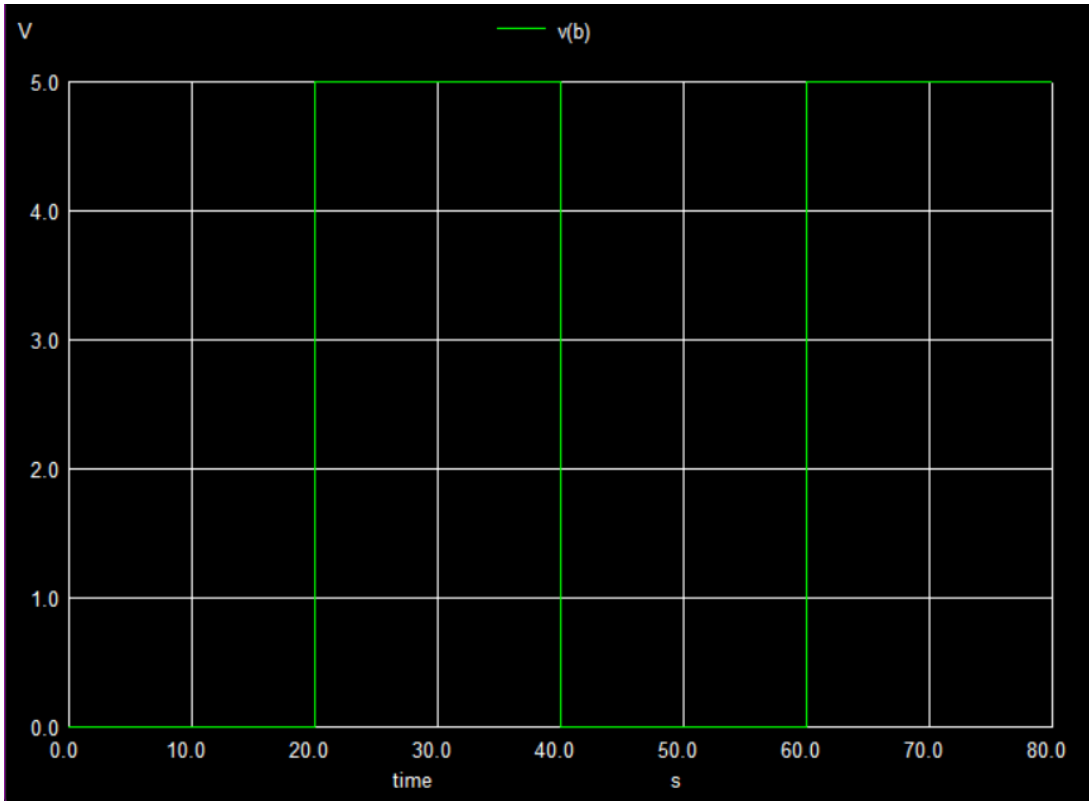


Fig. 2b: Analog signal for B

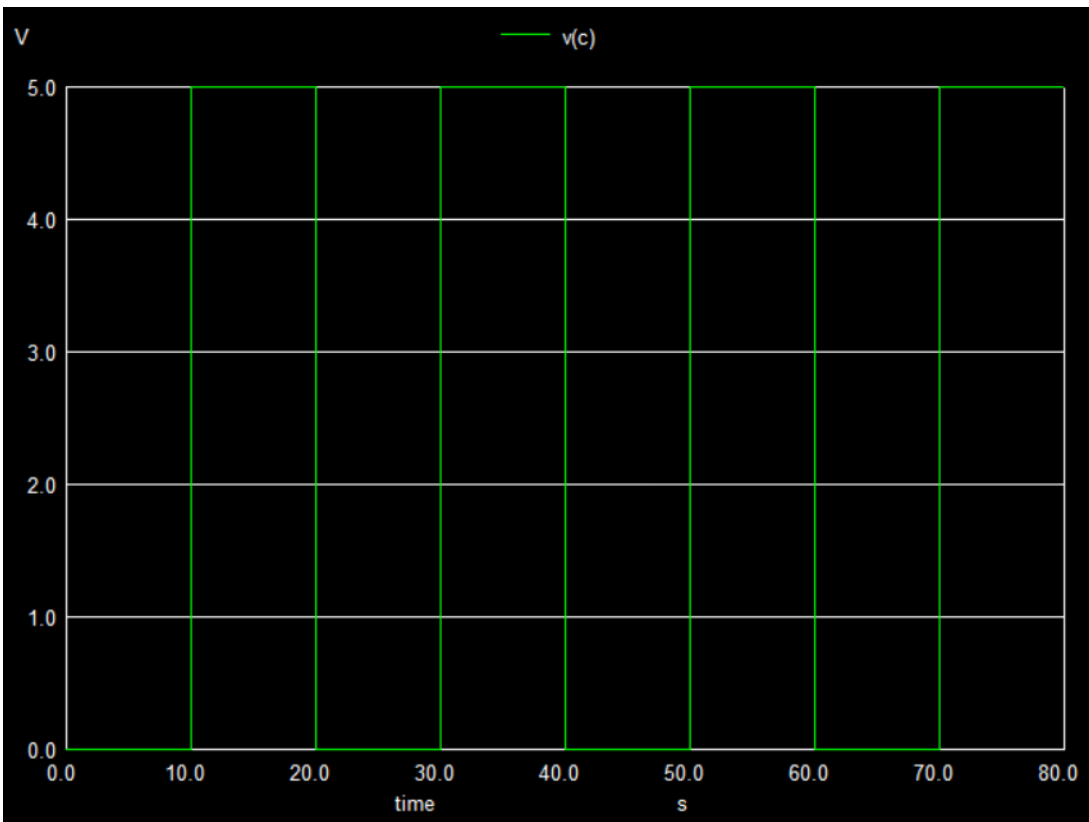


Fig. 2c: Analog signal for C

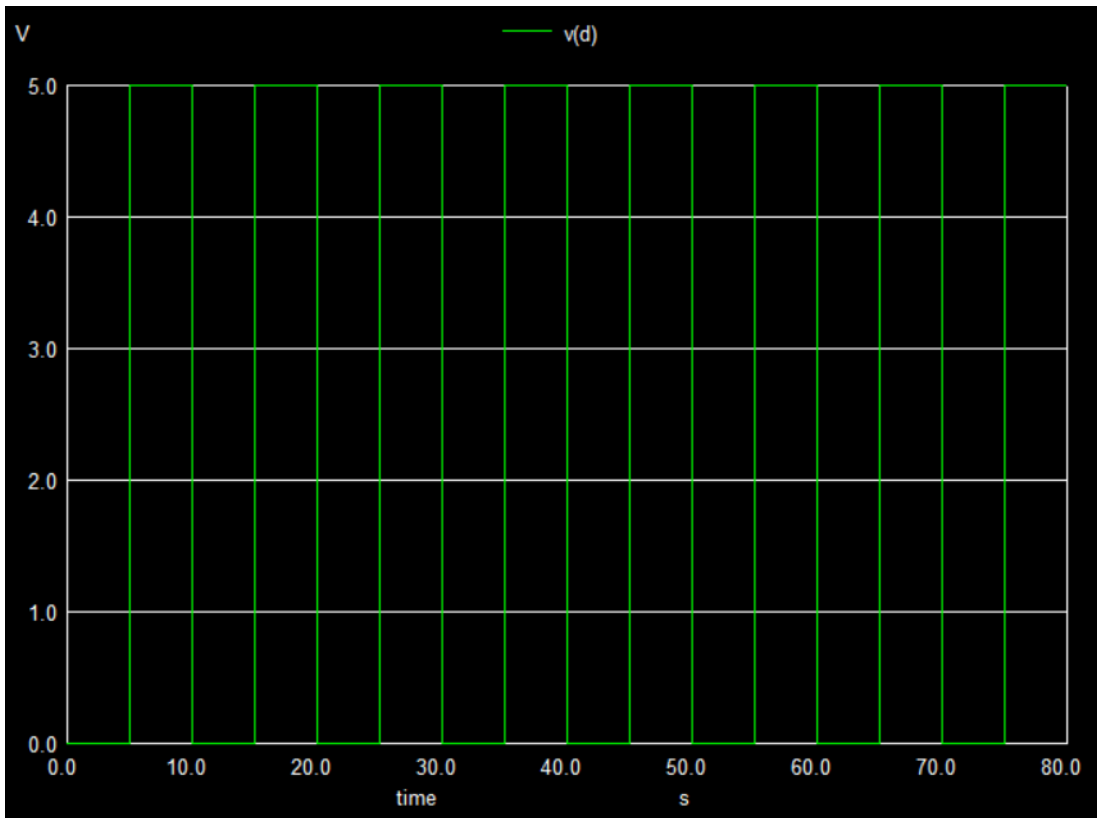


Fig. 2d: Analog signal for D (LSB)

Figures 2a through 2d show the analog signals for each of the inputs bits (BCD code).

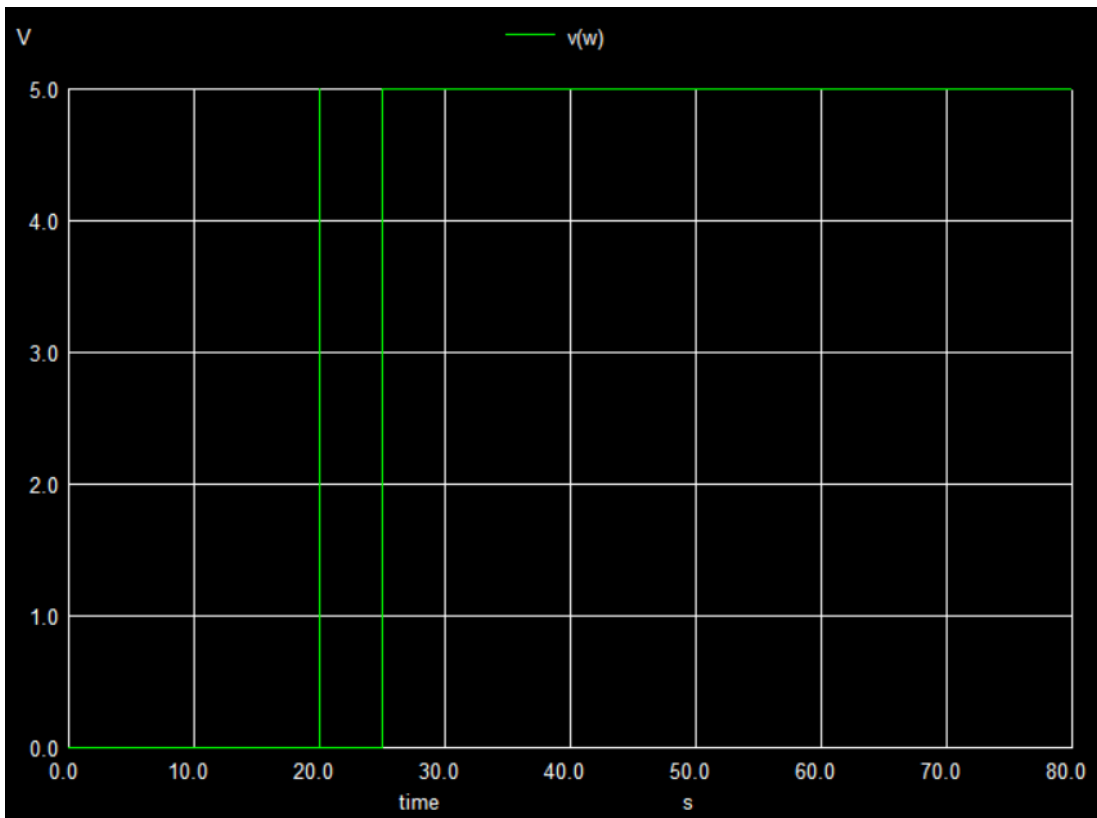


Fig. 3a: Analog signal for W (MSB)

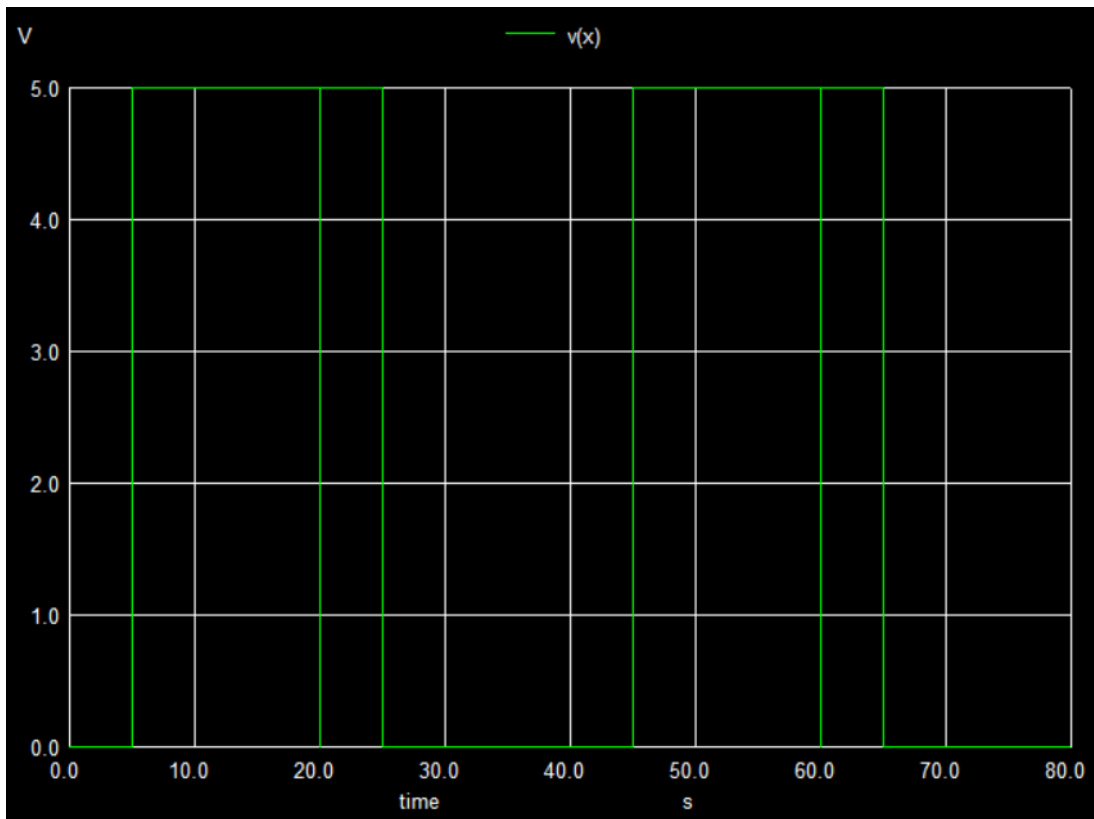


Fig. 3b: Analog signal for X

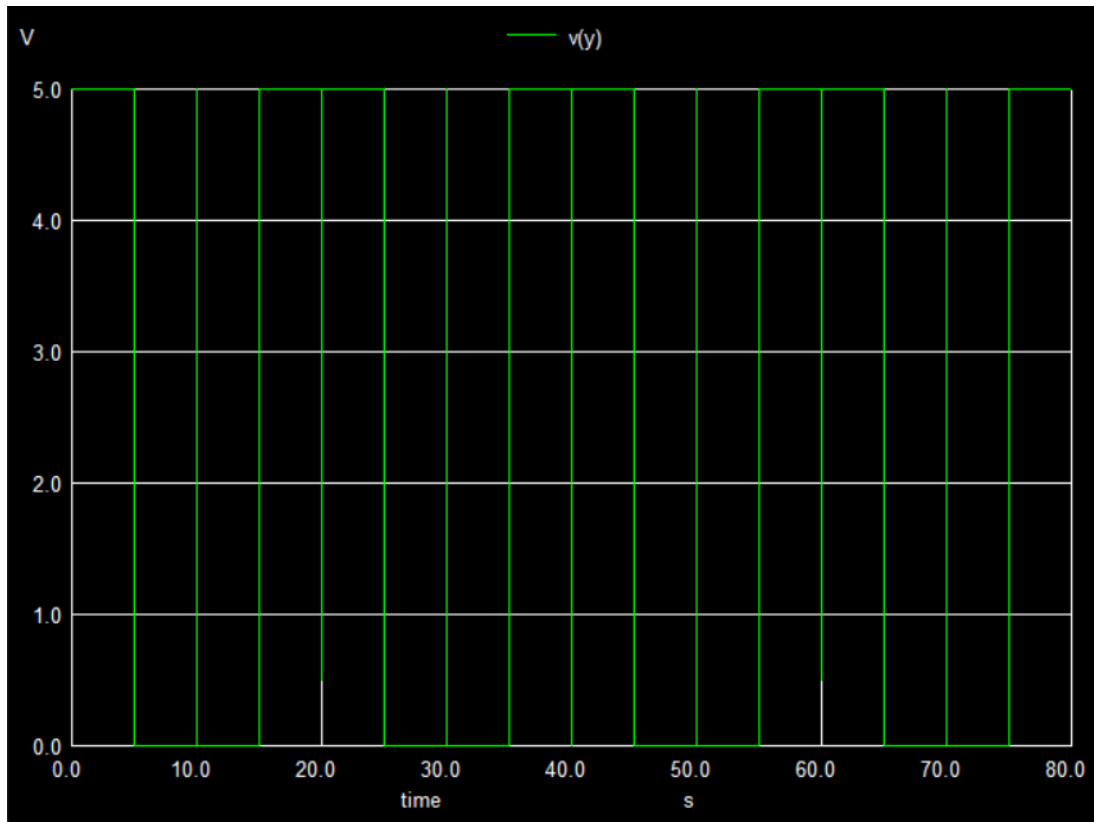


Fig. 3c: Analog signal for Y

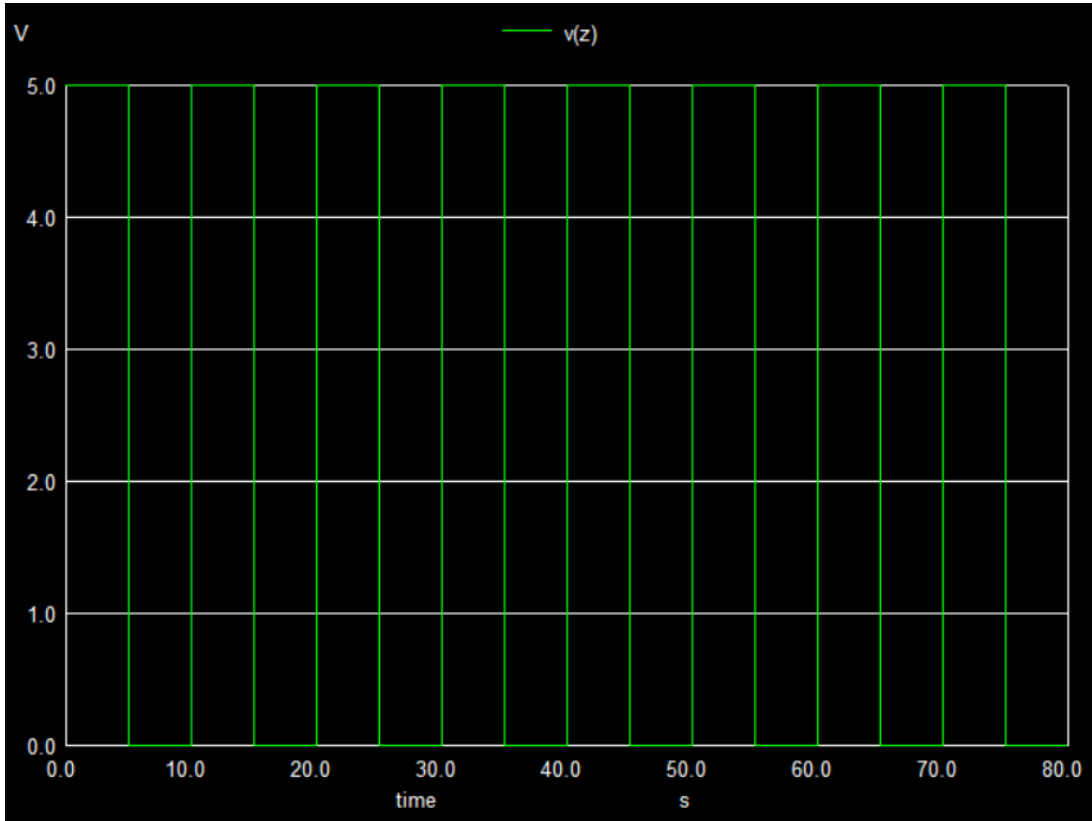


Fig. 3d: Analog signal for Z (LSB)

Figures 3a through 3d display show the output analog signals for each of the output bits (Excess-3 code).

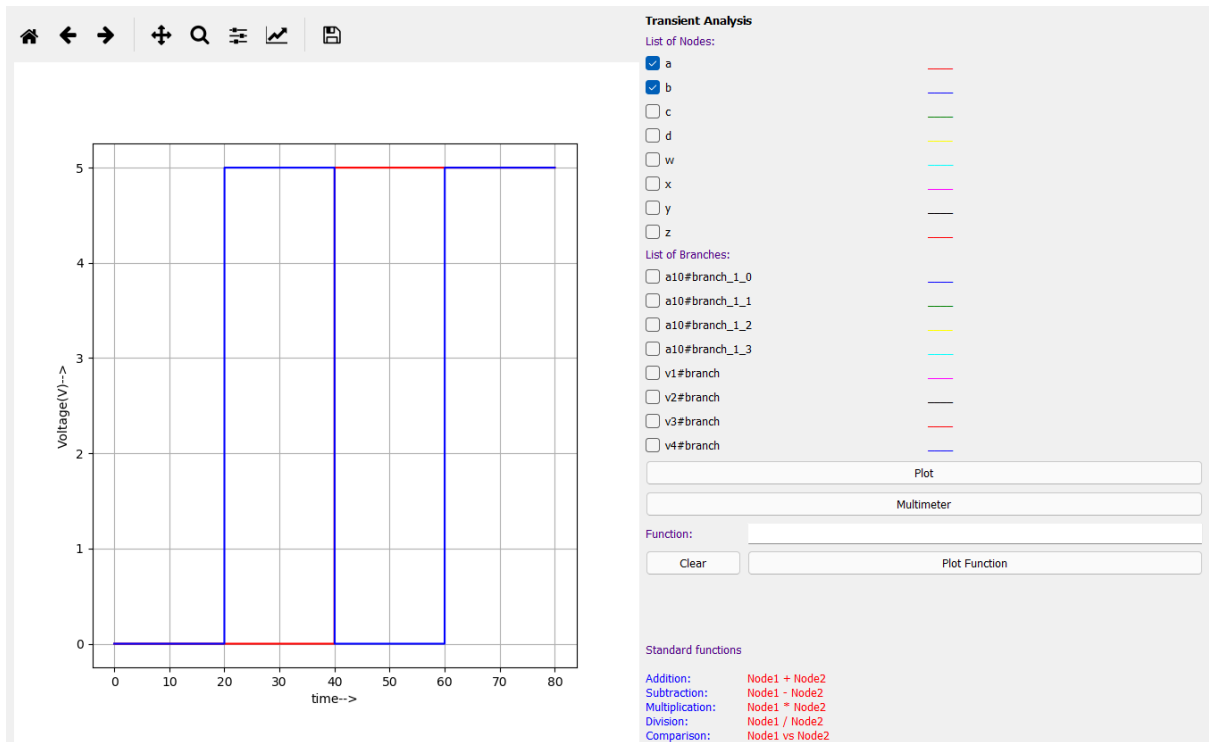


Fig. 4a: Python plots for A and B

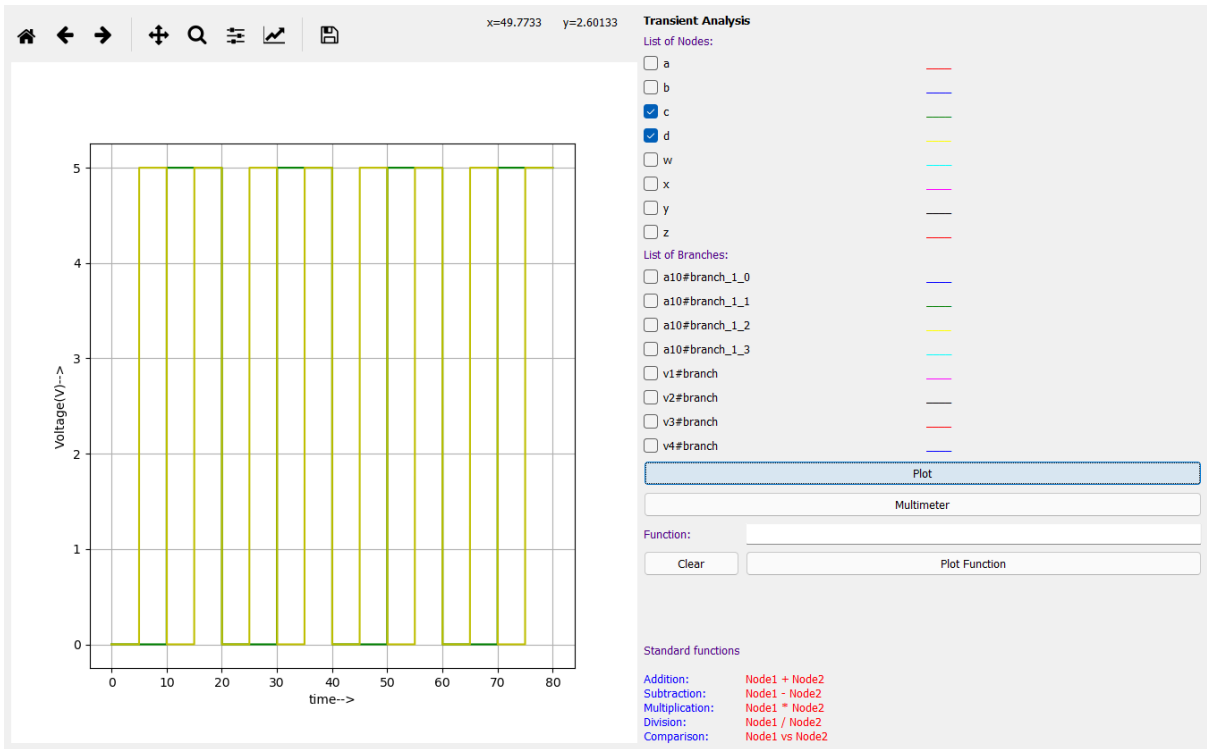


Fig. 4b: Python plots for C and D

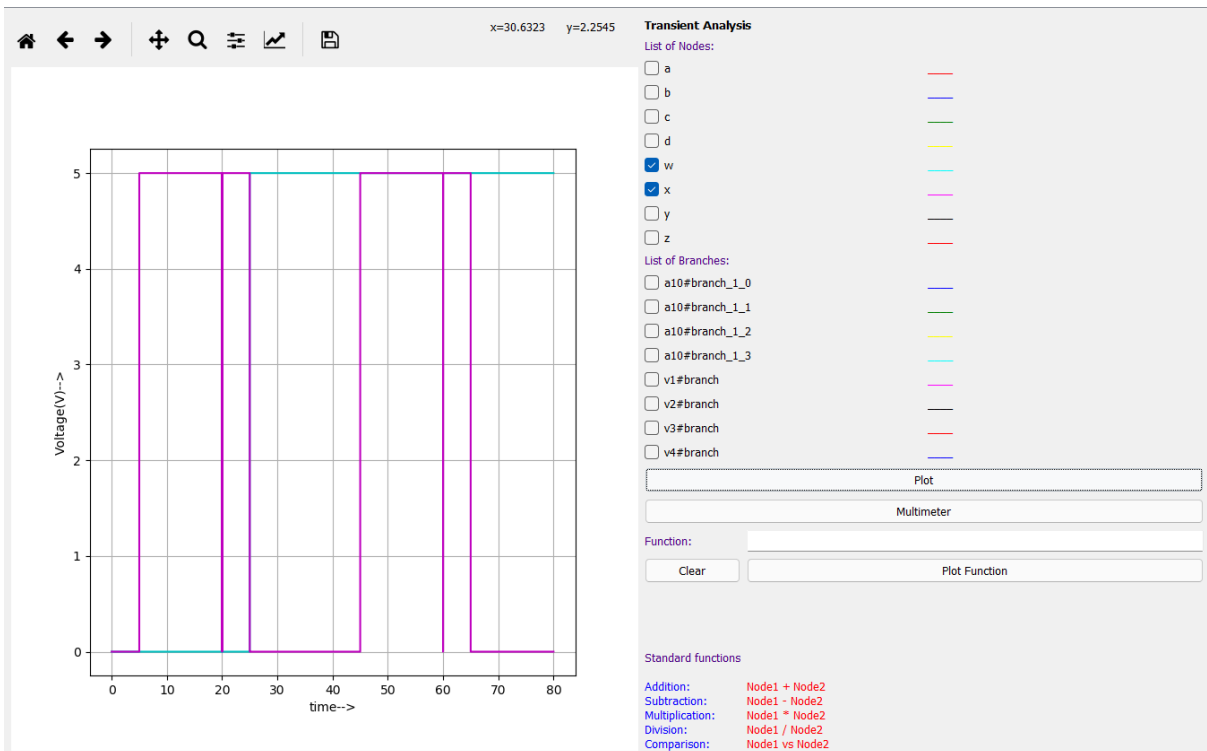


Fig. 4c: Python plots for W and X

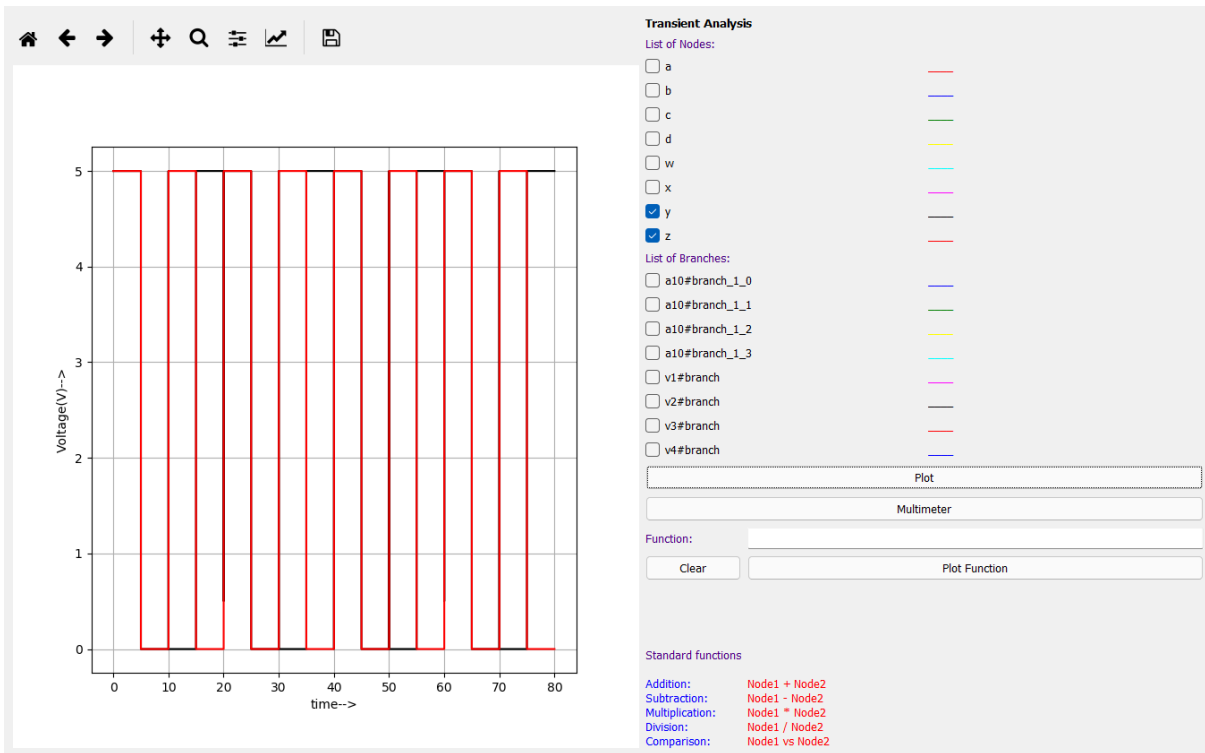


Fig. 4d: Python plots for Y and Z

Figures 4a through 4d show the python plots for the same signals for better visualisation.

Simulation parameters for reference:

Add parameters for pulse source v1

Enter initial value(Volts/Amps):	0
Enter pulsed value(Volts/Amps):	5
Enter delay time (seconds):	5
Enter rise time (seconds):	0
Enter fall time (seconds):	0
Enter pulse width (seconds):	5
Enter period (seconds):	10

Add parameters for pulse source v2

Enter initial value(Volts/Amps):	0
Enter pulsed value(Volts/Amps):	5
Enter delay time (seconds):	10
Enter rise time (seconds):	0
Enter fall time (seconds):	0
Enter pulse width (seconds):	10
Enter period (seconds):	20

Fig. 5a

Add parameters for pulse source v3

Enter initial value(Volts/Amps):	0
Enter pulsed value(Volts/Amps):	5
Enter delay time (seconds):	20
Enter rise time (seconds):	0
Enter fall time (seconds):	0
Enter pulse width (seconds):	20
Enter period (seconds):	40

Add parameters for pulse source v4

Enter initial value(Volts/Amps):	0
Enter pulsed value(Volts/Amps):	5
Enter delay time (seconds):	40
Enter rise time (seconds):	0
Enter fall time (seconds):	0
Enter pulse width (seconds):	40
Enter period (seconds):	80

Fig. 5b

Transient Analysis

Start Time	<input type="text" value="0"/>	Sec	▼
Step Time	<input type="text" value="10"/>	ms	▼
Stop Time	<input type="text" value="80"/>	Sec	▼

Fig. 5c

Source / Reference:

<https://www.javatpoint.com/conversion-of-bcd-to-excess-3-code-in-digital-electronics>
(BCD to Excess-3 conversion)