



**VIT**<sup>®</sup>  
Vellore Institute of Technology  
(Deemed to be University under section 3 of UGC Act, 1956)



## **Circuit Simulation Project**

<https://esim.fossee.in/circuit-simulation-project>

**Name of the Participant:** Dikshita Mehta (20BCE1056)

**Project Guide:** Dr R. Maheshwari

**Title of the Circuit:** 3-Bit Asynchronous Down Counter

### **Description:**

Counters are used to count the clock pulses. The clock pulses occur at regular intervals. They are used to measure the time and frequency.


In an asynchronous counter, an external clock is provided only for the first flip flop, therefore output of the first flip flop acts as a clock pulse for the second flip flop and so on.

Asynchronous counters are also known as ripple counters and are formed by the successive combination of trailing edge-triggered flip-flops.

Asynchronous counters are those whose output is free from the clock signal. Because the flip flops in asynchronous counters are supplied with different clock signals, there may be delay in producing output.

These are used in applications where low power consumption is required. And are also used in frequency divider circuits, ring and Johnson counters.

CIRCUIT DIAGRAM:

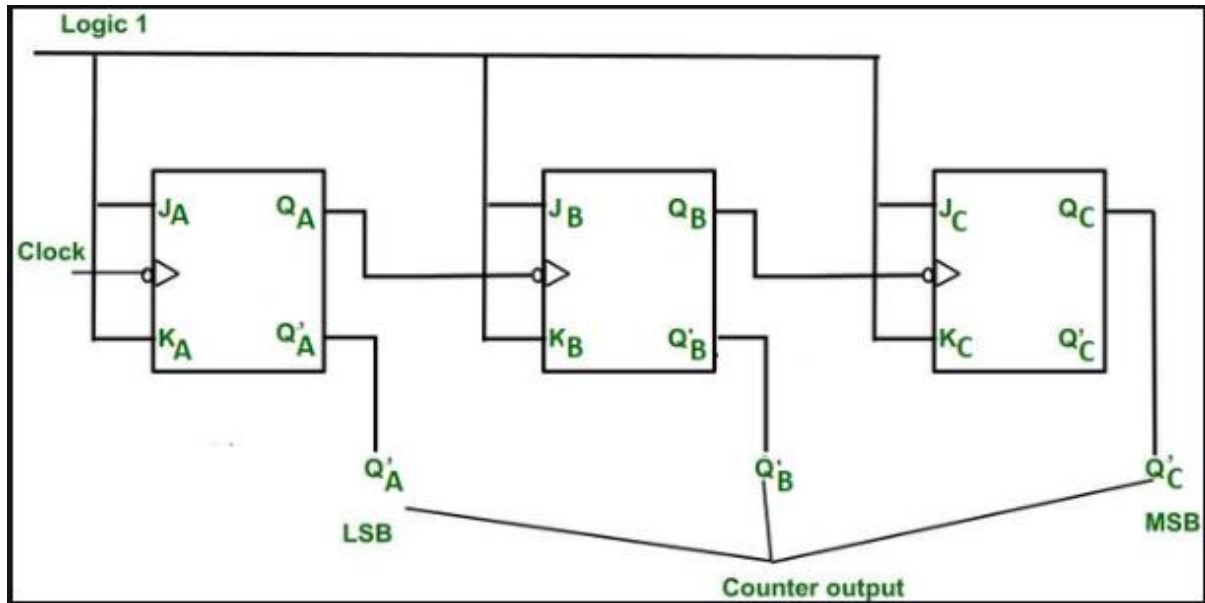


For a 3 bit asynchronous counter, 3 flip flops are required and  $2^3=8$  states can be generated.

In this implementation, the clock pulse is given to only the first flip flop. Therefore, the output of the first flip flop is fed as a clock to the second flip flop and the output of the second flip flop is fed as the clock for the third flip flop. But the complemented output is taken from each flip flop (i.e same as Up counter but output states are complemented). Here  $Q_a$  is LSB and  $Q_c$  is MSB.

TRUTH TABLE:

Clock	$Q_C$	$Q_B$	$Q_A$	$Q'_C$	$Q'_B$	$Q'_A$
Initially	0	0	0	1	1	1
1st	0	0	1	1	1	0
2nd	0	1	0	1	0	1
3rd	0	1	1	1	0	0
4th	1	0	0	0	1	1
5th	1	0	1	0	1	0
6th	1	1	0	0	0	1
7th	1	1	1	0	0	0

## e-Sim Schematic

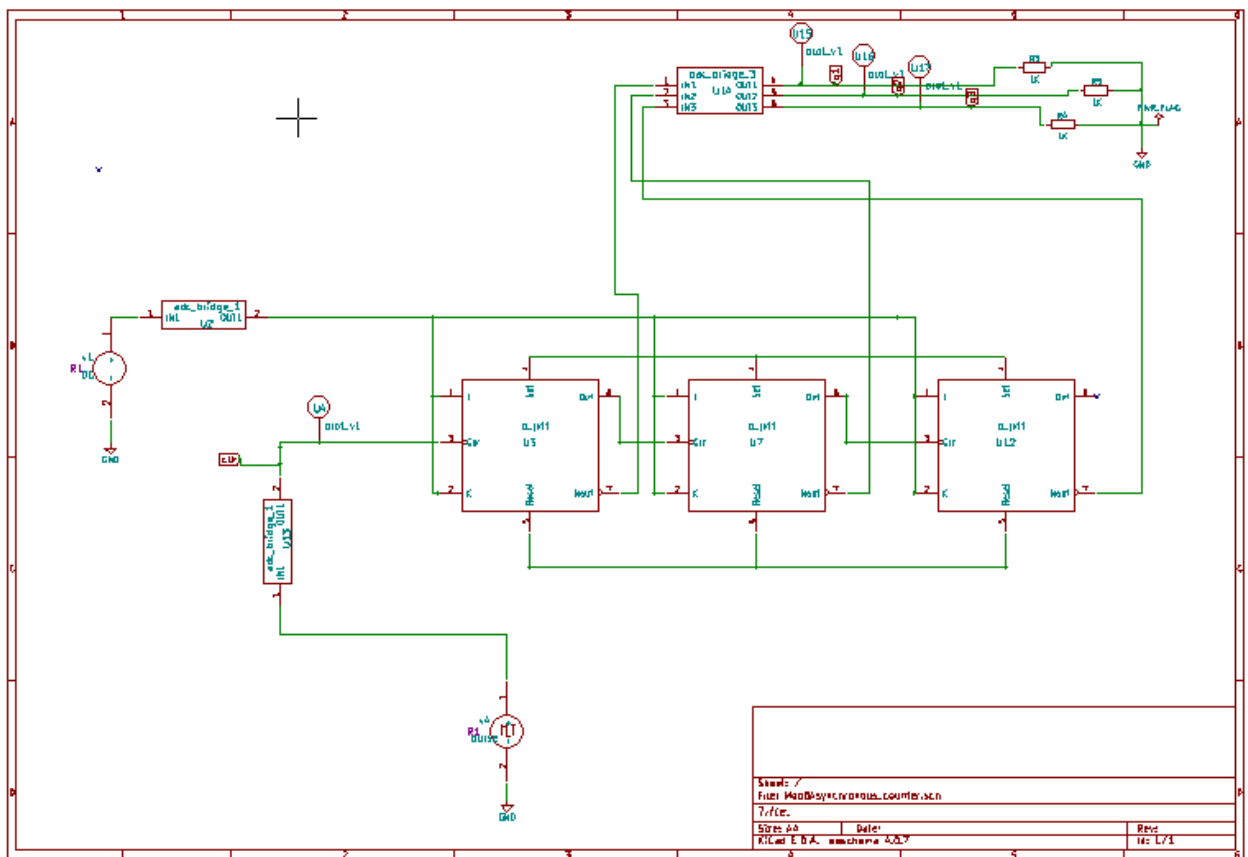


In this circuit,  $Q_1$  represents LSB and  $Q_3$  represents MSB.


### Simulation Results:

#### 1. NG Spice Waveforms:


$Q_1'$  (LSB):

 


$Q_2'$ :

 

### $Q'_3$ (MSB)

 


### Clk (Clock pulse):

 


## 2. Python Waveforms:


$Q'_1$  (LSB):

 


$Q_2'$ :

 

$Q_3'$  (MSB):

 

Transient Analysis:

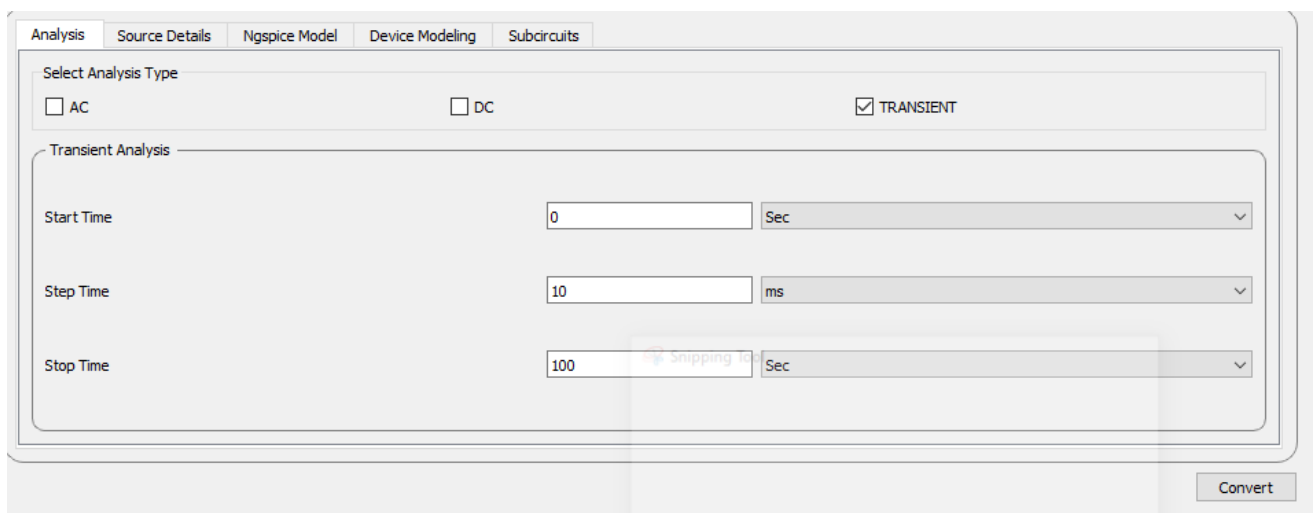



## Source Details:

Analysis Source Details Ngspice Model Device Modeling Subcircuits

Add parameters for pulse source v4

Enter initial value(Volts/Amps):	0
Enter pulsed value(Volts/Amps):	5
Enter delay time (seconds):	5
Enter rise time (seconds):	0
Enter fall time (seconds):	0
Enter pulse width (seconds):	5
Enter period (seconds):	10

Add parameters for DC source v1

Enter value(Volts/Amps):	5
--------------------------	---

Convert

## Conclusion:

Thus, 3-bit asynchronous down counter was designed and verified using JK flipflops on esim.

## References:

<https://www.geeksforgeeks.org/asynchronous-down-counter/>

<https://www.electronicshub.org/asynchronous-counter/>

<https://electronicscoach.com/asynchronous-counter.html>