

0	0	0	0	0	X	X	X	X
1	0	0	0	1	X	X	X	X
2	0	0	1	0	X	X	X	X
3	0	0	1	1	0	0	0	0
4	0	1	0	0	0	0	0	1
5	0	1	0	1	0	0	1	0
6	0	1	1	0	0	0	1	1
7	0	1	1	1	0	1	0	0
8	1	0	0	0	0	1	0	1
9	1	0	0	1	0	1	1	0
10	1	0	1	0	0	1	1	1
11	1	0	1	1	1	0	0	0
12	1	1	0	0	1	0	0	1
13	1	1	0	1	X	X	X	X
14	1	1	1	0	X	X	X	X
15	1	1	1	1	X	X	X	X

From the above truth table we observe,

$$W = AD + ACD$$

$$B = X'Y' + X'Z' + XYZ$$

$$C = Y'Z + YZ'$$

$$D = Z'$$

Circuit Diagram(s) :

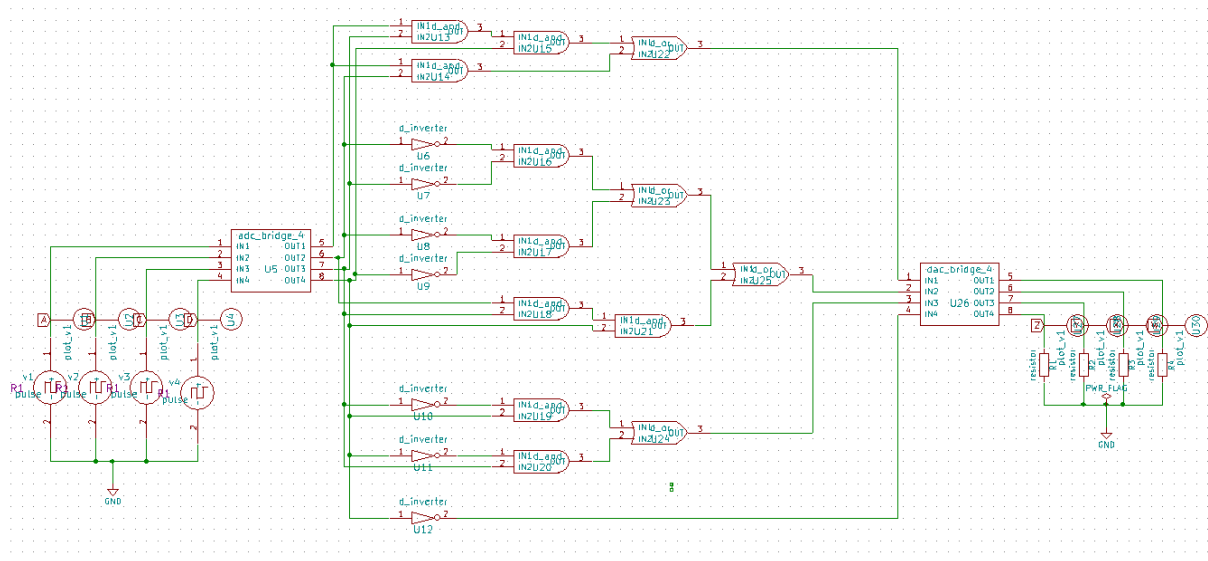


Fig. 1: Main Circuit

Fig. 1 represents the schematic for the main circuit. The pulse sources feed the inputs from 0000 to 1111. The ADC bridge is used to convert the analog voltage source inputs into digital bits to be used with the digital gates. The DAC bridge is used to convert the digital signals back to analog so that they can be plotted and viewed as output.

Results (Input, Output waveforms and/or Multimeter readings) :

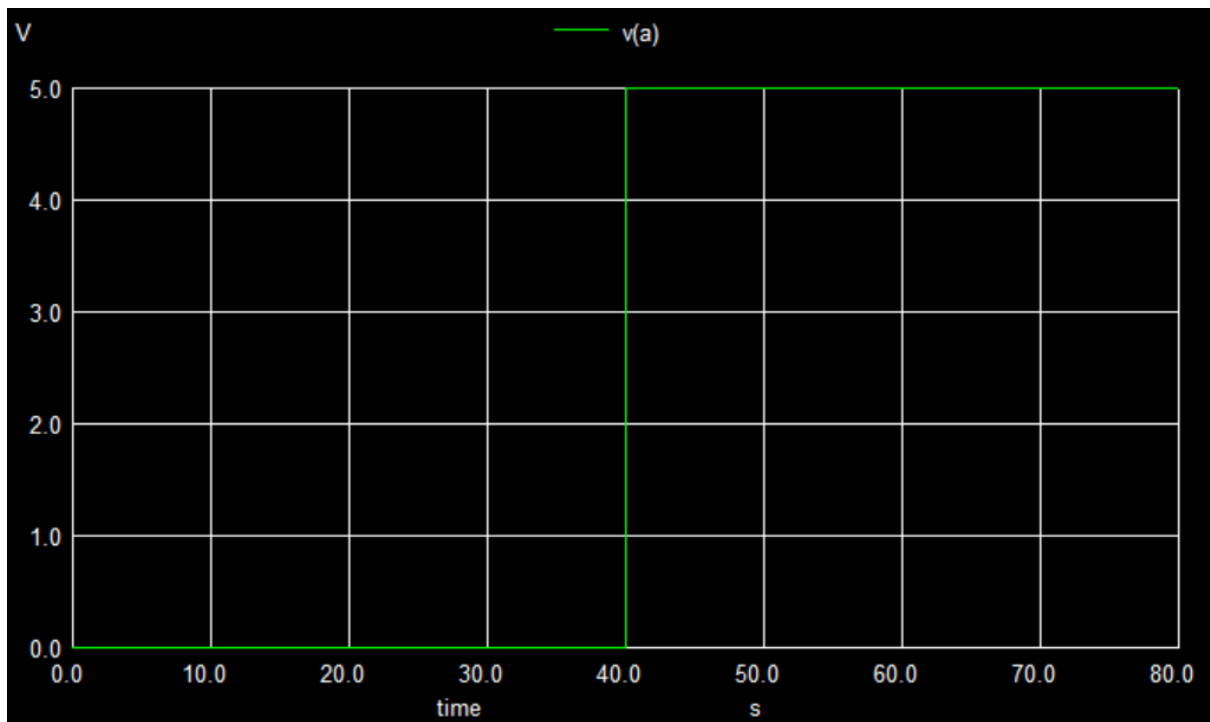


Fig. 2a: Analog signal for A (MSB)

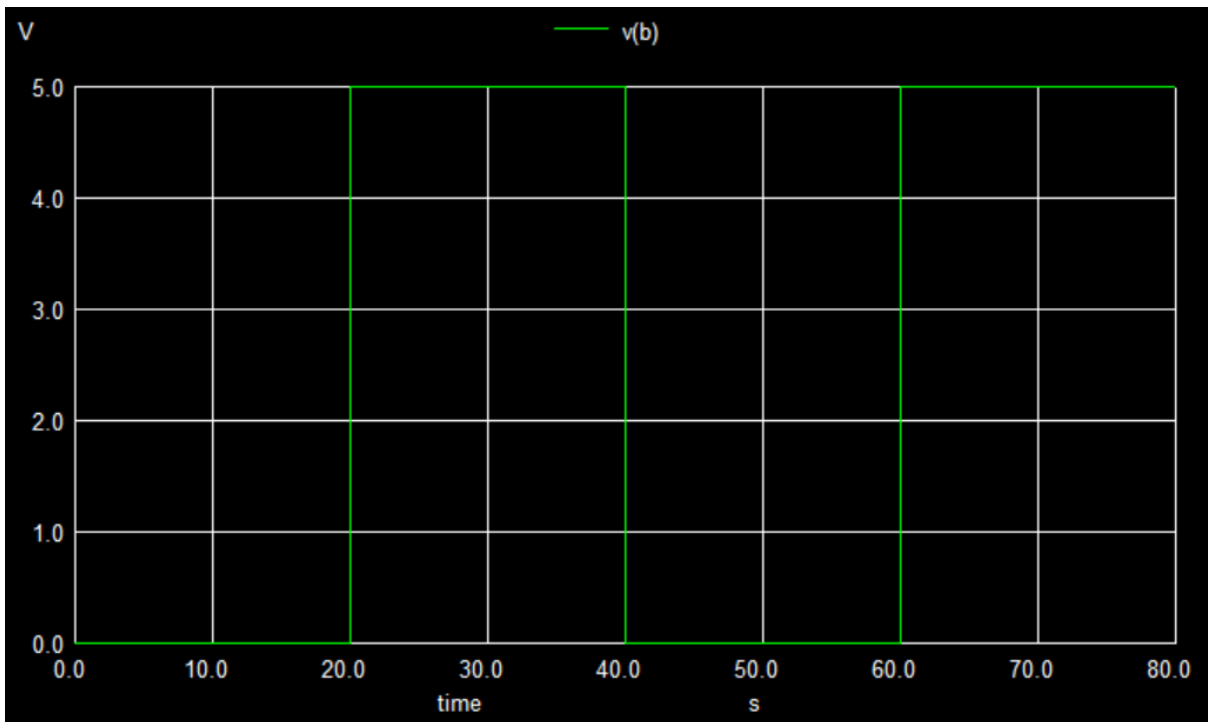


Fig. 2b: Analog signal for B

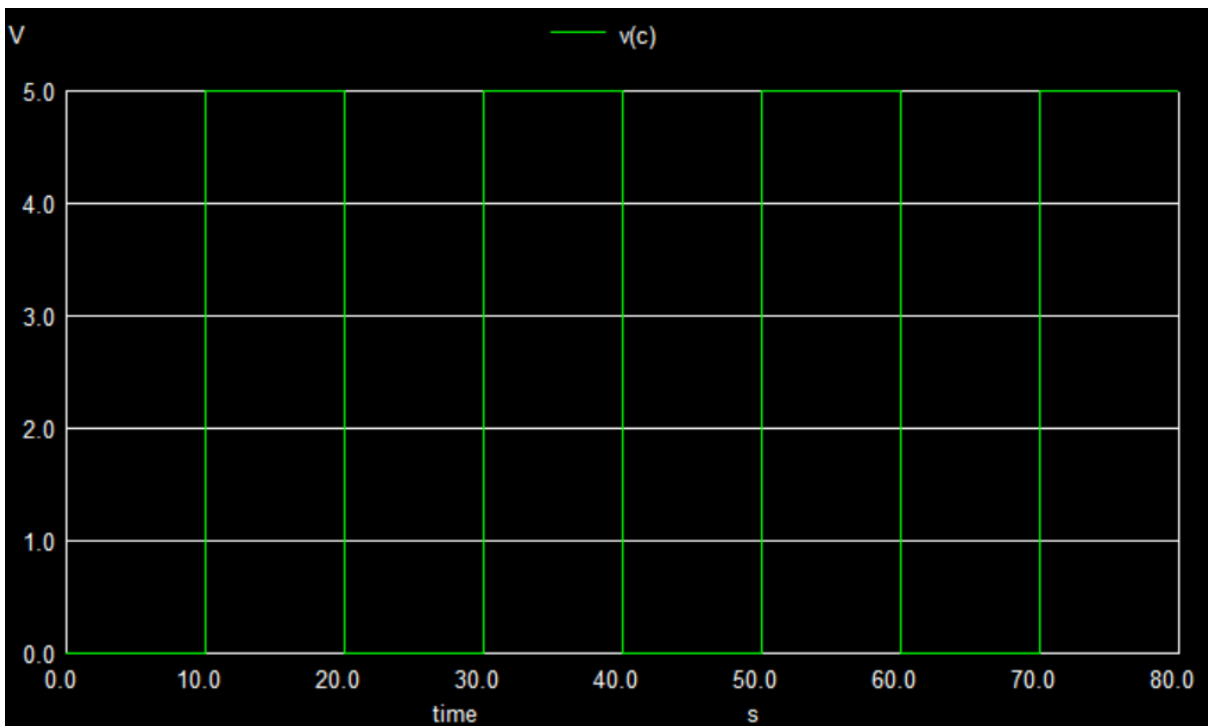


Fig. 2c: Analog signal for C

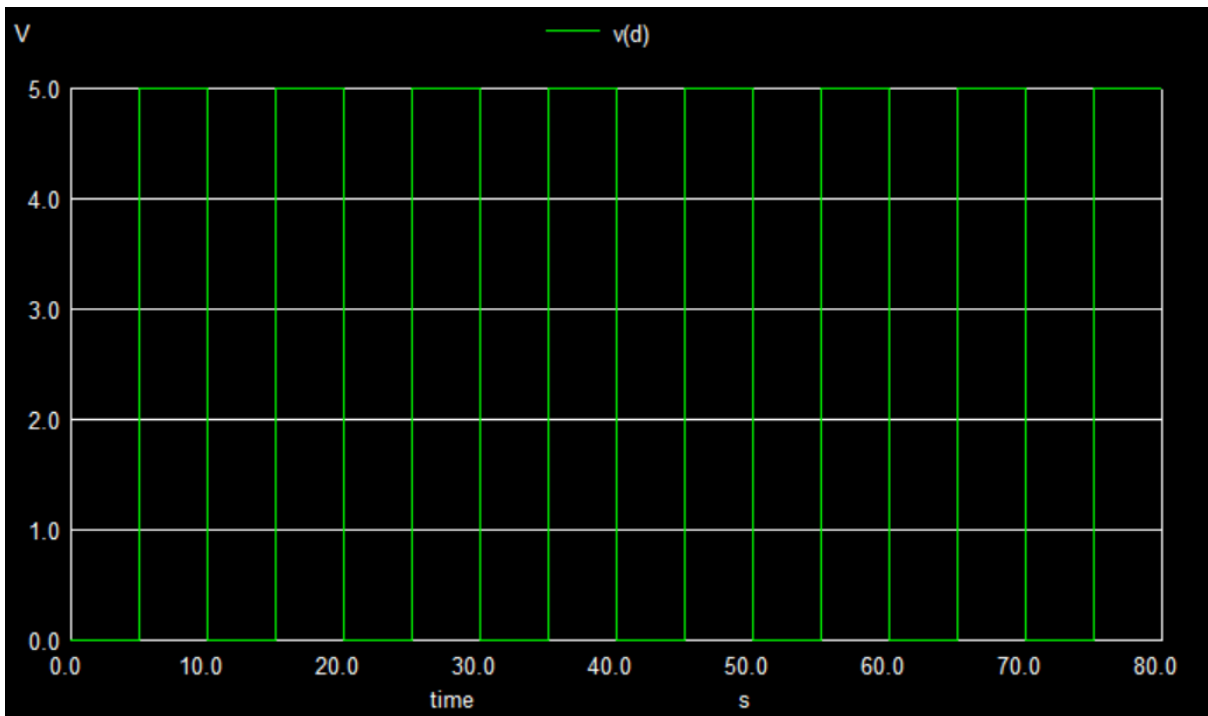


Fig. 2d: Analog signal for D (LSB)

Figures 2a through 2d show the analog signals for each of the inputs bits (Excess-3 Code).

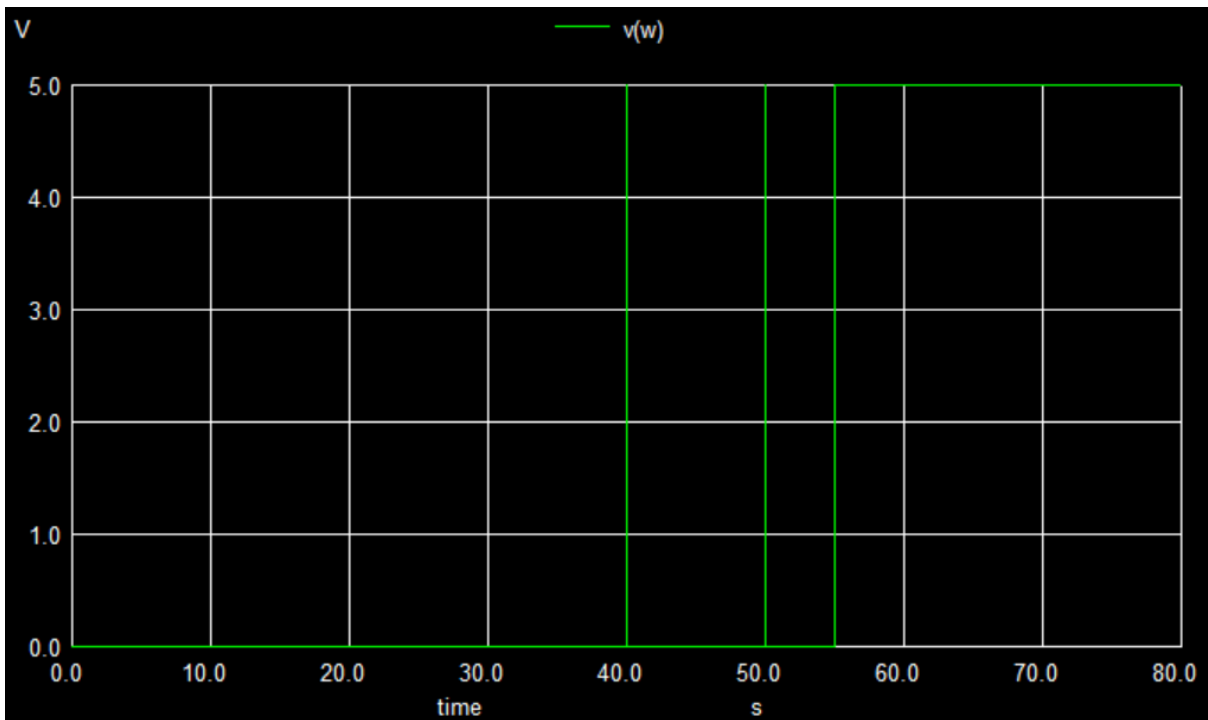


Fig. 3a: Analog signal for W (MSB)

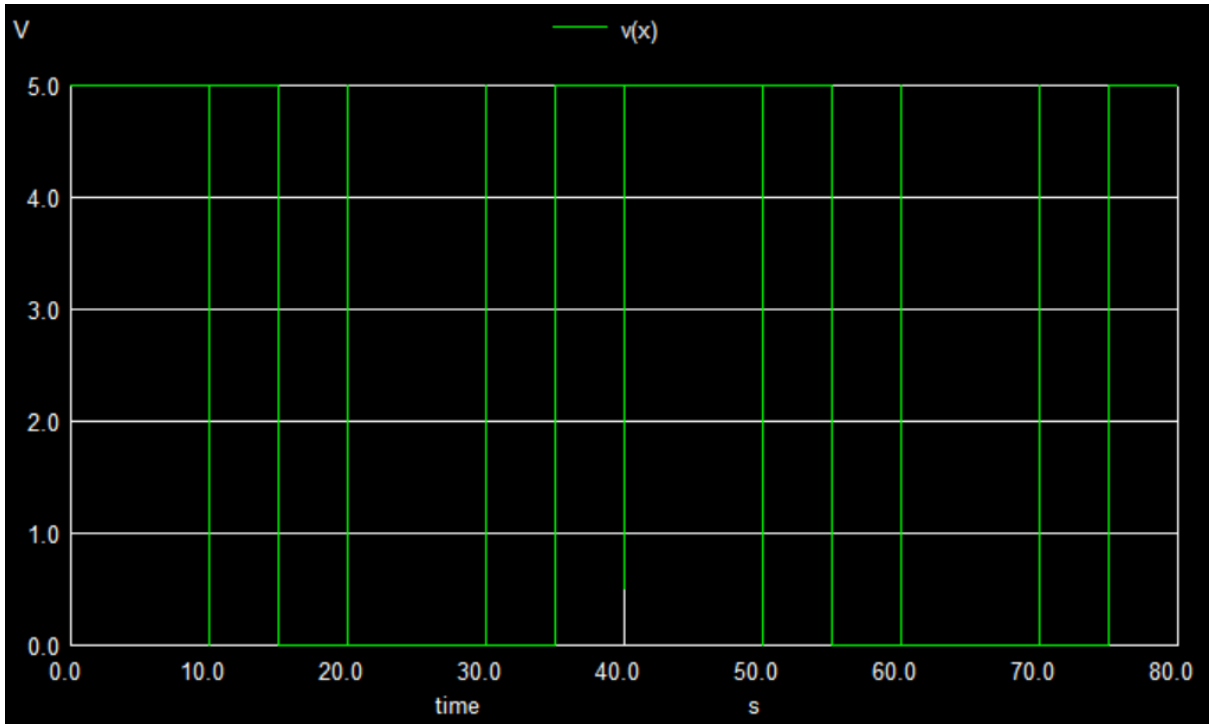


Fig. 3b: Analog signal for X

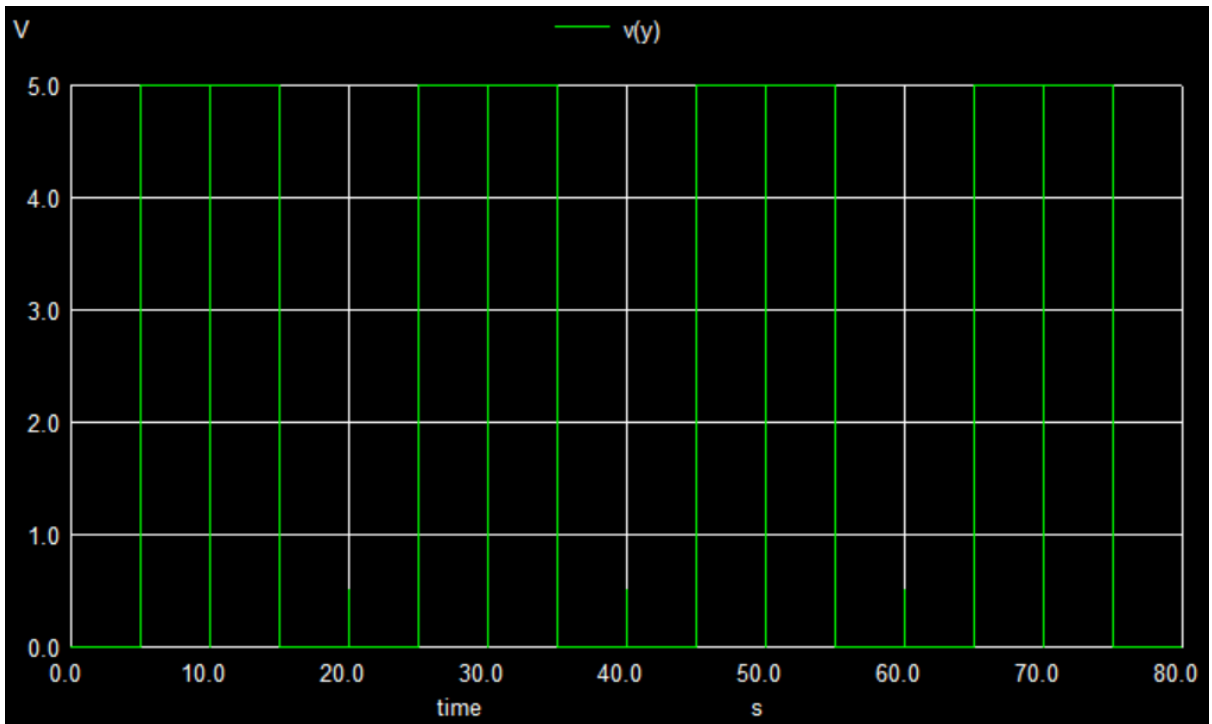


Fig. 3c: Analog signal for Y

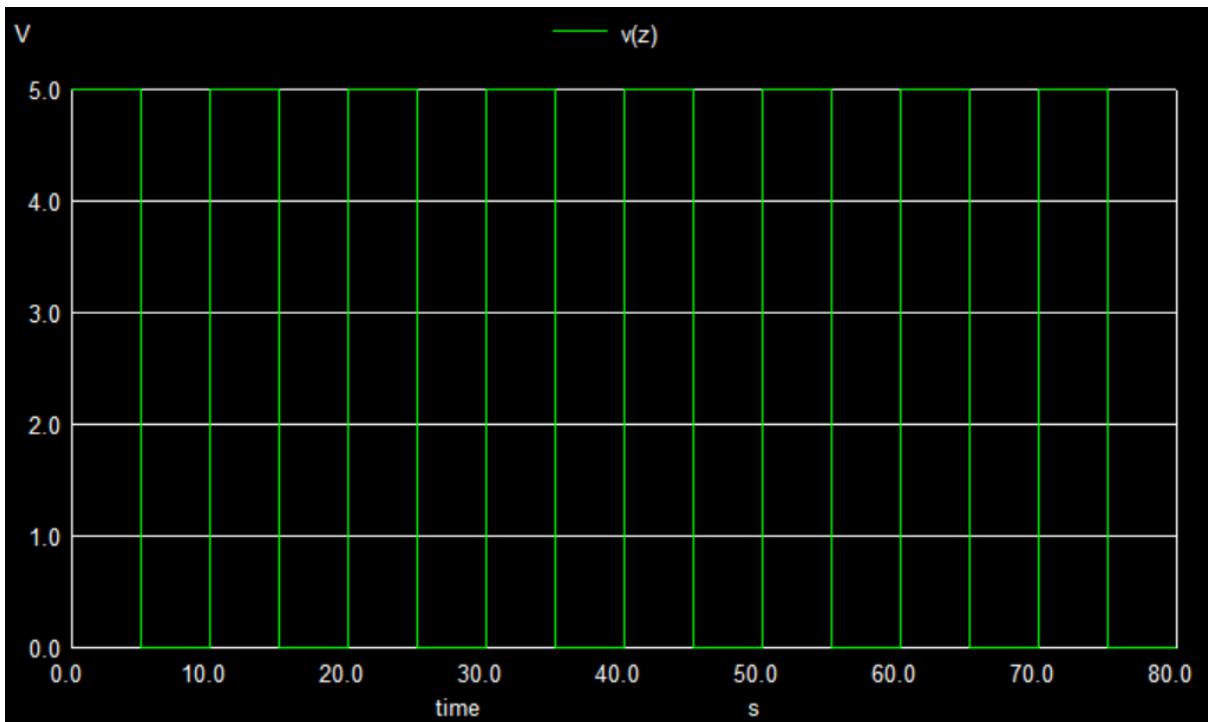


Fig.: 3d: Analog signal for Z (LSB)

Figures 3a through 3d display show the output analog signals for each of the output bits (Excess-3 code).

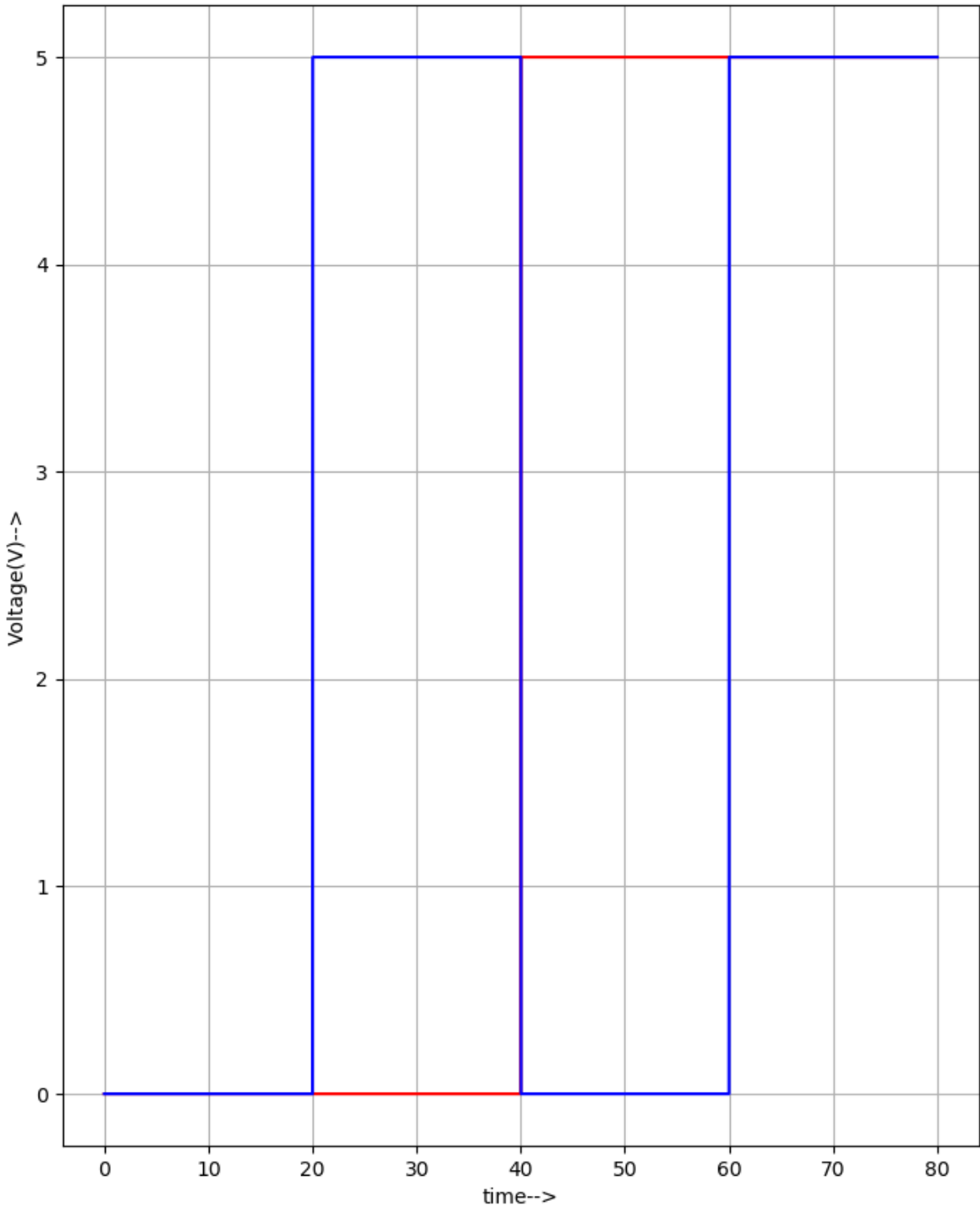


Fig. 4a: Python plots for A and B

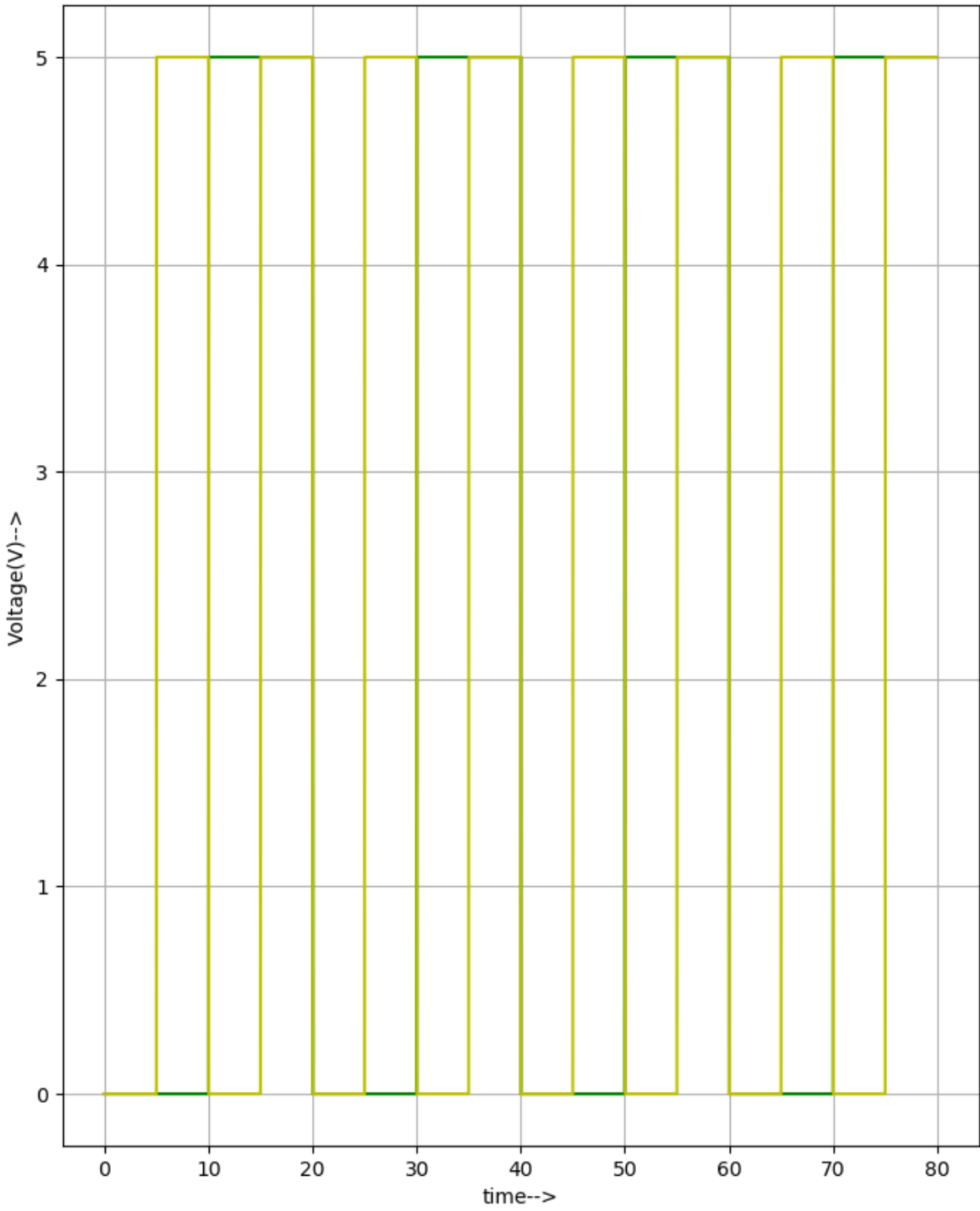


Fig. 4b: Python plots for C and D

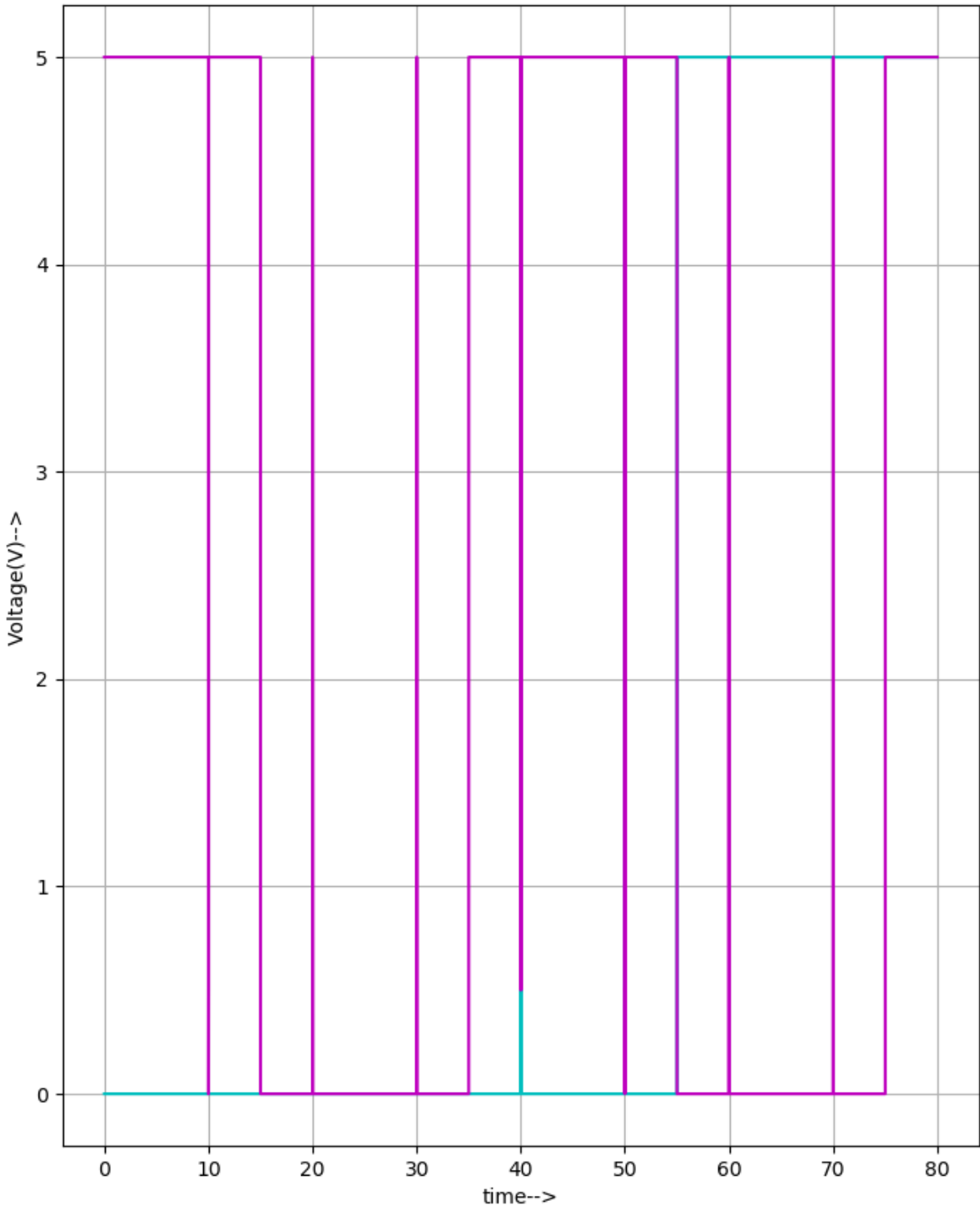


Fig. 4c: Python plots for W and X

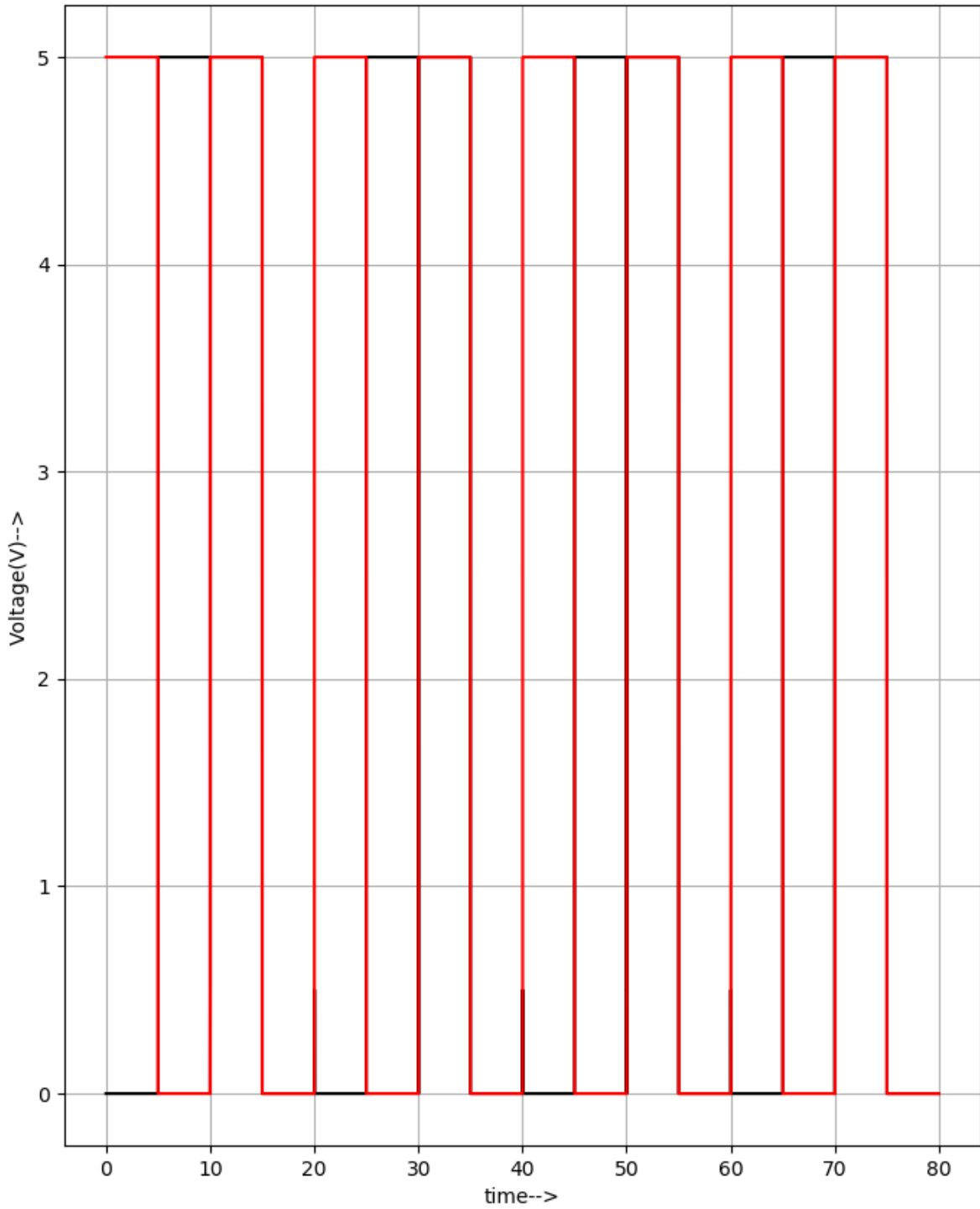


Fig. 4d: Python plots for Y and Z

Figures 4a through 4d show the python plots for the same signals for better visualisation.

Simulation parameter for reference:

Add parameters for pulse source v2	
Enter initial value(Volts/Amps):	<input type="text" value="0"/>
Enter pulsed value(Volts/Amps):	<input type="text" value="5"/>
Enter delay time (seconds):	<input type="text" value="20"/>
Enter rise time (seconds):	<input type="text" value="0"/>
Enter fall time (seconds):	<input type="text" value="0"/>
Enter pulse width (seconds):	<input type="text" value="20"/>
Enter period (seconds):	<input type="text" value="40"/>

Add parameters for pulse source v1	
Enter initial value(Volts/Amps):	<input type="text" value="0"/>
Enter pulsed value(Volts/Amps):	<input type="text" value="5"/>
Enter delay time (seconds):	<input type="text" value="40"/>
Enter rise time (seconds):	<input type="text" value="0"/>
Enter fall time (seconds):	<input type="text" value="0"/>
Enter pulse width (seconds):	<input type="text" value="40"/>
Enter period (seconds):	<input type="text" value="80"/>

Fig. 5a

Add parameters for pulse source v4	
Enter initial value(Volts/Amps):	<input type="text" value="0"/>
Enter pulsed value(Volts/Amps):	<input type="text" value="5"/>
Enter delay time (seconds):	<input type="text" value="5"/>
Enter rise time (seconds):	<input type="text" value="0"/>
Enter fall time (seconds):	<input type="text" value="0"/>
Enter pulse width (seconds):	<input type="text" value="5"/>
Enter period (seconds):	<input type="text" value="10"/>

Add parameters for pulse source v3	
Enter initial value(Volts/Amps):	<input type="text" value="0"/>
Enter pulsed value(Volts/Amps):	<input type="text" value="5"/>
Enter delay time (seconds):	<input type="text" value="10"/>
Enter rise time (seconds):	<input type="text" value="0"/>
Enter fall time (seconds):	<input type="text" value="0"/>
Enter pulse width (seconds):	<input type="text" value="10"/>
Enter period (seconds):	<input type="text" value="20"/>

Fig. 5b

Source/Reference(s) :

<https://www.javatpoint.com/conversion-of-bcd-to-excess-3-code-in-digital-electronics>

(Excess-3 to BCD conversion)