



VIT[®]
Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)



Circuit Simulation Project

<https://esim.fossee.in/circuit-simulation-project>

Name of the Participant: Shubhangi Agrawal (20BCE1161)

Project Guide: Dr R. Maheshwari

Title of the Circuit: DE Morgan's Verification Circuit

Description:

The designed circuit gives the verification of DE Morgan's laws.

DE Morgan's Theorem represents two of the most important rules of boolean algebra.

(i) $(A \cdot B)' = A' + B'$

Thus, the complement of the product of variables is equal to the sum of their individual complements.

(ii) $(A + B)' = A' \cdot B'$

Thus, the complement of the sum of variables is equal to the product of their individual complements.


The above two laws can be extended for n variables as

$(A_1 \cdot A_2 \cdot A_3 \dots A_n)' = A_1' + A_2' + \dots + A_n'$

And

$$(A_1 + A_2 + \dots + A_n)' = A_1' \cdot A_2' \cdot A_3' \dots A_n'$$

CIRCUIT DIAGRAM:

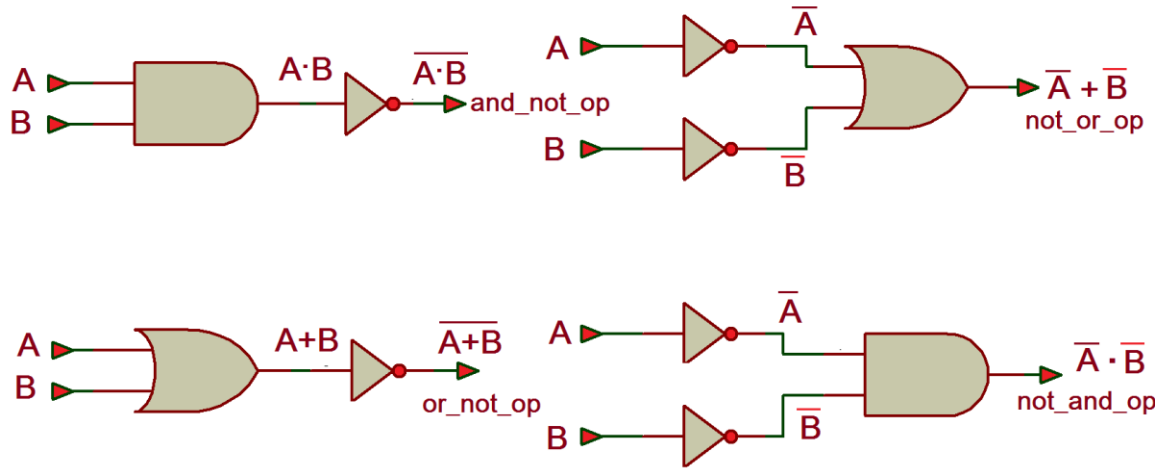


TRUTH TABLE:


Inputs		Truth Table Outputs For Each Term				
B	A	$A \cdot B$	$\overline{A \cdot B}$	\overline{A}	\overline{B}	$\overline{A} + \overline{B}$
0	0	0	1	1	1	1
0	1	0	1	0	1	1
1	0	0	1	1	0	1
1	1	1	0	0	0	0

e-Sim Schematic


B

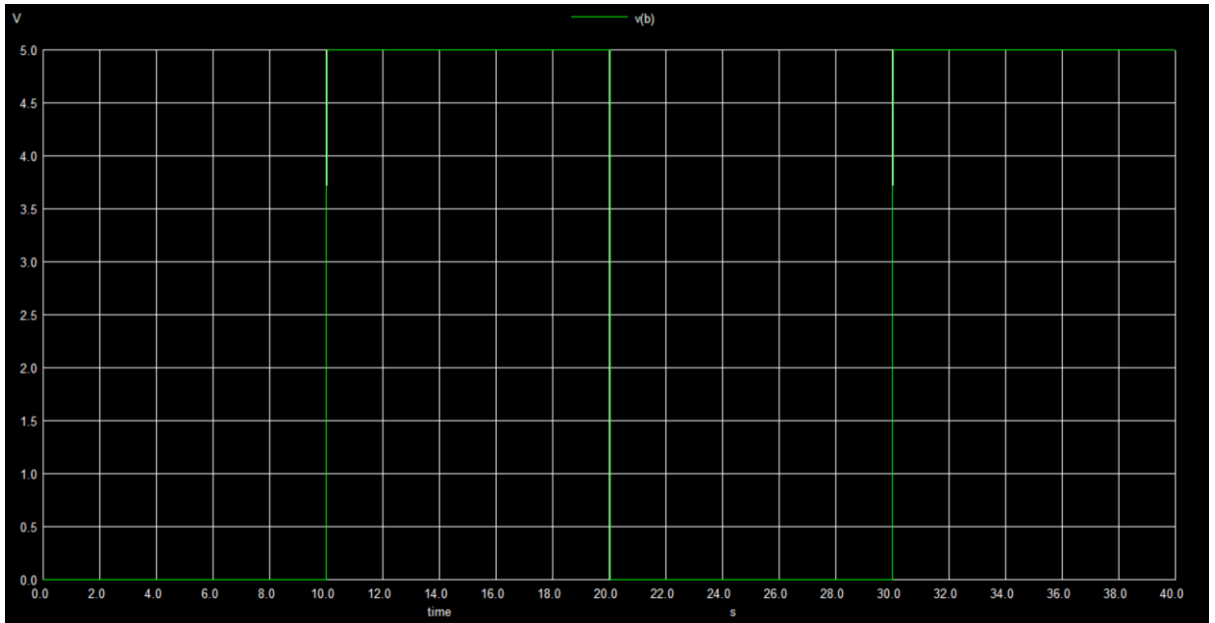


Y:(A'B')

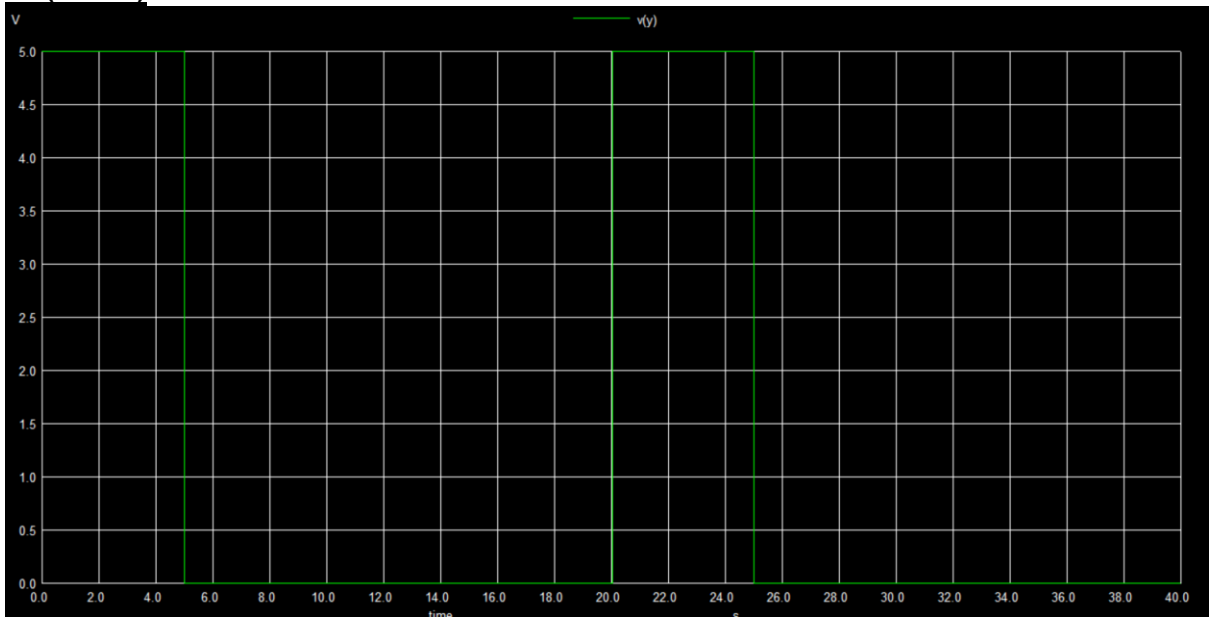


X: (A+B)'

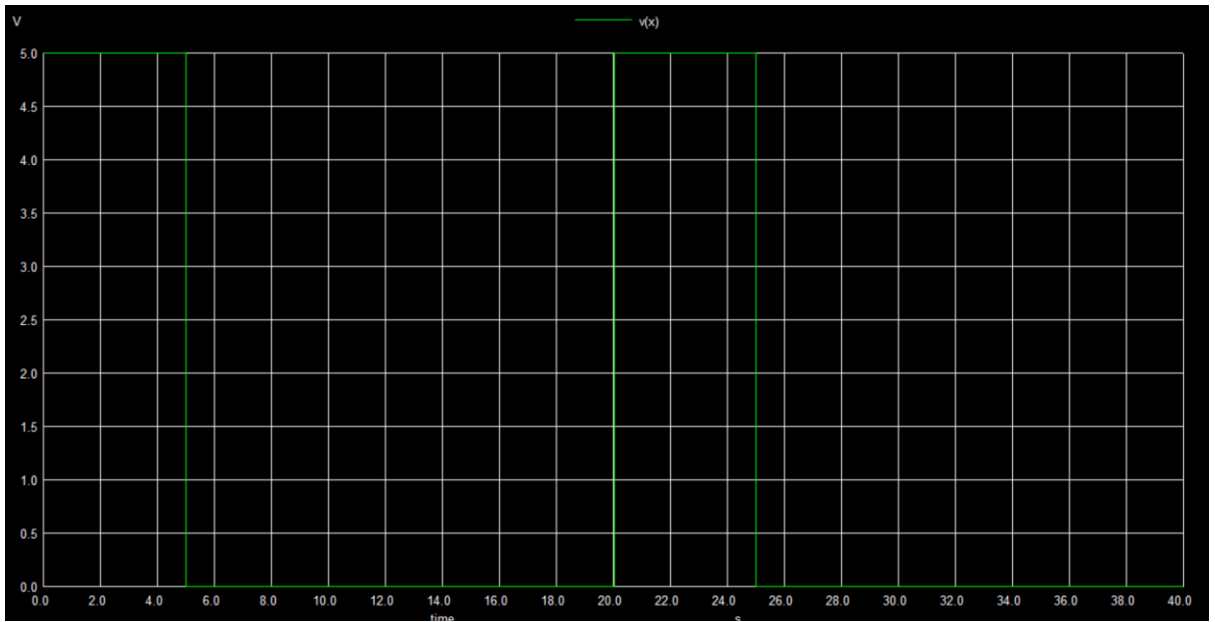

Q: (A'+B')

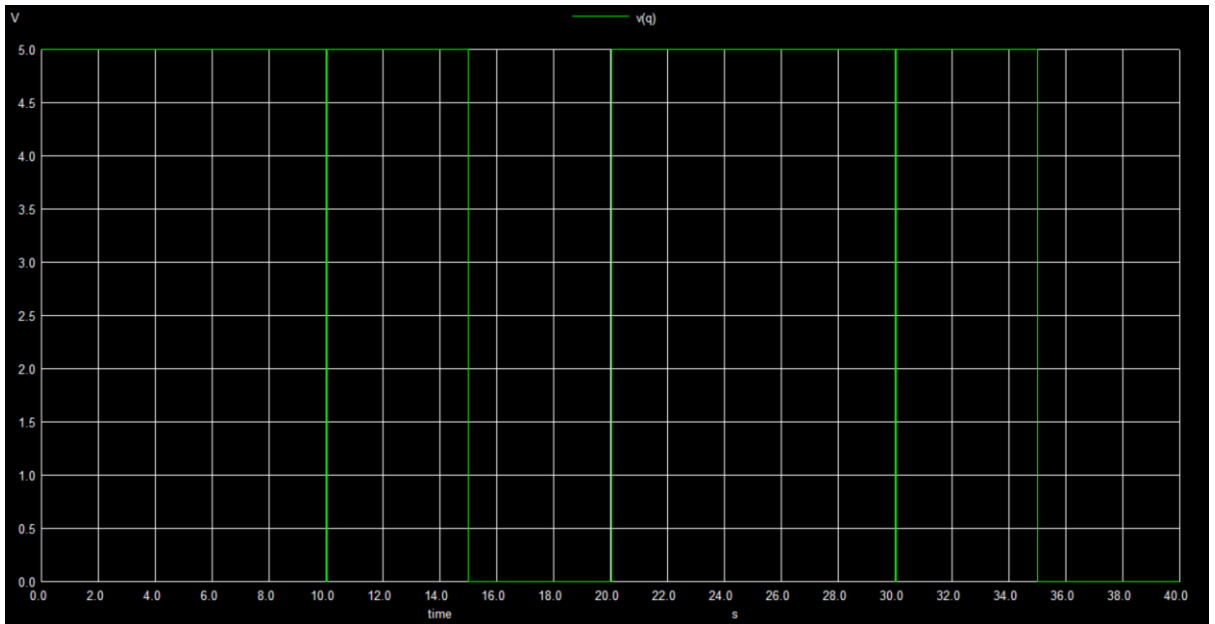


P: (AB)'

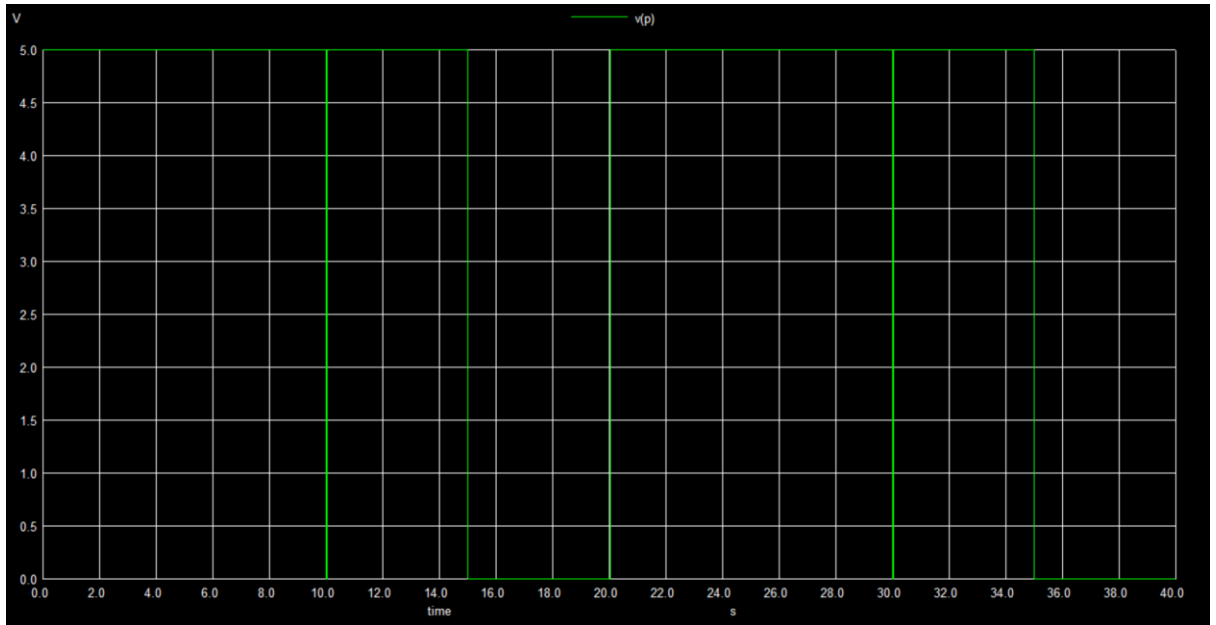


Python Waveforms:


A:

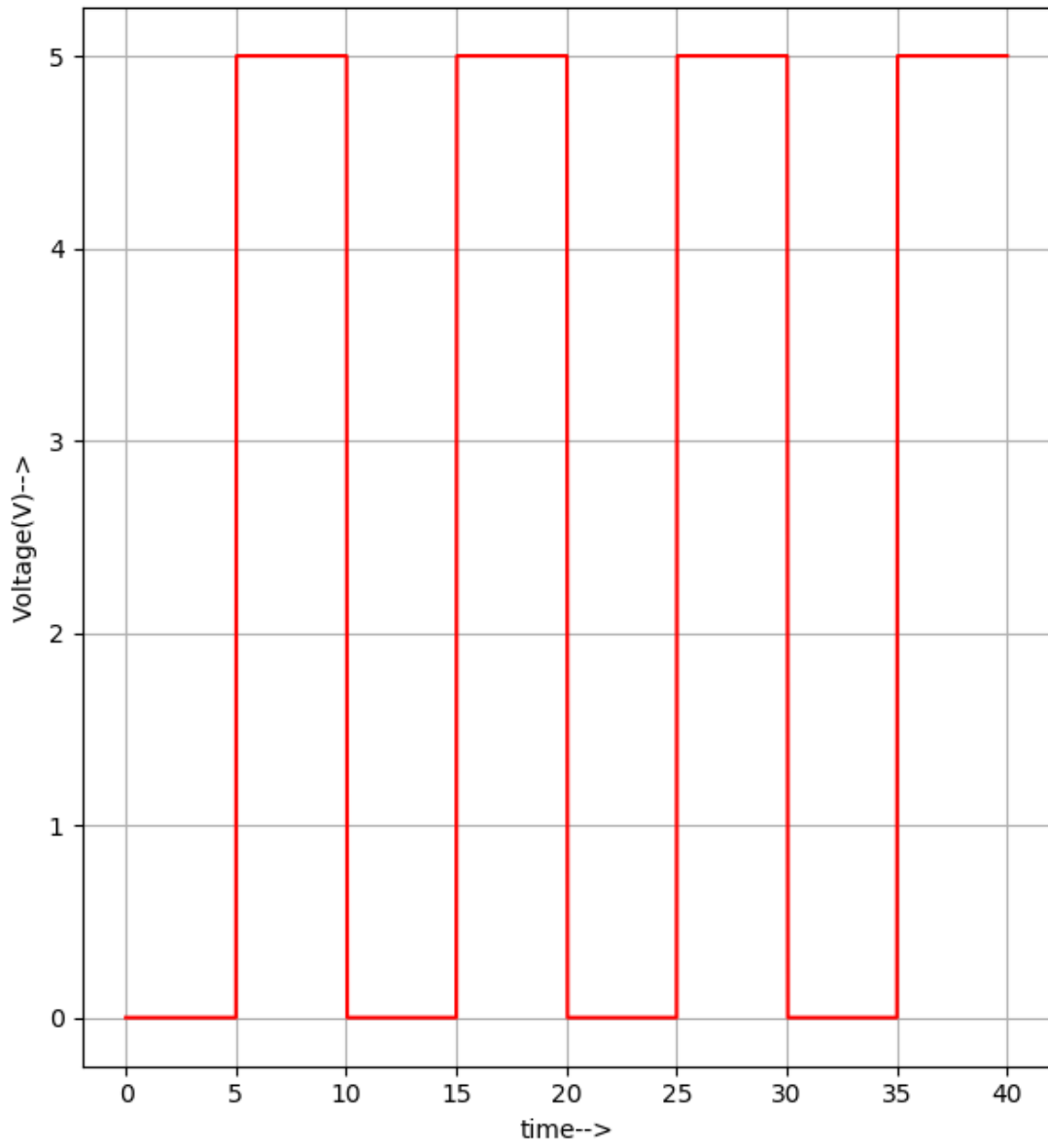


B:

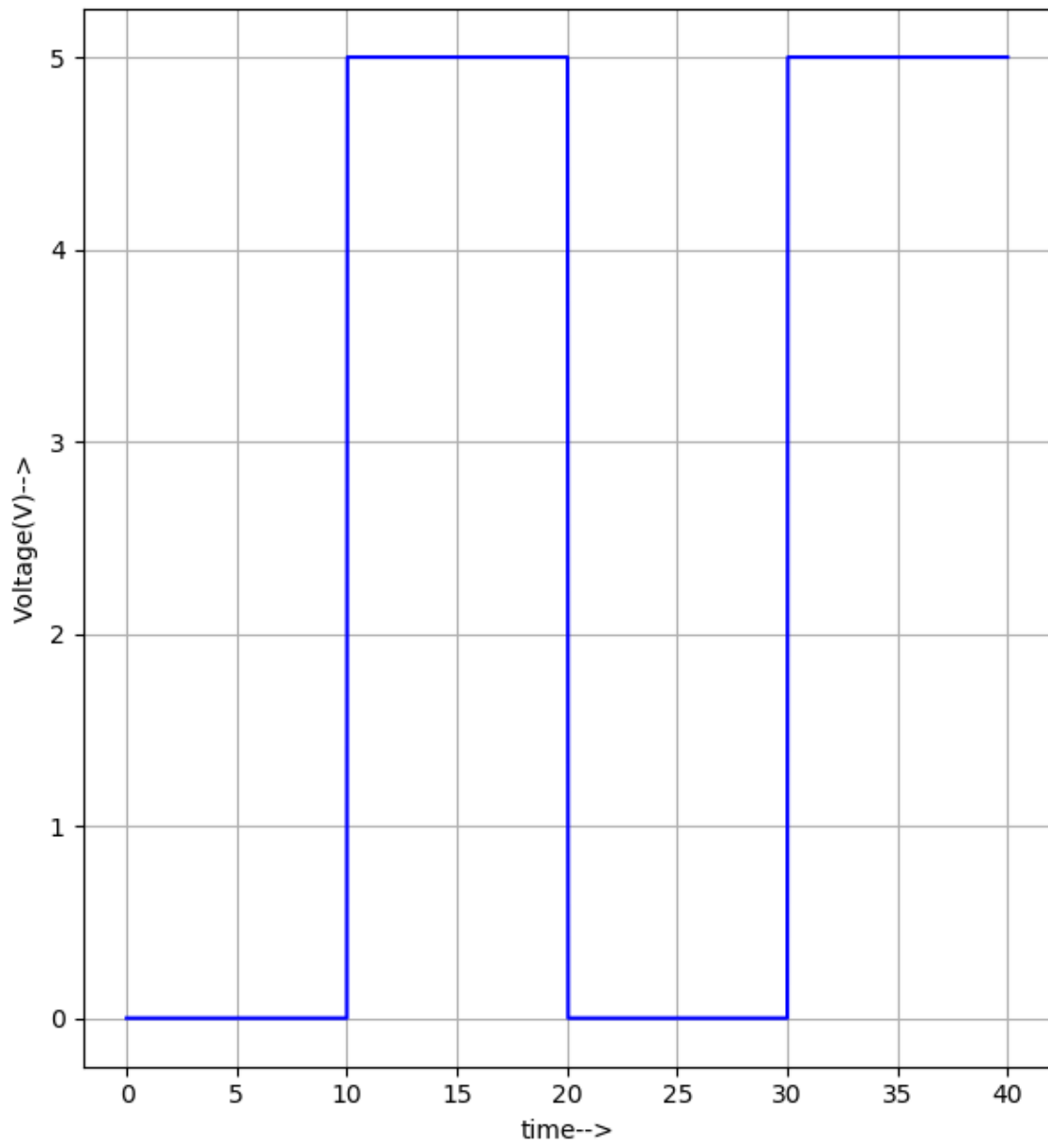


P: (AB)'

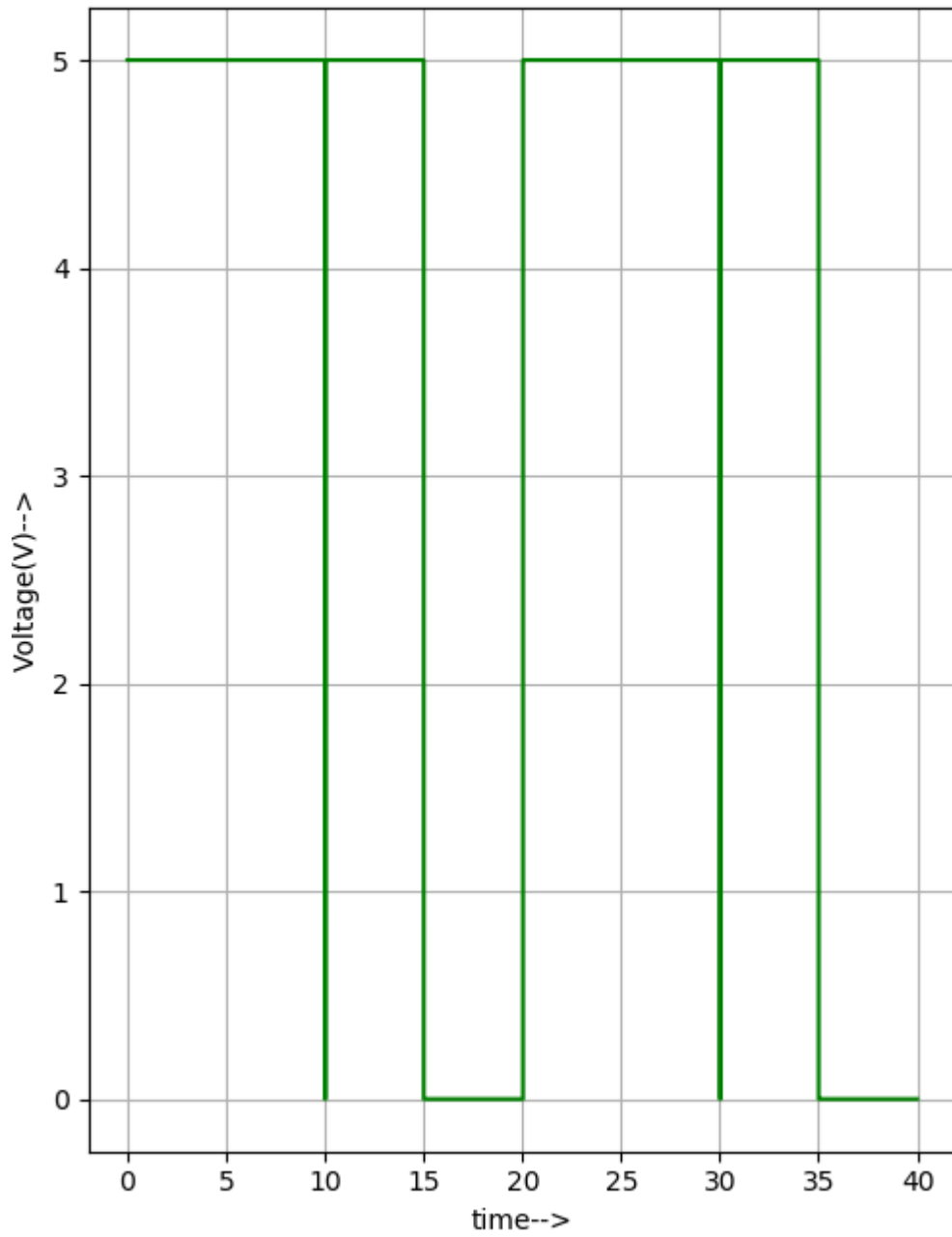


Q: (A'+B')

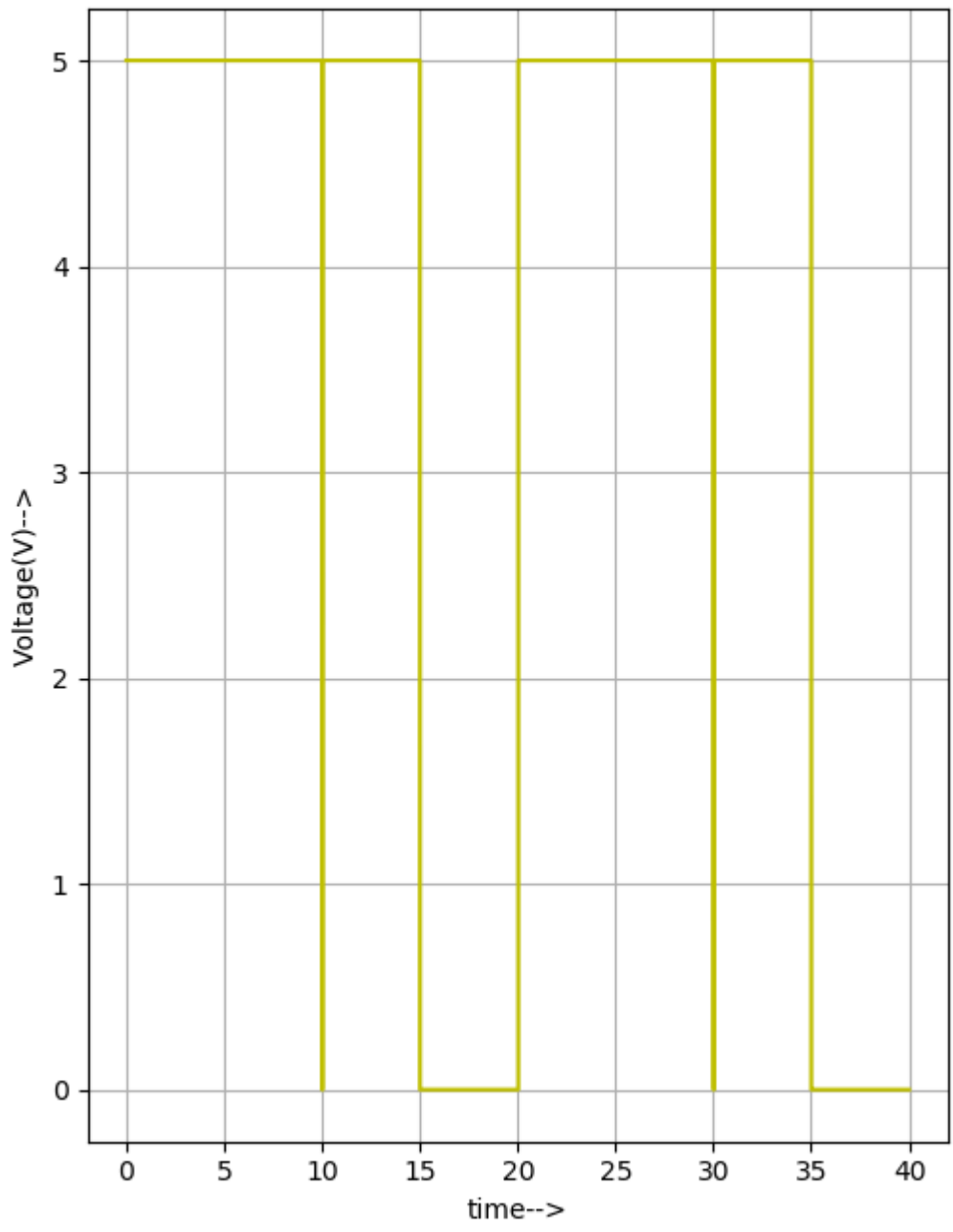

X: (A+B)'

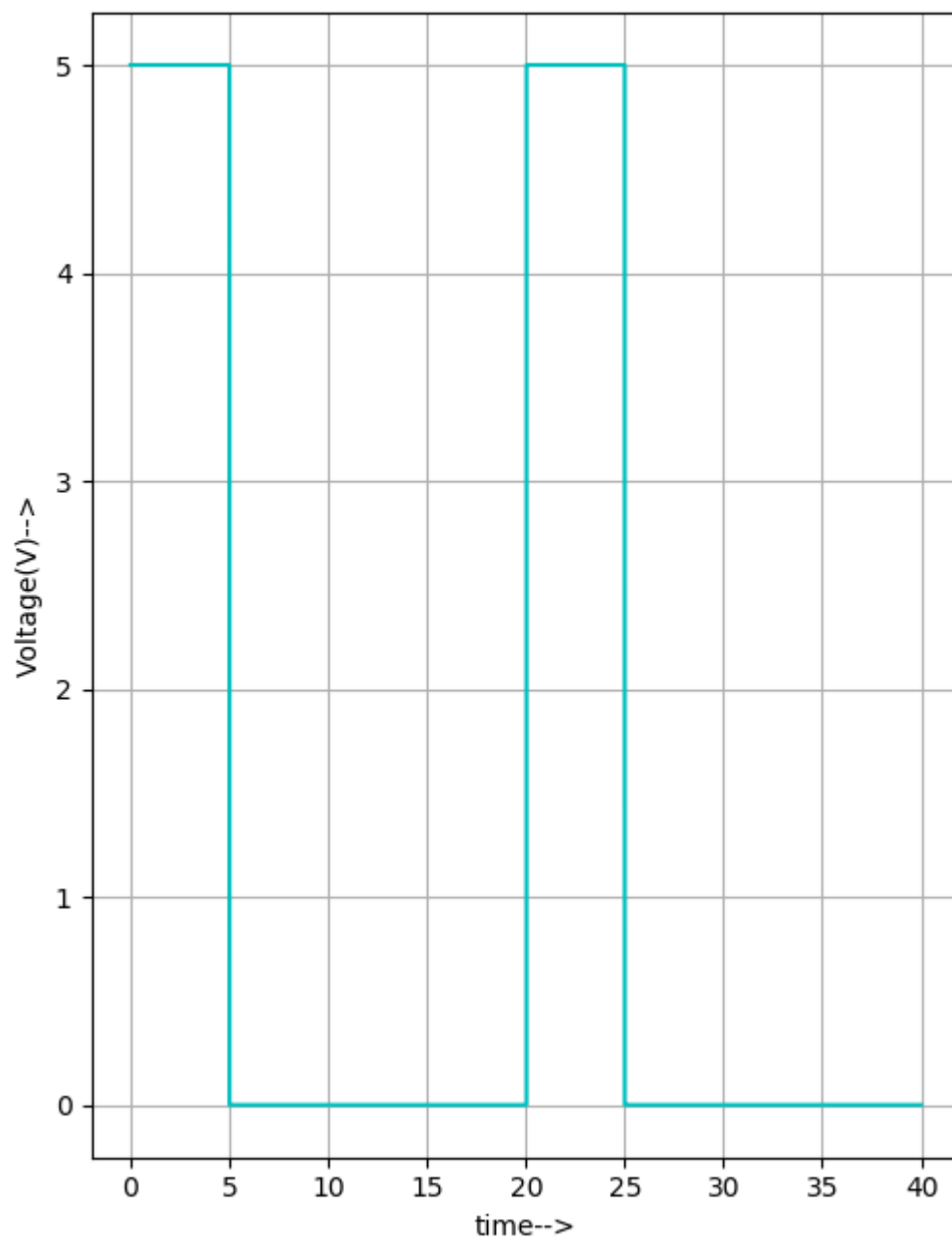

Y:(A'B')

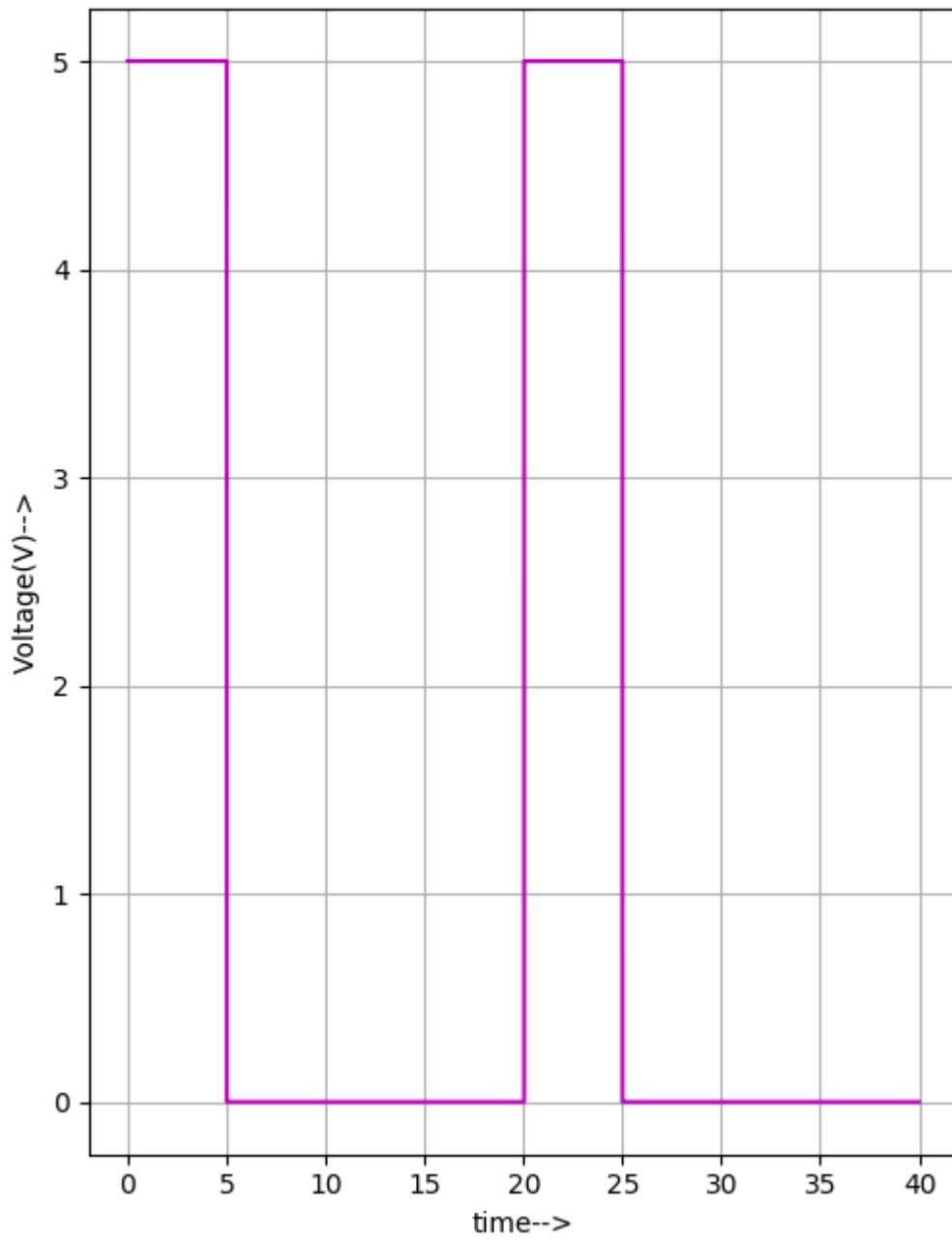

Transient Analysis:

Analysis Source Details Ngspice Model Device Modeling Subcircuits

Select Analysis Type

AC DC TRANSIENT

Transient Analysis

Start Time Sec

Step Time ms

Stop Time Sec

Source Details:

Analysis Source Details Ngspice Model Device Modeling Subcircuits

Add parameters for pulse source v1

Enter initial value(Volts/Amps):

Enter pulsed value(Volts/Amps):

Enter delay time (seconds):

Enter rise time (seconds):

Enter fall time (seconds):

Enter pulse width (seconds):

Enter period (seconds):

Add parameters for pulse source v2

Enter initial value(Volts/Amps):

Enter pulsed value(Volts/Amps):

Enter delay time (seconds):

Enter rise time (seconds):

Enter fall time (seconds):

Enter pulse width (seconds):

Enter period (seconds):

Conclusion:

Thus, the circuit was designed and DE Morgan's theorem has been verified.

References:

<https://www.electronics-tutorials.ws/boolean/demorgan.html>

<https://www.geeksforgeeks.org/boolean-algebraic-theorems/>