

Circuit Simulation Project

<https://esim.fossee.in/circuit-simulation-project>

Name of the participant : Siddharth Bhuthapuri

Project Guide: Dr. R. Maheswari

Title of the circuit : Designing of 3 to 8 line Decoder

Theory/Description :


A decoder is a combinational logic circuit that is used to change the code into a set of signals. It is the reverse process of an encoder. A decoder circuit takes multiple inputs and gives multiple outputs. A decoder circuit takes binary data of 'n' inputs into '2ⁿ' unique output.

This decoder circuit gives 8 logic outputs for 3 inputs . The circuit is designed with AND and NAND logic gates. It takes 3 binary inputs and activates one of the eight outputs. 3 to 8 line decoder circuit is also called a binary to an octal decoder.


Truth Table:

A	B	C	D0	D1	D2	D3	D4	D5	D6	D7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	1	0	0	0	0	0	0	1

Logic Circuit:

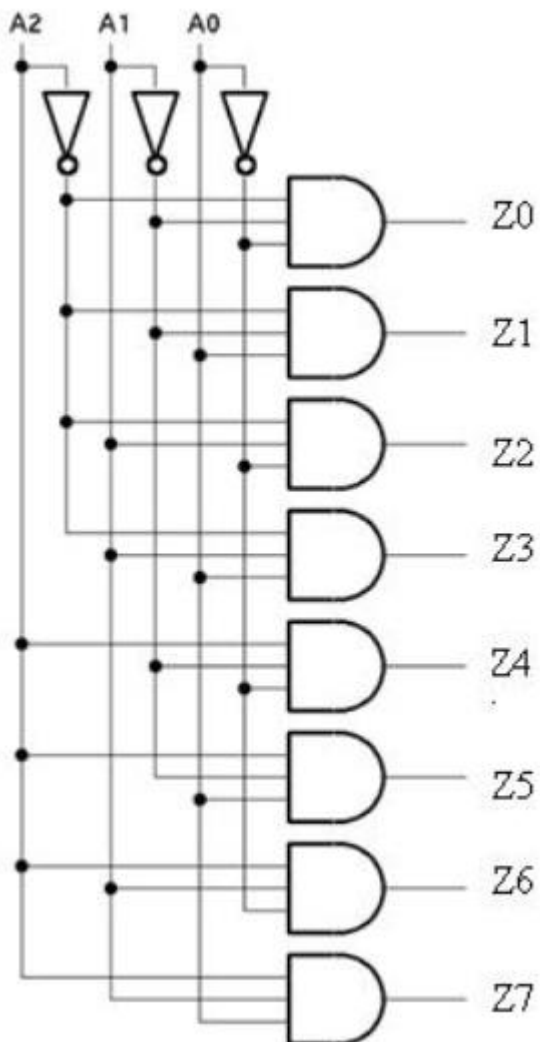

Circuit Diagram:

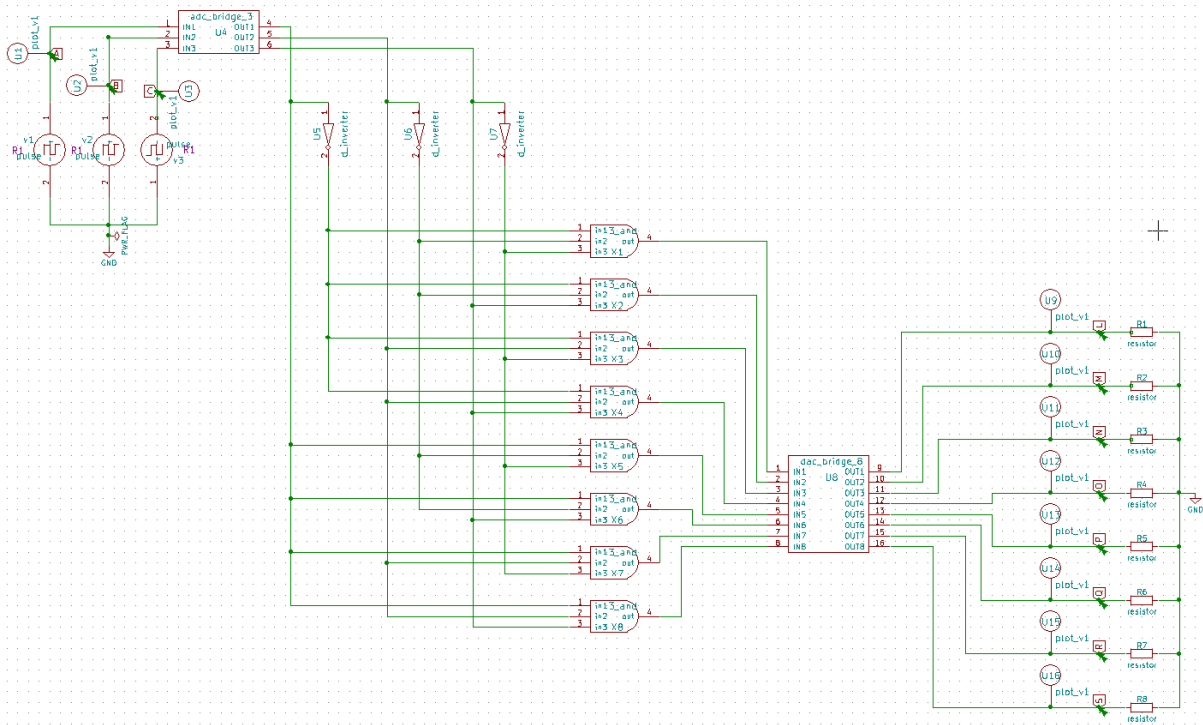

Source Details:

Add parameters for pulse source v1

Enter initial value(Volts/Amps):

Enter pulsed value(Volts/Amps):

Enter delay time (seconds):

Enter rise time (seconds):

Enter fall time (seconds):

Enter pulse width (seconds):

Enter period (seconds):

Add parameters for pulse source v2

Enter initial value(Volts/Amps):

Enter pulsed value(Volts/Amps):

Enter delay time (seconds):

Enter rise time (seconds):

Enter fall time (seconds):

Enter pulse width (seconds):

Enter period (seconds):

Add parameters for pulse source v3

Enter initial value(Volts/Amps):

Enter pulsed value(Volts/Amps):

Enter delay time (seconds):

Enter rise time (seconds):

Enter fall time (seconds):

Enter pulse width (seconds):

Enter period (seconds):

Analysis:

Analysis Source Details Ngspice Model Device Modeling Subcircuits

Select Analysis Type

AC DC TRANSIENT


Transient Analysis

Start Time	<input type="text" value="0"/>	Sec	▼
Step Time	<input type="text" value="10"/>	ms	▼
Stop Time	<input type="text" value="40"/>	Sec	▼


Results:

Ngspice plot-Input Waveforms:


A:

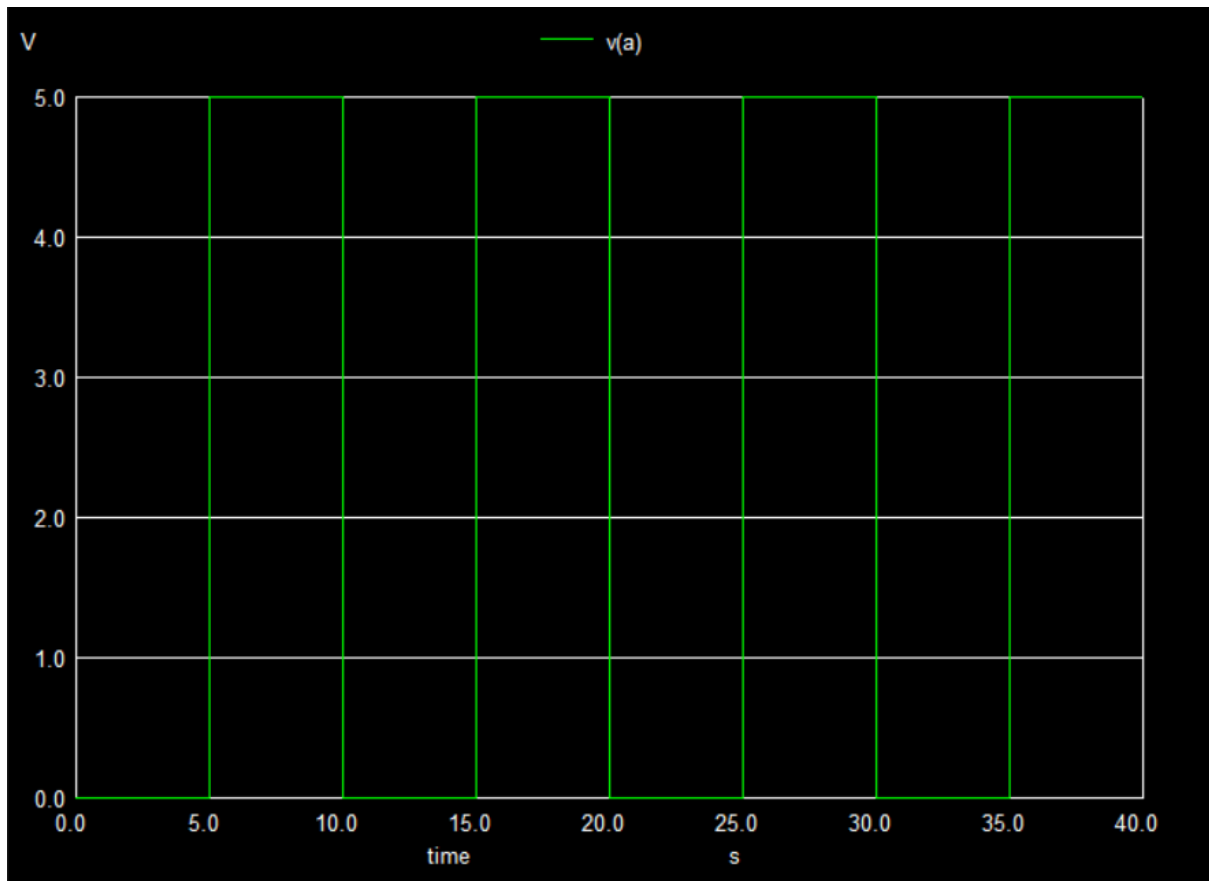

B:

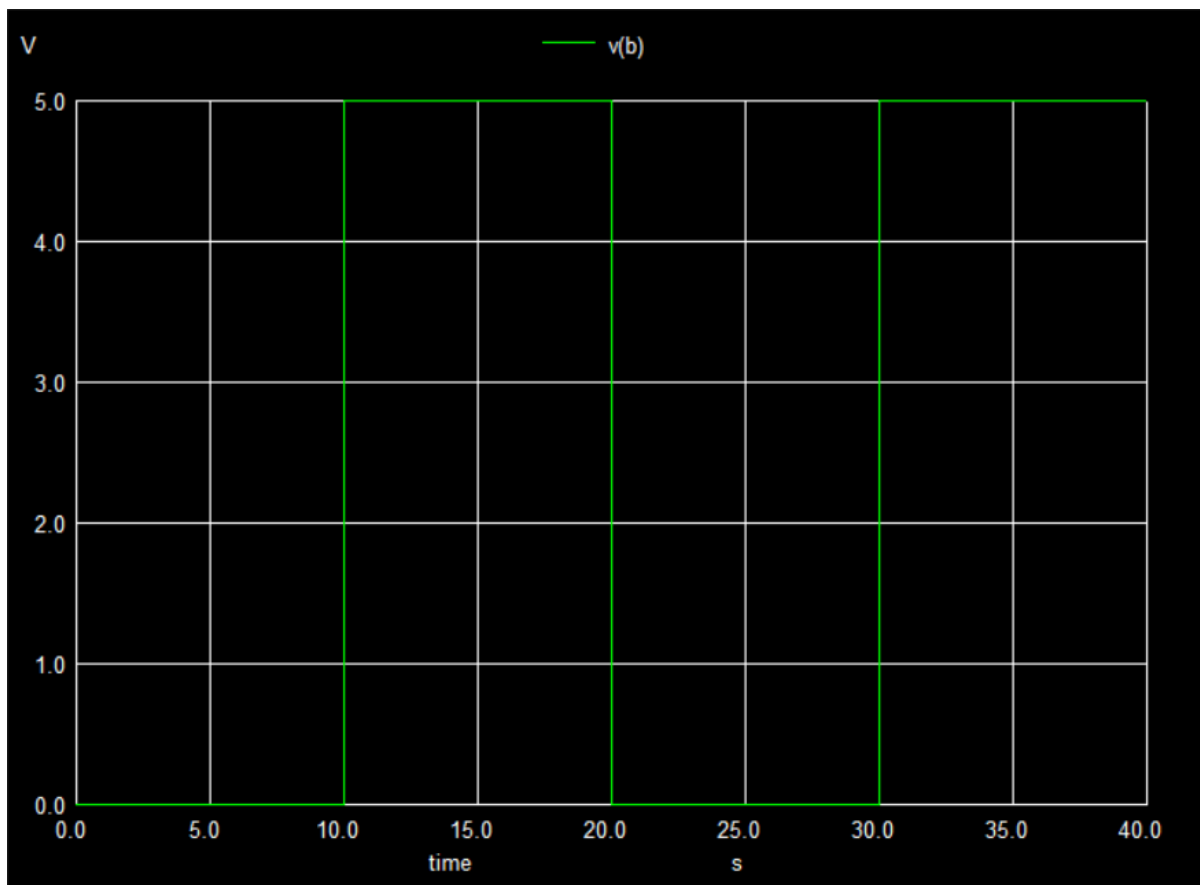


C:

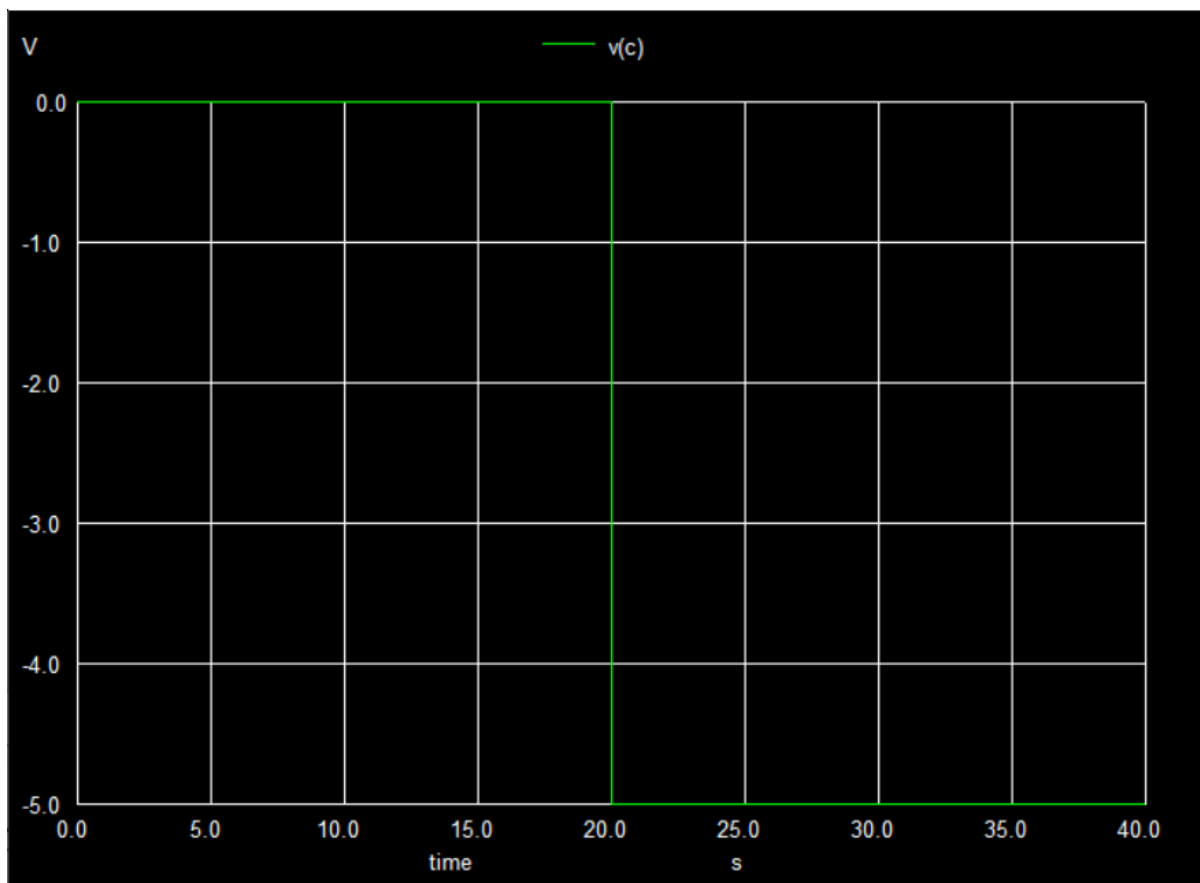


Ngspice plot-Output Waveforms:


L:

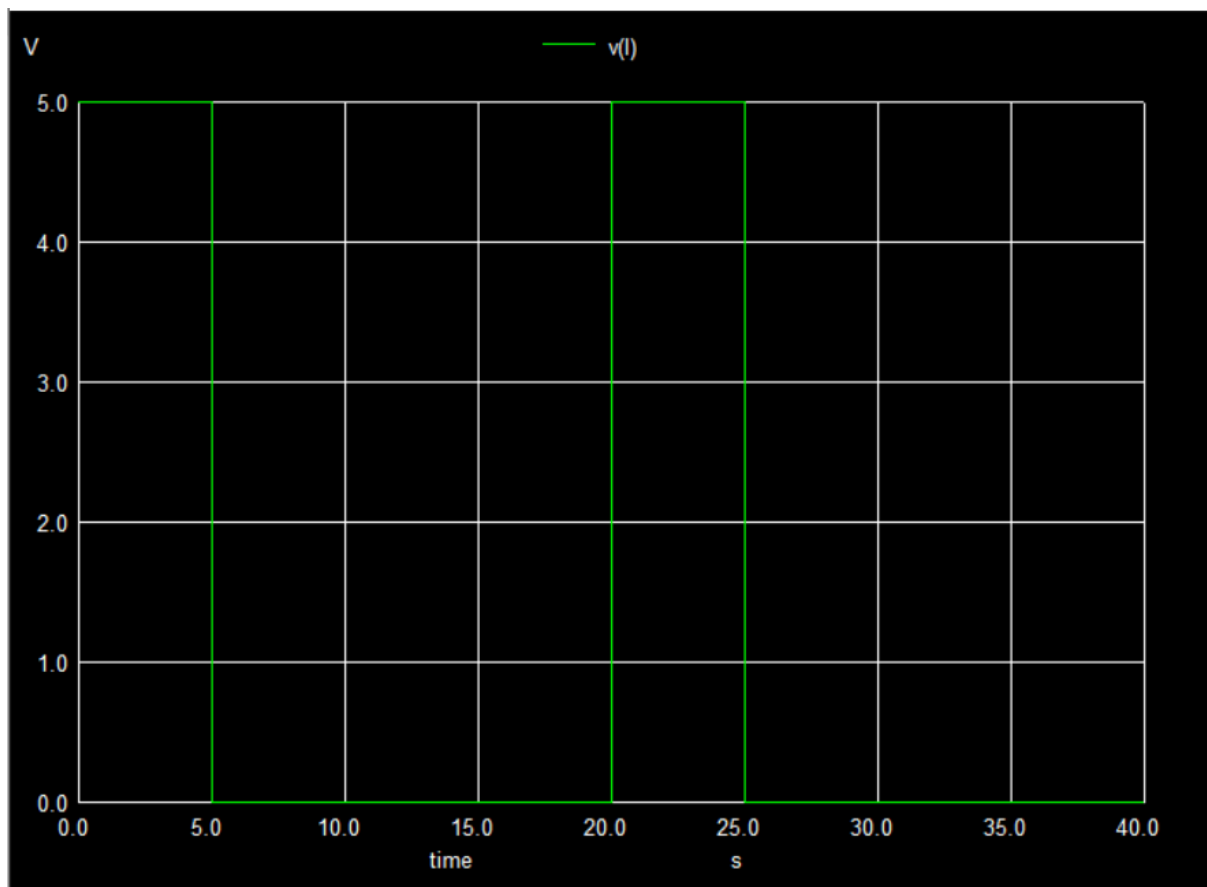


M:

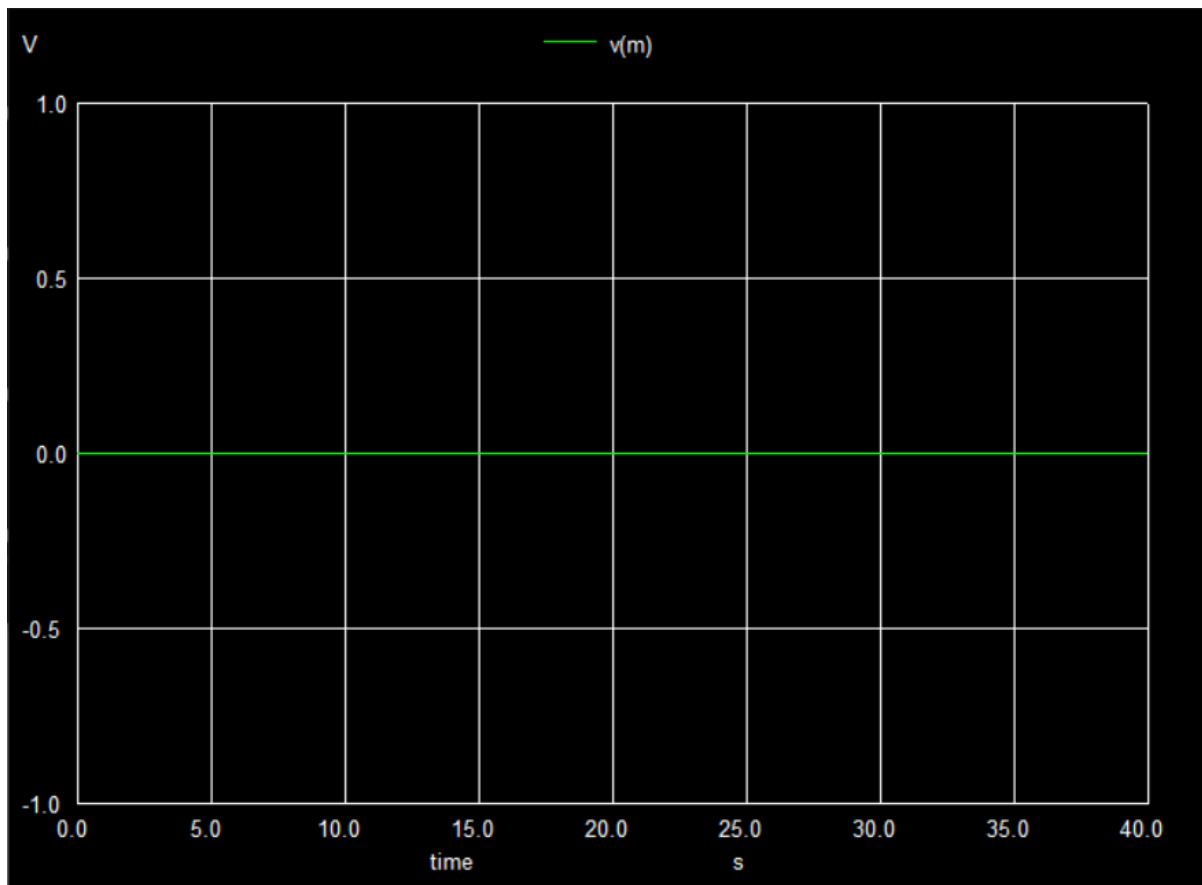


N:

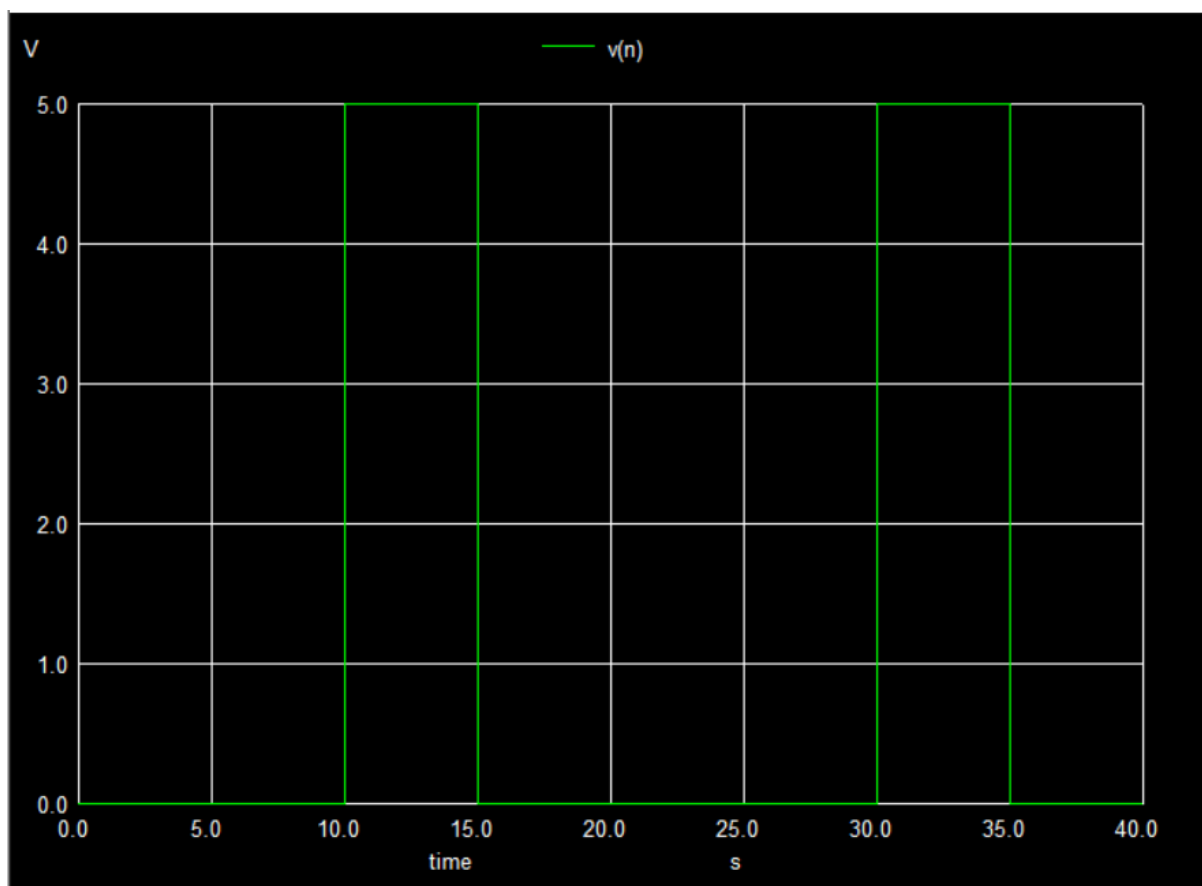


O:

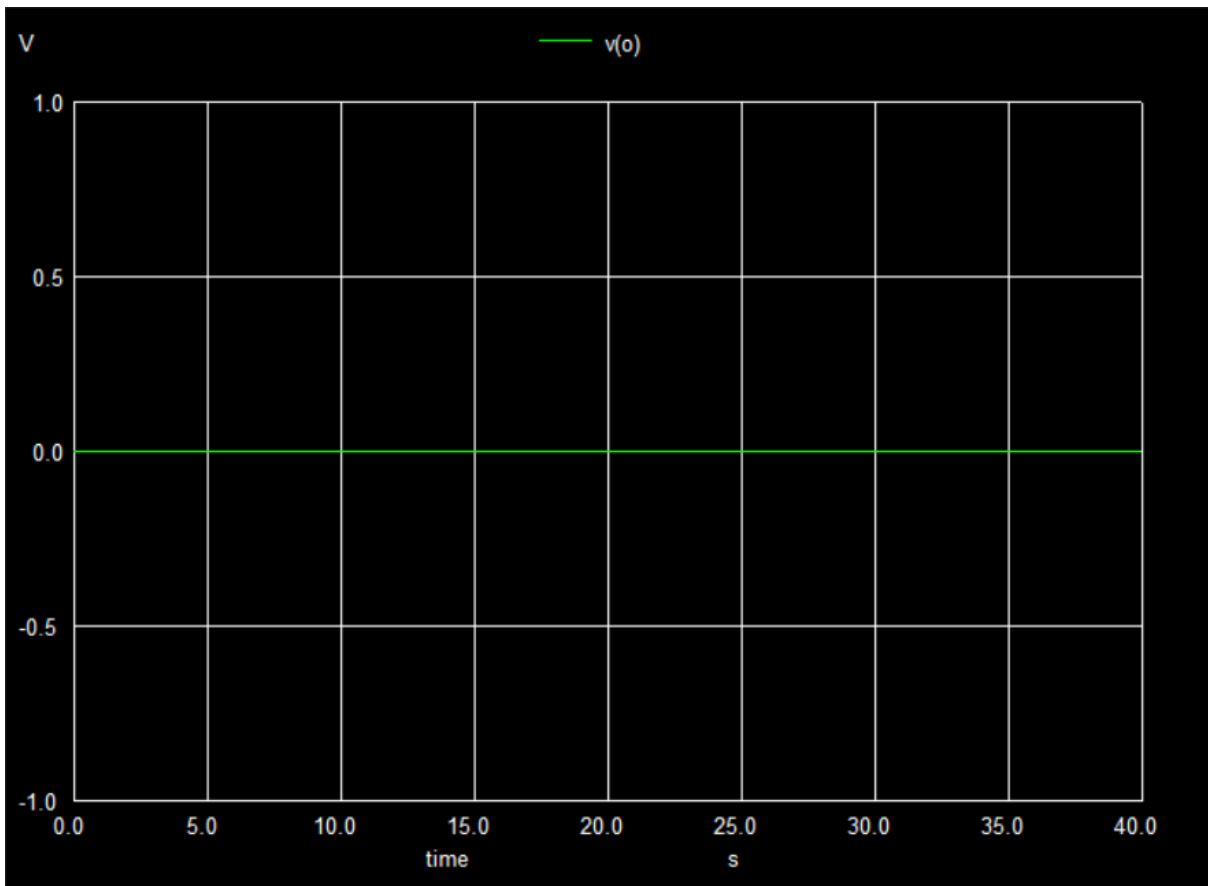


P:

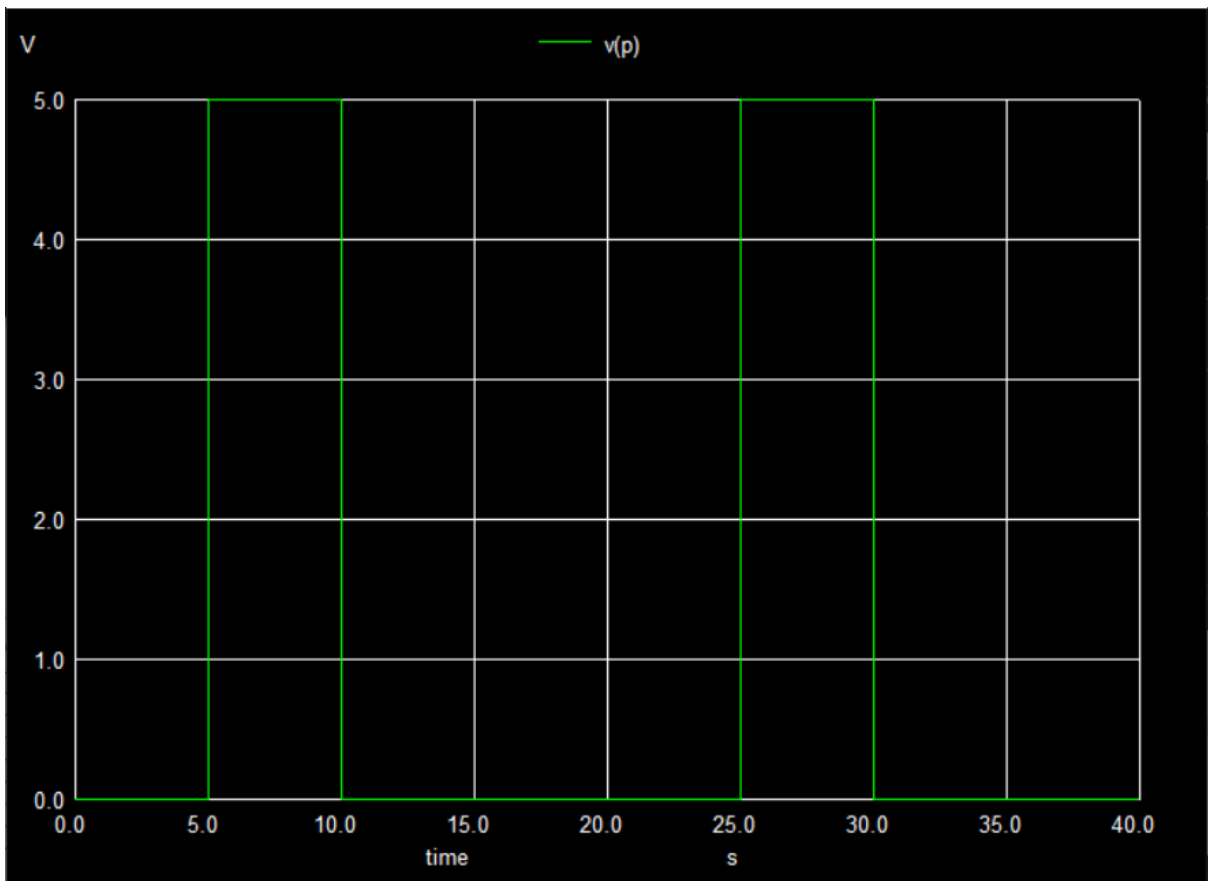


Q:

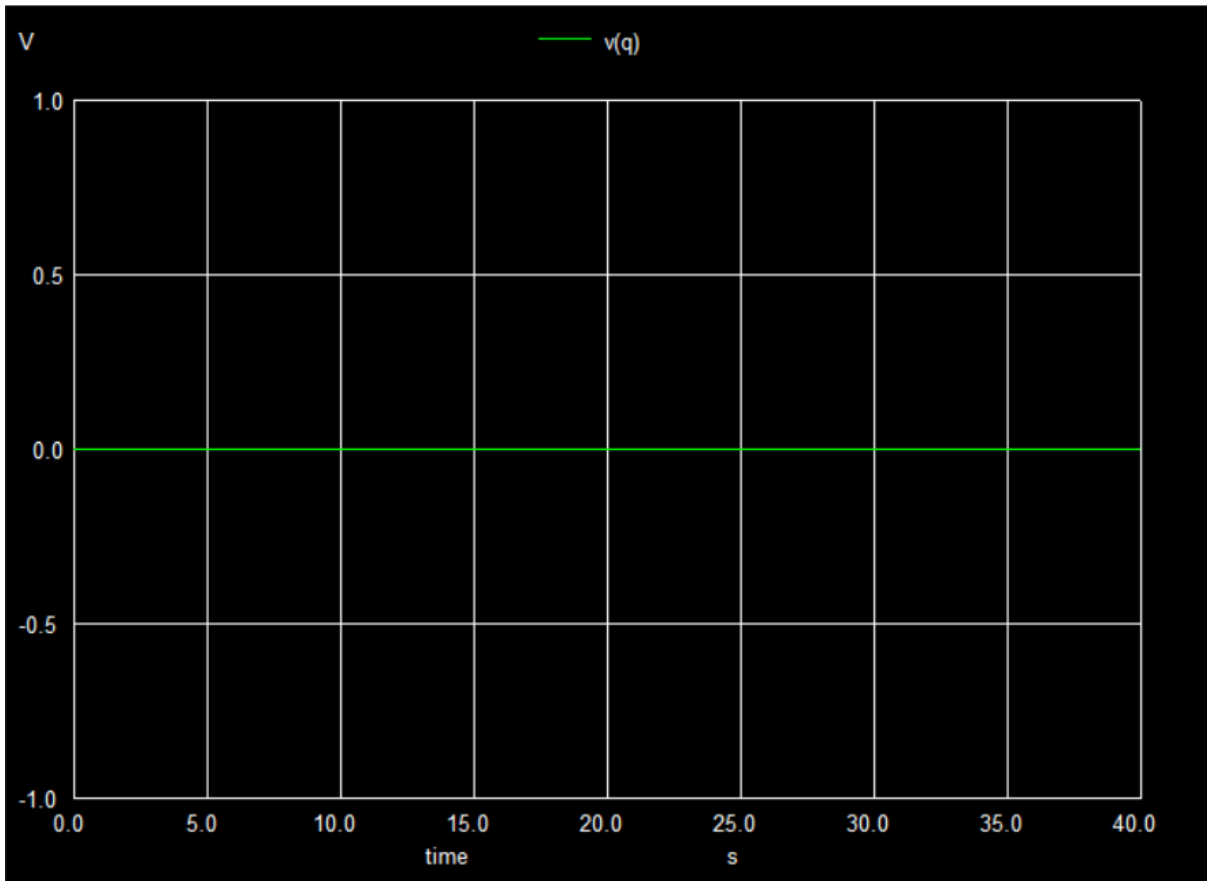

R:

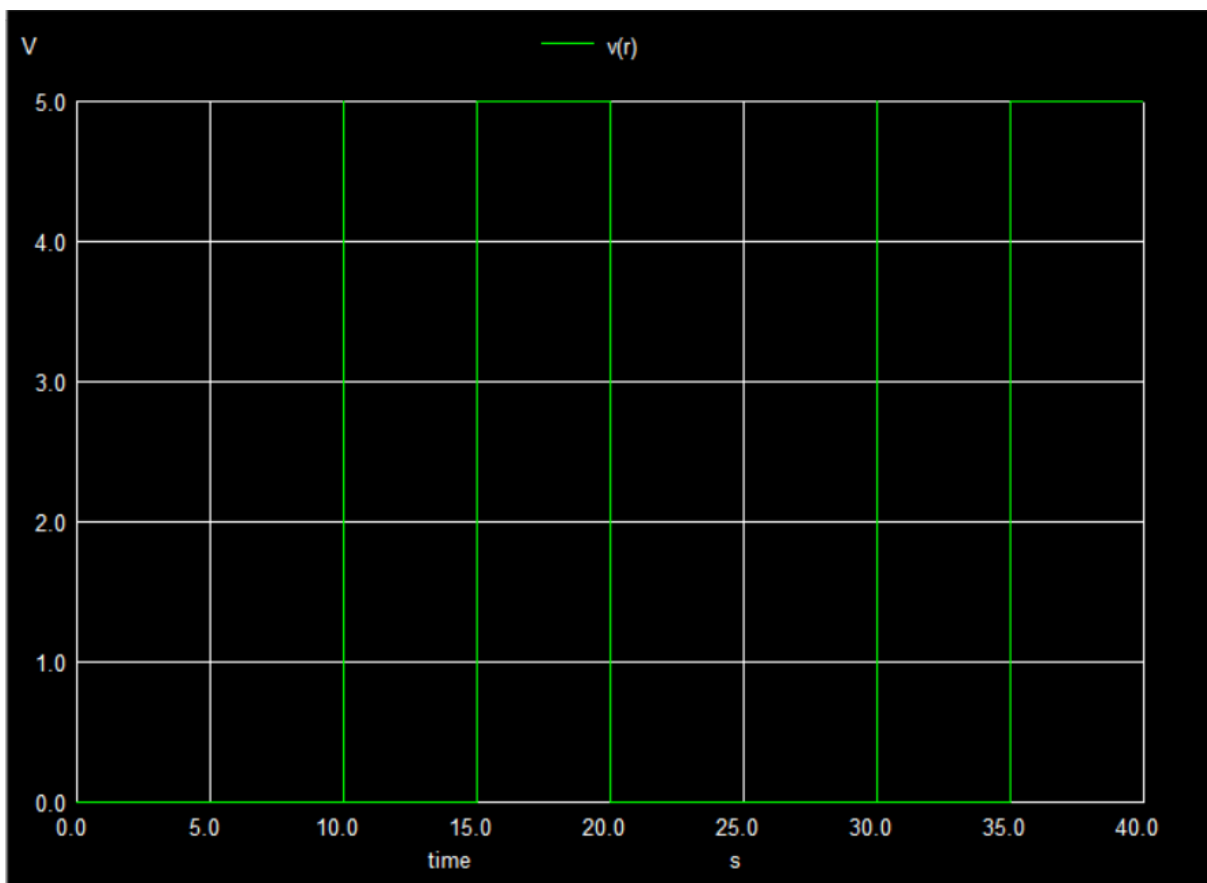


S:

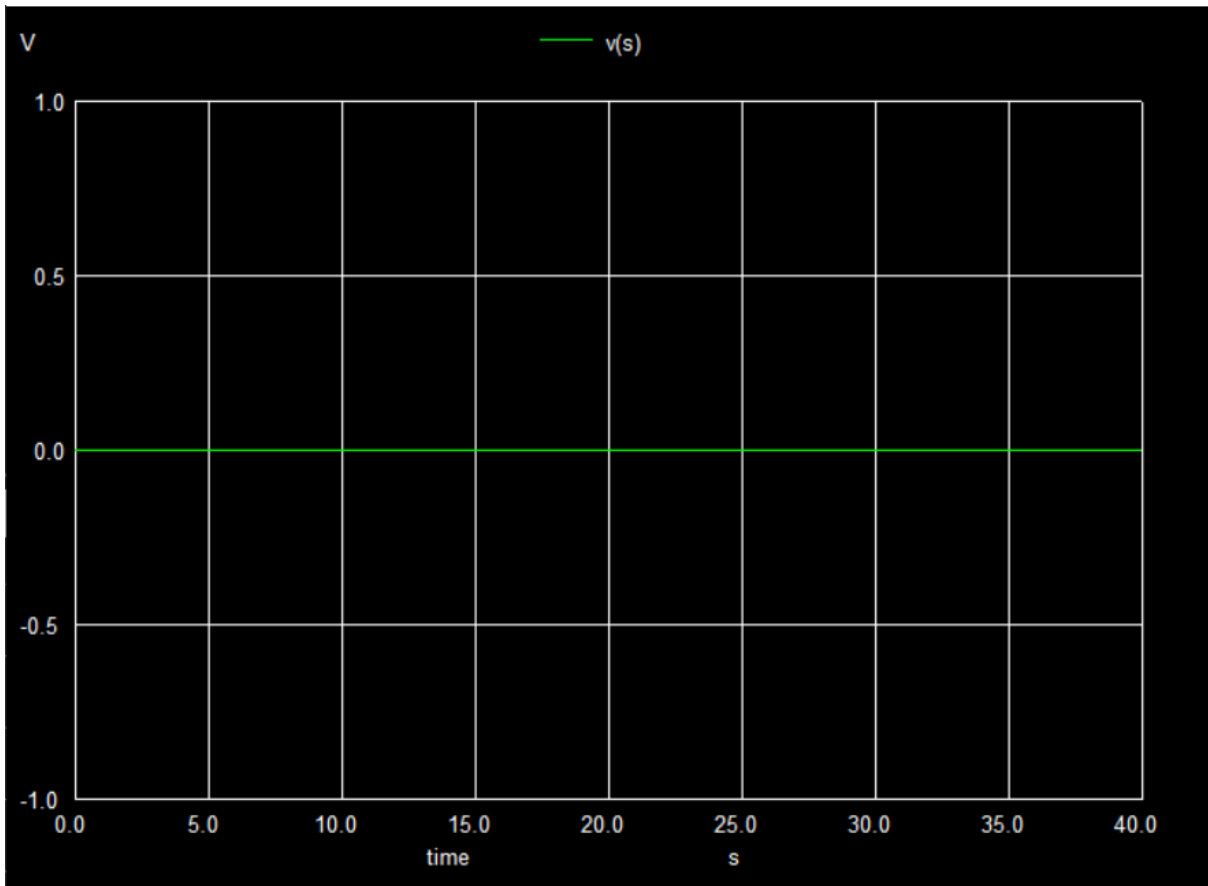


Python plot-Input Waveforms:


A:

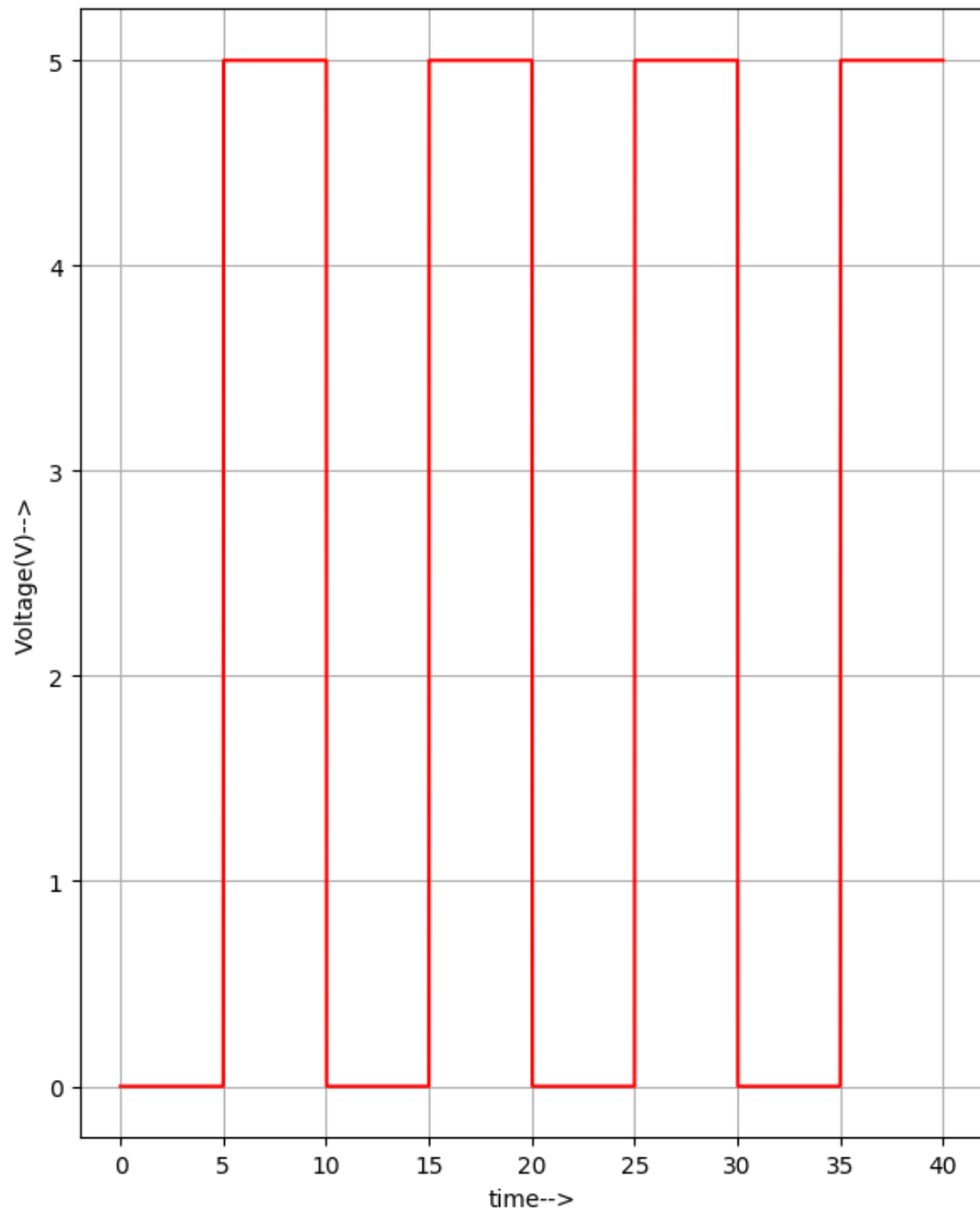

B:

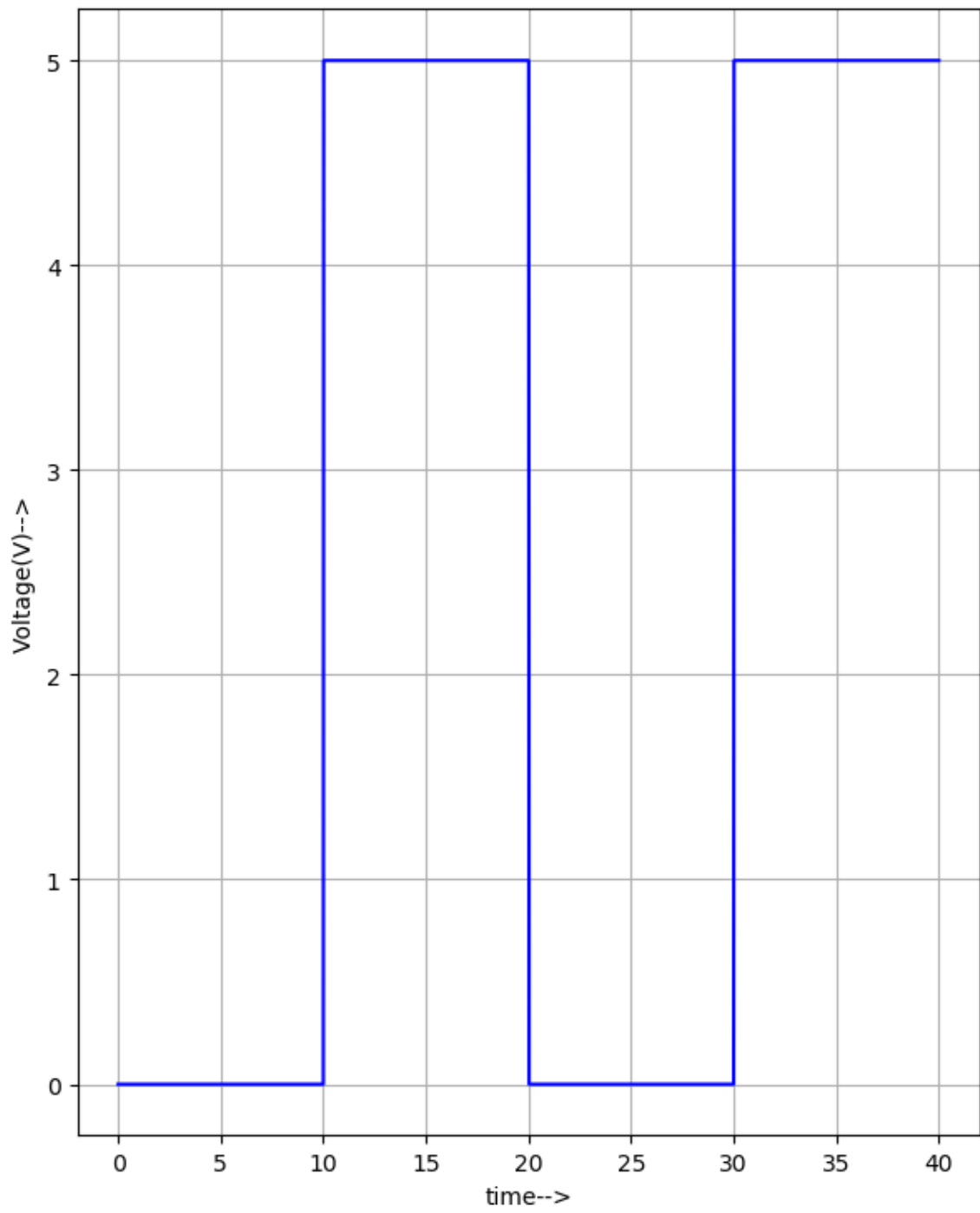


C:

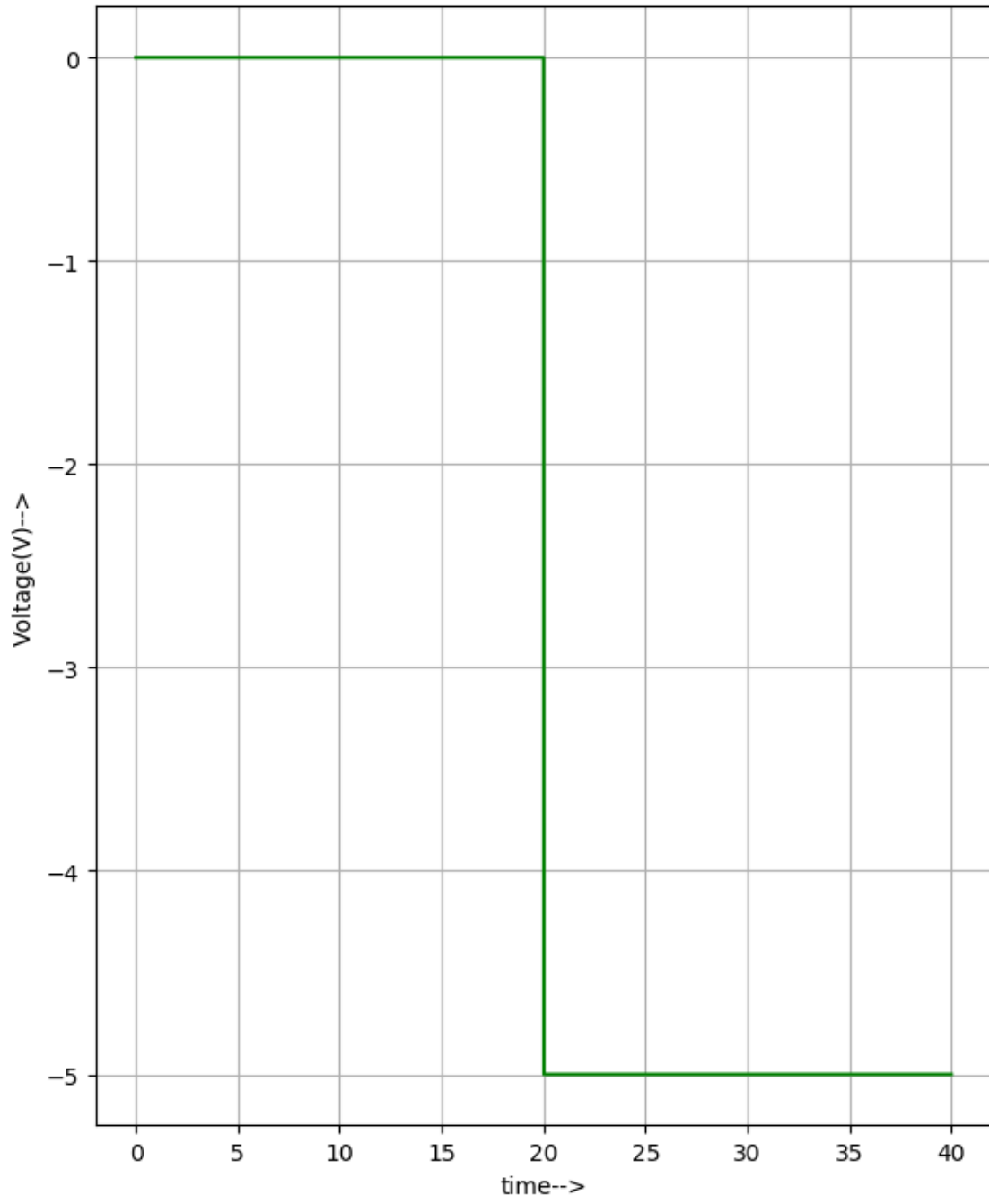


Python plot-Output Waveforms:


L:

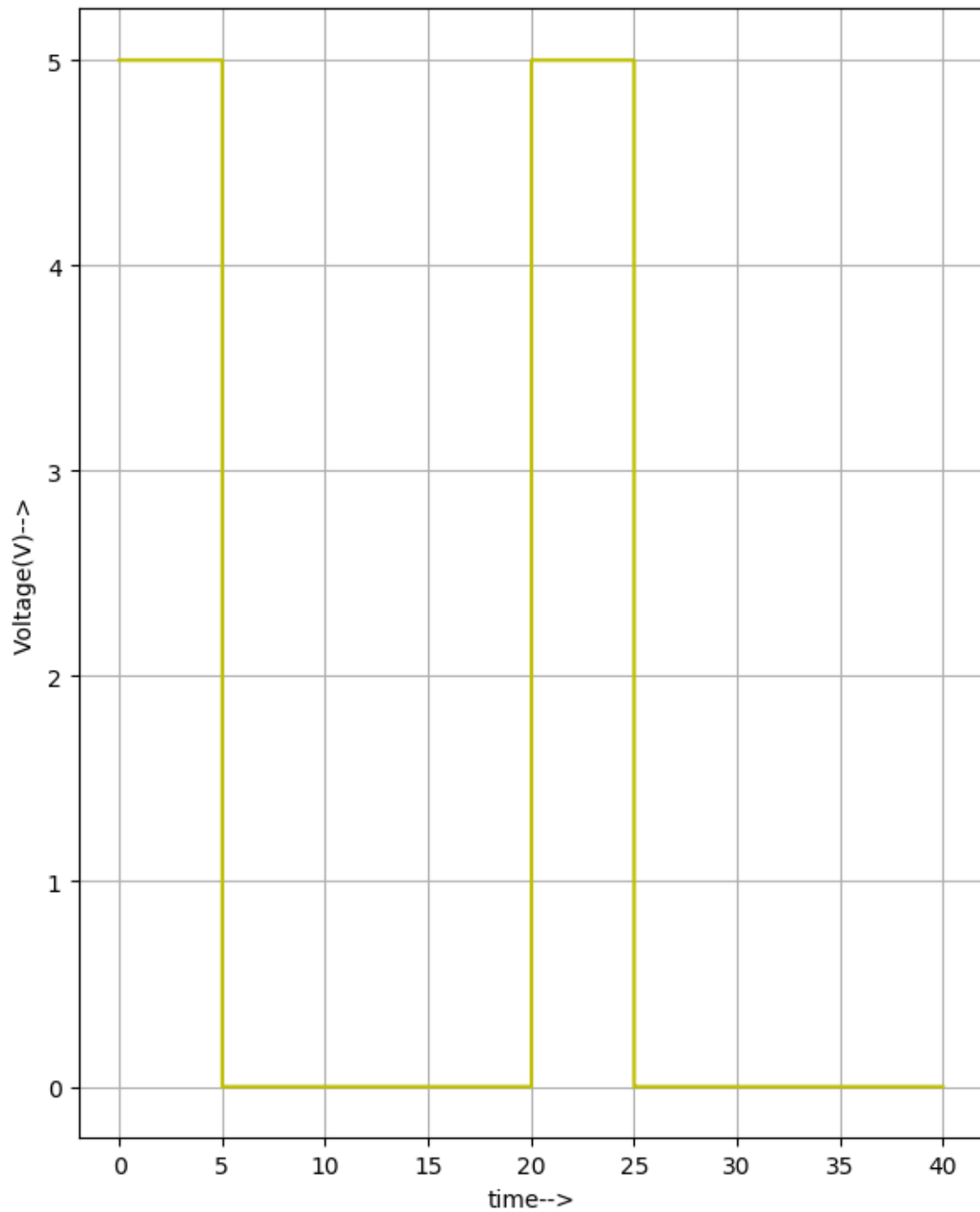


M:

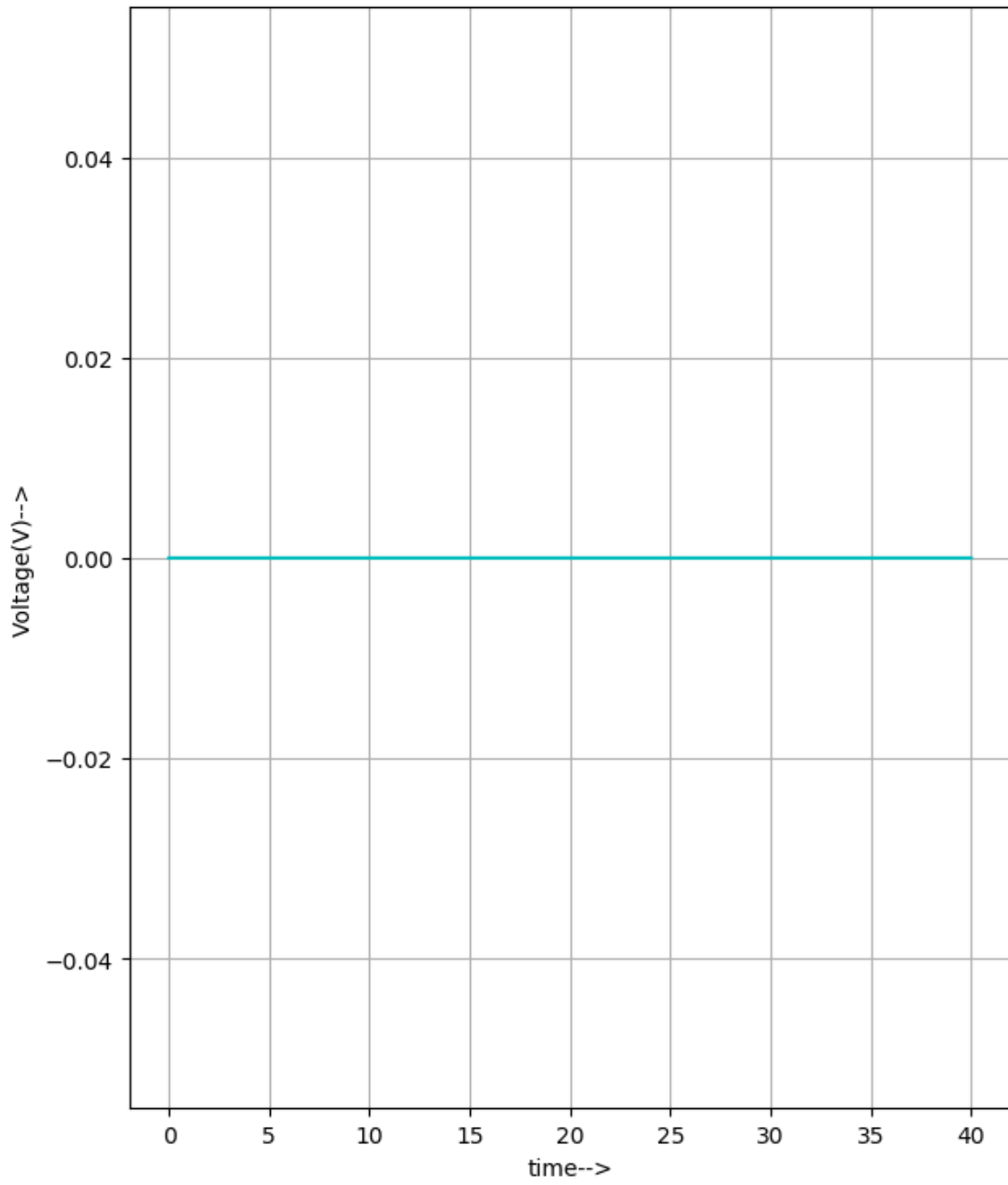


N:

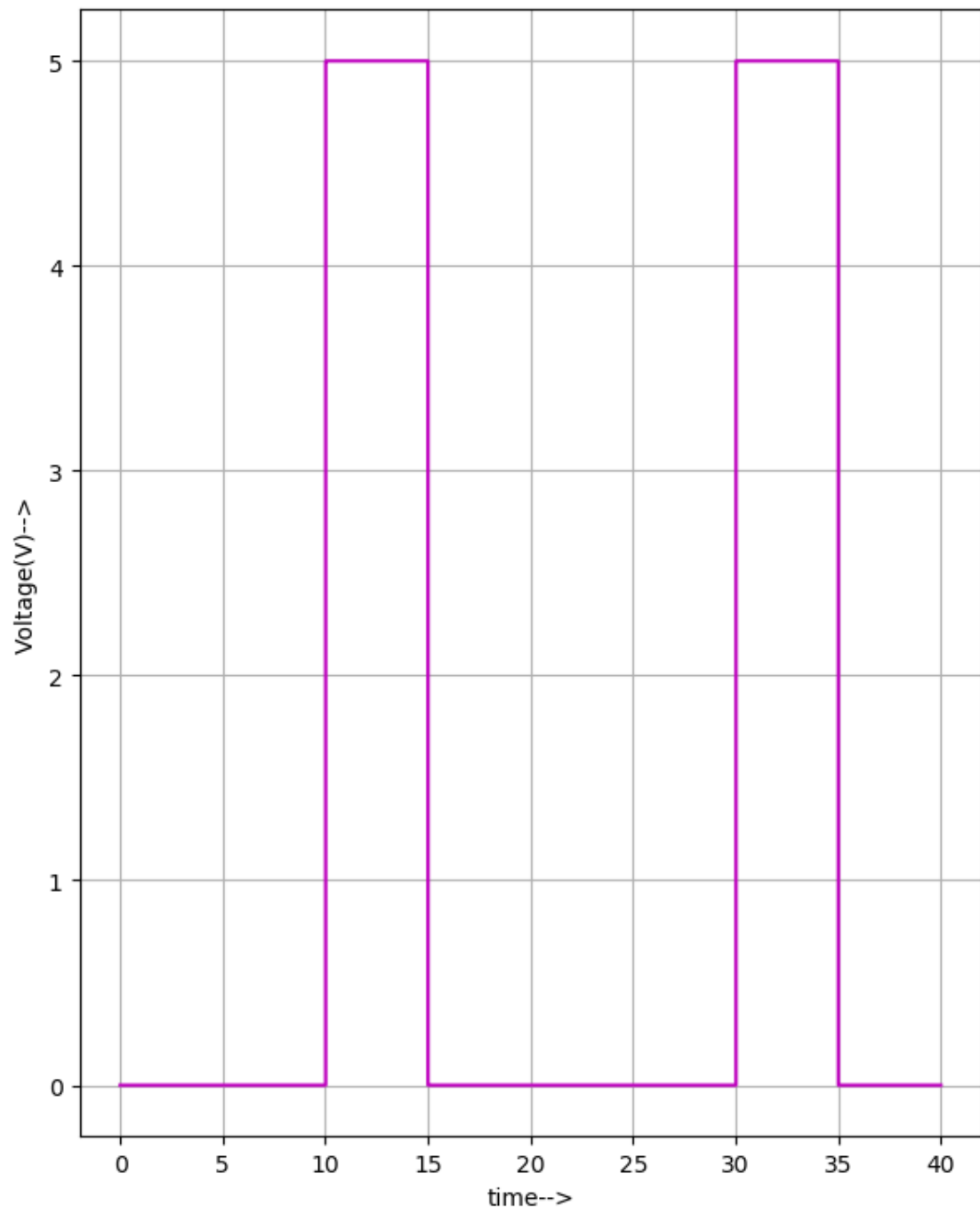


O:

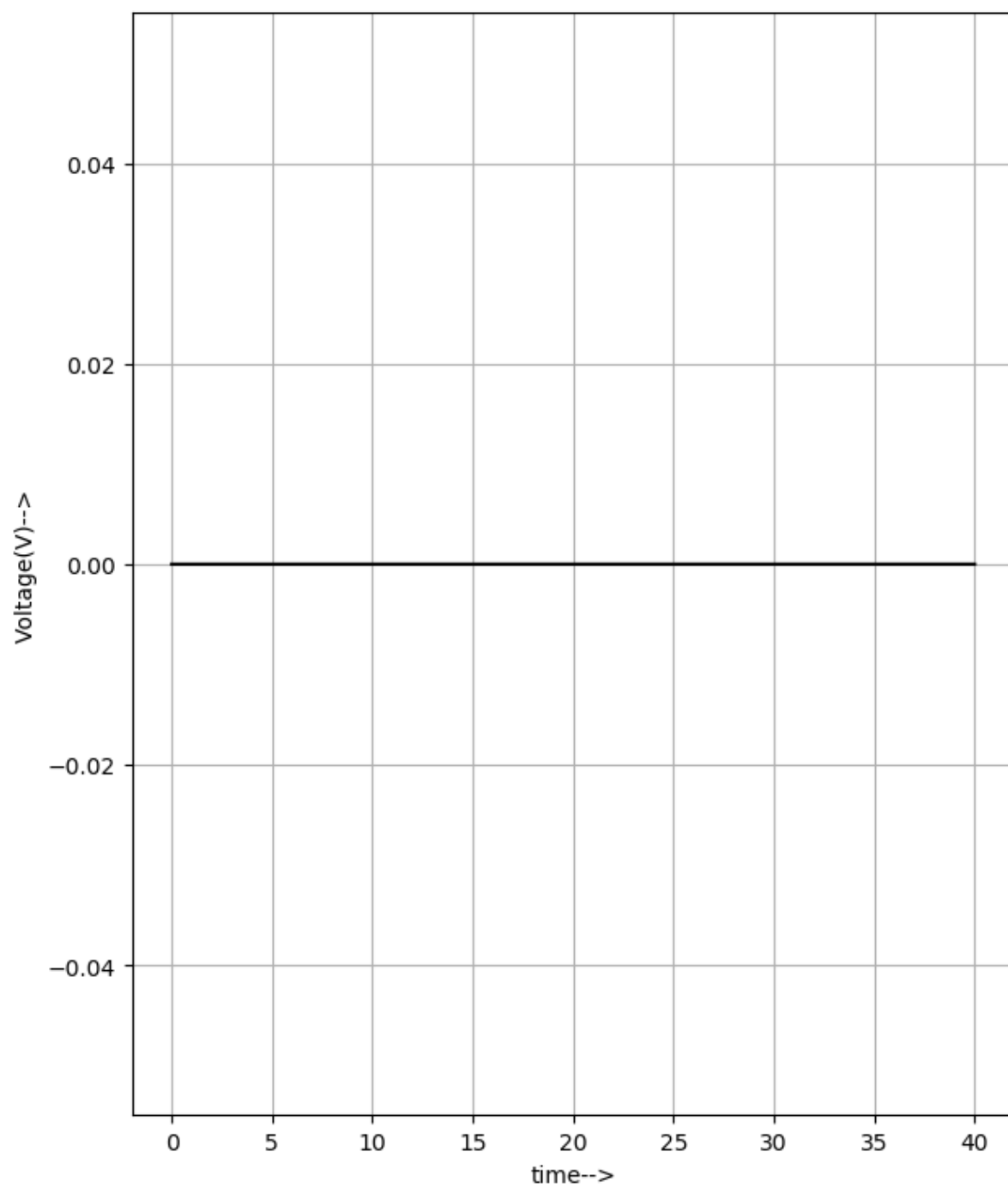


P:

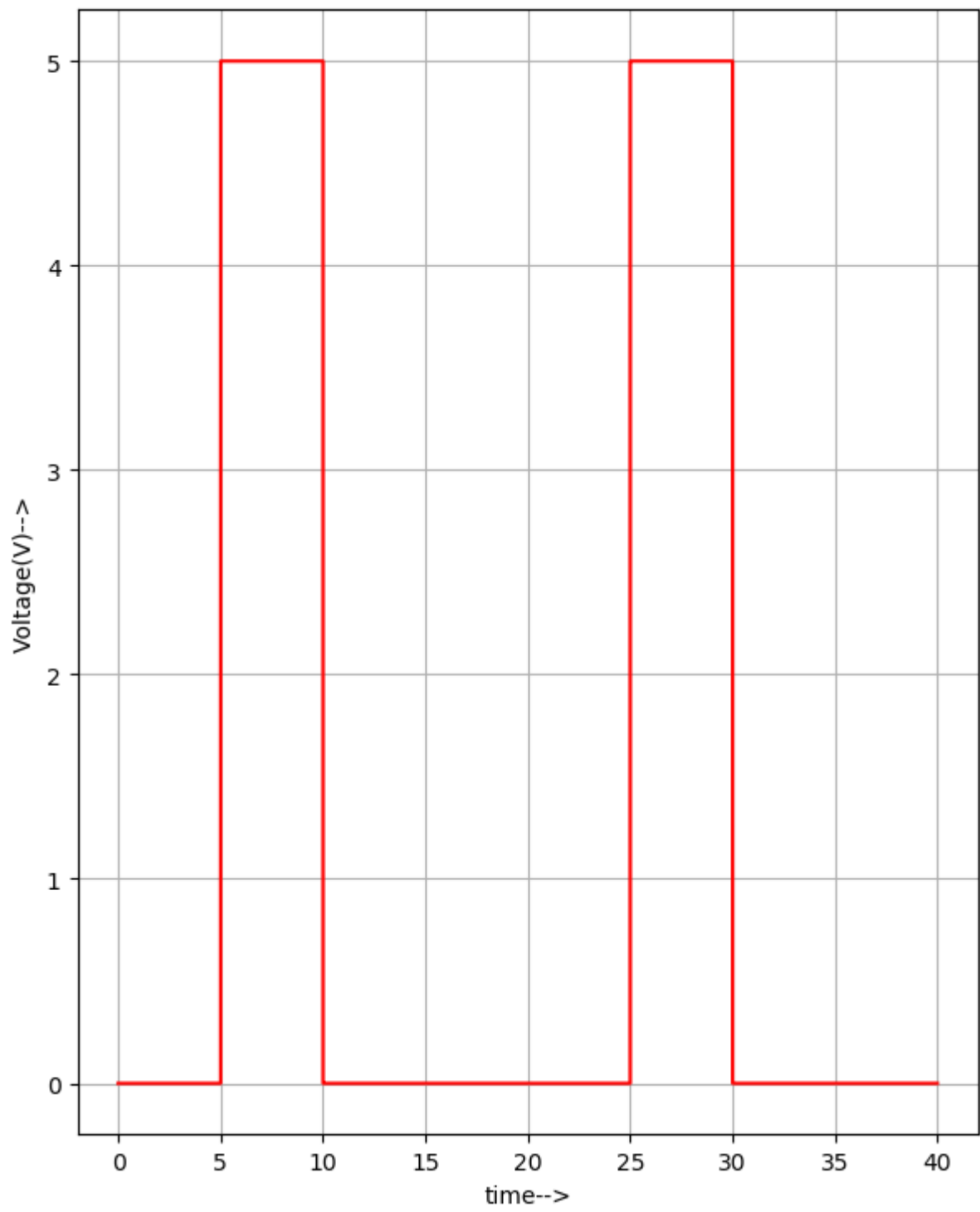


Q:

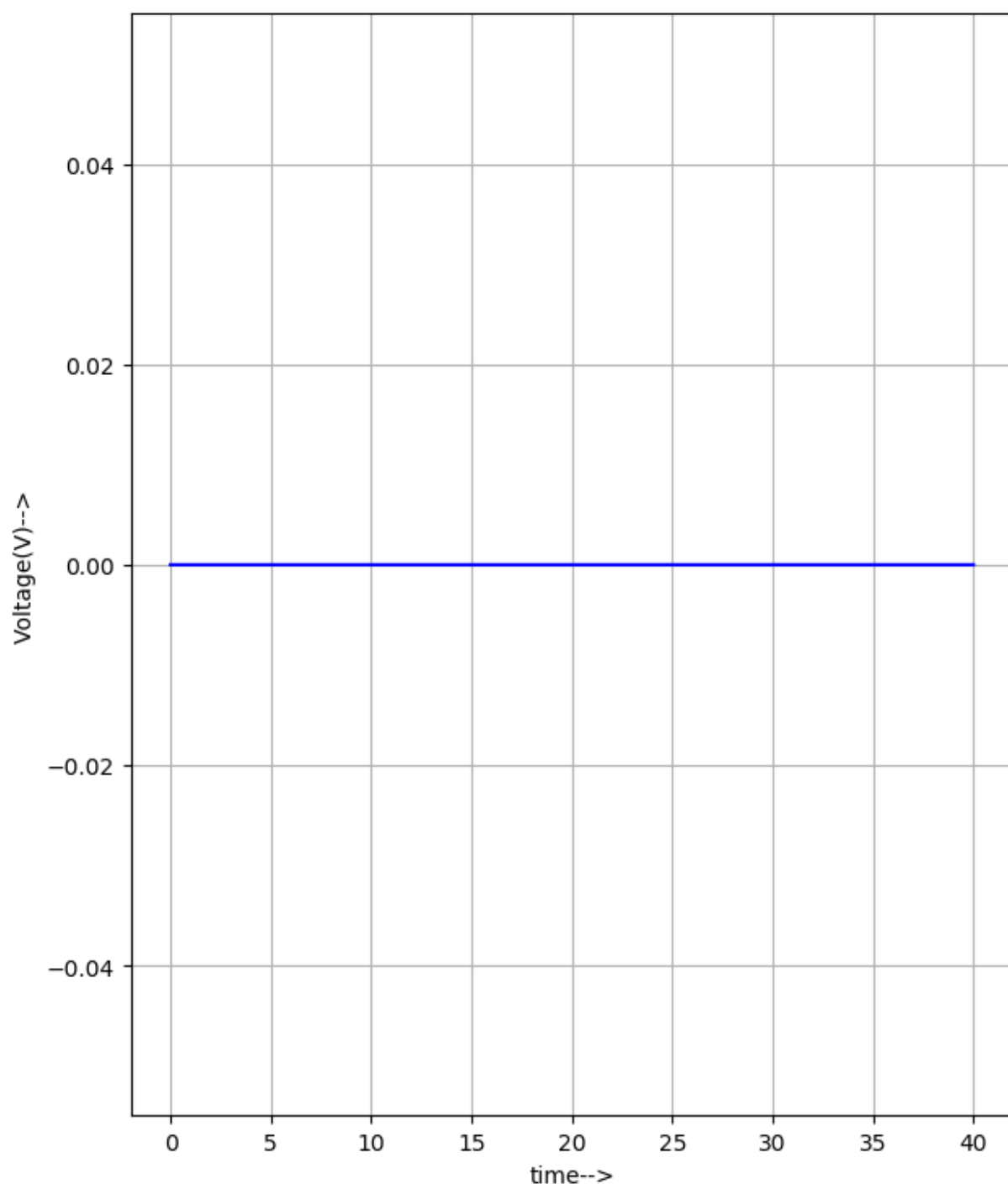

R:

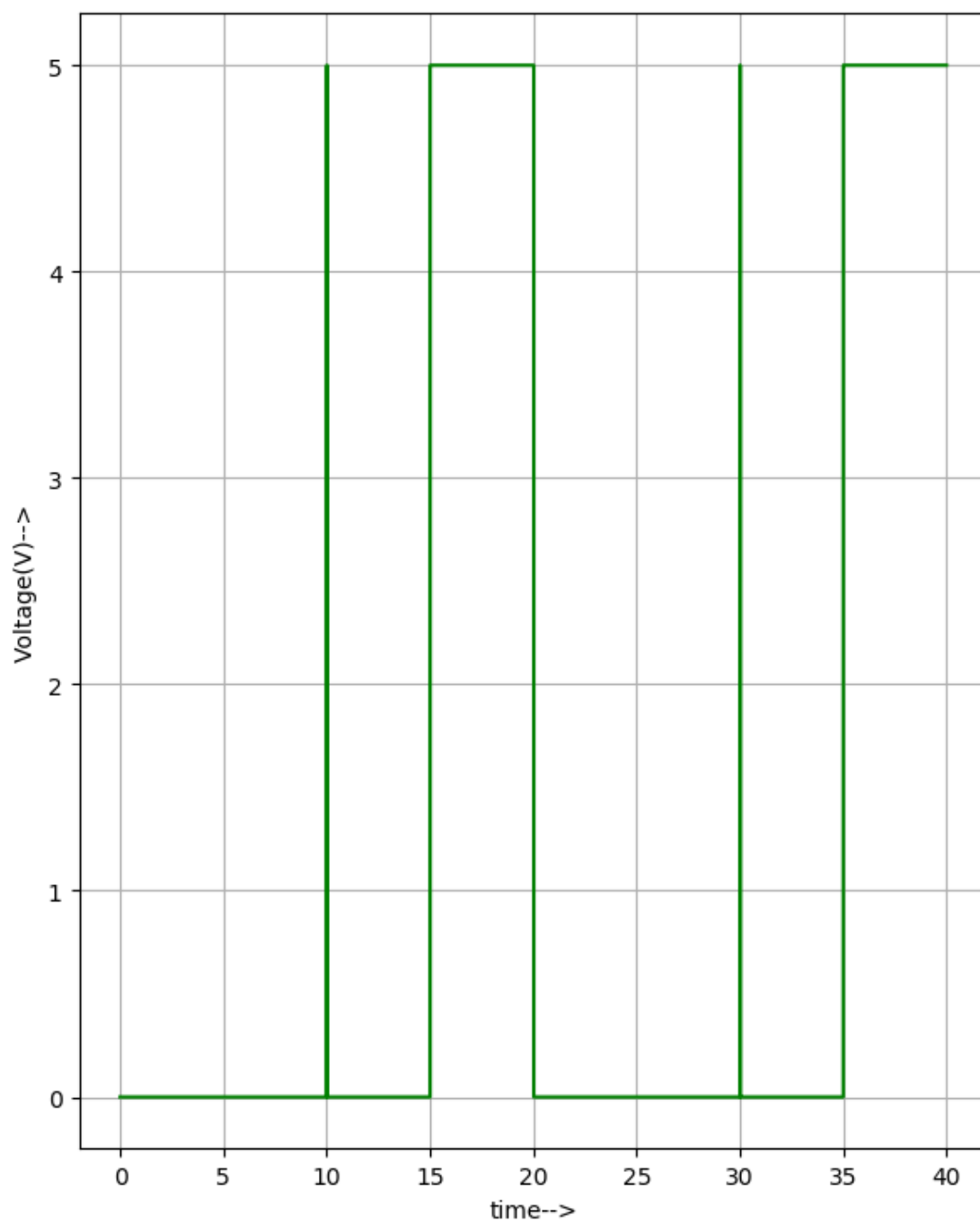

S:

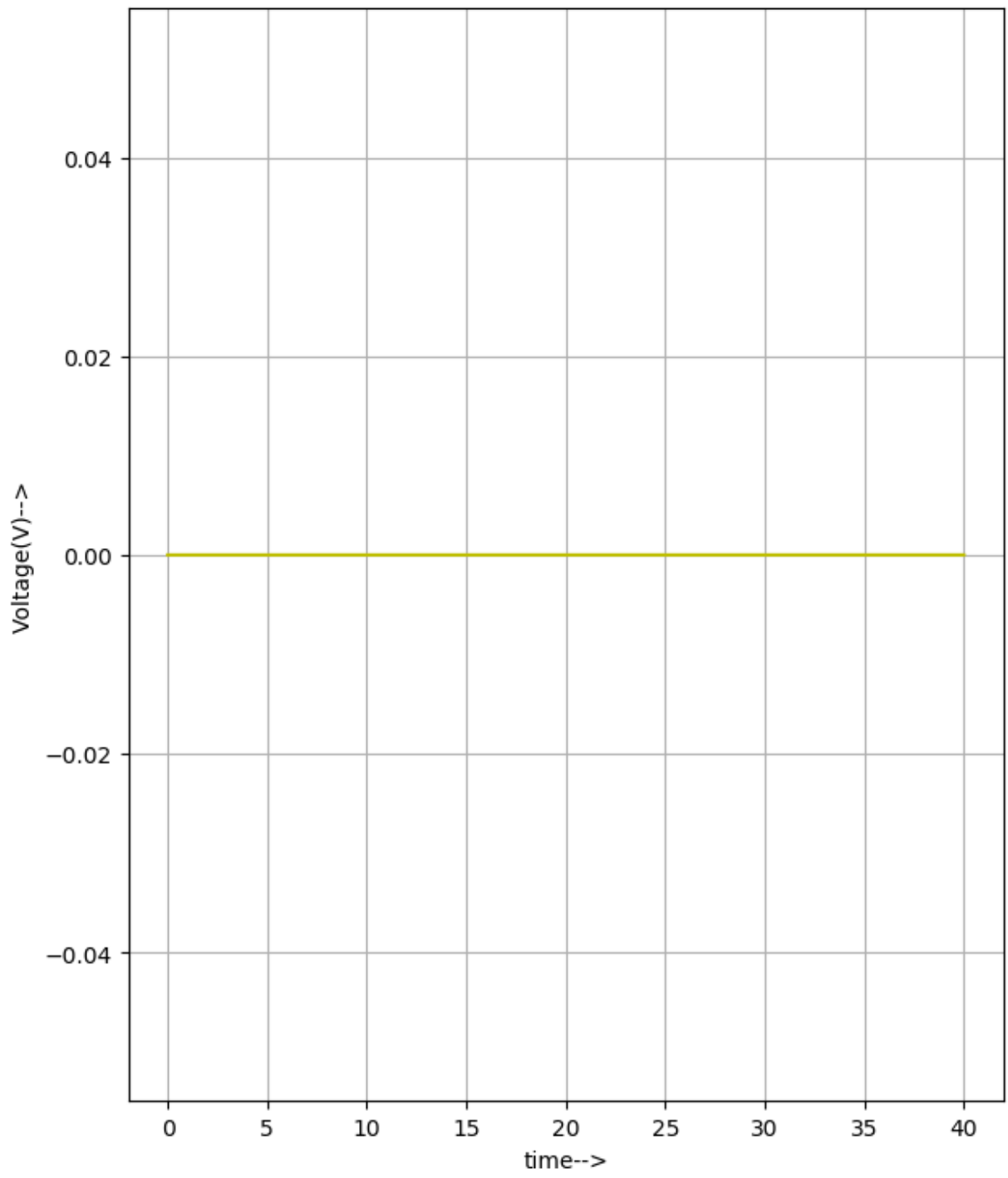

Source/Reference(s):

<https://www.elprocus.com/designing-3-line-to-8-line-decoder-demultiplexer/>