


Name of the participant: MS SUSMITHA K

Title of the circuit: 9'S COMPLEMENT OF A BCD DIGIT


Theory:

If the number is binary, then use 1's complement and 2's complement. But in case, when the number is a decimal number, we will use the 9's and 10's complement. The 9's complement is used to find the subtraction of a decimal numbers. The 9's complement of a number is calculated by subtracting each digit of the number by 9. With the help of 9's complement, the process of subtraction is done in a much easier way.

Logic Diagram:

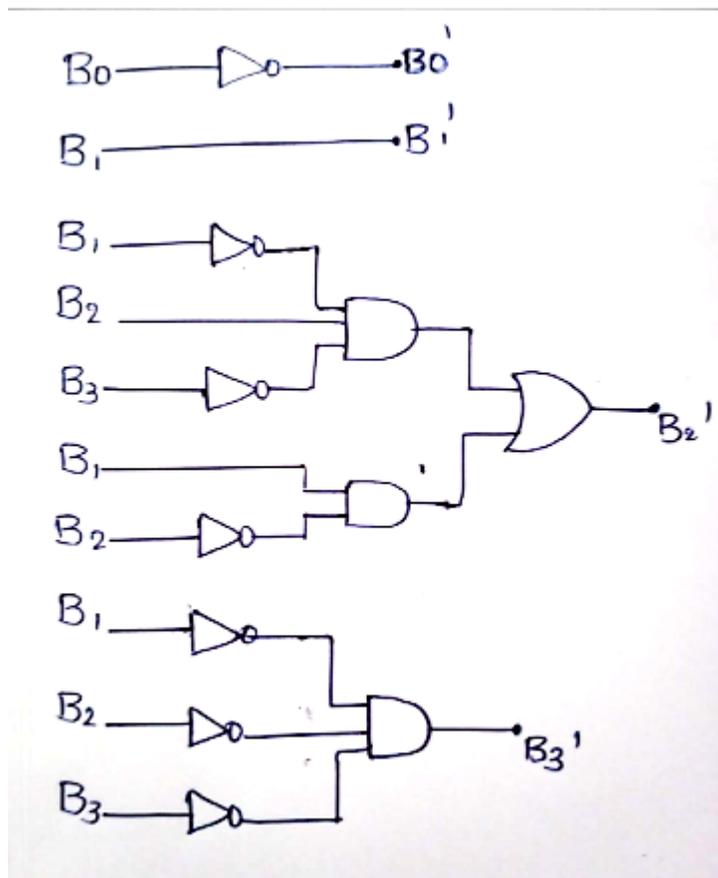

Schematic:

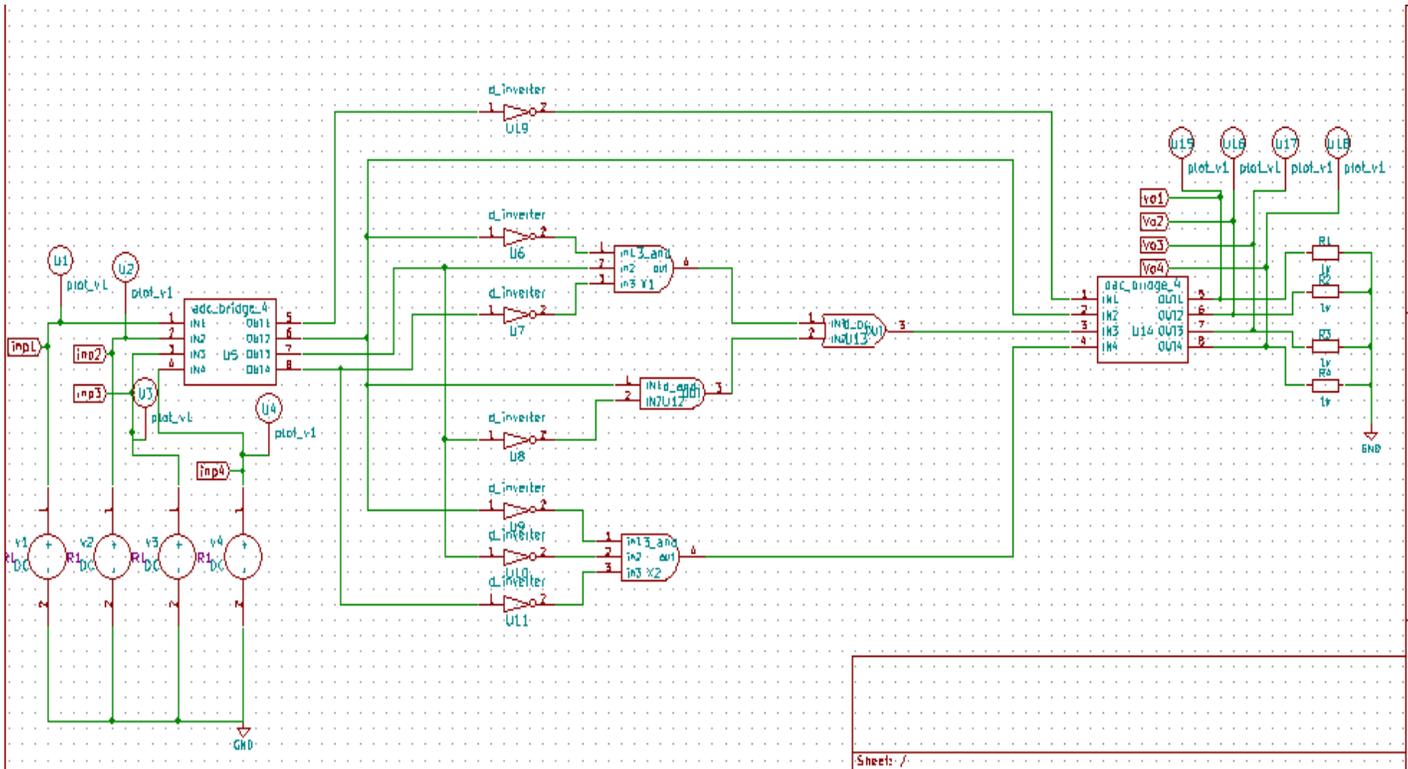

Results(Input Waveforms and/or Multimeter readings):

Add parameters for DC source v1

Enter value(Volts/Amps):

Add parameters for DC source v2

Enter value(Volts/Amps):



Add parameters for DC source v3



Enter value(Volts/Amps):

Add parameters for DC source v4

Enter value(Volts/Amps):

Ngspice plots:

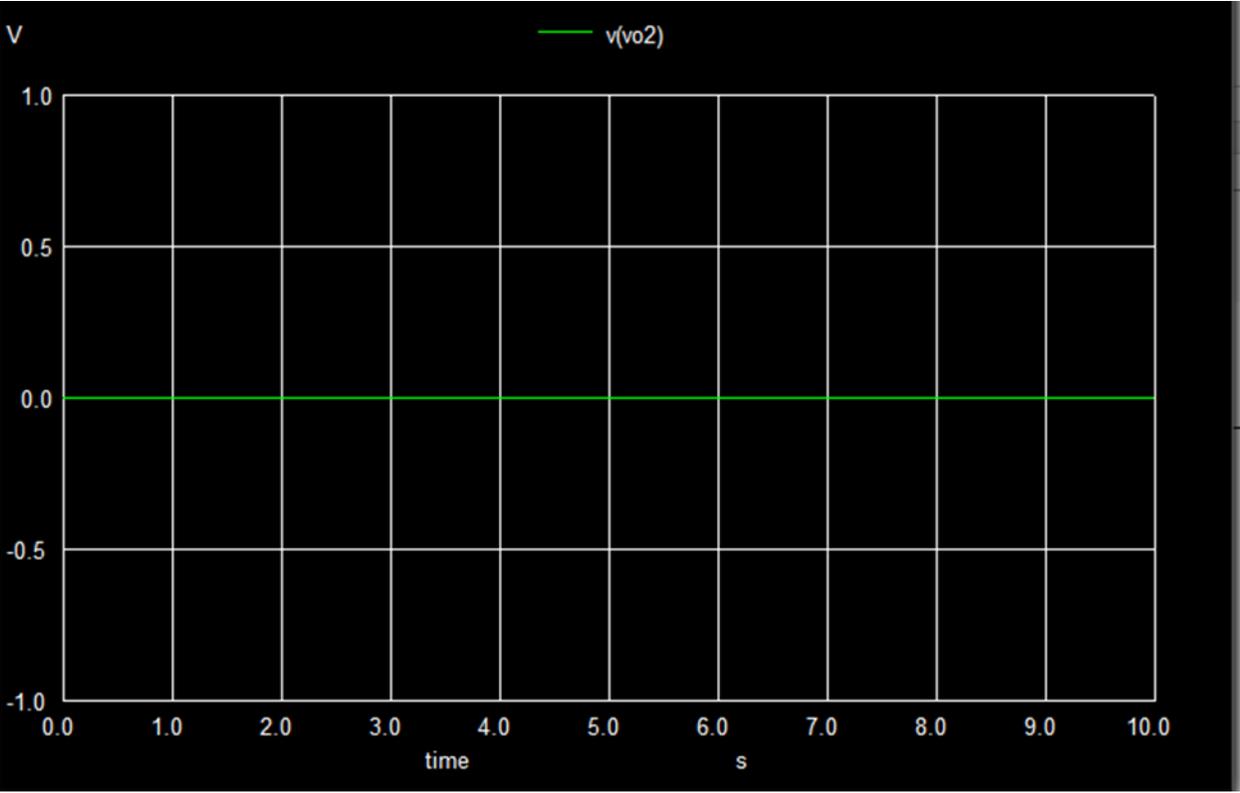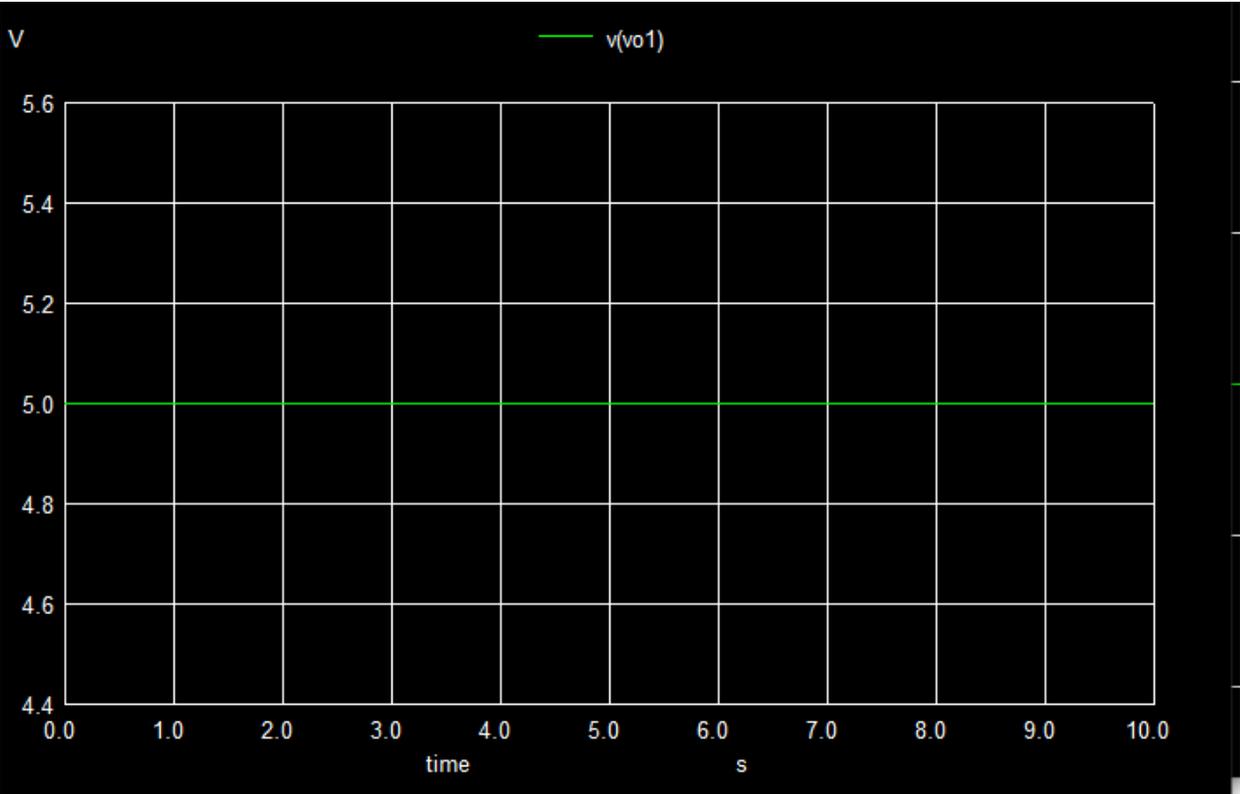

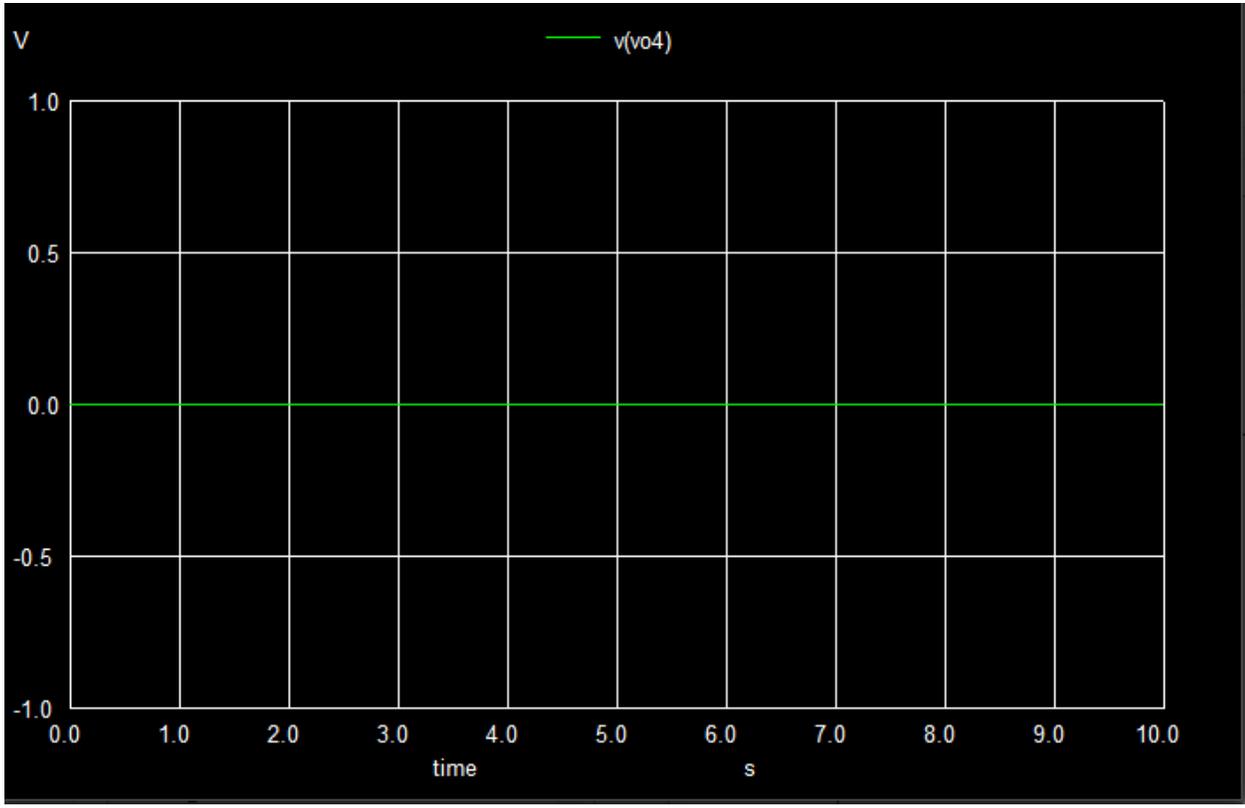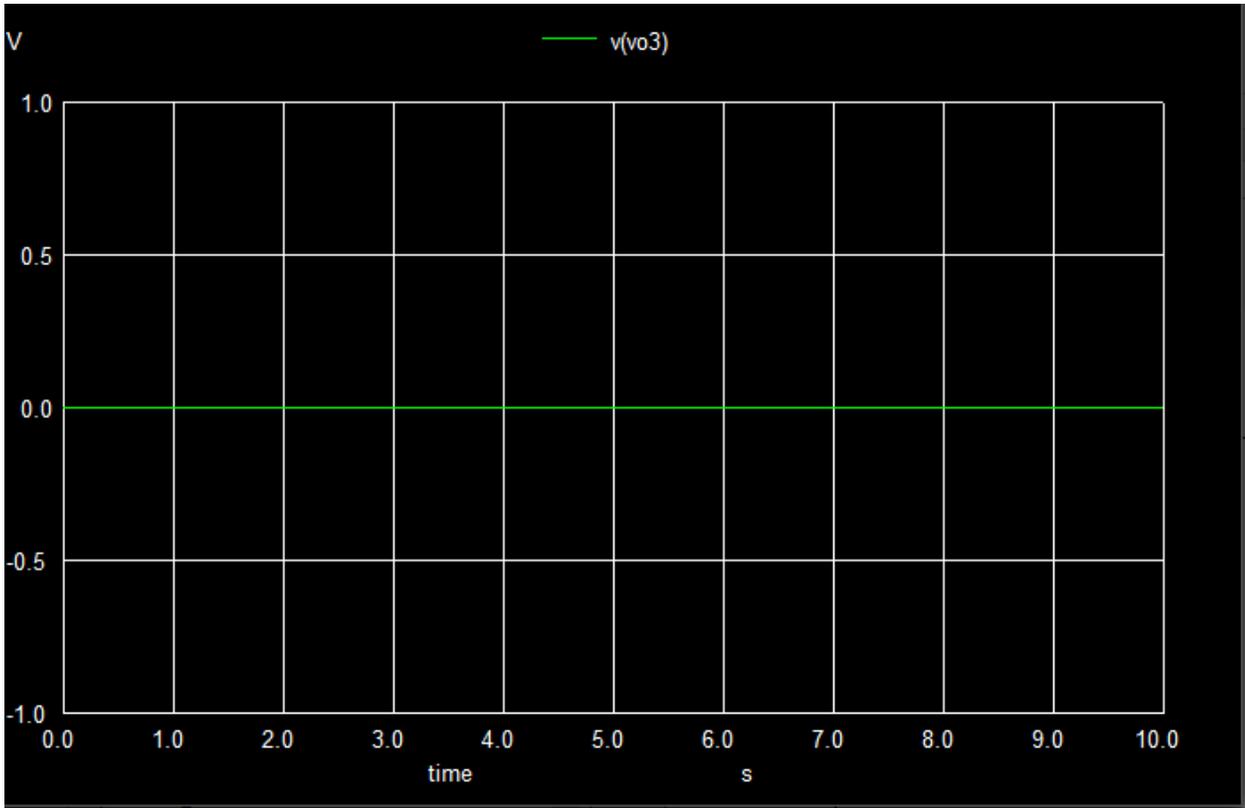

Reference:

<https://www.instructables.com/BINARY-CODE-CONVERTER-USING-9S-COMPLEMENT/>