

Circuit Simulation Project

<https://esim.fossee.in/circuit-simulation-project>

Name of the Participant: Anuj Singh Chauhan
Project Guide: Dr R. Maheshwari
Title of the circuit: Mod-7 Twisted Ring Counter Using J-K Flip Flop

Theory:

A twisted ring counter, also known as Johnson counter or walking ring counter, is a shift register in which the complement of the output of the last register is given as the input of the first register and circulates a stream of ones followed by zeros around the ring.


For example after every clock cycle the parallel output of the counter is as follows:

0000, 1000, 1100, 1110, 0111, 0011, 0001, 0000

As there are only 7 distinct states hence it's a Mod -7 counter.

In this project I have implemented Mod-7 Twisted Ring Counter using 4 J-K flip flops. So to make the J-K flip flop act like D flip flop we have to give the input to J and complement of the input to K. By using this principal I constructed this Mod-7 Twisted Ring Counter.

Circuit Diagram:

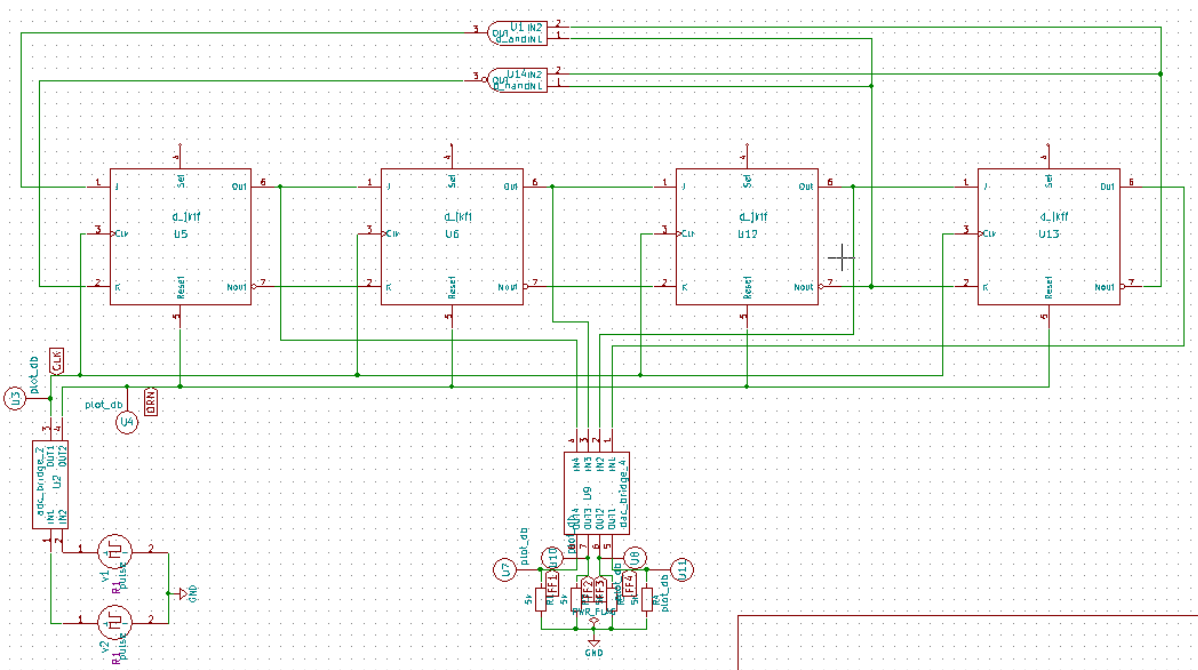


Results:


Add parameters for pulse source v2	
Enter initial value(Volts/Amps):	0
Enter pulsed value(Volts/Amps):	5
Enter delay time (seconds):	5
Enter rise time (seconds):	0
Enter fall time (seconds):	0
Enter pulse width (seconds):	5
Enter period (seconds):	10

Add parameters for pulse source v1	
Enter initial value(Volts/Amps):	5
Enter pulsed value(Volts/Amps):	0
Enter delay time (seconds):	5
Enter rise time (seconds):	0
Enter fall time (seconds):	0
Enter pulse width (seconds):	0
Enter period (seconds):	80


Fig 1: Source Details

 


Plot 1: Clock Signal

 


Plot 2: Orientation Signal

 


Plot 3: Output of Flip Flop 1

 


Plot 4: Output of Flip Flop 2

 

Plot 5: Output of Flip Flop 3

 

Plot 6: Output of Flip Flop 4

 

Plot 7: Output of All the Flip Flops

Hence the pattern formed here is 0000, 1000, 1100, 1110, 0111, 0011, 0001, and 0000.

Source/Reference(s):

<https://www.geeksforgeeks.org/n-bit-johnson-counter-in-digital-logic/>

https://www.electronics-tutorials.ws/sequential/seq_6.html