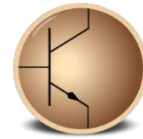




VIT[®]
Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)



CIRCUIT SIMULATION PROJECT

<https://esim.fossee.in/circuit-simulation-project>

Name of the participant: Sam Meshach D

Project Guide: Dr. Maheswari. R

Title of the circuit:

2 - BIT MAGNITUDE COMPARATOR

THEORY/DESCRIPTION:

A magnitude digital Comparator is a combinational circuit that compares two digital or binary numbers to find out whether one binary number is equal, less than or greater than the other binary number.

A comparator used to compare two binary numbers each of two bits is called a 2-bit Magnitude comparator. It consists of four inputs and

three outputs to generate less than, equal to and greater than between two binary numbers.

The truth table for a 2-bit comparator is given below:

INPUT				OUTPUT		
A1	A0	B1	B0	A<B	A=B	A>B
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

From the above truth table K-map for each output can be drawn as follows:

A > B

A1A0 \ B1B0	B1B0			
	00	01	11	10
00	0	0	0	0
01	1	0	0	0
11	1	1	0	1
10	1	1	0	0

A = B

A1A0 \ B1B0	B1B0			
	00	01	11	10
00	1	0	0	0
01	0	1	0	0
11	0	0	1	0
10	0	0	0	1

$A < B$

	B_1B_0	00	01	11	10
A_1A_0	00	0	1	1	1
	01	0	0	1	1
	11	0	0	0	0
	10	0	0	1	0

From the above K-maps logical expressions for each output can be expressed as follows:

$$A > B: A_1B_1' + A_0B_1'B_0' + A_1A_0B_0'$$

$$A = B: A_1'A_0'B_1'B_0' + A_1'A_0B_1'B_0 + A_1A_0B_1B_0 + A_1A_0'B_1B_0'$$


$$: A_1'B_1' (A_0'B_0' + A_0B_0) + A_1B_1 (A_0B_0 + A_0'B_0')$$

$$: (A_0B_0 + A_0'B_0') (A_1B_1 + A_1'B_1')$$

$$: (A_0 \text{ Ex-nor } B_0) (A_1 \text{ Ex-nor } B_1)$$


$$A < B: A_1'B_1 + A_0'B_1B_0 + A_1'A_0'B_0$$

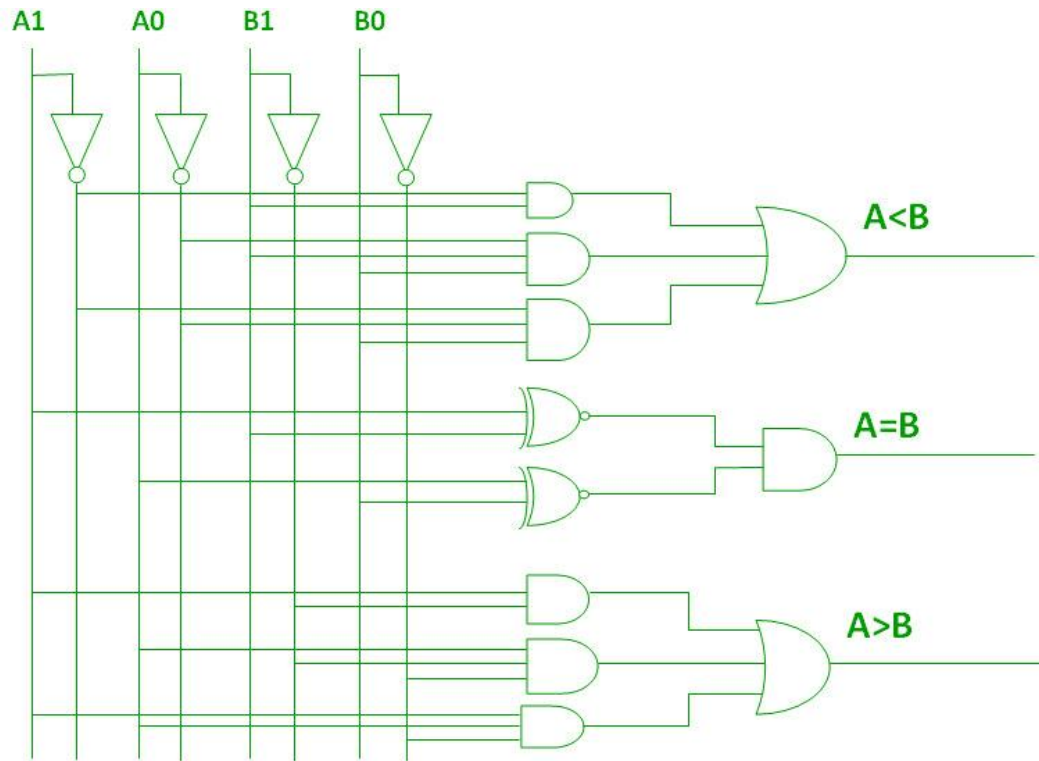
By using these Boolean expressions, we can implement a logic circuit for this comparator as given below:



ESIM CIRCUIT DIAGRAM FOR 2 - BIT MAGNITUDE

COMPARATOR :

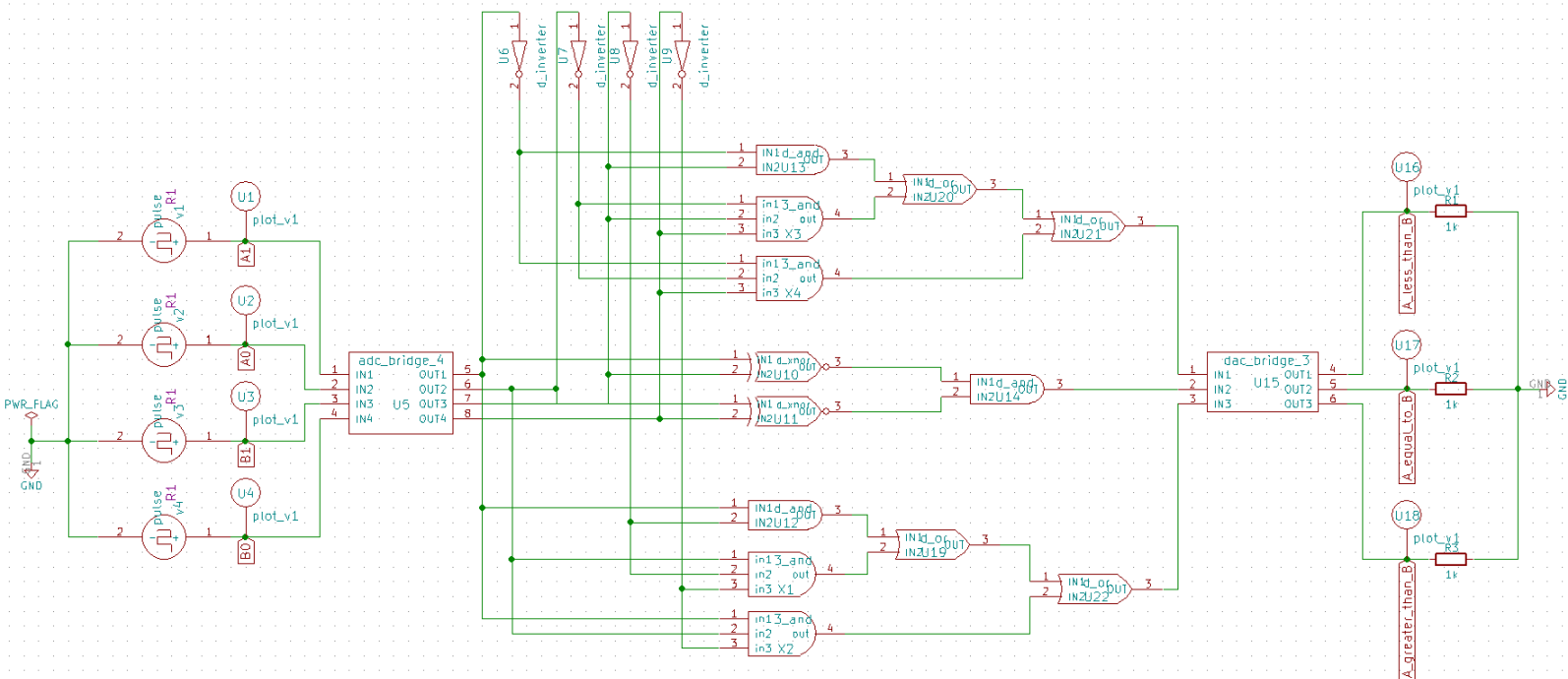

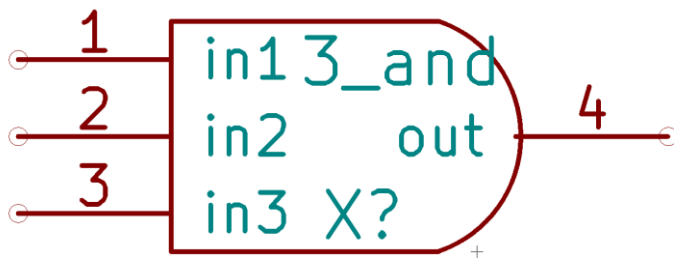


Subcircuit Symbol for 3-Input AND Gate (already exists in eSim_Subckt)


RESULT/OUTPUT:

- NGSPICE PLOTS:


INPUTS:

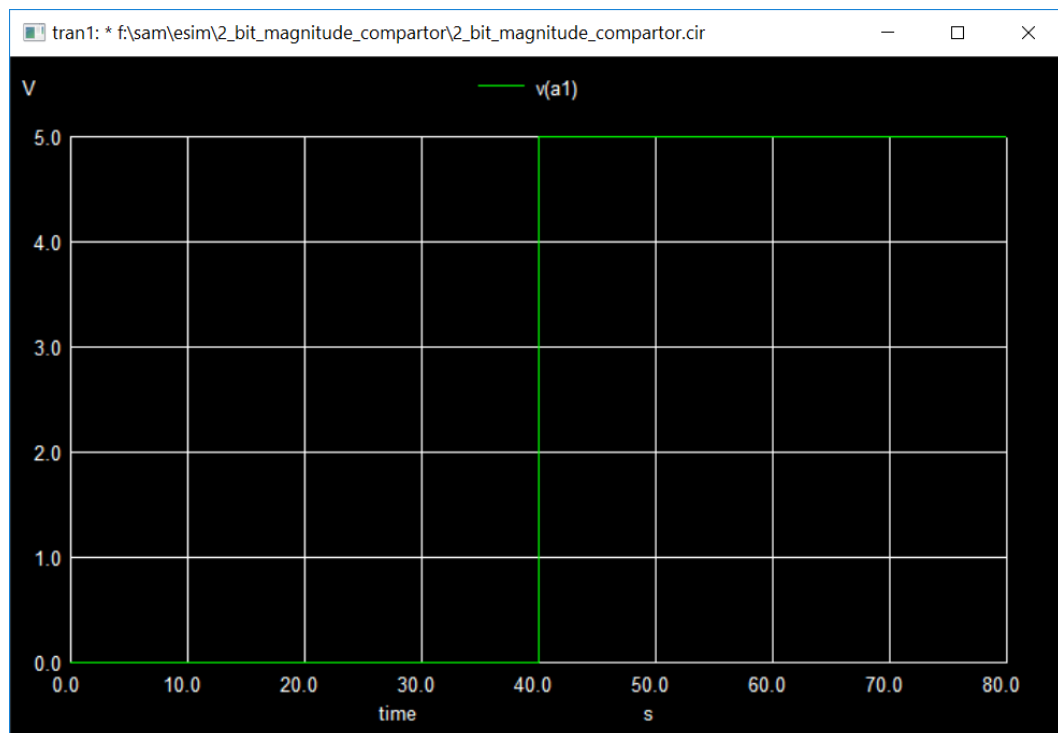


A1

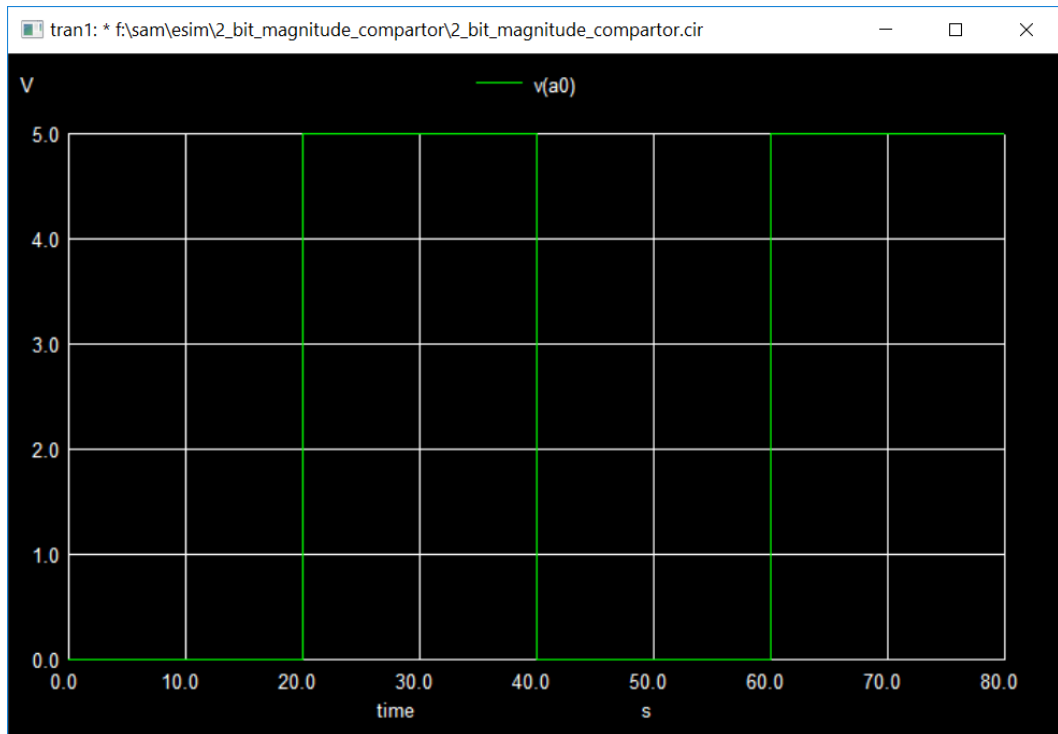

A0

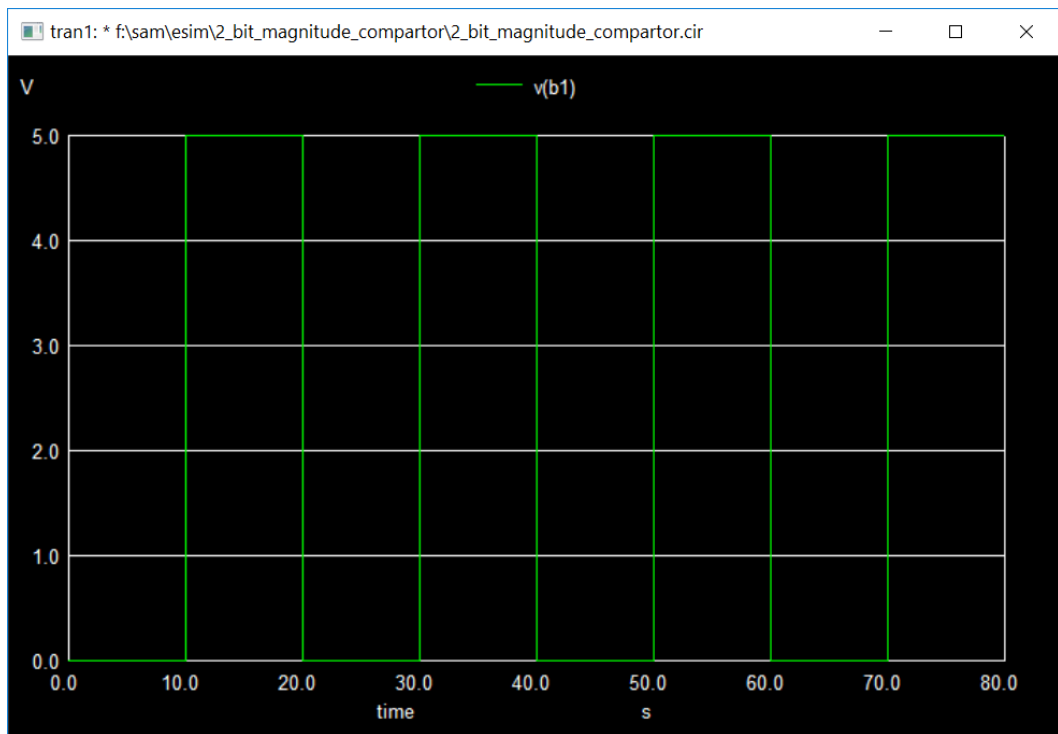


B1

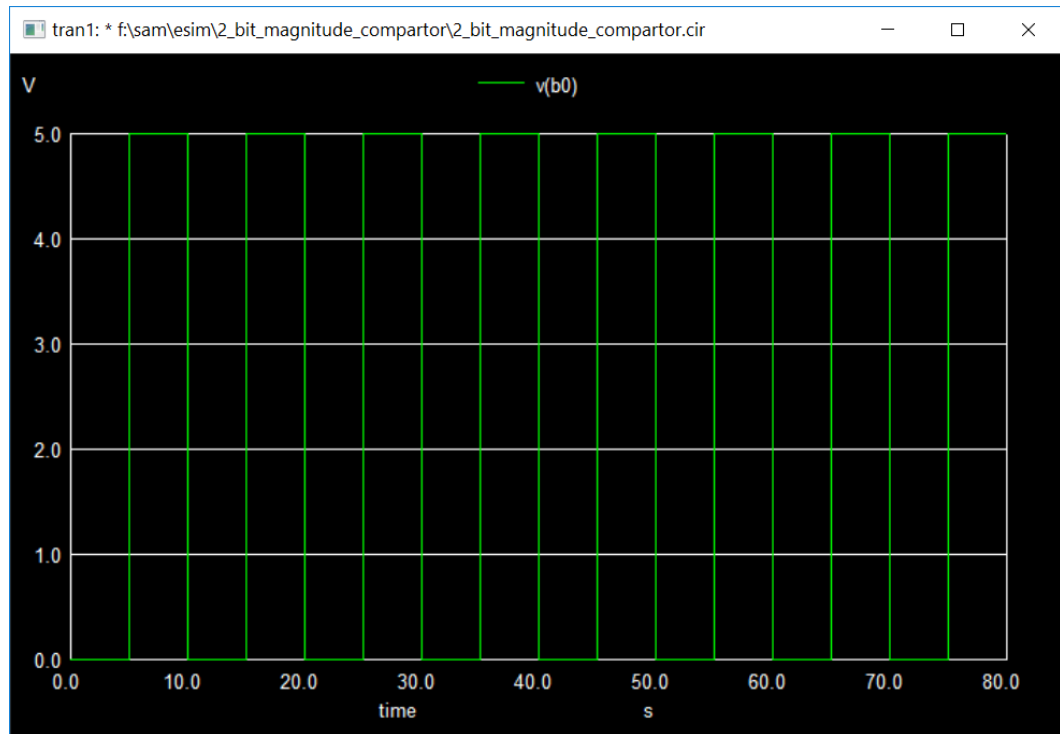


B0


OUTPUTS:

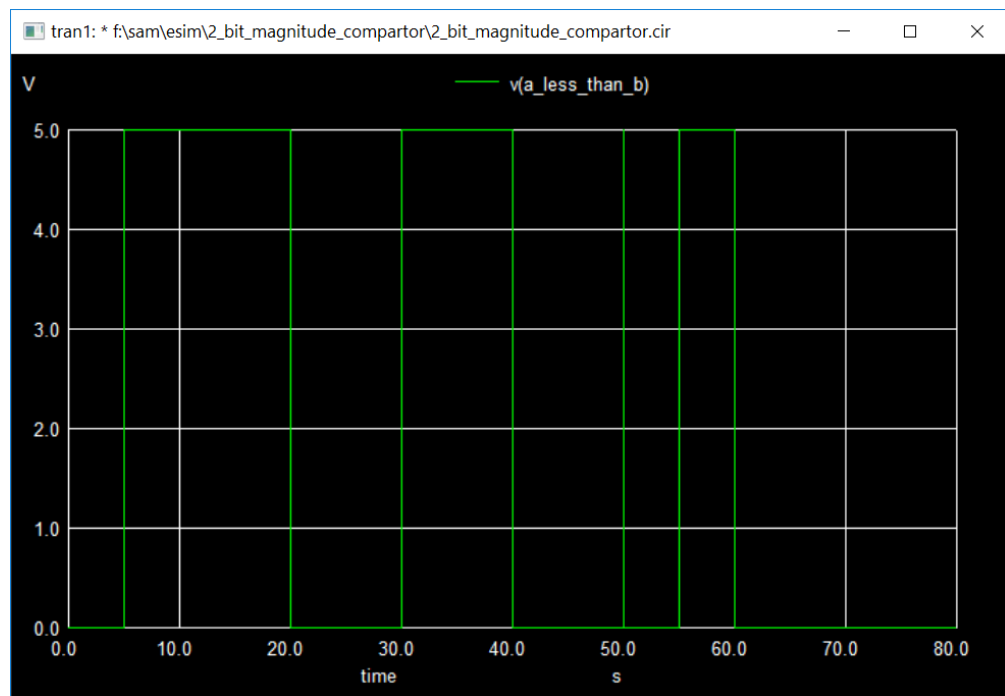

A < B

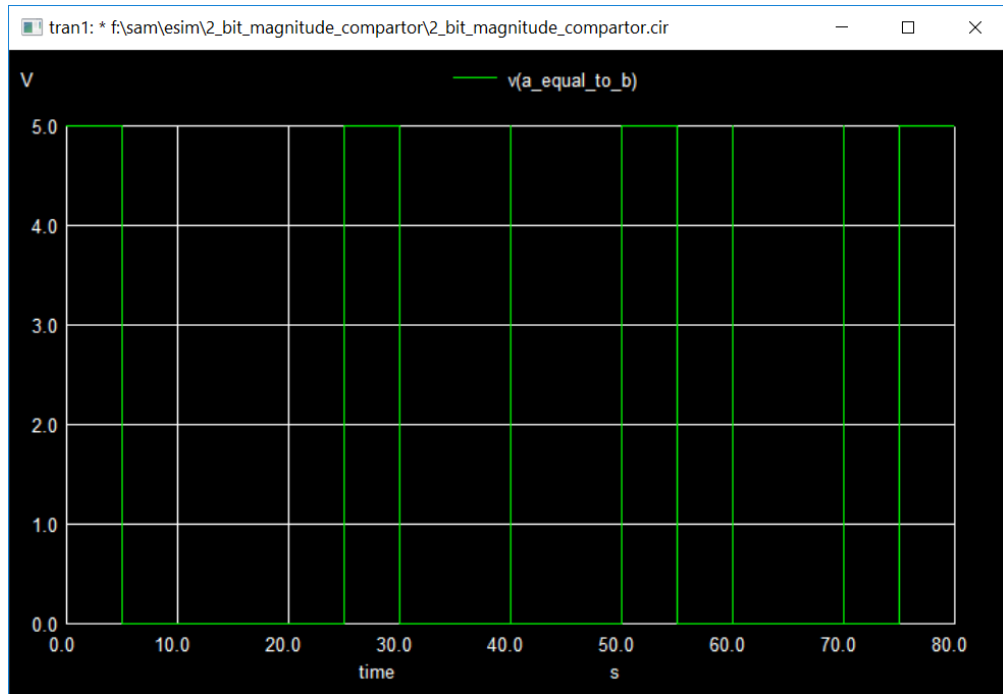


$A = B$

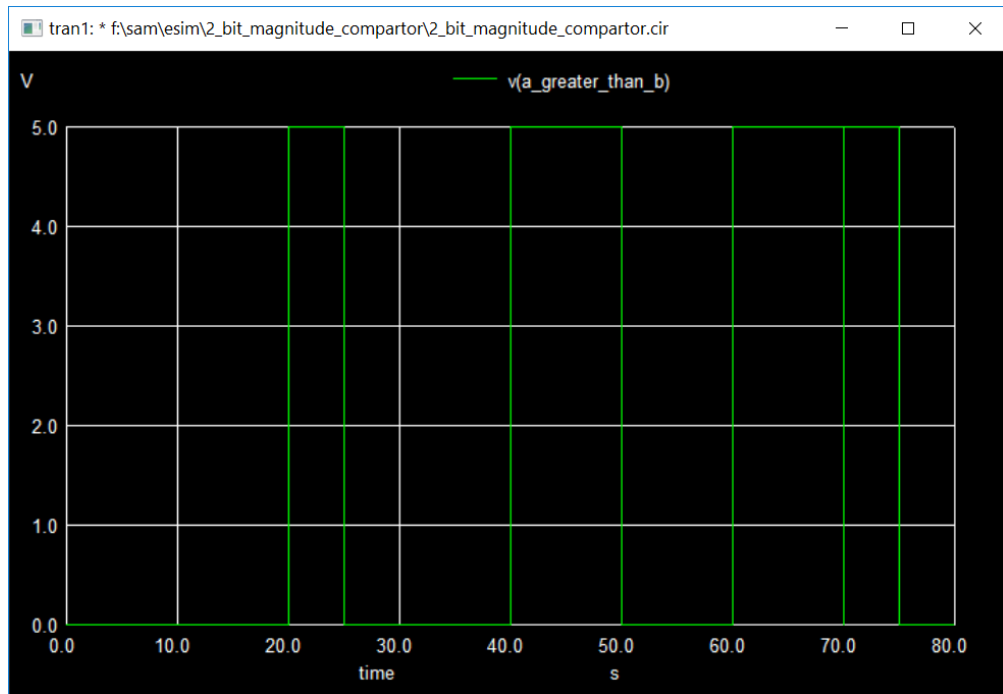


$A > B$

- **PYTHON PLOTS:**


INPUTS:

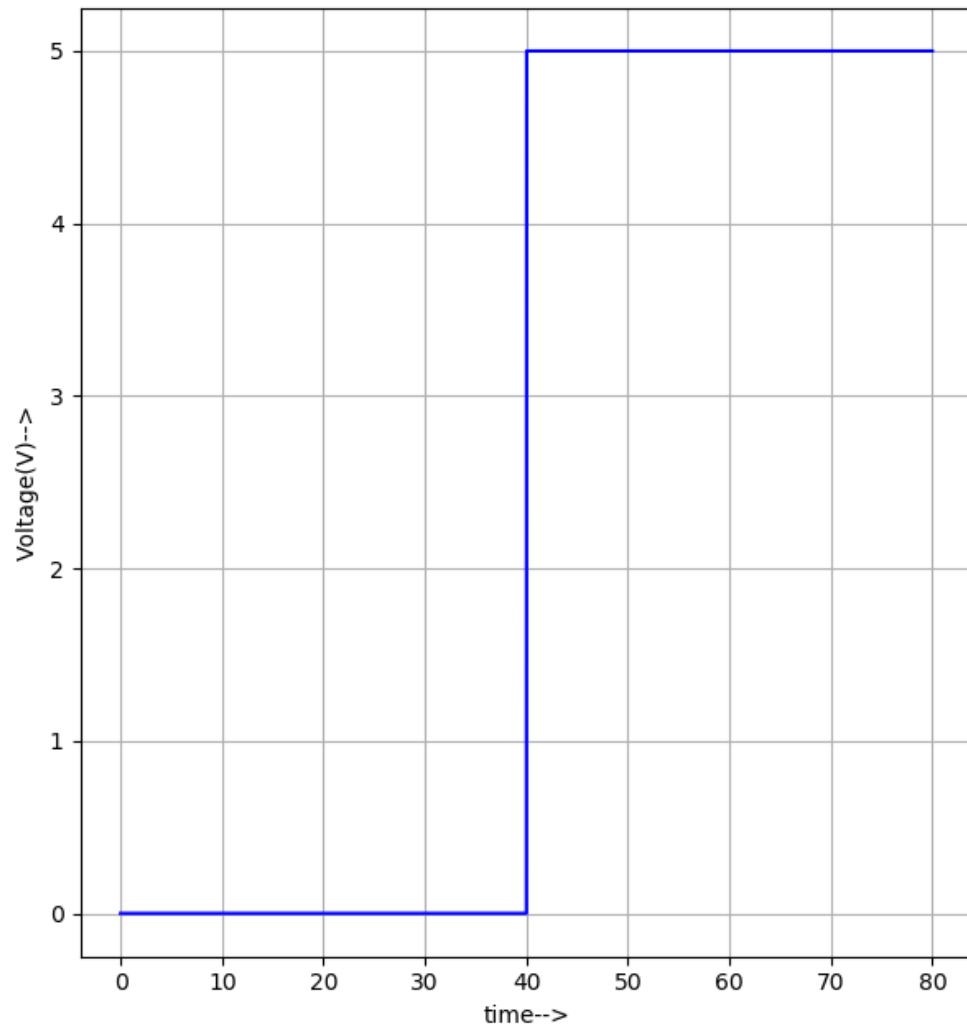


A1

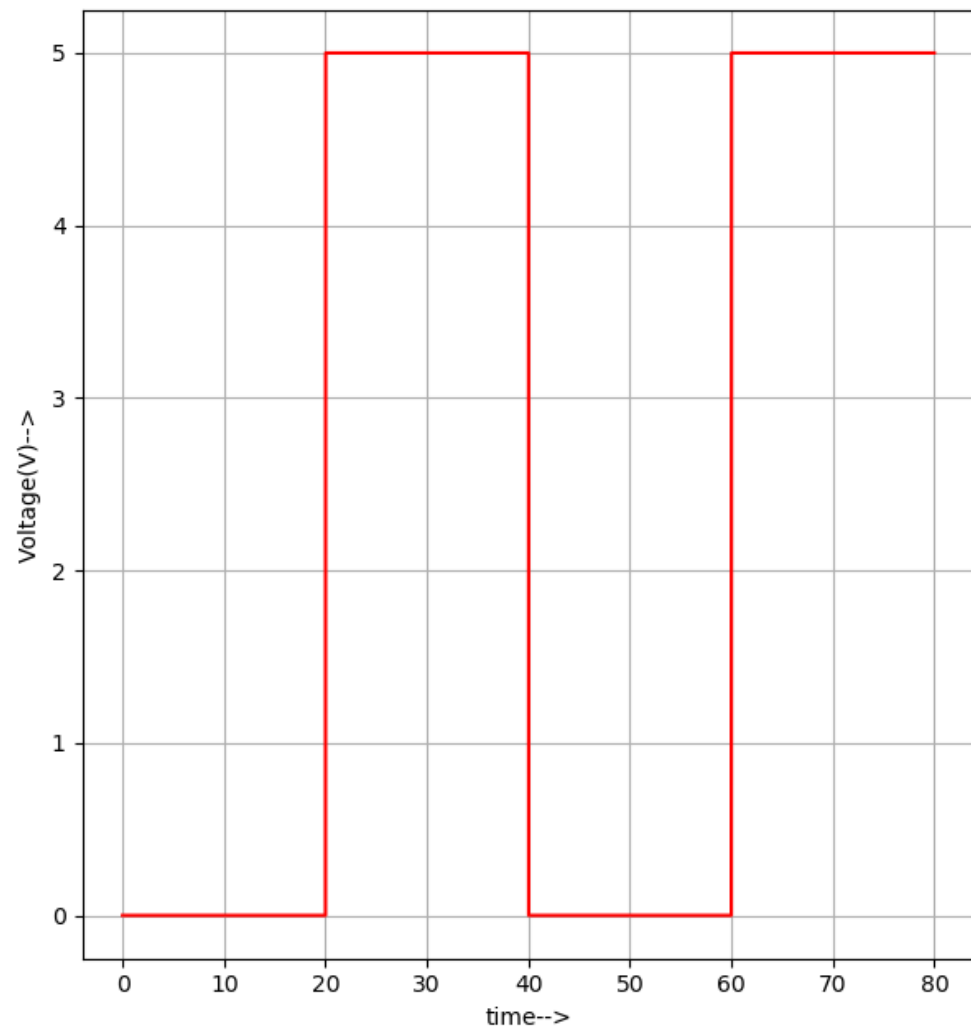

A0

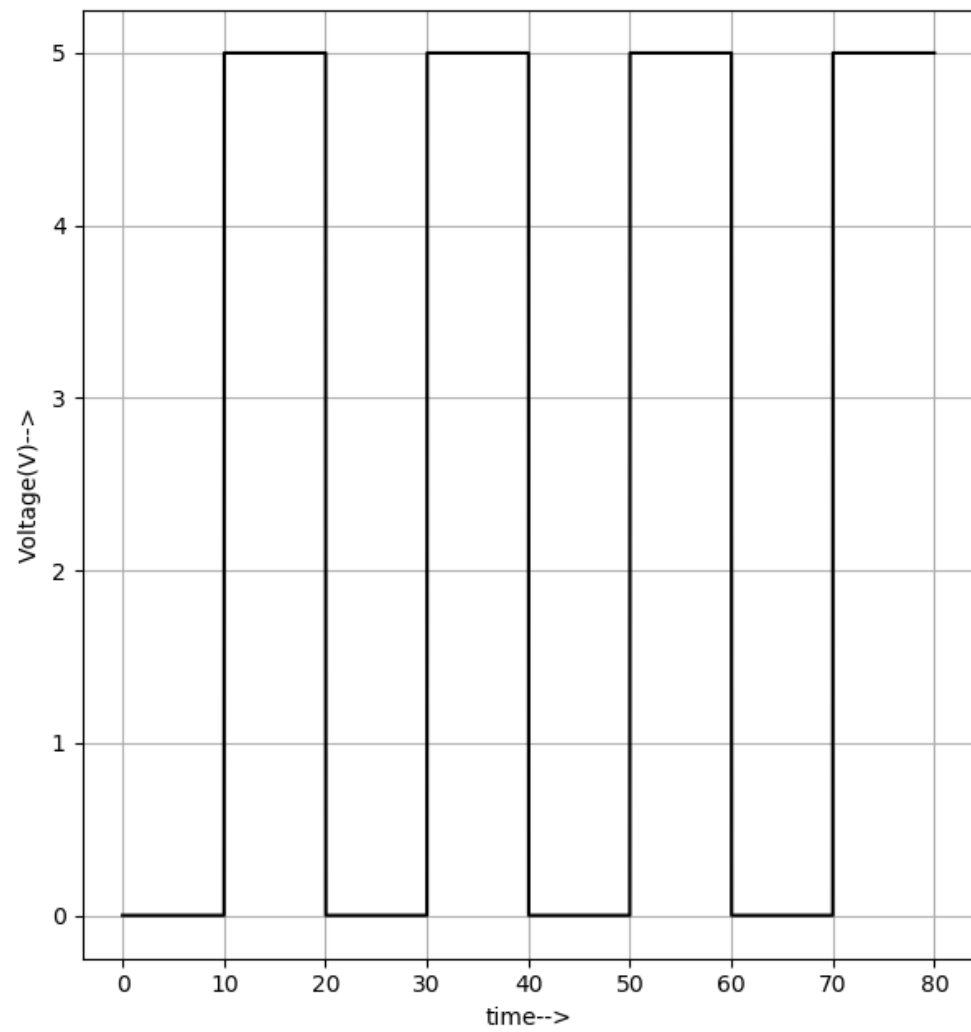


B1

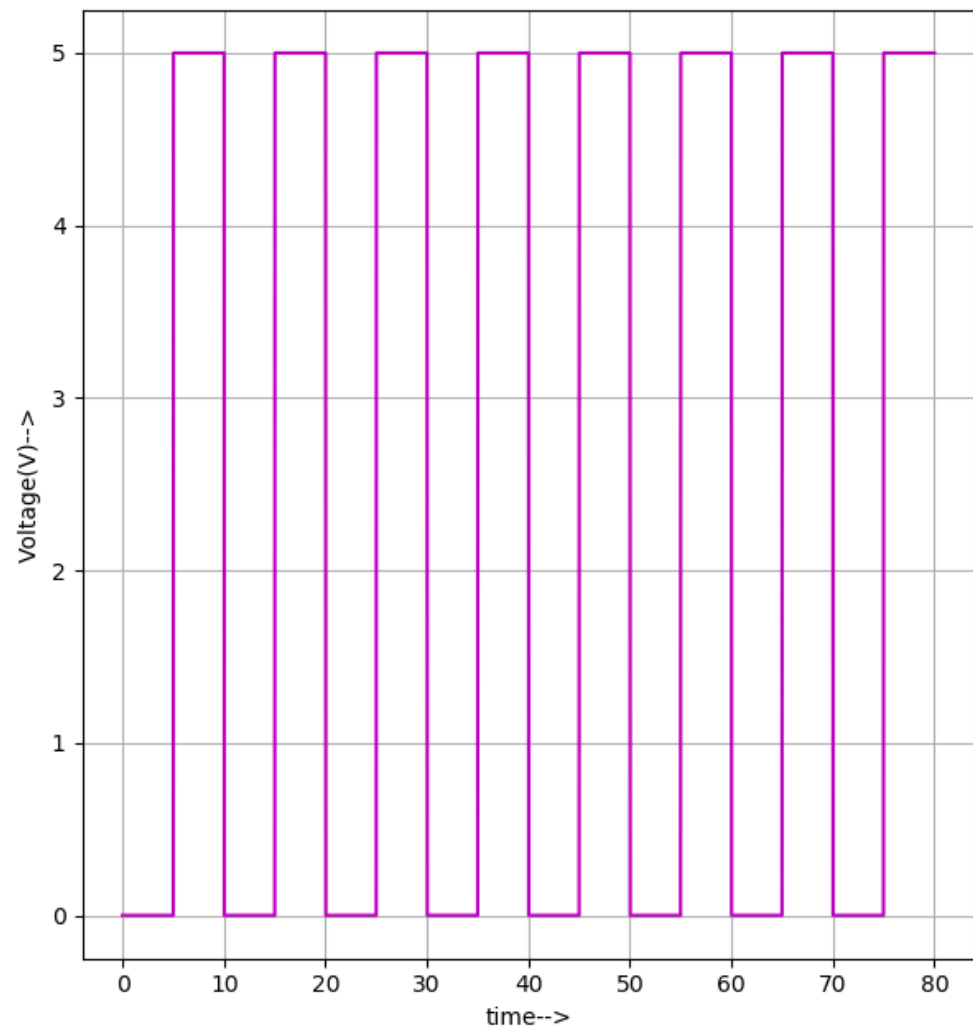


B0


OUTPUTS:

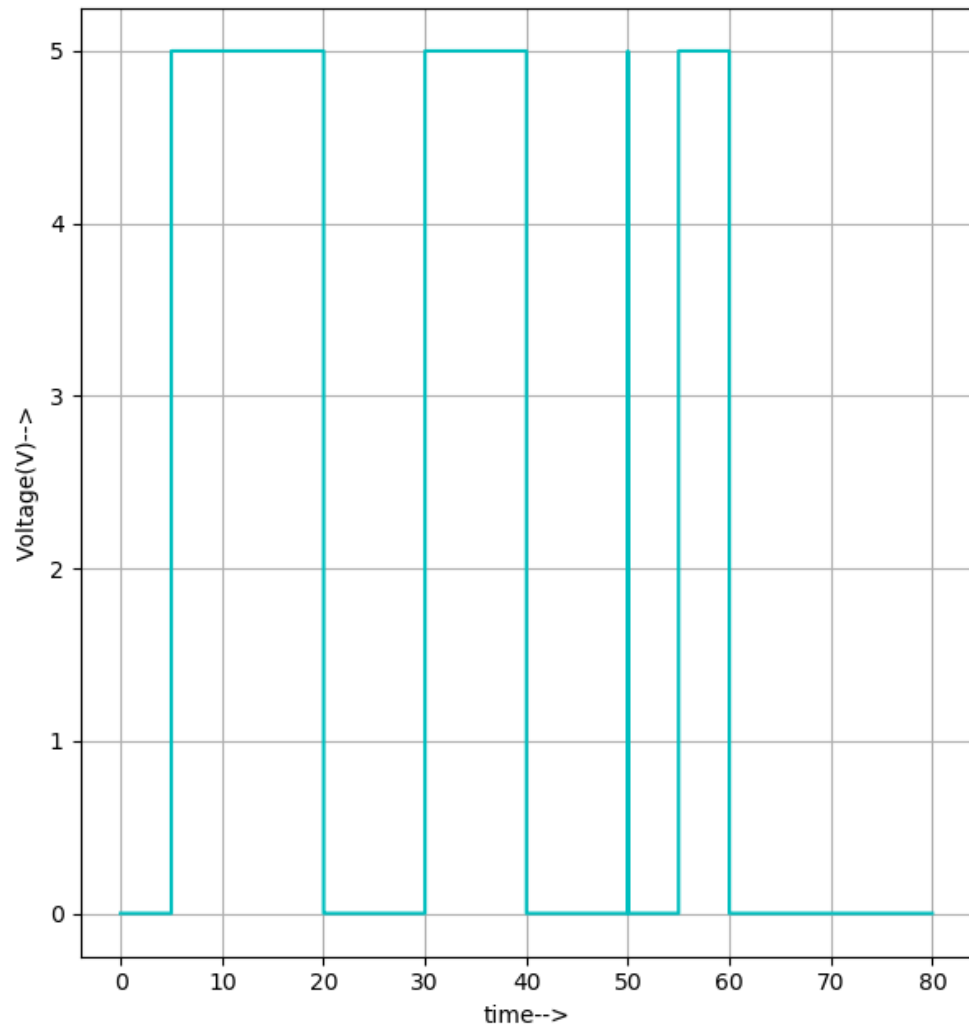

A < B

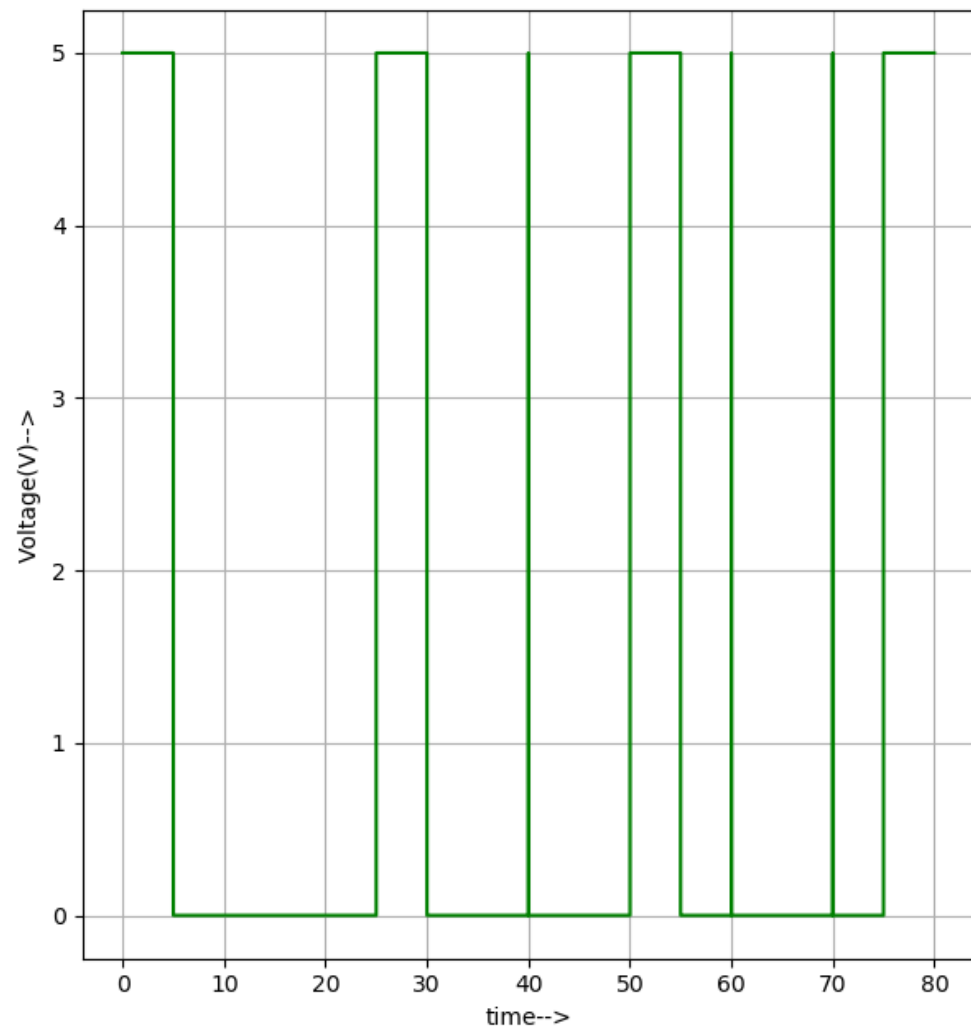

A = B

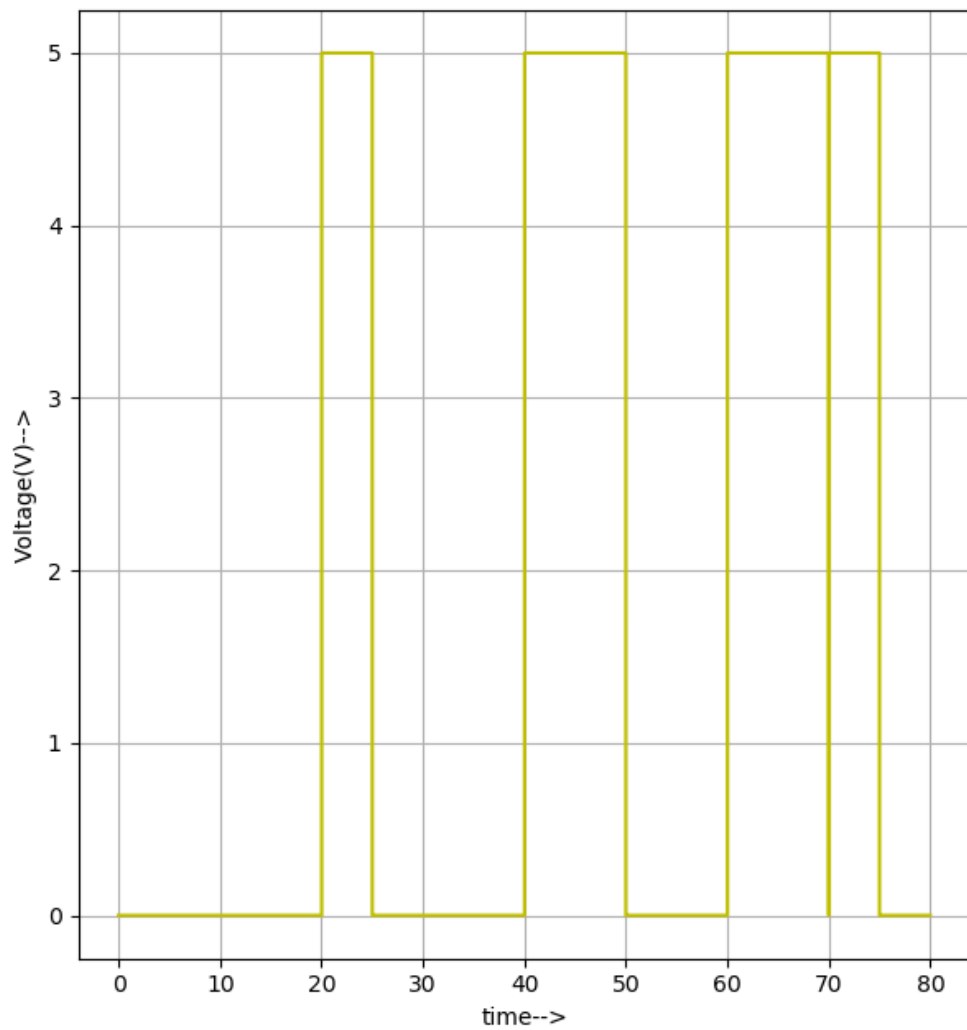

A > B

Source/Reference(s):

<https://www.geeksforgeeks.org/magnitude-comparator-in-digital-logic/>