



# Circuit Simulation Project

Name of Participant: Siddhant Sharma

Project Guide: Dr. Maheswari. R

Title of the Project

Design of XNOR gate using NAND gate in eSIM

## Theory:-

### XNOR Gate

The XNOR gate is the complement of the XOR gate. It is a hybrid gate. Simply, it is the combination of the XOR gate and NOT gate. The output level of the XNOR gate is high only when both of its inputs are the same, either 0 or 1. The symbol of the XNOR gate is the same as XOR, only complement sign is added. Sometimes, the XNOR gate is also called the **Equivalence gate**.

### NAND GATE:


In digital electronics, a NAND gate (NOT-AND) is a **logic gate which produces an output which is false only if all its inputs are true**; thus its output is complement to that of an AND gate. A LOW (0) output results only if all the inputs to the gate are HIGH (1); if any input is LOW (0), a HIGH (1) output results. A NAND gate is a universal gate, meaning that any other gate can be represented as a combination of NAND gates.

### 2-input Ex-NOR gate

It is a simple form of the hybrid gate XNOR. In this type of XNOR gate, there are only two input values and an output value. There are  $2^2=4$  possible combinations of inputs. The output level is high when both inputs are set to high(1). The Boolean expression of 2-input XNOR gate is as follows:

$$Y=(A\oplus B)'$$


$$Y=((AB)'+AB)$$


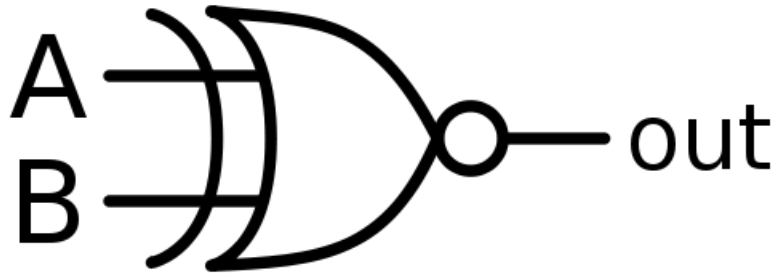


### TRUTH TABLE

Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

### CIRCUIT DIAGRAM

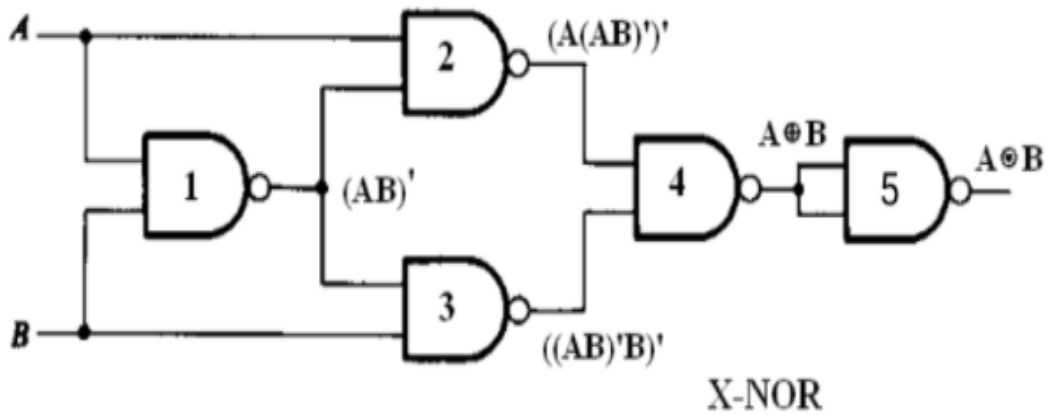


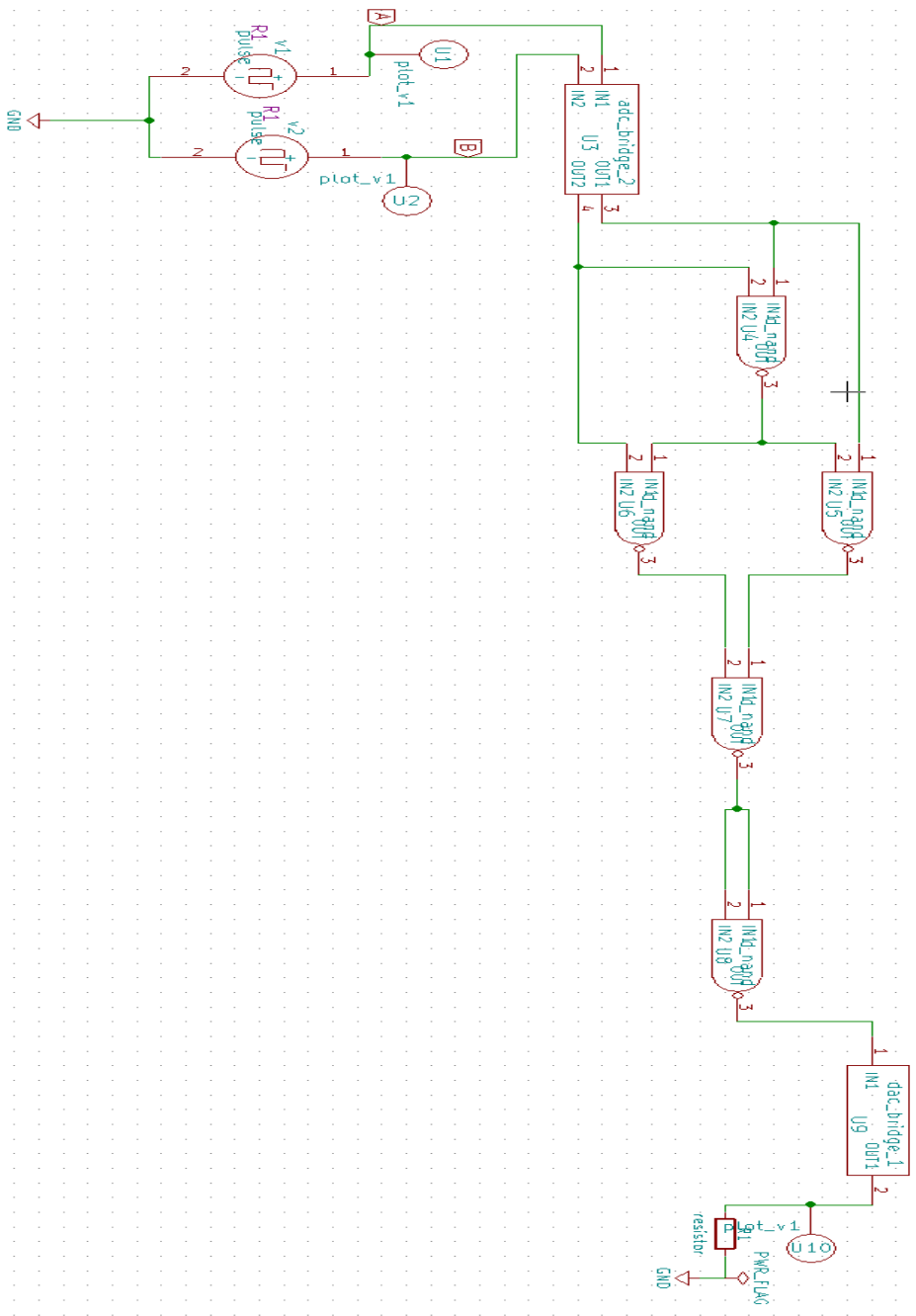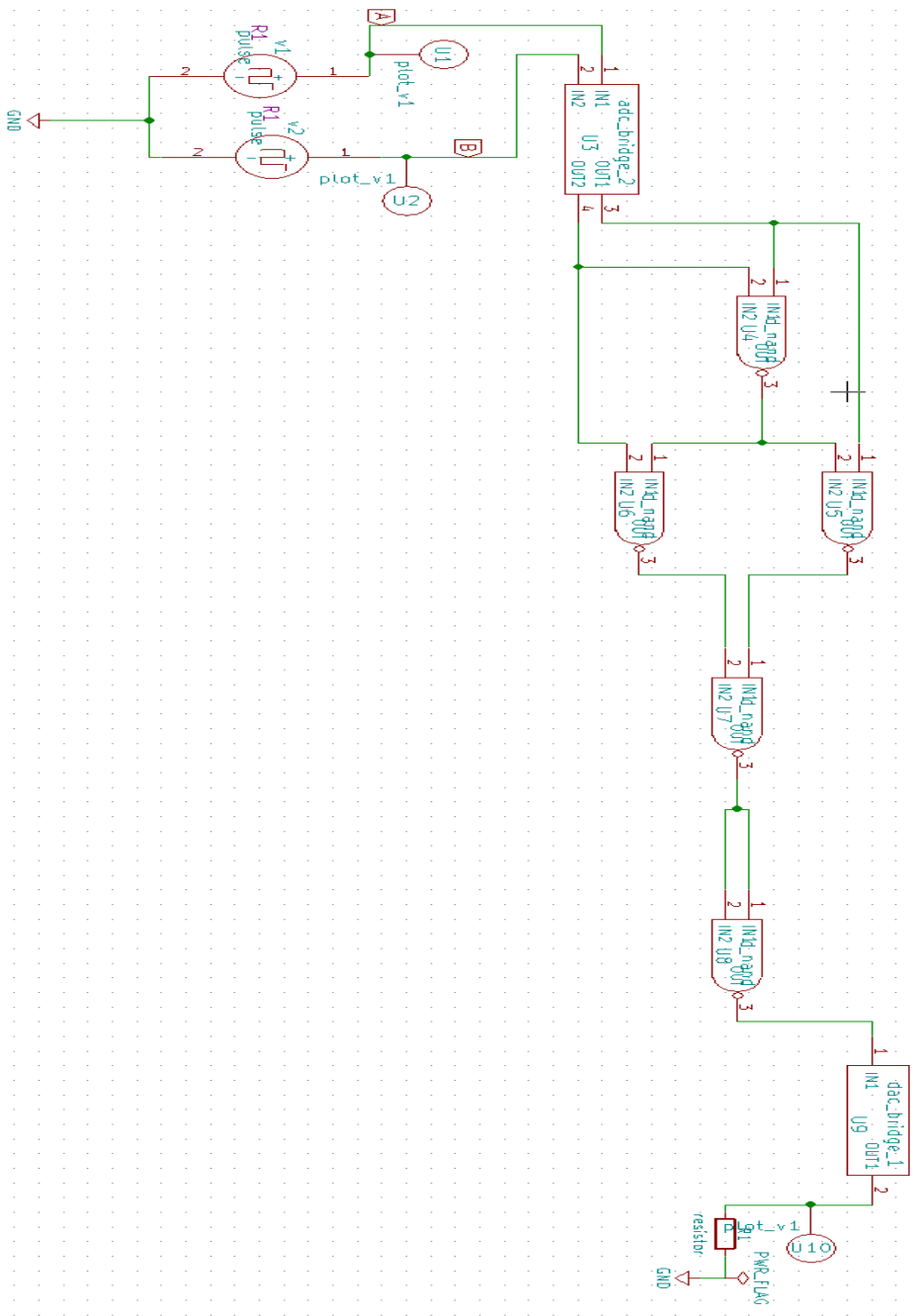


# Input:

## Python Charts

**a**

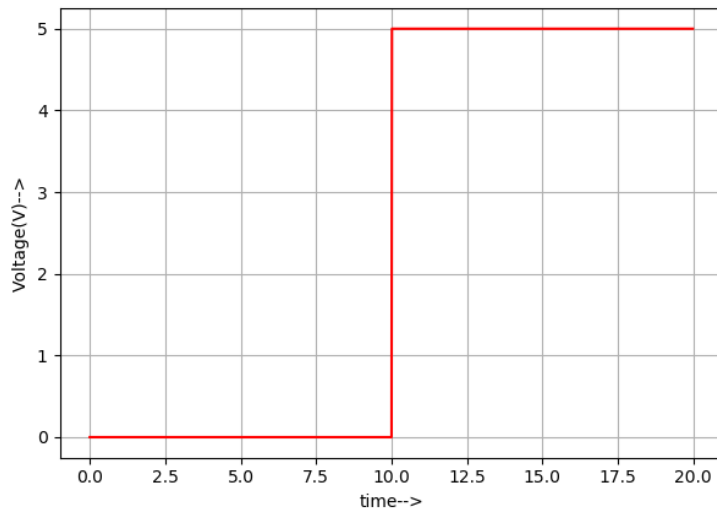


**b**

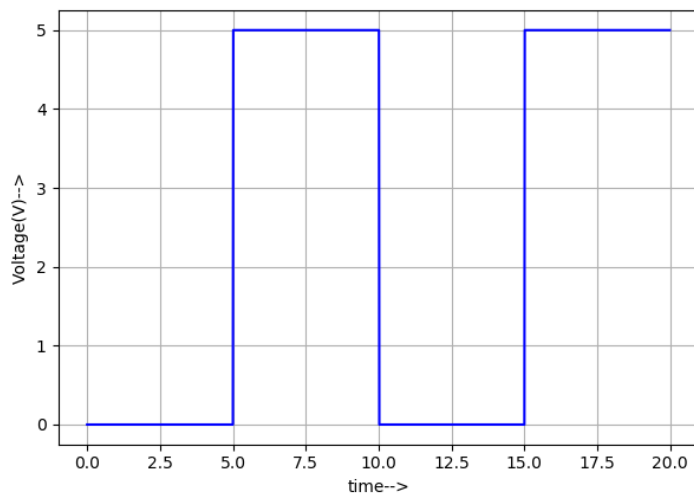


# Graph Chart:



a

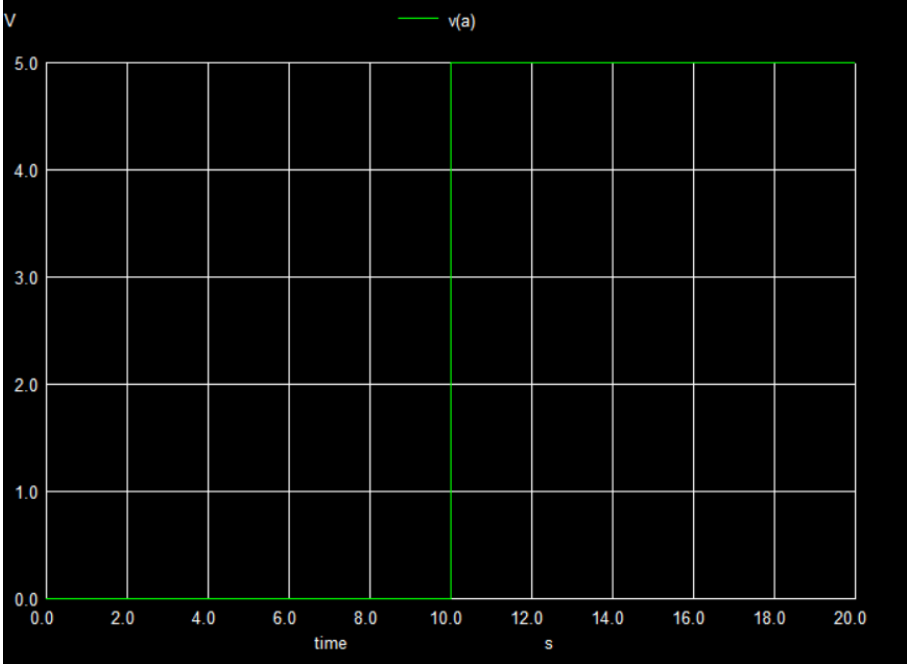

**b**

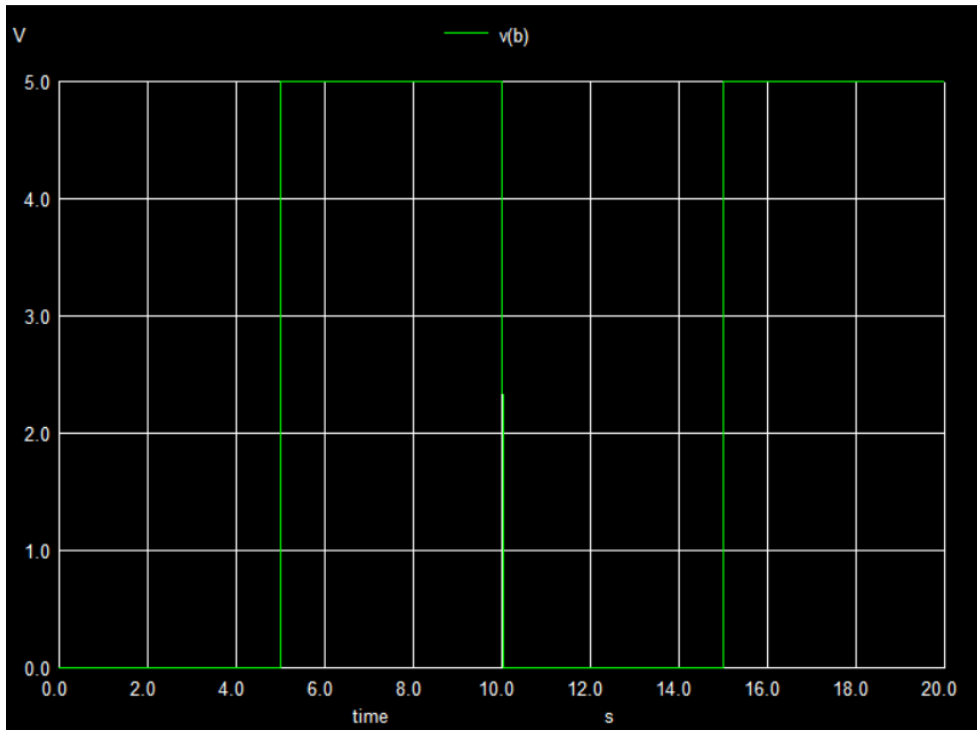

## Output:

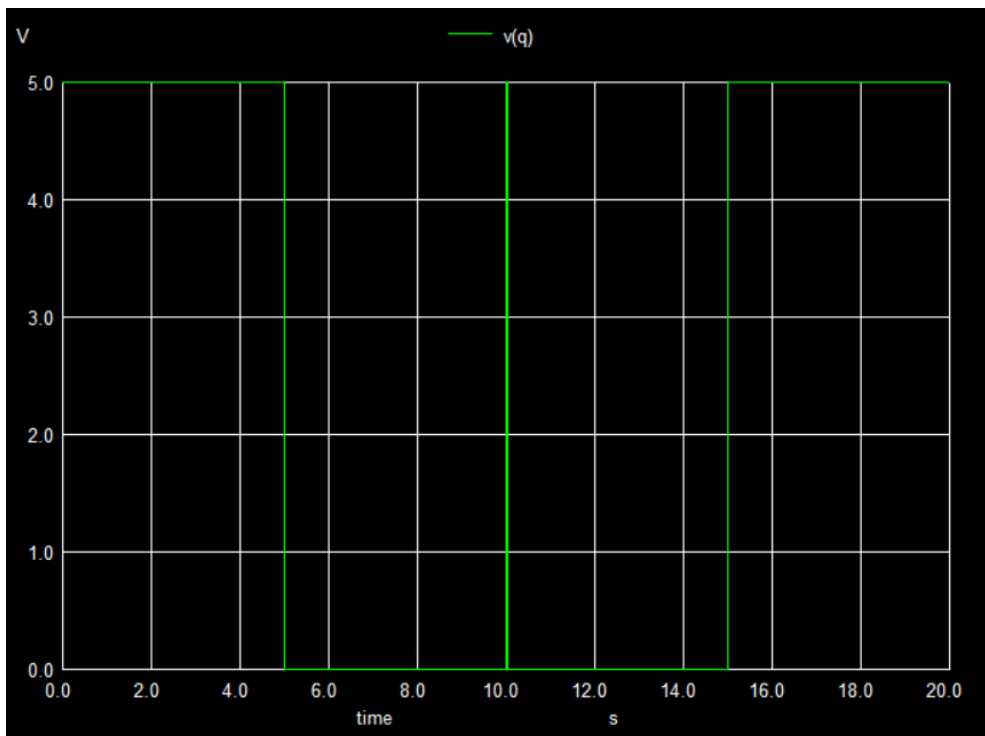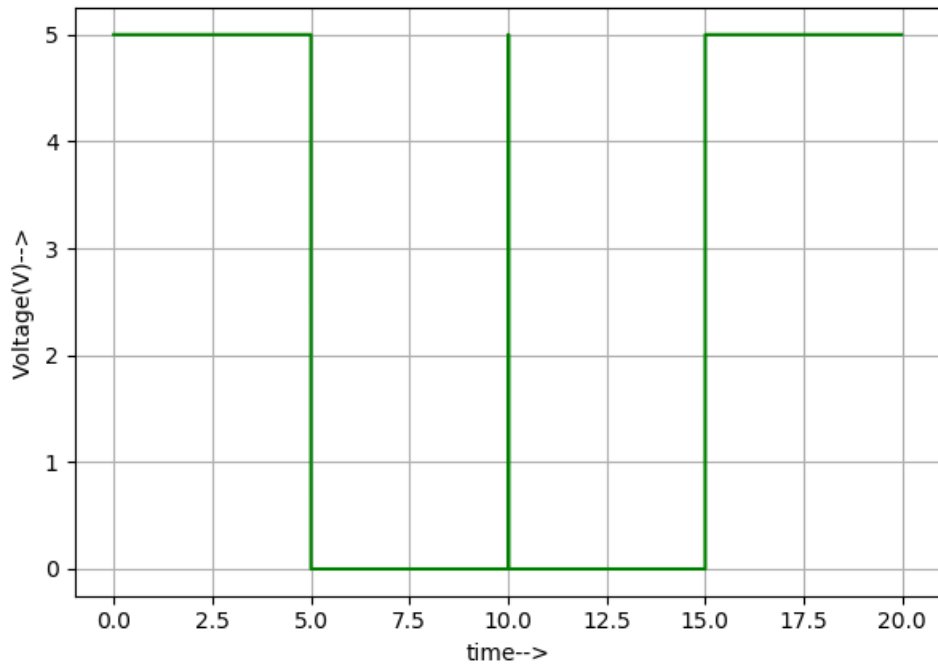



# References:

<https://commons.wikimedia.org/wiki/File:Xnor-gate-en.svg>

<https://www.youtube.com/watch?v=JCoAF5c-Hjs>

<https://vlsiuniverse.b>

<logspot.com/2016/11/xnor-gate-using-nand.html>

[https://en.wikipedia.org/wiki/NAND\\_gate#:~:text=In%20digital%20electronics%2C%20a%20NAND,HIGH%20\(1\)%20output%20results.](https://en.wikipedia.org/wiki/NAND_gate#:~:text=In%20digital%20electronics%2C%20a%20NAND,HIGH%20(1)%20output%20results.)