

# Circuit Simulation Project

<https://esim.fossee.in/circuit-simulation-project>

Name of the participant: Mrs. Nivedita S. Padole

Title of the circuit: Single Phase Diode Bridge Rectifier with CR Load.

Theory/Description:

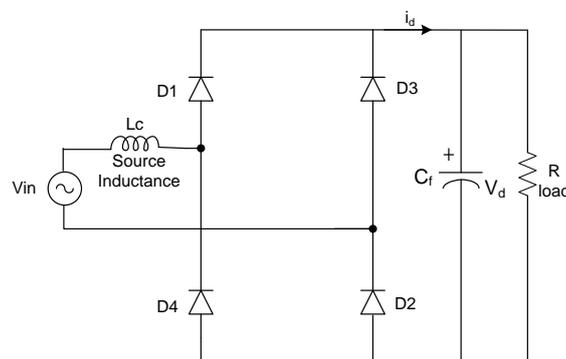


Figure 1: A diode bridge rectifier with CR Load

A diode bridge rectifier with capacitance resistance (CR) load is shown in Fig. 1. In this configuration a practical voltage source having  $L_s$  as a source inductance is considered. Capacitor  $C_f$  is used to filter out the rectified DC output voltage to make the DC output voltage smooth. The equivalent resistance  $R$  represents the load. The output DC voltage is used for various applications such as input to the voltage fed inverter or chopper (DC-DC Converter). During the positive half cycle, diode D1 and D2 conduct with the  $+V_o$  across the load. During the negative half cycle, diode D3 and D4 are forward biased, resulting in  $+V_o$  across the load. The capacitor will charge after every half cycle near the peak voltage  $V_m$ . The capacitor then discharges with a load time constant  $C_f \cdot R$ . The value of load current is always proportional to the supply voltage. In a practical circuit, the capacitor is charged through a series resistor to minimize high inrush current; during steady state, the resistor is bypassed through the diode. The output voltage ripple is minimized by using a high rating of capacitor, with large energy storage the load current is always smooth.

The output voltage is given by the equation (1),

$$V_d = V_m \sin \theta \quad (1)$$

Where,

$V_d$  = Capacitor/Output voltage

$V_m$  = Maximum/Peak Input voltage

$\Theta$  = Theta is angle at which capacitor start charging

### Circuit Diagram(s):

The circuit schematic of diode bridge rectifier with source inductance in eSim is shown below:

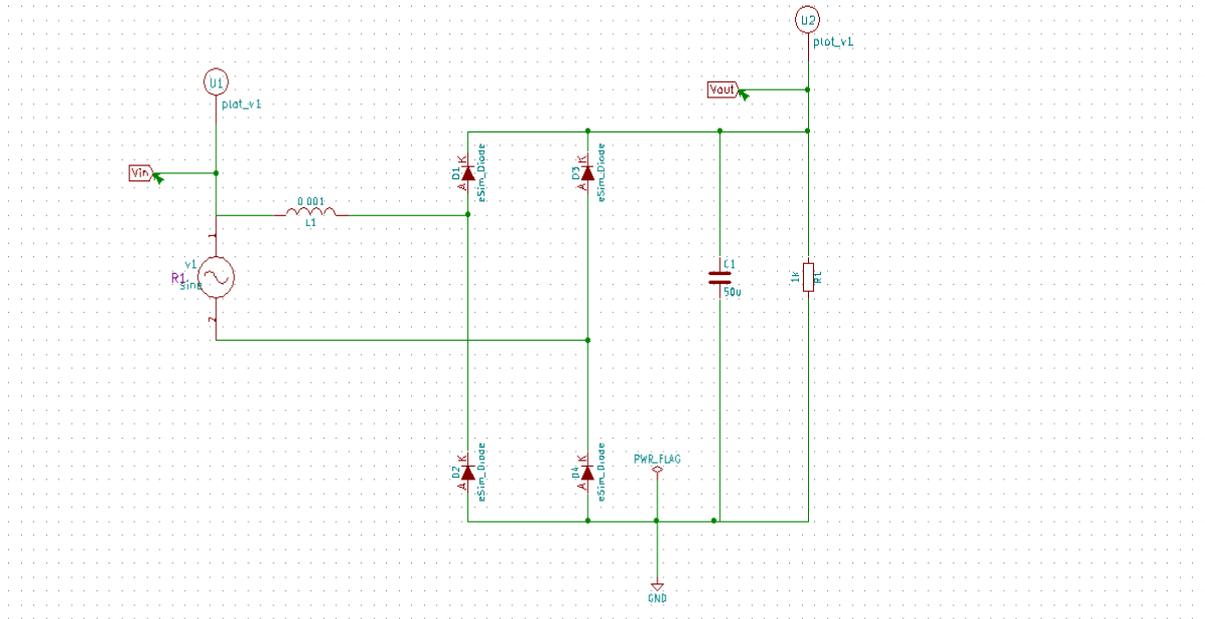


Figure 2. Schematic diagram of a diode bridge rectifier with CR Load

### Results (Input, Output waveforms and/or Multimeter readings) :

#### Ngspice Plots:

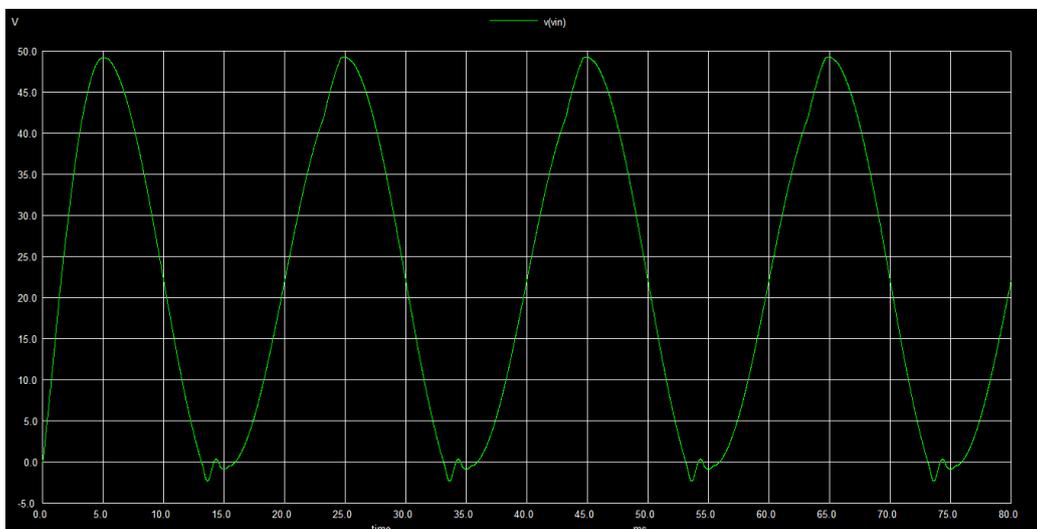


Figure 3: Input Voltage of a diode bridge rectifier with source inductance

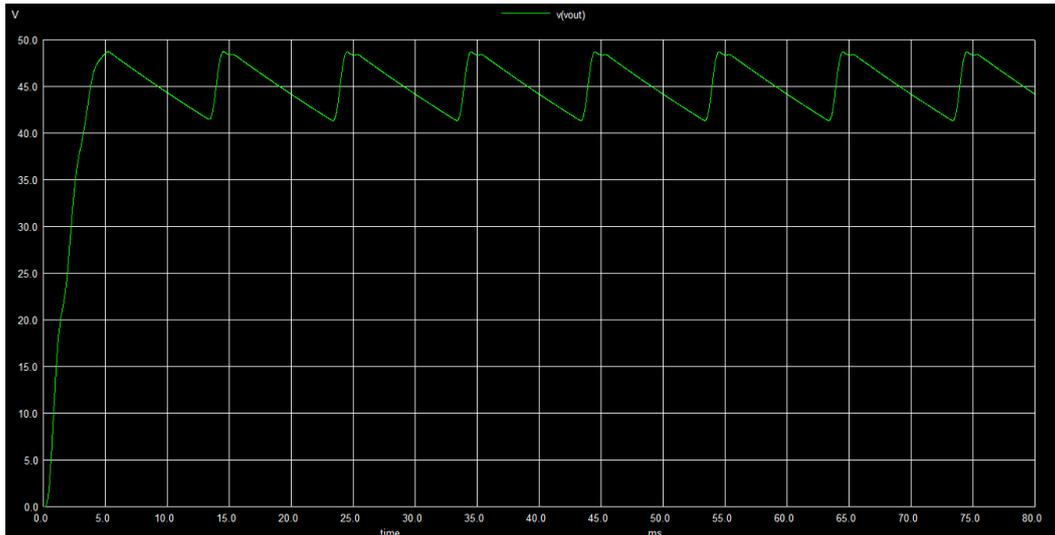


Figure 4: Output Voltage a diode bridge rectifier with source inductance

### Python Plots:

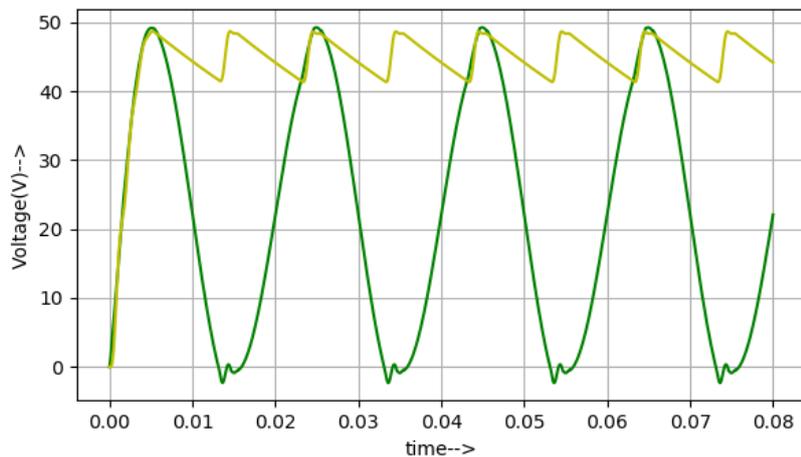
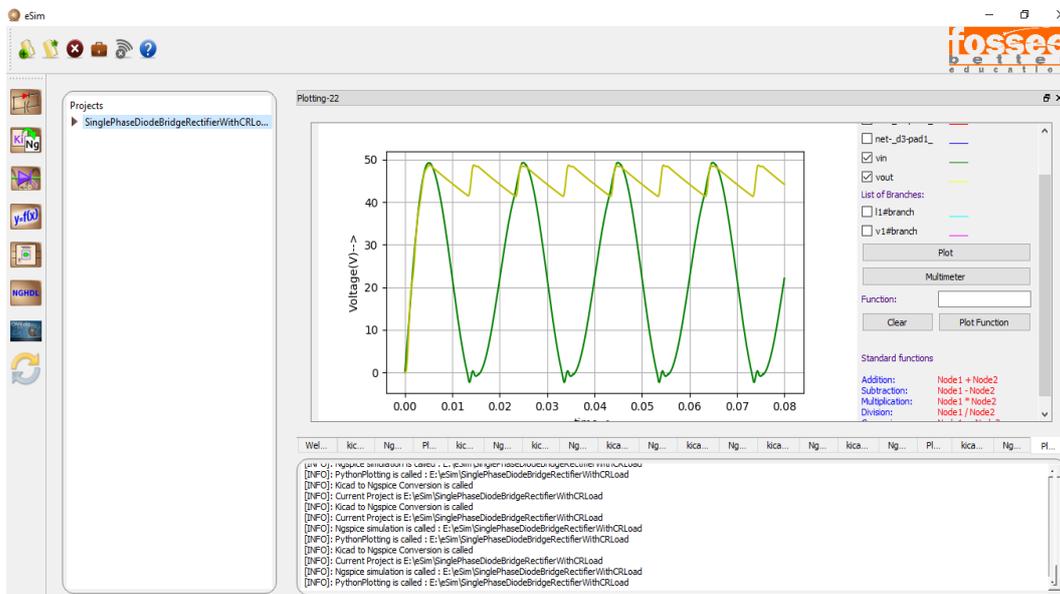


Figure 5: Output Voltage of a diode bridge rectifier with source inductance and CR Load

**Conclusion:** Thus, the effect of source inductance on the performance of a diode bridge rectifier with CR load has been studied by simulating the circuit in eSim.

**Source/Reference(s) :** Modern Power Electronics and AC Drives by Bimal K. Bose