

Octal to Binary Encoder

Parth Deshpande

BITS Pilani, KK Birla Goa Campus

8 April 2022

Abstract


The goal of the design is to make an encoder that will have input as an octal number with 8 bits and the output will be its binary form with 3 bits. The design will use CMOS technology to make NAND gates that will be used in making the encoder.

Keywords

Encoder, octal, binary, CMOS, NAND

Introduction

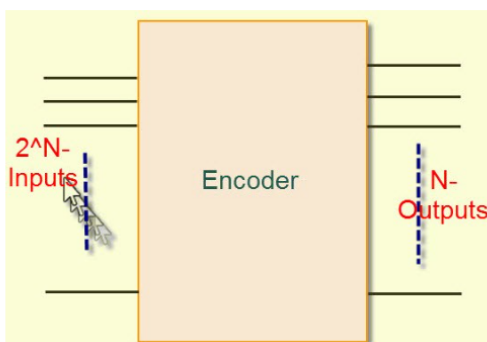In digital domain, encoders are an important part of the circuit. They are useful in converting data from one form to another. It can also be useful in transmitting data in easier ways.



This is the basic schematic of an encoder. The input will be 2^N bits and the output will be N bits.

Truth Table




Inputs							
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
1	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0
0	0	1	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	0	0	1	0	0	0
0	0	0	0	0	1	0	0
0	0	0	0	0	0	1	0
0	0	0	0	0	0	0	1

Outputs

x	y	z
1	1	1
1	1	0
1	0	1
1	0	0
0	1	1
0	1	0
0	0	1
0	0	0

The output is in the active-low format. This is due to NAND gates used in the circuit design.


Circuit

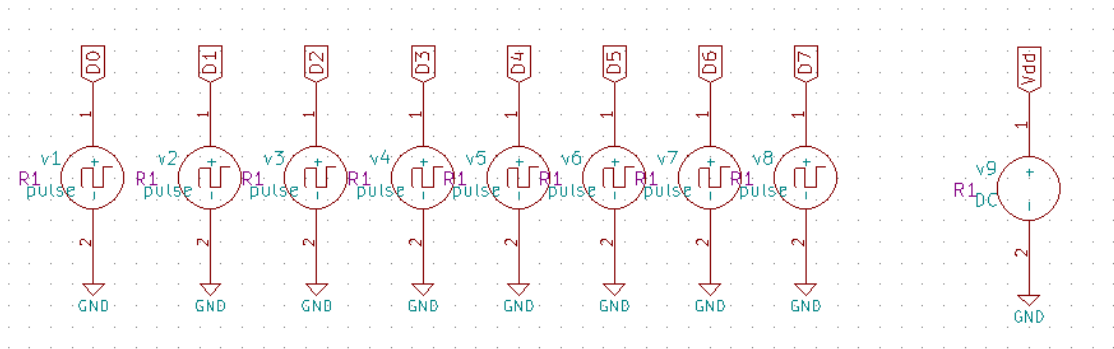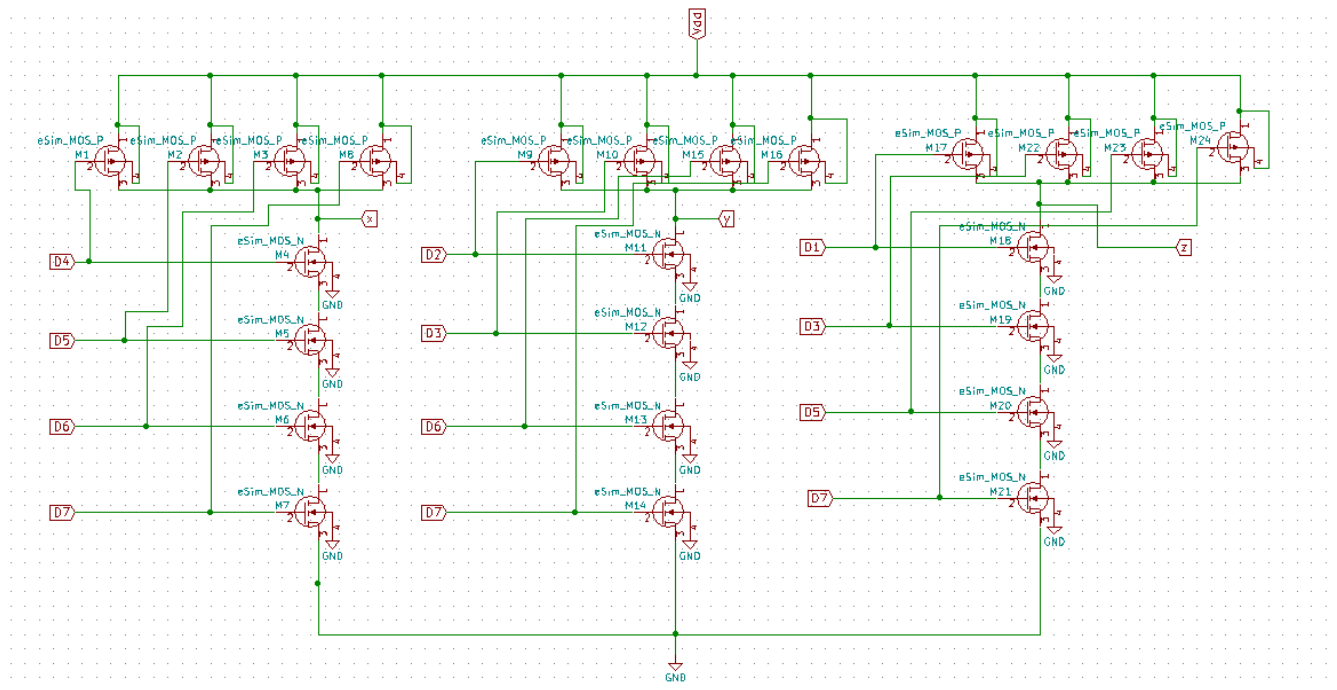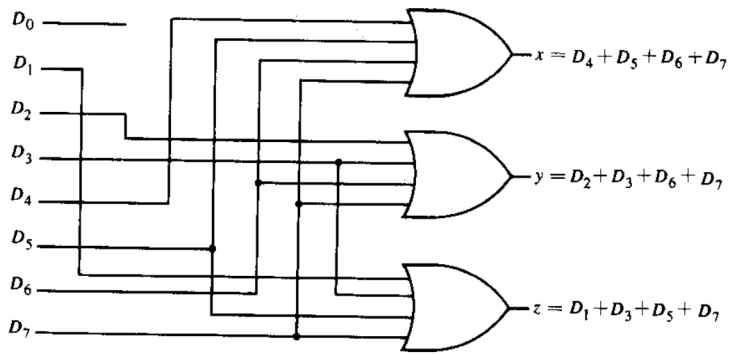



D0-D7 are the inputs. Vdd is the power source.


Plots

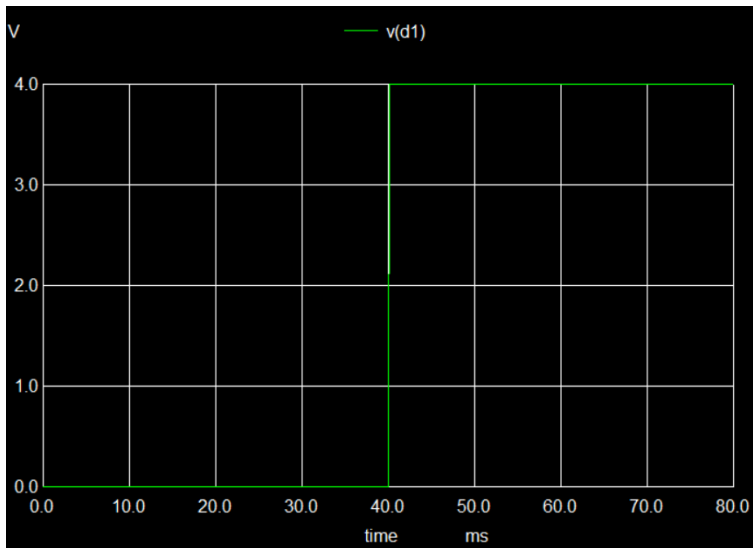When the input is 01000000 (only D1 is high)



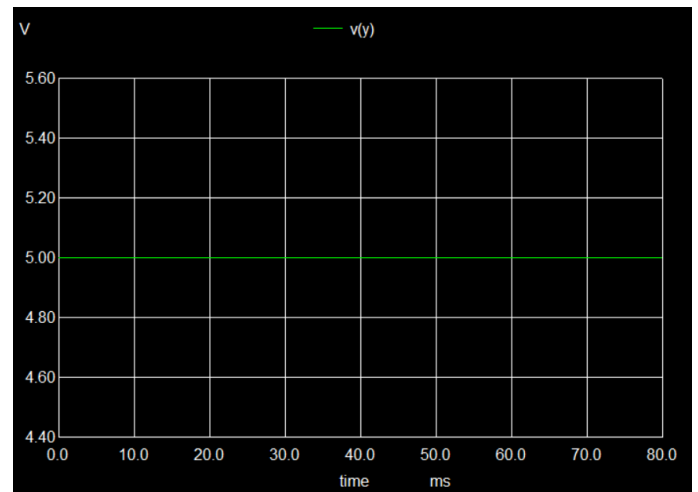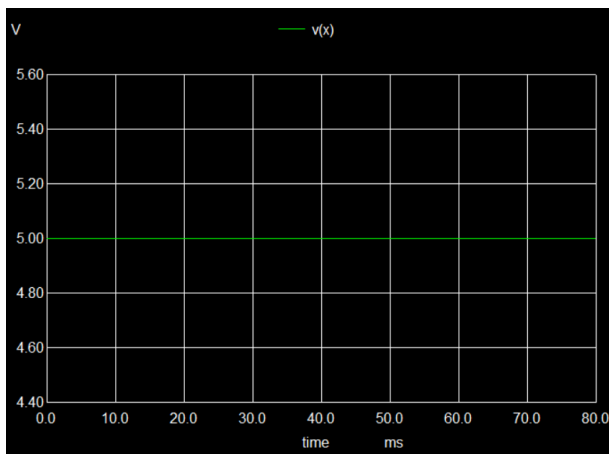The expected output is $xyz = 110$
(according to truth table)



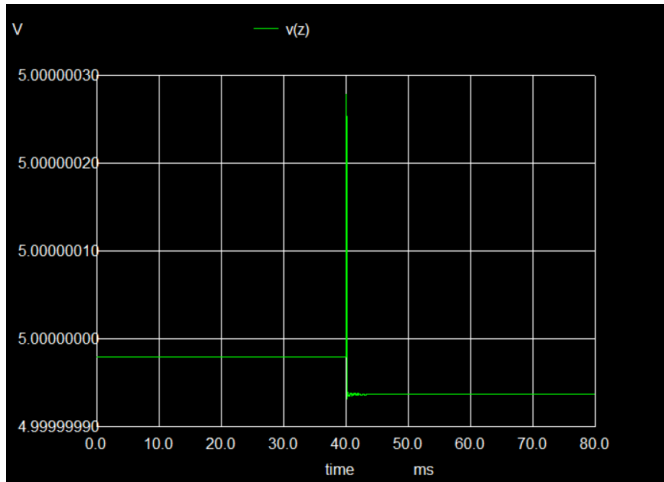

As it can be seen x and y outputs are always high, while z output goes low after 40ms mark. The exact voltage to 0 is not obtained due difficulty getting appropriate aspect ratios.

Similar results can be obtained for every octal number.

References

[1] B Razavi *Design of Analog CMOS Integrated Circuits* Tata Mcgraw Hill, 2002

[2] Morris Mano *Digital Design* " Prentice Hall 1995