

# **FET Based Master Slave Negative Edge Triggered Flipflop Using Sky130PDK**

## **Theory:**

A negative-edge triggered D type master-slave flip-flop consists of a pair of D-latches, positive latch (master) and negative latch (slave) connected in series. The latches are designed using mux by giving feedback from output to one of the inputs of 2:1 mux in. The mux is constructed using the transmission gates. The transmission gate is a bidirectional circuit which is made by connecting the pfet and nfet in parallel. The clock is given to the select lines of the mux so that the entire circuit behaves as the master slave negative edge triggered flipflop. During the high level of the clock, the master samples the input and the slave retains the previous output through feedback. At low level of the clock, the slave will go to transparent mode and samples the output of the master and the master will go to the hold mode, retaining the previous value. Thus, the output of master slave negative edge triggered flipflop changes once in one clock cycle during the high to low transition of clock. The transistors for designing all the circuits were used from the **SKY130PDK library** in eSim.

## **Schematic Diagram:**

The circuit schematic of the FET based master slave negative edge triggered flipflop using sky130pdk in eSim is as shown below:

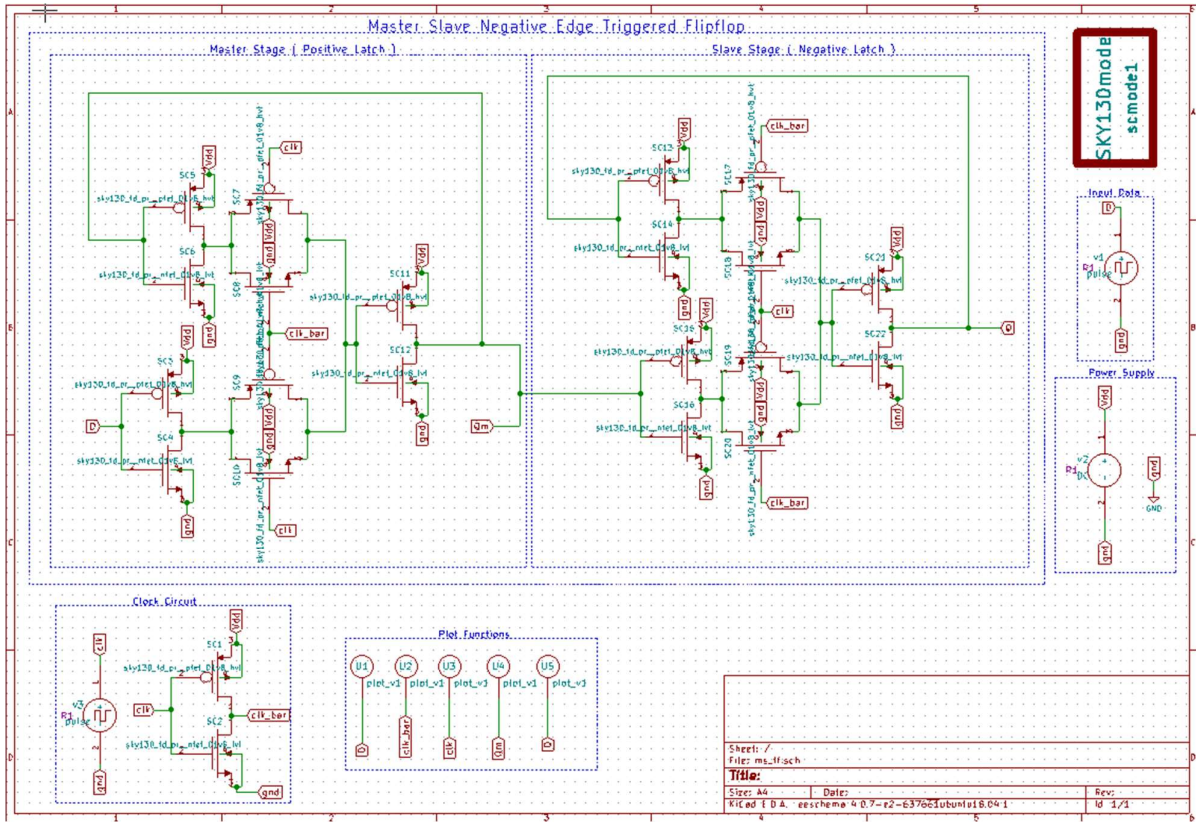


Figure 1: Schematic of the Master Slave Negative Edge Triggered Flipflop

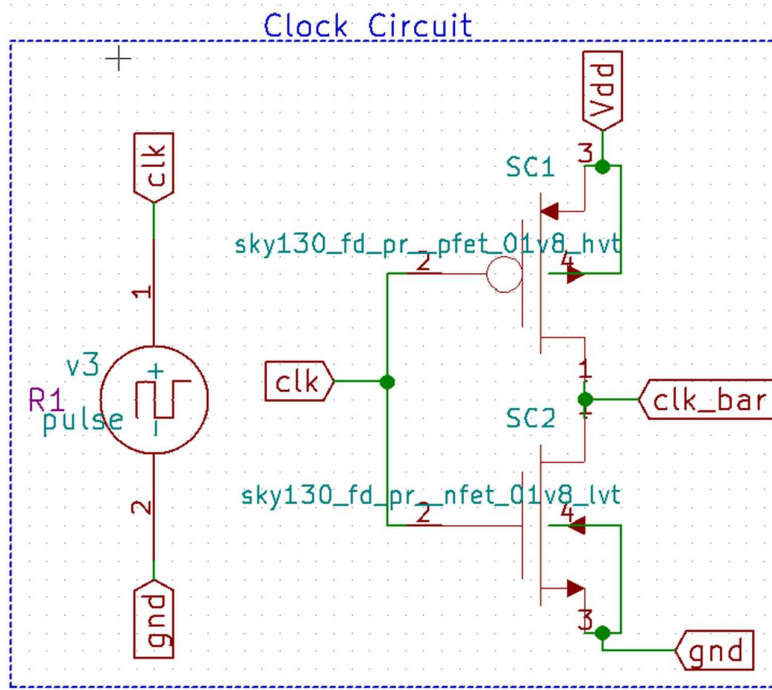


Figure 2: Clock Circuit

## Simulation Results:

### 1. Ngspice Plots:

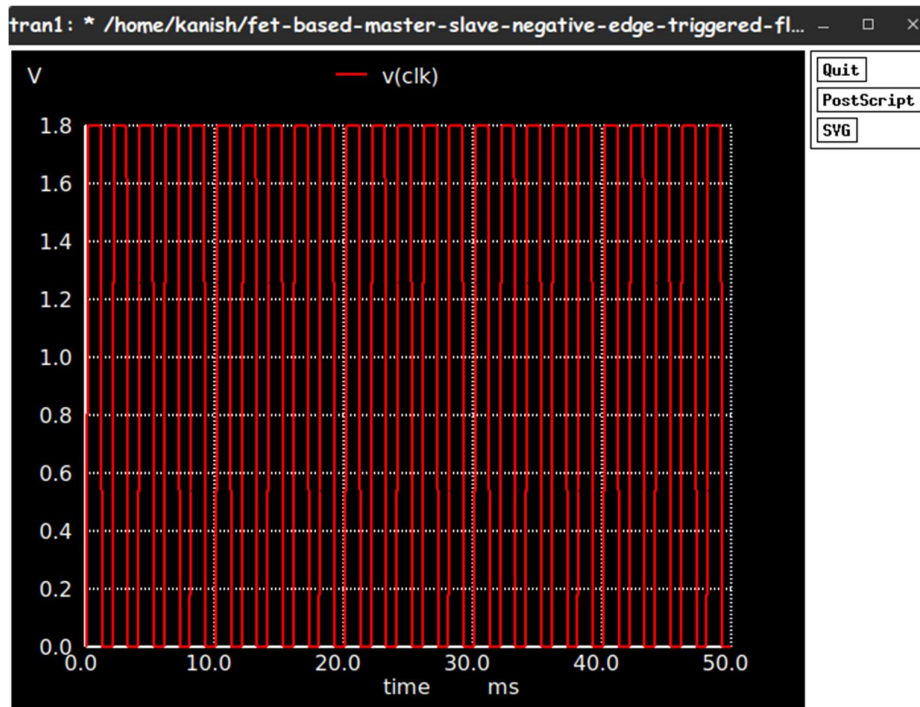


Figure 3: Clock Signal

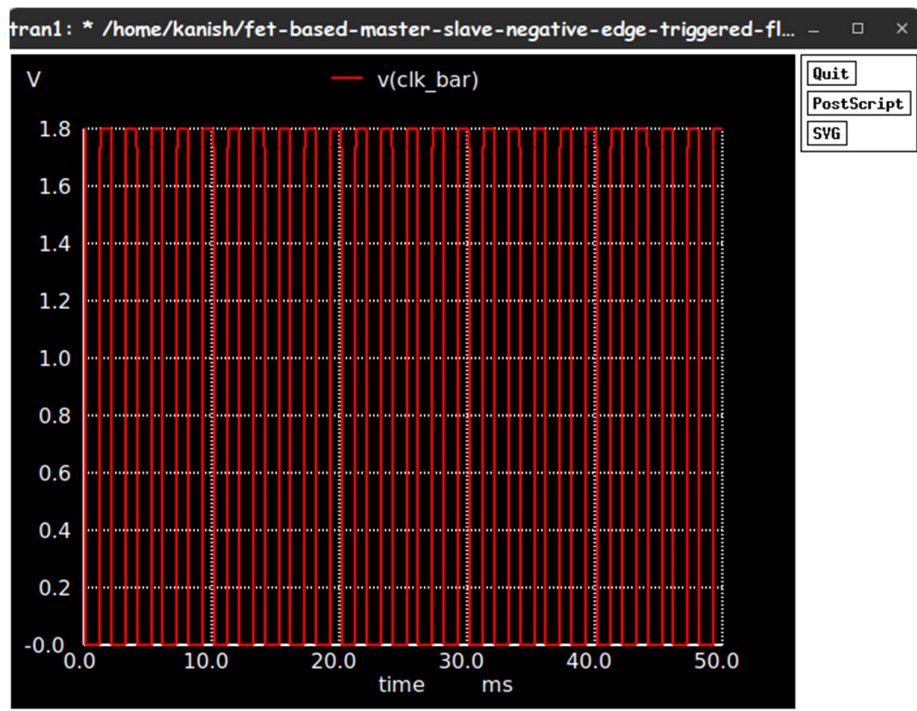


Figure 4: Clock bar Signal

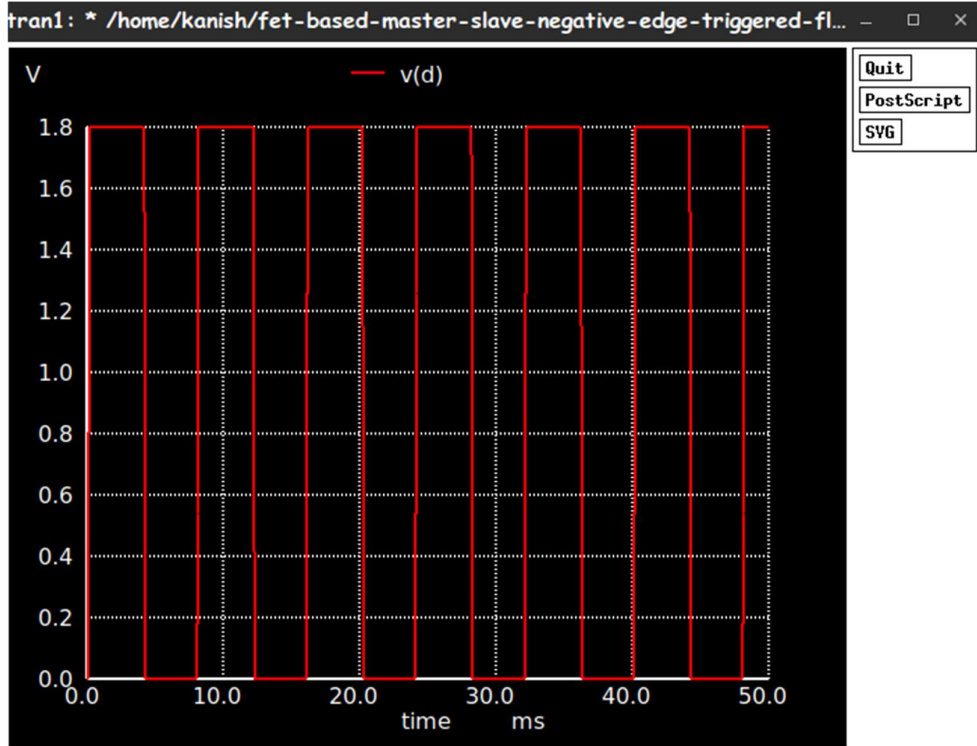


Figure 5: Input Data (D)

 


Figure 6: Master Output

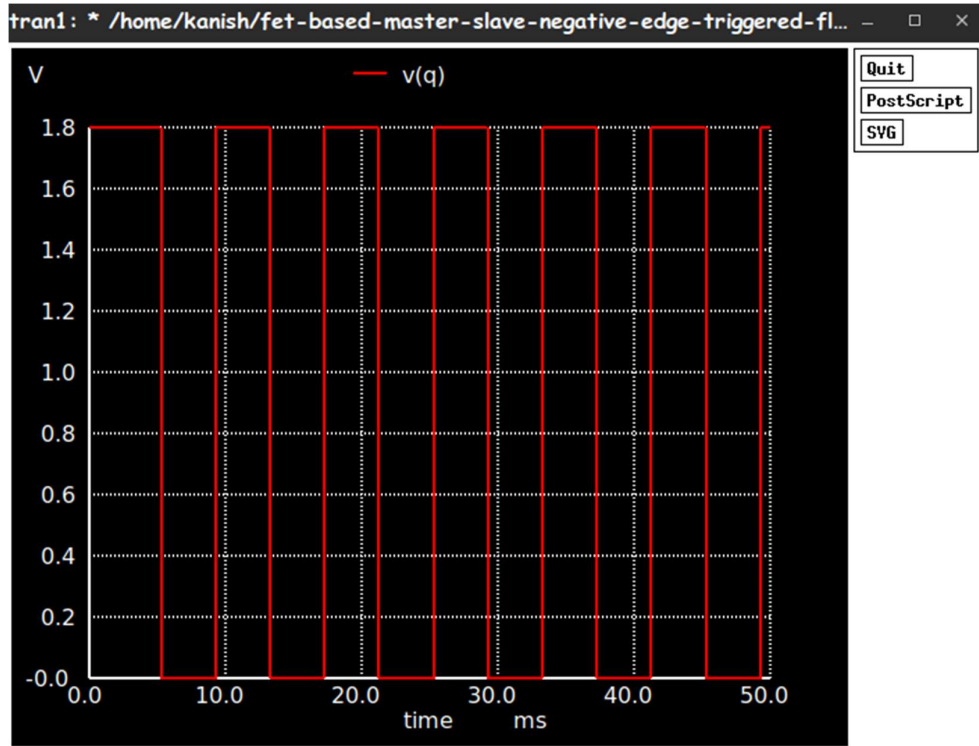


Figure 7: Master Slave Negative Edge Triggered Flipflop Output

 


Figure 8: Combined Waveforms of the Master Slave Negative Edge Triggered Flipflop using SKY130PDK



## 2. Netlist

```
ms_ff.cir.out
* /home/kanish/fet-based-master-slave-negative-edge-triggered-flipflop-using-sky130pdk/ms_ff/ms_ff.cir
.include "/usr/share/local/sky130_fd_pr/models/sky130_fd_pr_model_linear.model.spice"
.include "/usr/share/local/sky130_fd_pr/models/sky130_fd_pr_model_diode_pd2nw_11v0.model.spice"
.lib "/usr/share/local/sky130_fd_pr/models/sky130.lib.spice" tt
.include "/usr/share/local/sky130_fd_pr/models/sky130_fd_pr_model_inductors.model.spice"
.include "/usr/share/local/sky130_fd_pr/models/sky130_fd_pr_model_diode_pw2nd_11v0.model.spice"
.include "/usr/share/local/sky130_fd_pr/models/sky130_fd_pr_model_r+c.model.spice"
.include "/usr/share/local/sky130_fd_pr/models/sky130_fd_pr_model_pnp.model.spice"
v2 vdd gnd dc 1.8
v3 clk gnd pulse(0 1.8 0.1m 0.1m 0.1m 1m 2m)
xsc1 clk_bar clk vdd vdd sky130_fd_pr_pfet_01v8_hvt
xsc2 clk_bar clk gnd gnd sky130_fd_pr_nfet_01v8_lvt
xsc7 net_sc10-pad3_clk_bar net_sc5-pad1_vdd sky130_fd_pr_pfet_01v8_hvt
xsc9 net_sc10-pad3_clk_bar net_sc10-pad1_vdd sky130_fd_pr_pfet_01v8_hvt
xsc8 net_sc5-pad1_clk_bar net_sc10-pad3_gnd sky130_fd_pr_nfet_01v8_lvt
xsc10 net_sc10-pad1_clk_bar net_sc10-pad3_gnd sky130_fd_pr_nfet_01v8_lvt
xsc18 net_sc13-pad1_clk_bar net_sc17-pad1_gnd sky130_fd_pr_nfet_01v8_lvt
xsc20 net_sc15-pad1_clk_bar net_sc17-pad1_gnd sky130_fd_pr_nfet_01v8_lvt
xsc4 net_sc10-pad1_d gnd gnd sky130_fd_pr_nfet_01v8_lvt
xsc3 net_sc10-pad1_d vdd vdd sky130_fd_pr_pfet_01v8_hvt
xsc6 net_sc5-pad1_qm gnd gnd sky130_fd_pr_nfet_01v8_lvt
xsc5 net_sc5-pad1_qm vdd vdd sky130_fd_pr_pfet_01v8_hvt
xsc11 qm net_sc10-pad3_vdd vdd sky130_fd_pr_pfet_01v8_hvt
xsc12 qm net_sc10-pad3_gnd gnd sky130_fd_pr_nfet_01v8_lvt
xsc21 q net_sc17-pad1_vdd vdd sky130_fd_pr_pfet_01v8_hvt
xsc22 q net_sc17-pad1_gnd gnd sky130_fd_pr_nfet_01v8_lvt
xsc15 net_sc15-pad1_qm vdd vdd sky130_fd_pr_pfet_01v8_hvt
xsc16 net_sc15-pad1_qm gnd gnd sky130_fd_pr_nfet_01v8_lvt
xsc13 net_sc13-pad1_q vdd vdd sky130_fd_pr_pfet_01v8_hvt
xsc14 net_sc13-pad1_q gnd gnd sky130_fd_pr_nfet_01v8_lvt
v1 d gnd pulse(0 1.8 0.1m 0.1m 0.1m 4m 8m)
* u1 d plot_v1
* u2 clk_bar plot_v1
* u3 clk plot_v1
* u4 qm plot_v1
* u5 q plot_v1
* s c m o d e
.tran 1e-03 50e-03 0e-00
* Control Statements
.control
run
print allv > plot_data_v.txt
print alli > plot_data_i.txt
plot v(d)+6 v(clk_bar)+9 v(clk)+12 v(qm)+3 v(q)
write ms_ff.raw all
.endc
.end
```

Figure 9: Netlist

## 3. GAW - Gtk Analog Wave viewer Plot

 


Figure 10: Combined Waveform in GTK Analog Viewer

## **Conclusion:**

Thus, we have implemented the FET based master slave negative edge triggered flipflop using Sky130PDK in eSim and the appropriate waveforms are obtained.

## **References:**

1. Morris Mano & Michael D Ciletti, "Digital Design: With an Introduction to Verilog HDL, 5th Edition, Pearson Education, 2013
2. Neil H.E. Weste, David Money Harris —CMOS VLSI Design: A Circuits and Systems Perspective.
3. <https://www.sciencedirect.com/topics/computer-science/master-slave-flip#:~:text=A%20negative%2Dedge%20triggered%20D,edge%20of%20the%20clock%20pulse.>
4. <https://skywater-pdk.readthedocs.io/en/main/>