

Title of The Experiment:

A Two Stage Common Emitter Amplifier In a Cascade Configuration with NPN and PNP Transistor.

Theory:

A two-stage common-emitter amplifier with NPN and PNP transistors in a cascade configuration is a type of BJT amplifier that utilizes two transistor stages, one NPN and one PNP, connected in a specific arrangement to achieve desired amplification characteristics.

NPN common-emitter stage: This stage acts as a conventional inverting amplifier. When a positive input voltage is applied to the base of the NPN transistor, it increases the collector current, leading to a decrease in the output voltage (due to the voltage divider formed by the collector resistor and load).

PNP common-emitter stage: This stage also inverts the input signal. However, since it's a PNP transistor, the current flow direction and biasing conditions are reversed compared to the NPN stage.

Design:

- 1) Source Resistance, $R_s=0.5K$ (ohm)
- 2) Voltage Divider Resistance, $R_1=100K$ (ohm)
- 3) Voltage Divider Resistance, $R_2=50K$ (ohm)
- 4) Resistance Connected to Collector (NPN), $R_{c1}=5K$ (ohm)
- 5) Resistance Connected to Collector (PNP), $R_{c2}=1.5K$ (ohm)
- 6) Resistance Connected to Emitter (NPN), $R_{e1}=2K$ (ohm)
- 7) Resistance Connected to Emitter (PNP), $R_{e2}=2K$ (ohm)
- 8) Coupling Capacitor, $C_{c1}=C_{c2}=100\mu F$
- 9) Emitter Capacitance, $C_{e1}=C_{e2}=50\mu F$

Schematic Diagram:

A Circuit Schematic of a Two Stage Common Emitter Amplifier In a Cascade Configuration with npn and pnp transistor using e-sim as shown below:

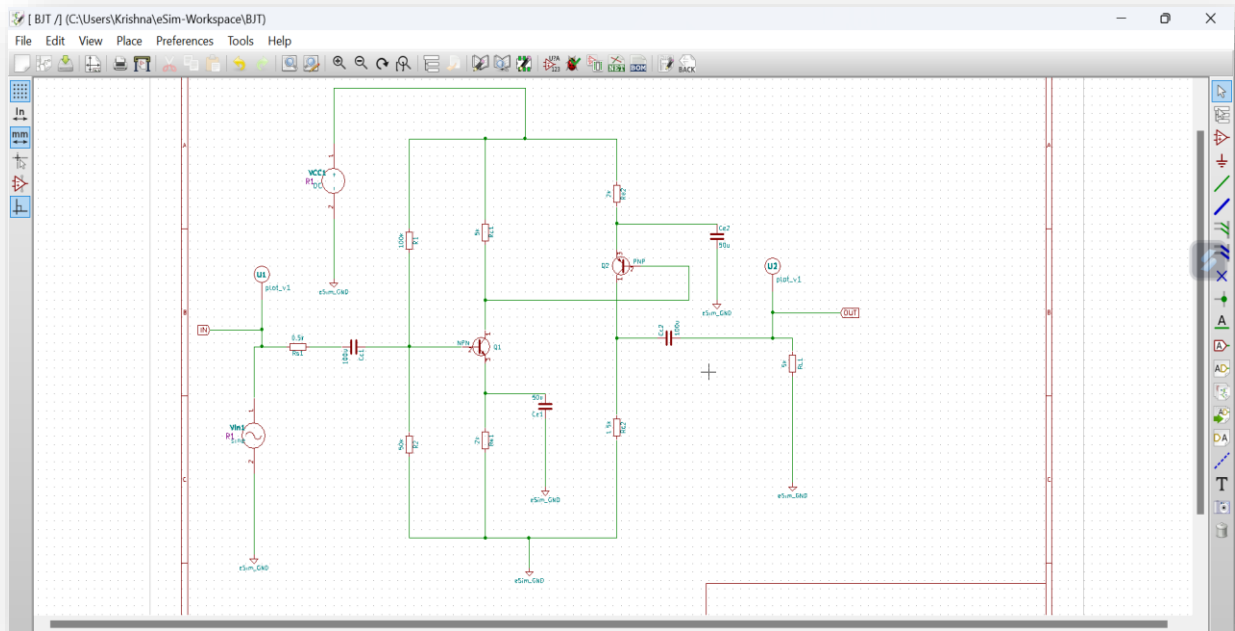


Figure 1: A Two Stage Common Emitter Cascade Amplifier in a Cascade Configuration with npn and pnp transistor

Simulation Results:

1. Ngspice plots:

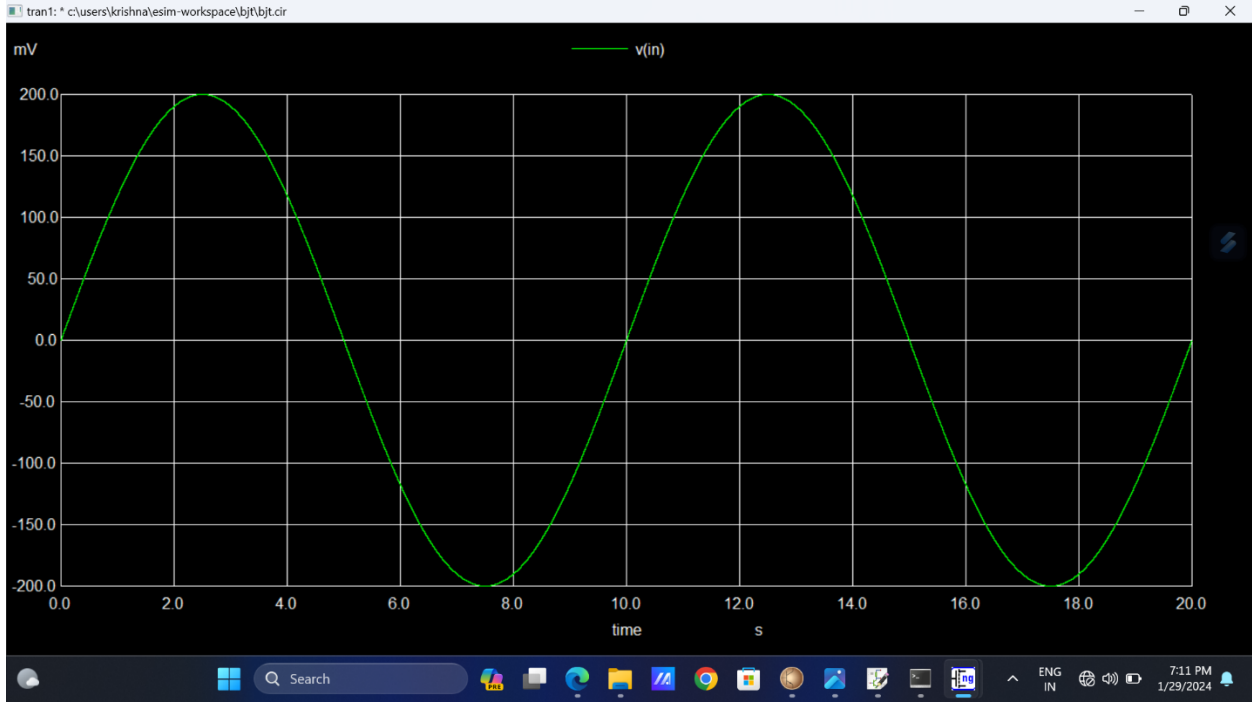


Figure 2: Ngspice Input Plot

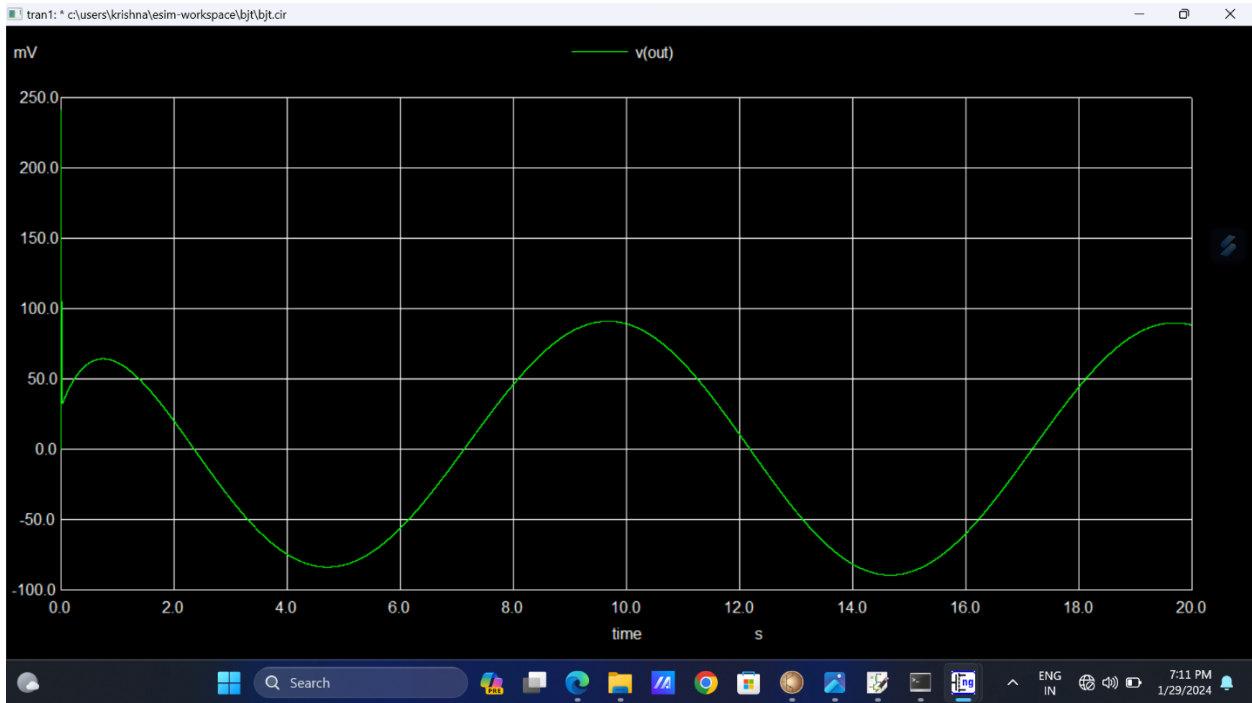


Figure 3: Ngspice Output Plot

2. Python Plots:

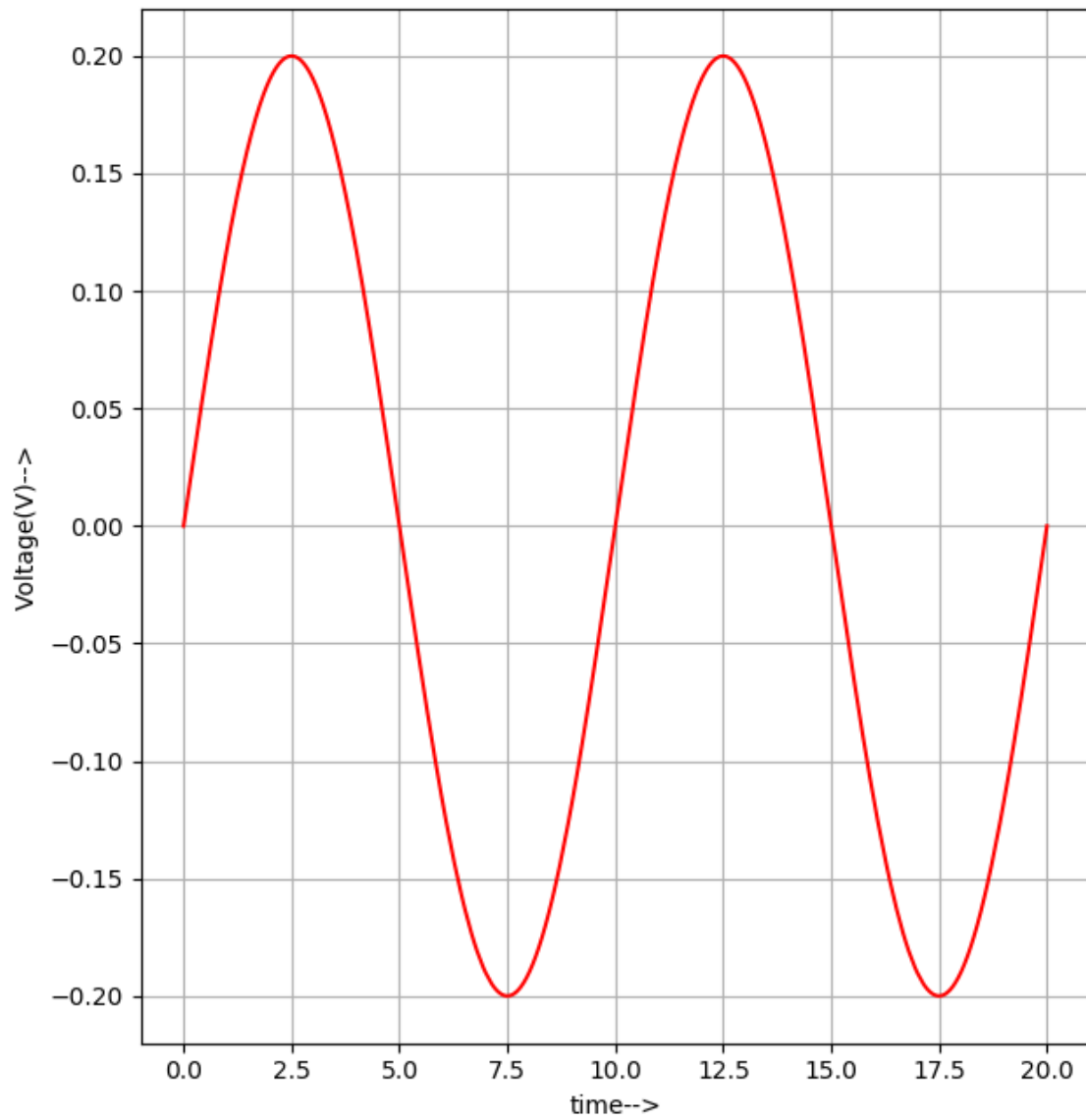


Figure 4: Python Plot Input

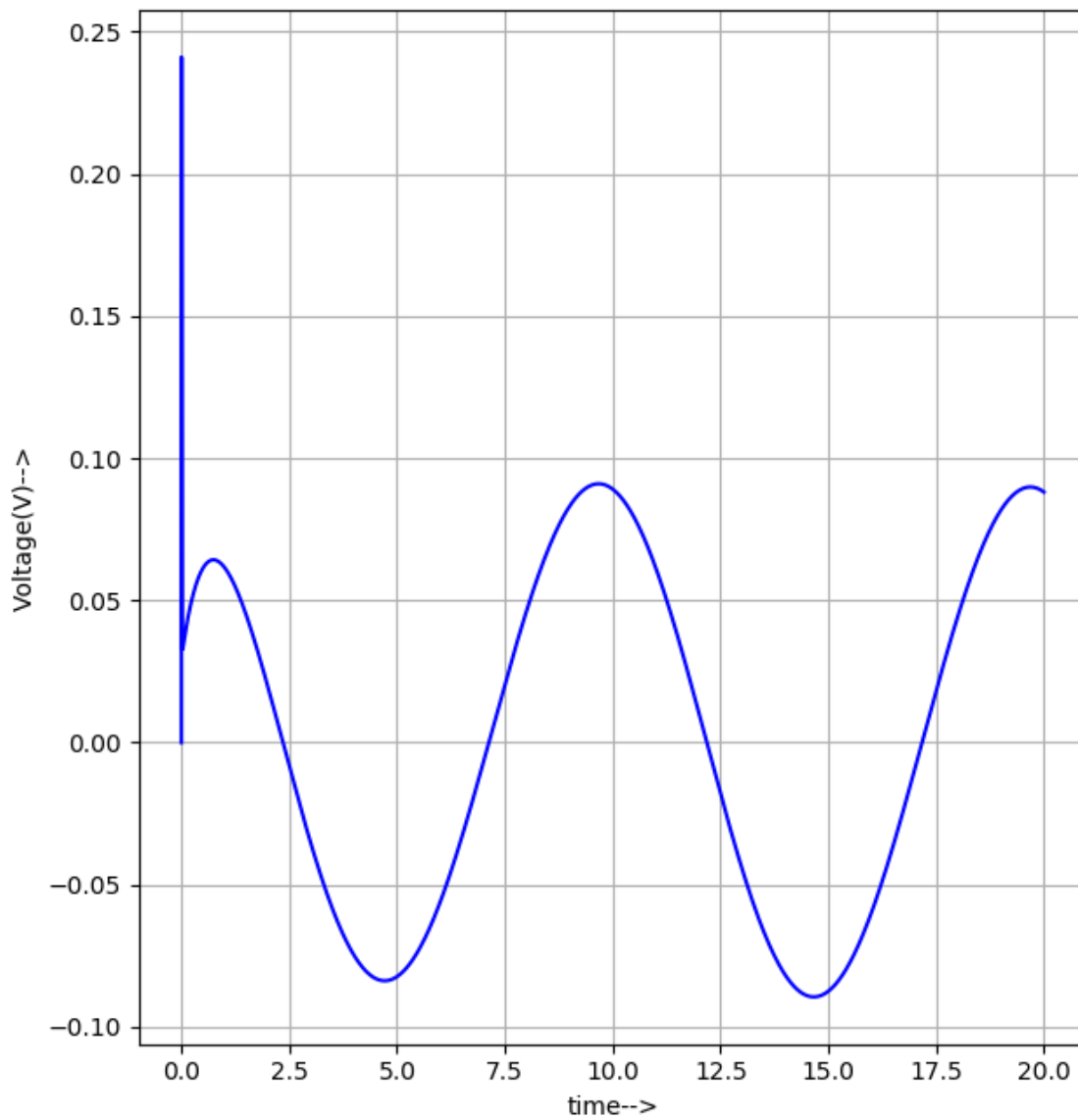


Figure 5: Python Plot Output

Conclusion:

Thus, we have study, analysis, stimulate the BJT cascade amplifier using e-sim.

Reference:

Electronics Circuits Analysis and Design (THIRD EDITION) by Donald A Neamen
Chapter 6 Basic BJT Amplifier page number:441