

Title of the Experiment

MOSFET based Class B Push Pull Amplifier

Theory

Push-pull amplifiers employ a pair of "complementary," or matching, transistors, one of which is an NPN type and the other a PNP type. The input signal that both power transistors receive is the same, with the same amplitude but opposite phase. Therefore, the "two-halves" that are produced are put back together at the output terminal, with one transistor amplifying just half, or 180°, of the input waveform cycle, and the second transistor amplifying the remaining half, or 180°, of the input waveform cycle. This kind of amplifier circuit's conduction angle is therefore just 180 degrees, or 50% of the input signal. The clever term "push-pull" refers to the pushing and pulling action of the transistors' alternate half cycles.

Schematic Diagram

The circuit schematic of the Class B Push-Pull Amplifier in eSim is as shown below

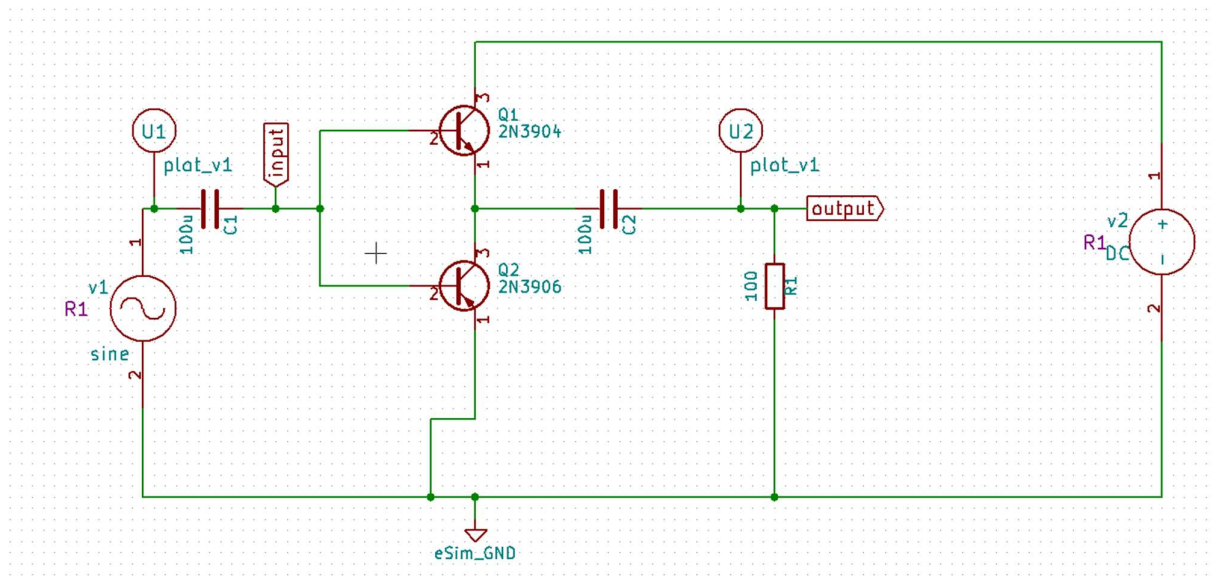


Figure 1: Schematic Diagram of Class B Amplifier

Simulation Results

1. NGSpice

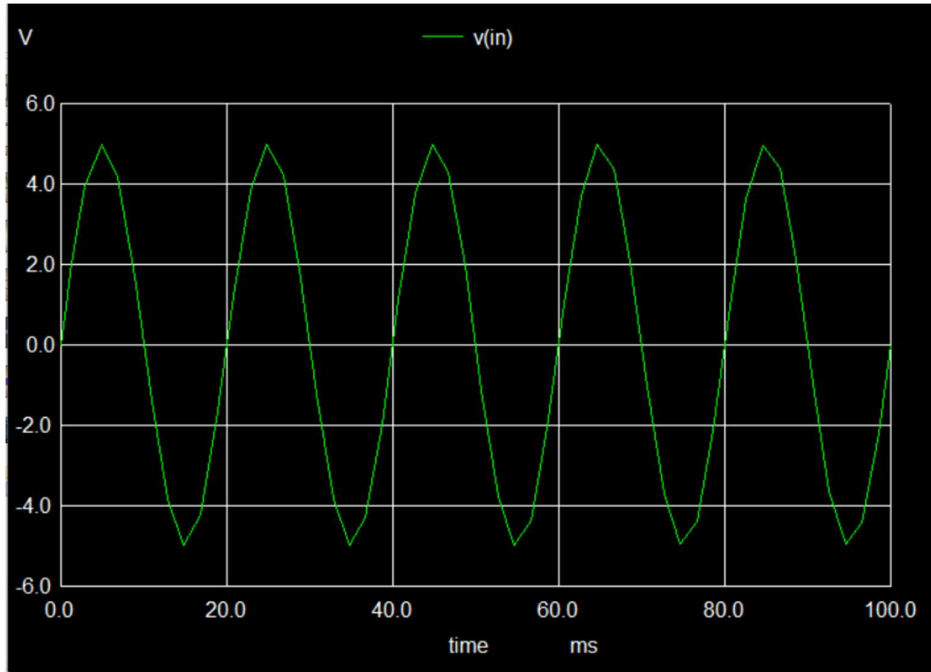


Figure 2: Input Signal given to the Class B Amplifier

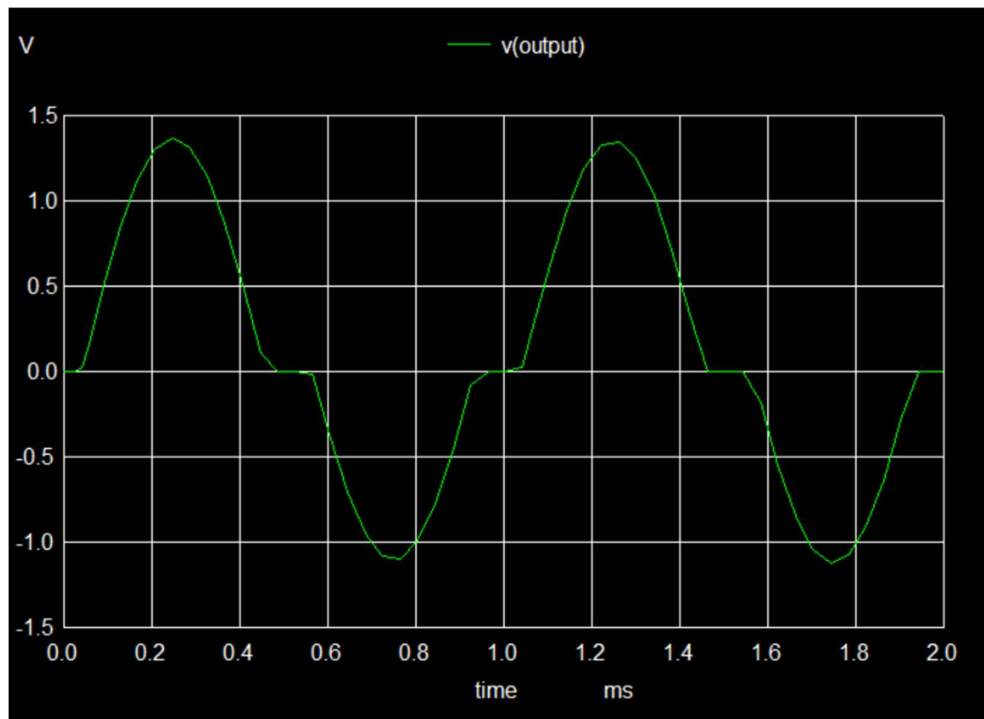


Figure 3: Output Signal given from the Class B Amplifier

2. Python Plot

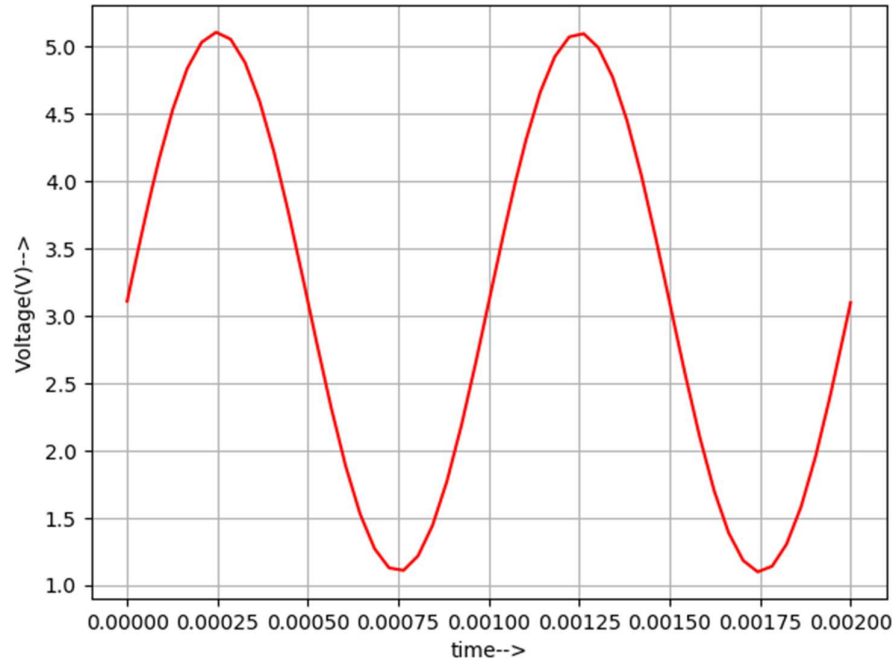


Figure 4: Input Signal given to the Class B Amplifier

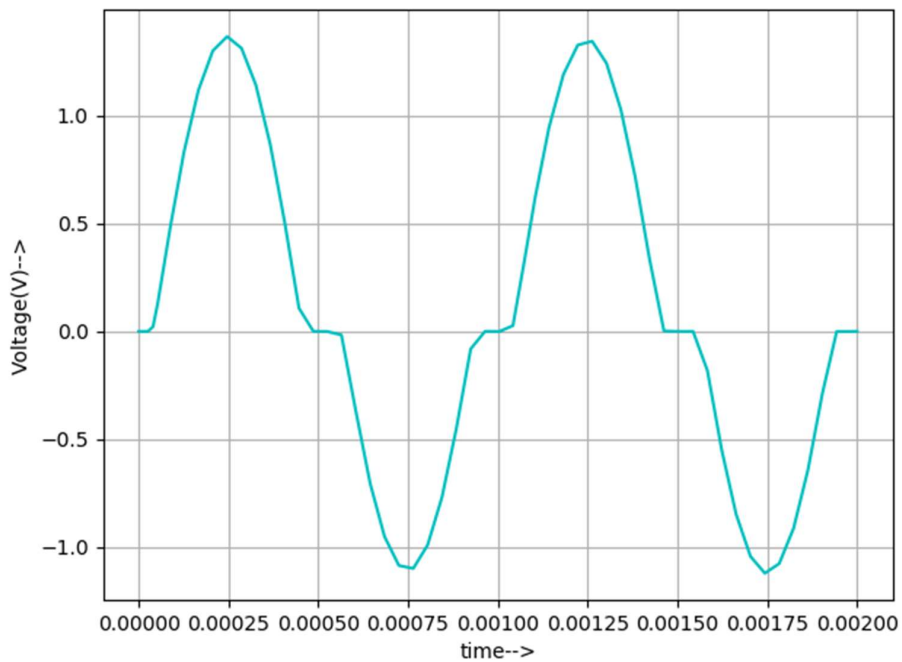


Figure 5: Output Signal given from the Class B Amplifier

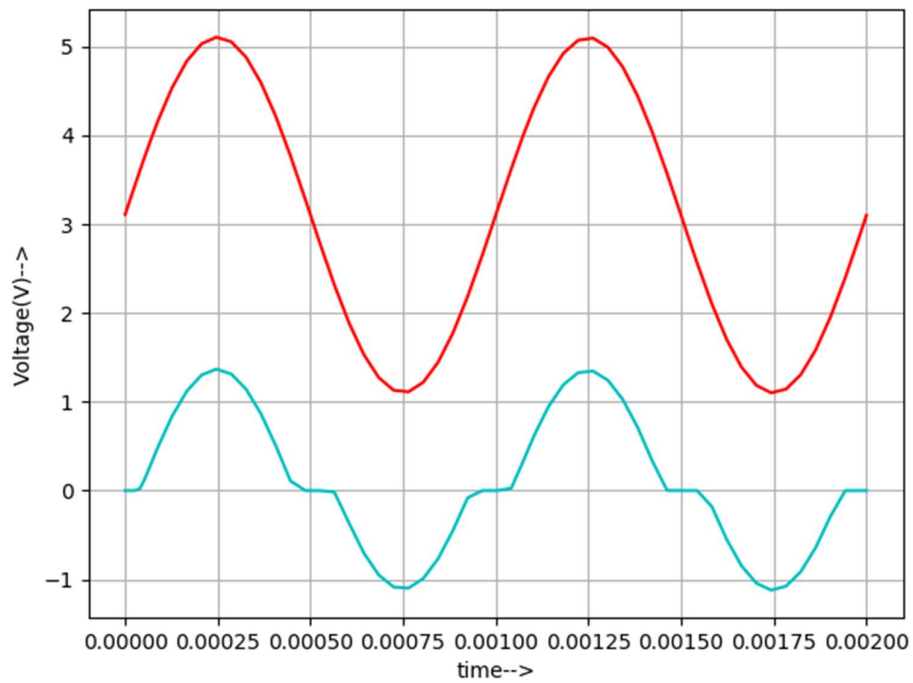


Figure 6: Transient Analysis of Class B Amplifier

Conclusion

Therefore, we have successfully verified the transient analysis of the Class B Push Pull Amplifier and achieved the appropriate waveforms.

References

https://www.electronics-tutorials.ws/amplifier/amp_6.html

https://www.tutorialspoint.com/amplifiers/class_b_power_amplifier.htm

<https://www.elprocus.com/class-b-amplifier/>

<https://www.allaboutcircuits.com/technical-articles/introduction-to-class-b-power-amplifiers/>