

## CIRCUIT SIMULATON PROJECT

**Name of the Participant:** MIR MOUSAM ALI

**Name of the institution:** ALIAH UNIVERSITY

### Title of the experiment:-


***Implementation Of 2 Input Exclusive-OR Gate Using Emitter Coupled Logic***

### Theory:-

XOR gate is also known as the Exclusive OR gate or Ex-OR gate. It gives the output 1 (High) if an odd number of inputs is high. This can be understood in the Truth Table. It can have an infinite number of inputs and only one output. In most cases, two-input or three-input XOR gates are used. Here I implement two input XOR Gate.

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

**Truth Table of XOR Gate**

 


**Exclusive-OR Gate**

Emitter-coupled logic (ECL) is a non-saturated digital logic family. Since transistors do not saturate, it is possible to achieve propagation delays of 2 ns and even below 1ns. This logic family has the lowest propagation delay of any family and is used mostly in systems requiring very-high speed operation. A XOR circuit of the ECL family is shown in Schematic Diagram. The main outputs provide XOR functions. Each input is connected to the base of a transistor. The two voltage levels are about  $-0.8$  V for the high state and about  $-1.8$  V for the low state. The circuit consists of differential amplifier, a temperature- and voltage-compensated bias network, and emitter-follower output.
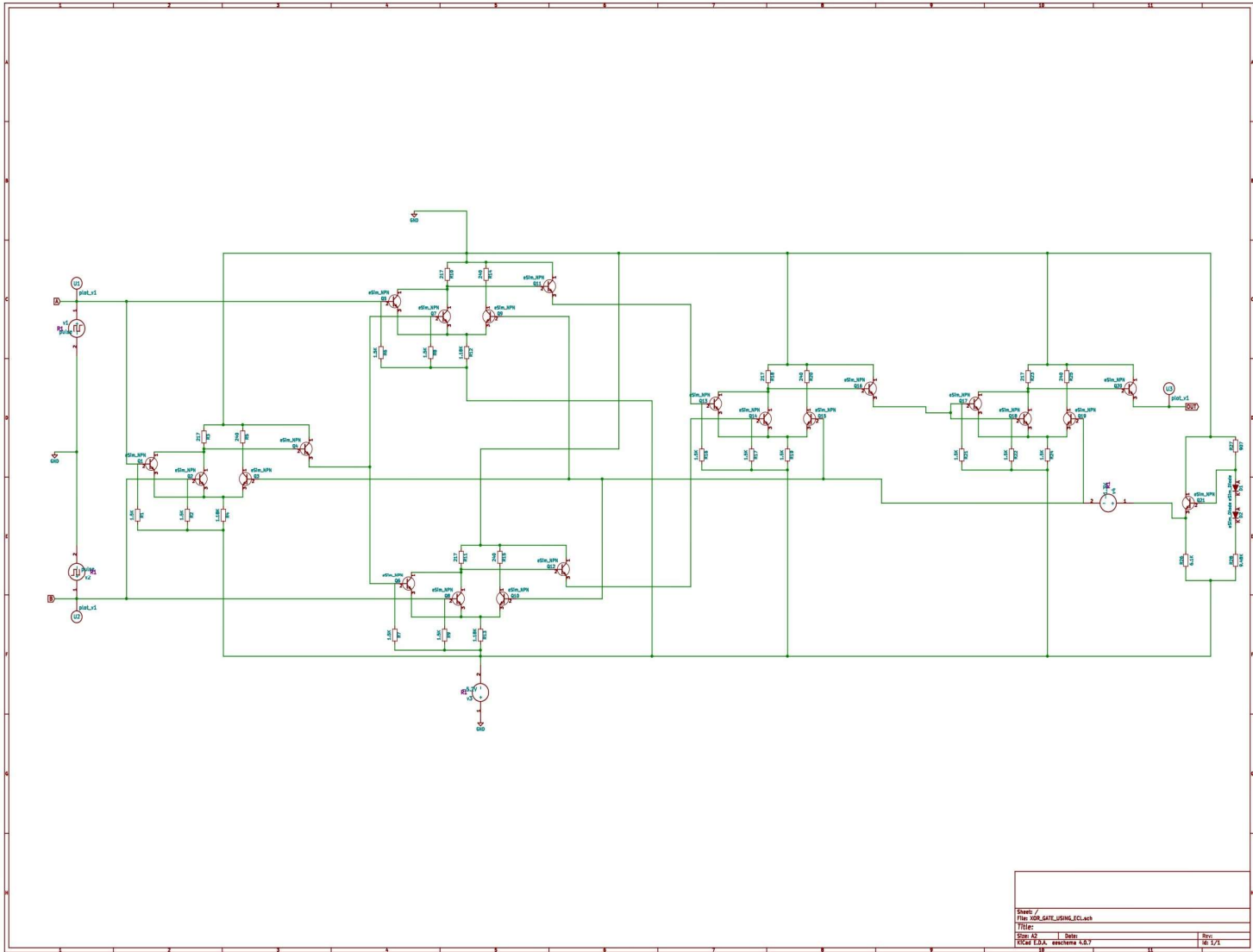
### Schematic Diagram:-


The circuit schematic of 2 Input Exclusive-Or Gate Using Emitter Coupled Logic in eSim is as shown below:




**Exclusive-OR Gate using ECL logic**

**Simulation Results:-**


- **Nqspice Plots :**

 

**Ngspice Input-1 Plot**

 

**Ngspice Input-2 Plot**

 


Ngspice Output Plot

• Python Plot:




Python Plot Input-1


### Python Plot Input-1

 


### Python Plot Input-2

 

### Python Plot Output

 

Python Plot of XOR Gate

 

### Conclusion :-

Thus, we have studied the Implementation Of two Input Exclusive-OR Gate Using Emitter Coupled Logic using eSim and we get the appropriate waveform.

### References :-

- Digital Logic and Computer Design by M. MORRIS MANO
- [https://faculty-web.msoe.edu/johnsontimoi/CE3101/files3101/emitter\\_coupled\\_logic\\_implementation.pdf](https://faculty-web.msoe.edu/johnsontimoi/CE3101/files3101/emitter_coupled_logic_implementation.pdf)
- <https://www.geeksforgeeks.org/emitter-coupled-logic/>
- [ECL NOR/OR GATE](#)
- [Lecture - 19 Quantitative analysis of ECL 10k Series gates](#)