

Variable nine pulse AC converter

Circuit simulation done by

Kanimozhi. K

**Department of Electrical and Electronics Engineering
St. Xavier's Catholic college of engineering, Chunkankadai.**

Theory/Description:

In this project, three nine waves are generated using the nine-phase sine wave generator. A nine-phase sine wave generator typically involves using three sets of three-phase sine wave generators, each set being phase-shifted by 120 degrees. This approach allows for the generation of nine sine waves with different phases. transistor stages configured in a cross coupled manner, having equivalent RC timing constants across their bases.

Circuit explanation:

- JFETs (Junction Field-Effect Transistors) are three-terminal semiconductor devices that can be used for various analog circuit applications, including amplification and switching. In a JFET, the gate-to-source voltage controls the flow of current between the drain and source terminals.**

- **The JFETs could be configured in various amplifier topologies, such as common source, common drain, or common gate configurations. These configurations determine the input-output characteristics and gain of the amplifier.**
- **The above mutual push and pull procedure induces and settles into a continuous sequential train of conduction across the transistors causing the intended three phase signal pattern to appear across the collectors of the transistors. Owing to the gradual charge and discharge pattern of the capacitors, the resultant signal shape is a pure sine wave .**

eSim circuit diagram:

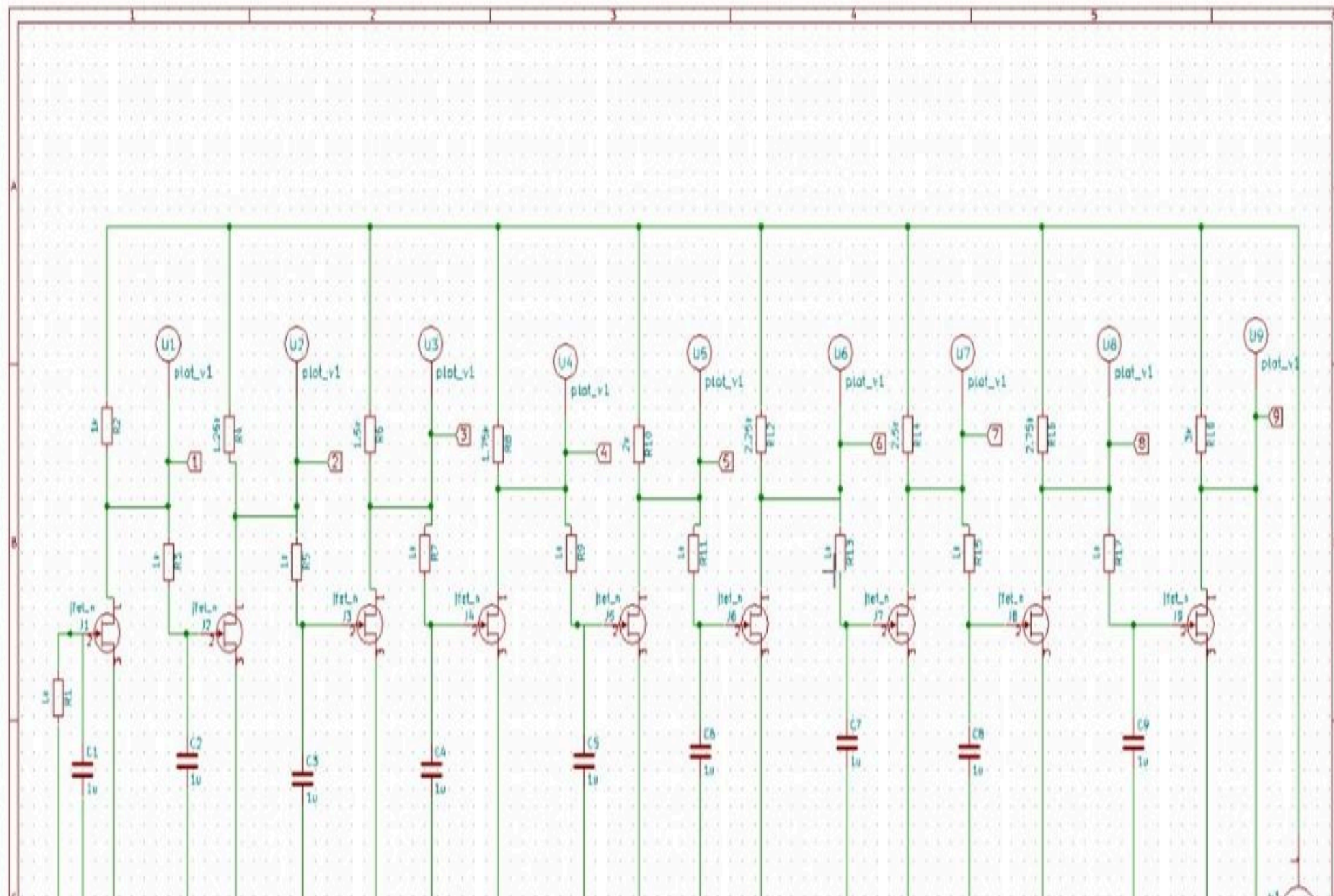


Fig: eSim circuit diagram (switch on condition)

Simulation Results:

Analysis Source Details Ngspice Model Device Modeling Subcircuits

Select Analysis Type

AC

DC

TRANSIENT

Transient Analysis

Start Time

0

ms

Step Time

0.1

ms

Stop Time

0.04

Sec

Convert

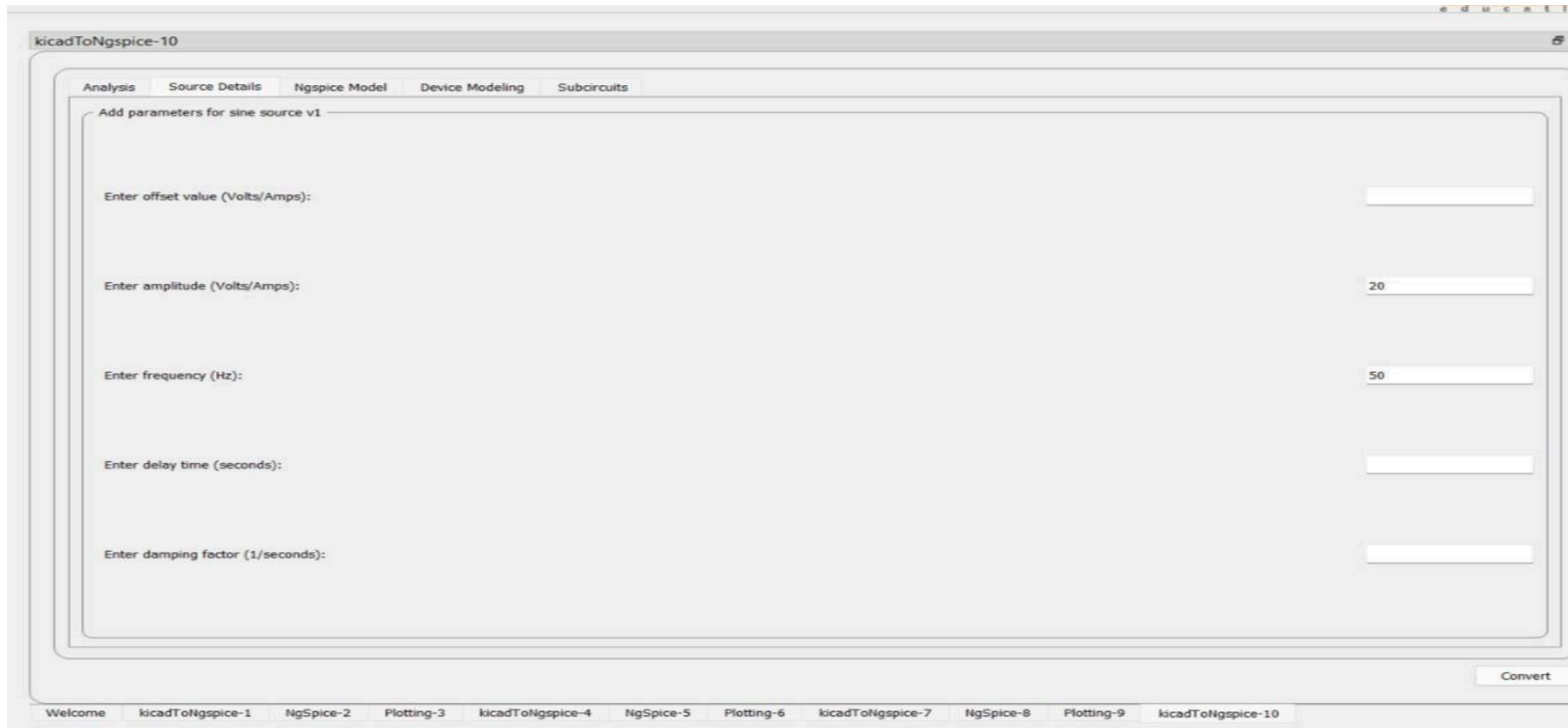


Fig:Kicad to NgSpice

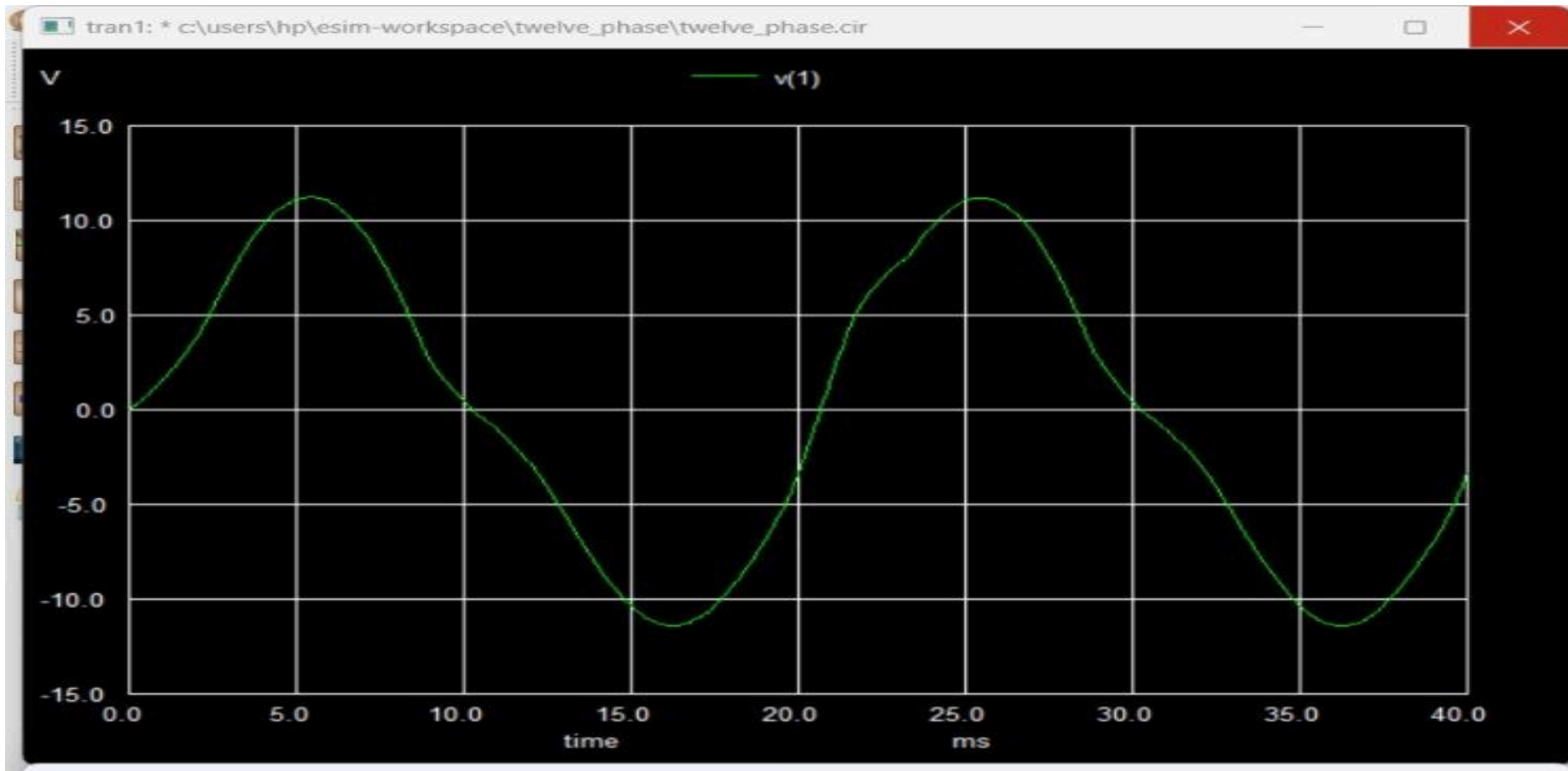


Figure : Ngspice output Sine Wave 1

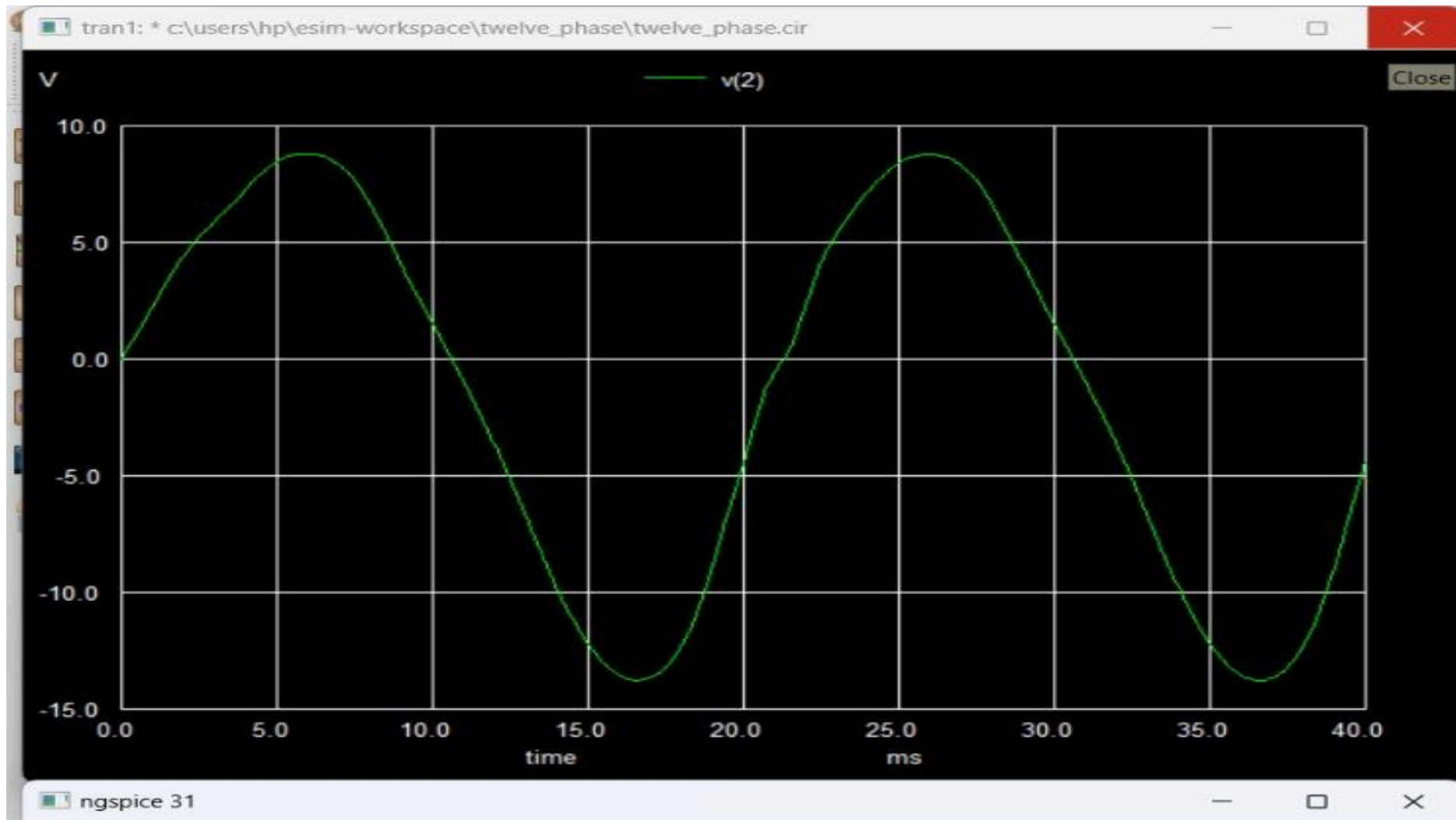


Figure : Ngspice output Sine Wave 2

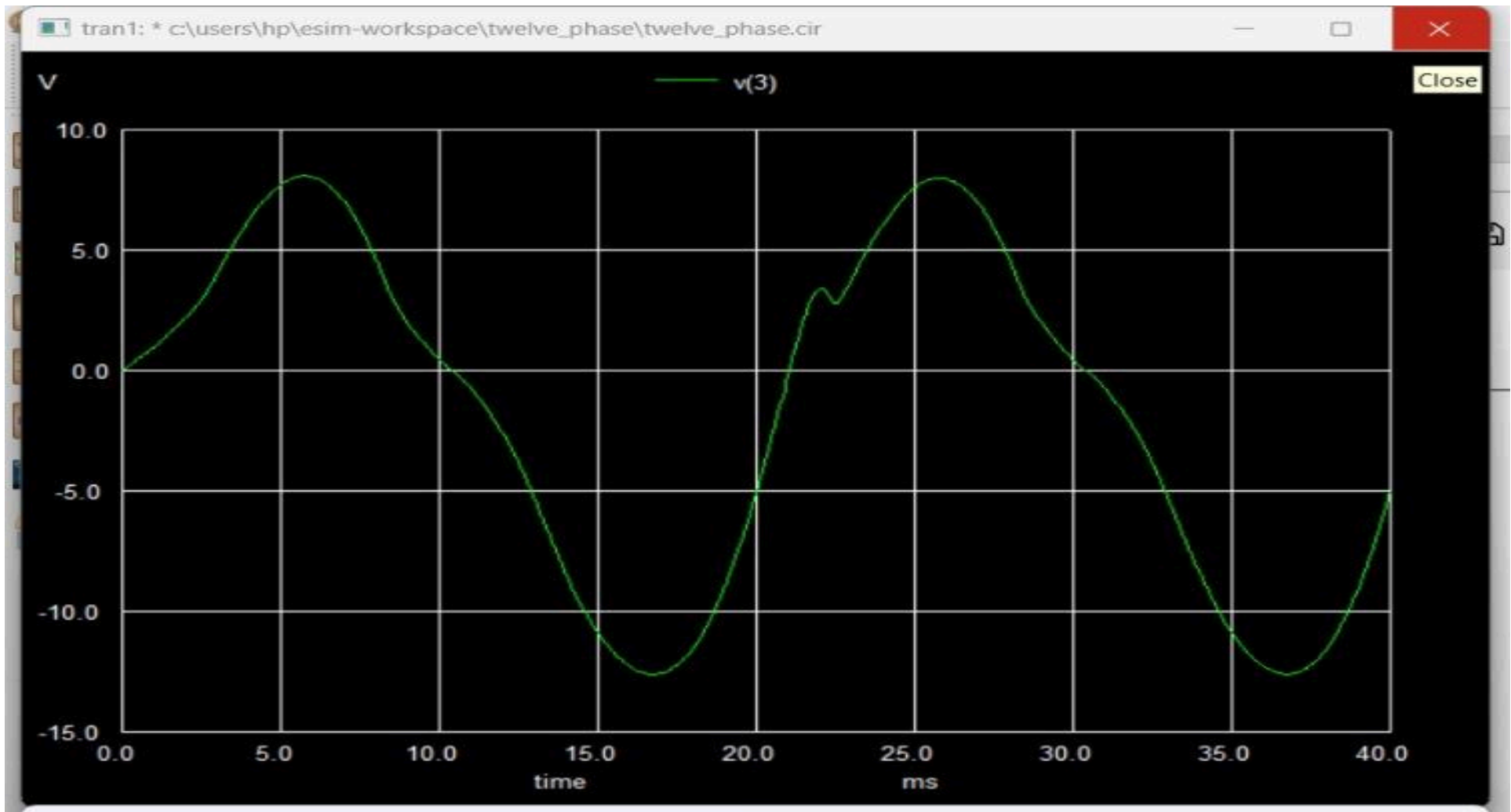


Figure : Ngspice output Sine Wave 3

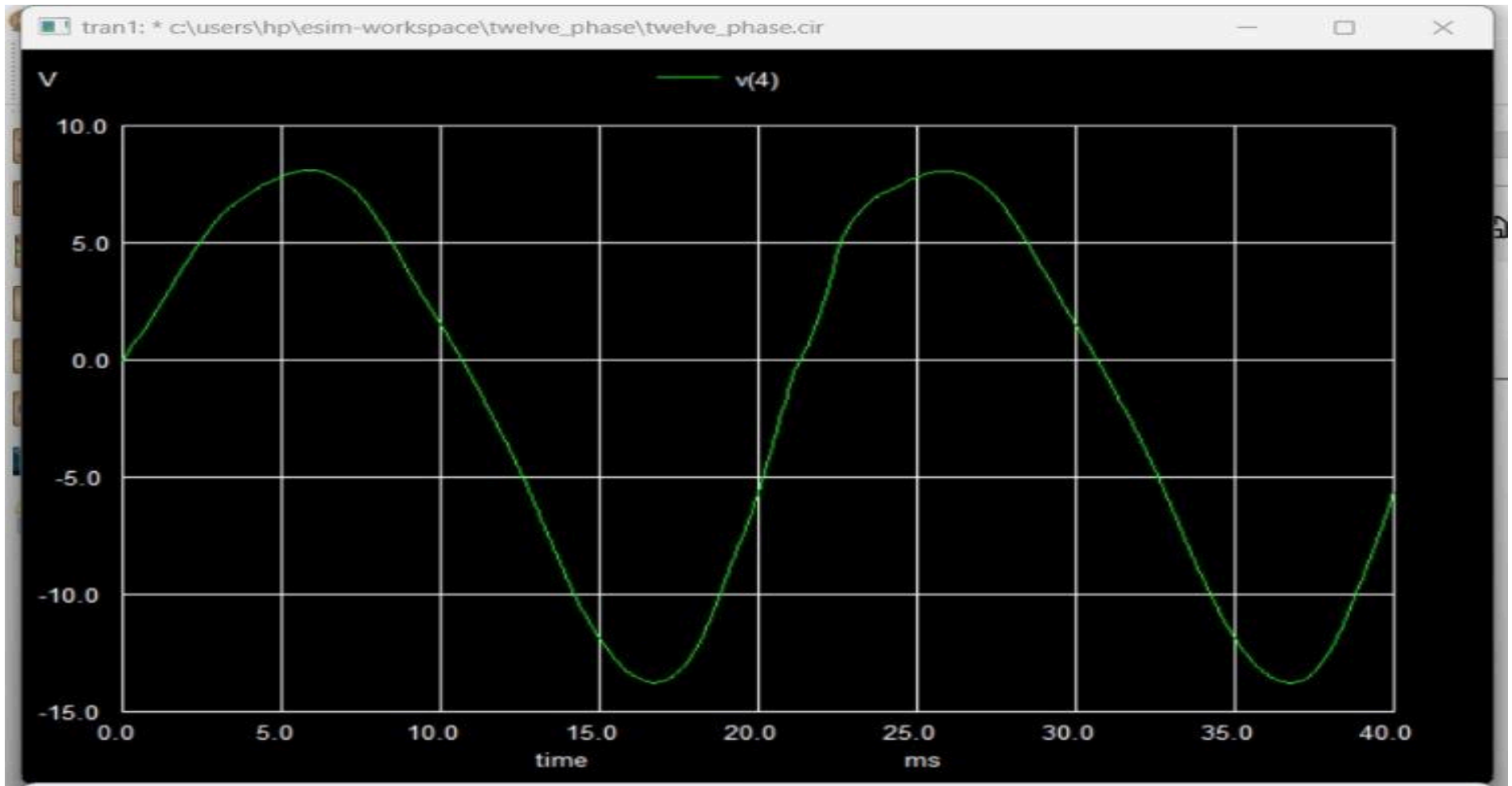


Figure : Ngspice output Sine Wave 4

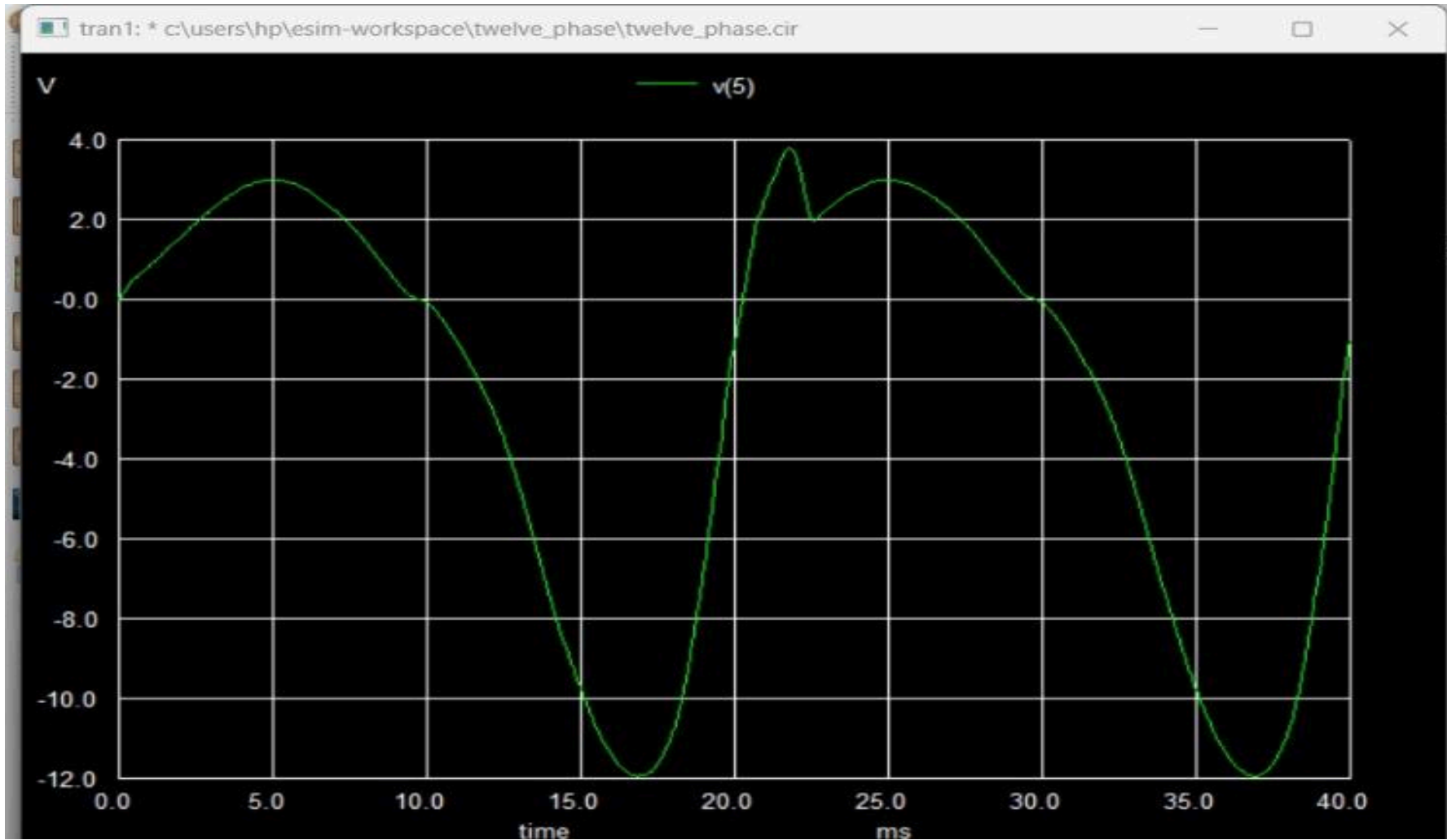


Figure : Ngspice output Sine Wave 5

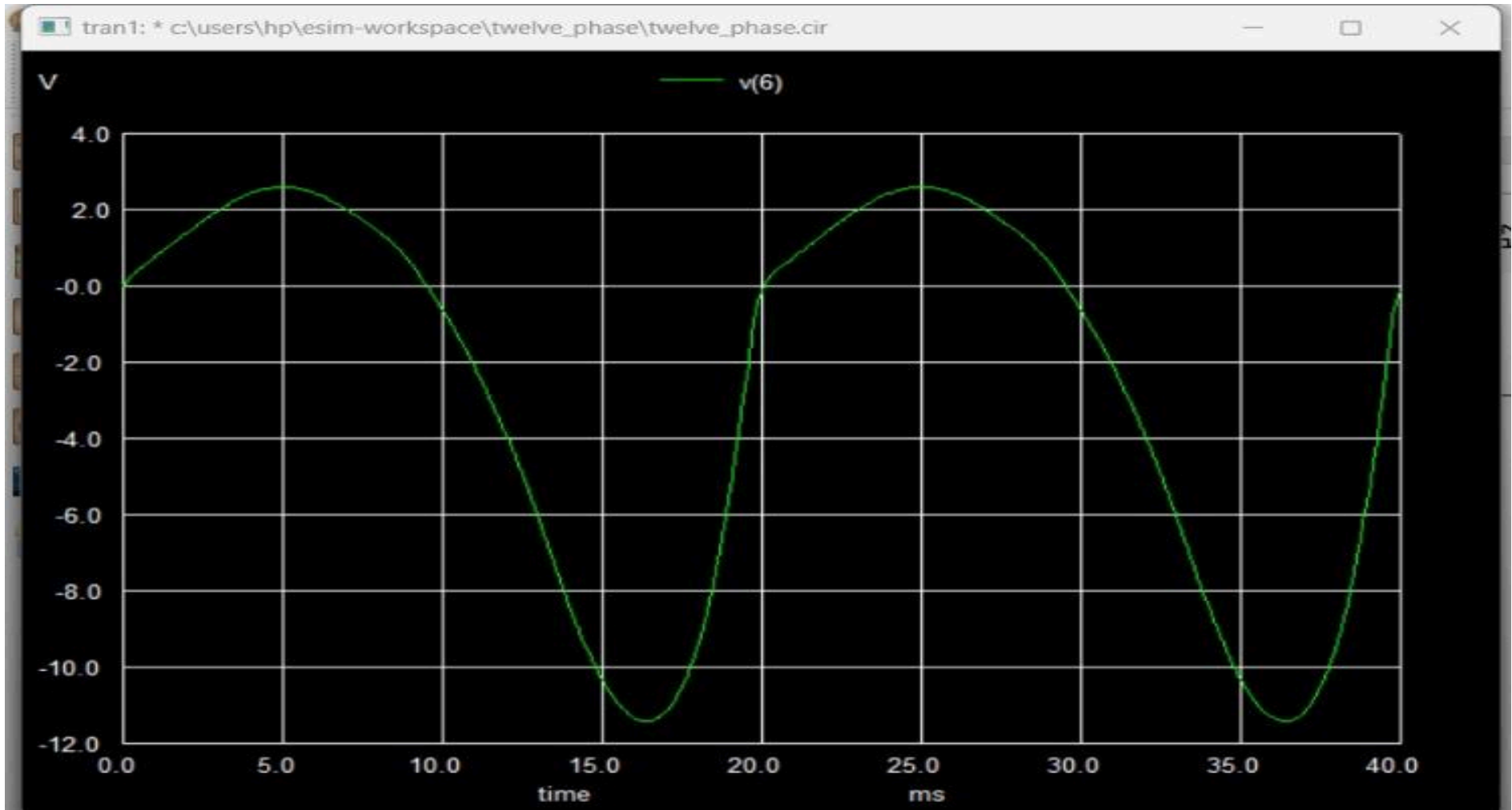


Figure : Ngspice output Sine Wave 6

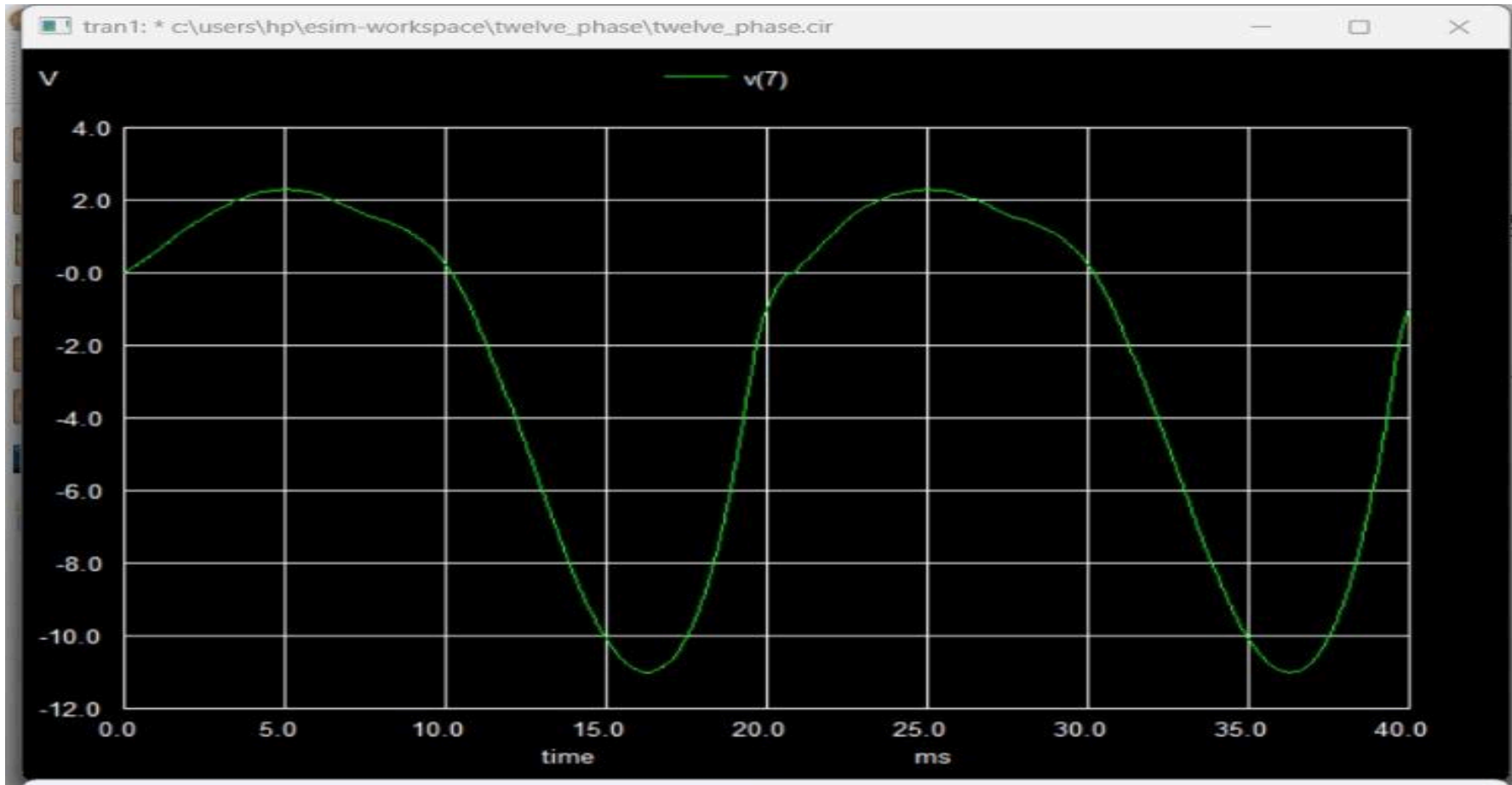


Figure : Ngspice output Sine Wave 7

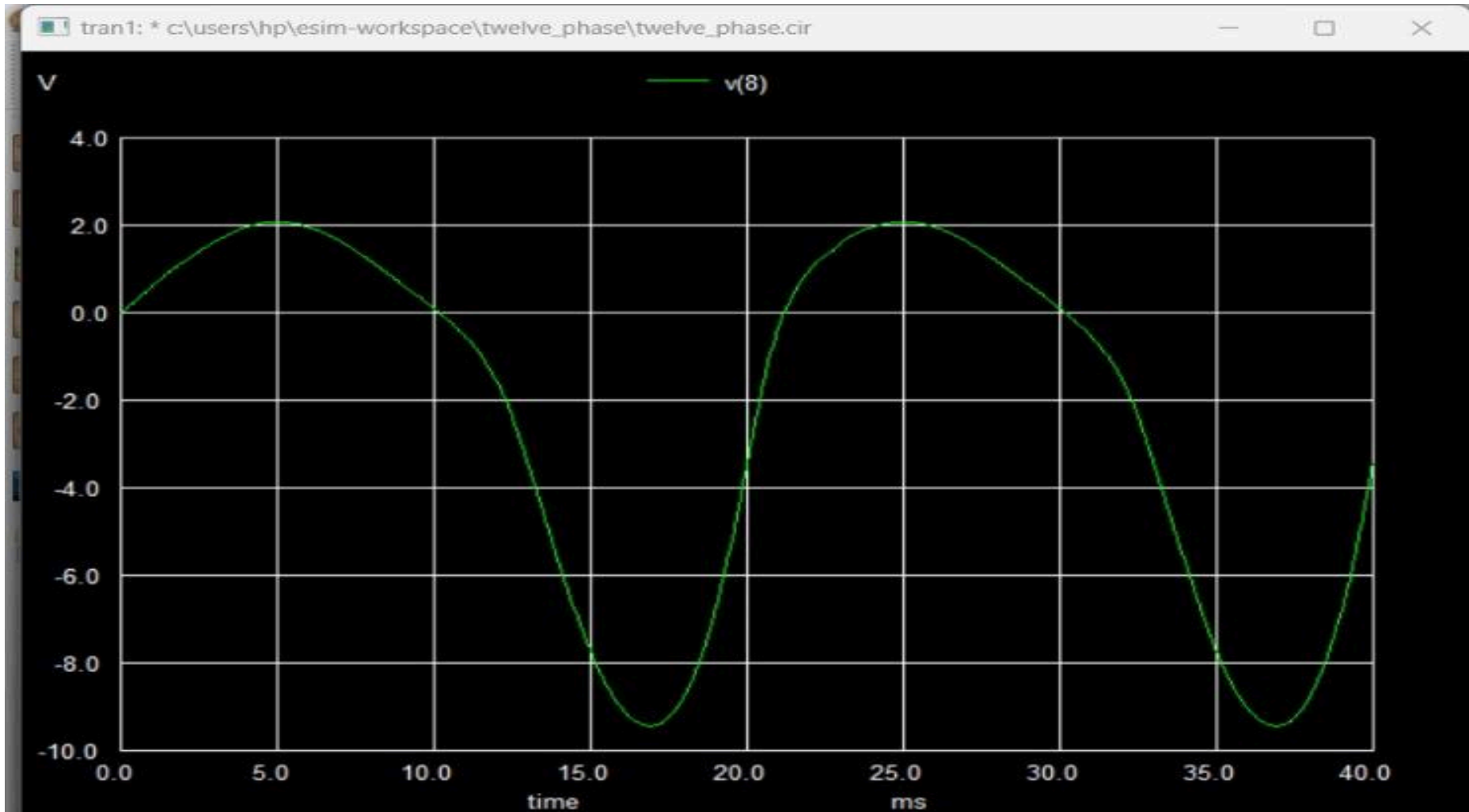


Figure : Ngspice output Sine Wave 8


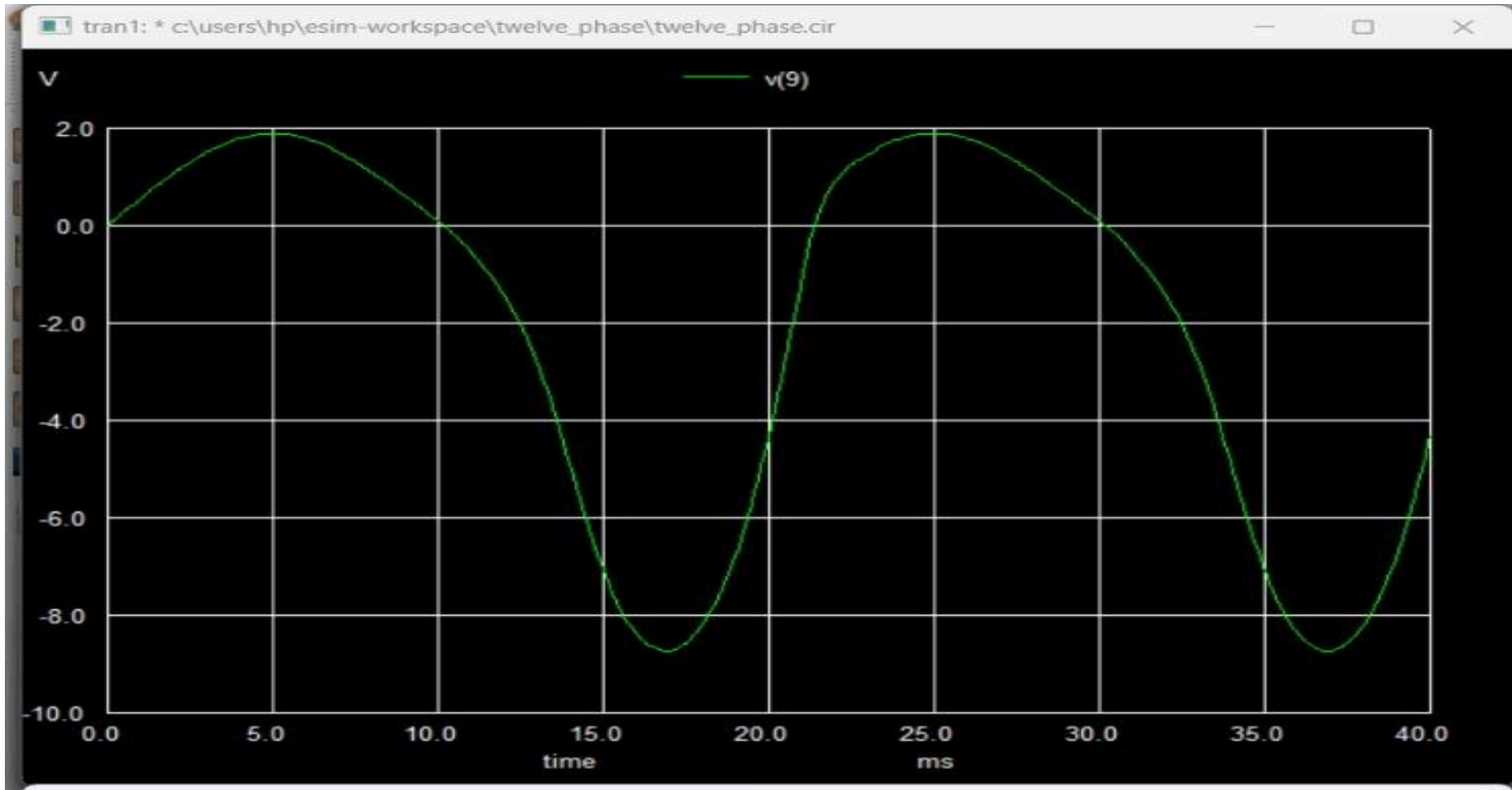
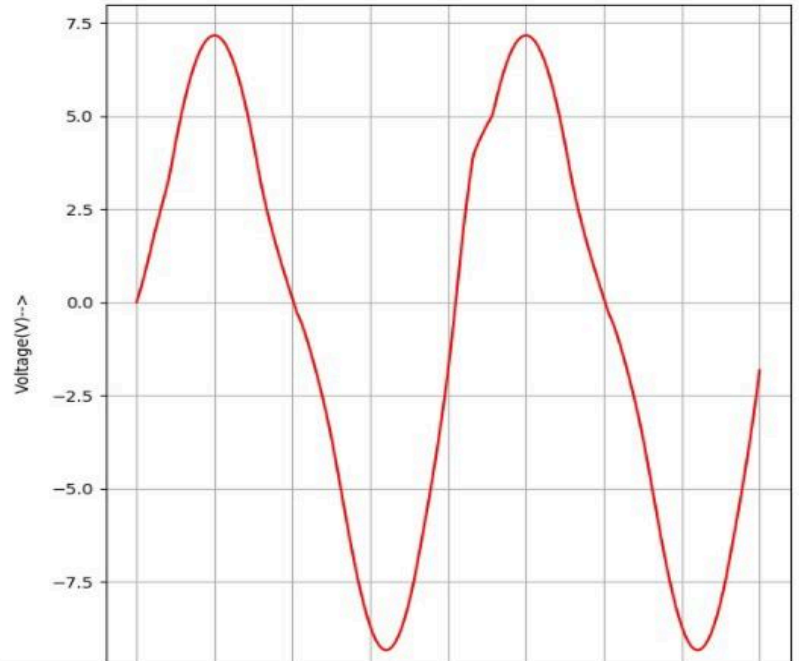
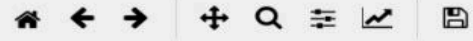


Figure : Ngspice output Sine Wave 9

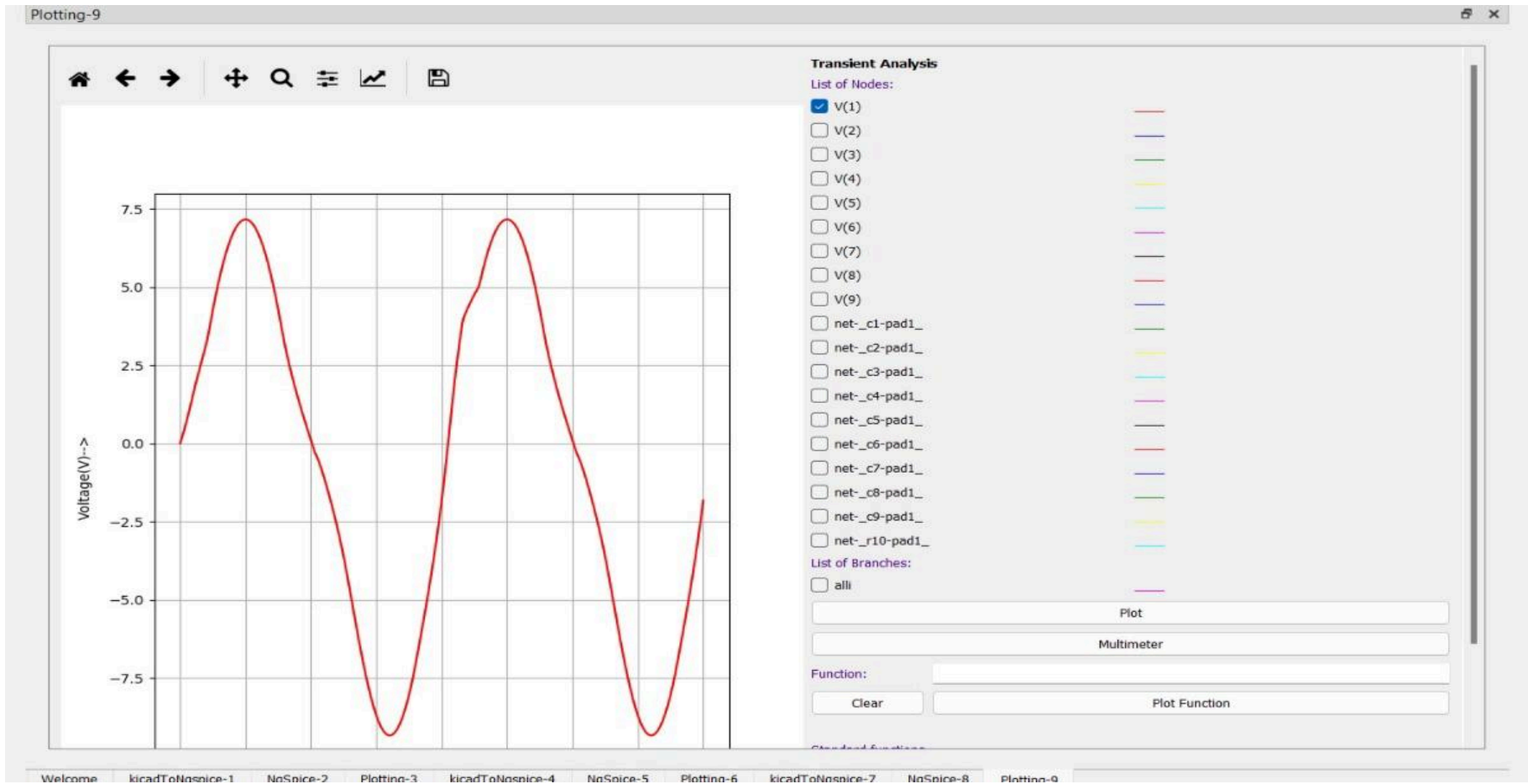

Transient Analysis

List of Nodes:

- V(1)
- V(2)
- V(3)
- V(4)
- V(5)
- V(6)
- V(7)
- V(8)
- V(9)
- net_c1-pad1_
- net_c2-pad1_
- net_c3-pad1_
- net_c4-pad1_
- net_c5-pad1_
- net_c6-pad1_
- net_c7-pad1_
- net_c8-pad1_
- net_c9-pad1_
- net_r10-pad1_

List of Branches:



- all

Plot

Multimeter

Function:

Clear Plot Function

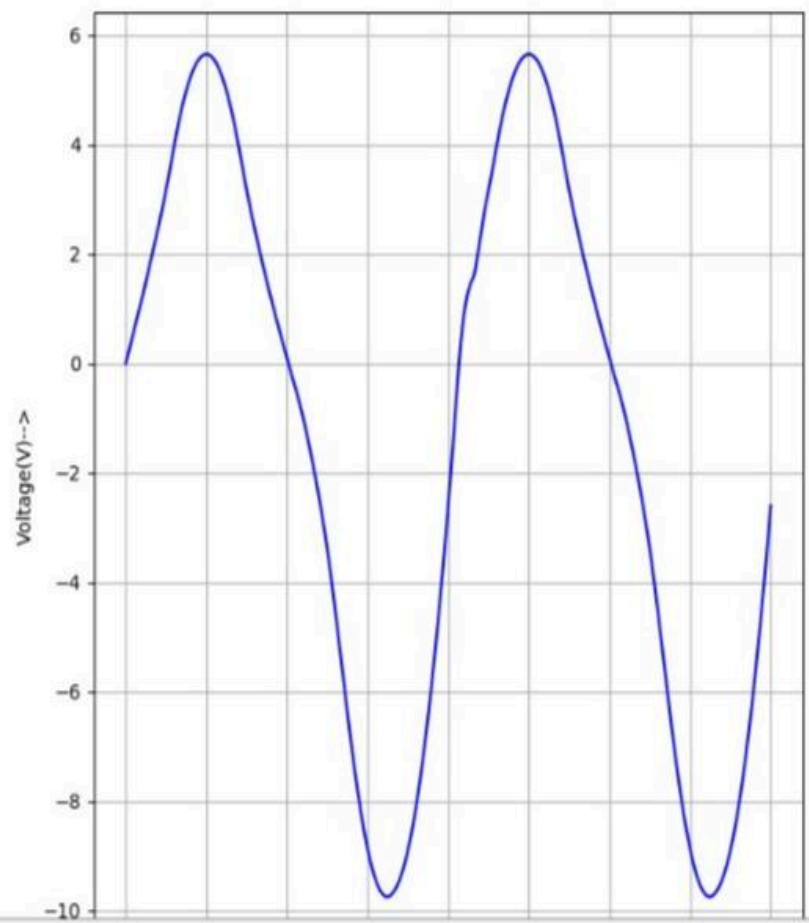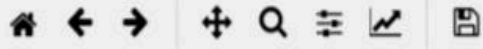

Transient Analysis

List of Nodes:

- V(1)
- V(2)
- V(3)
- V(4)
- V(5)
- V(6)
- V(7)
- V(8)
- V(9)
- net_c1-pad1_
- net_c2-pad1_
- net_c3-pad1_
- net_c4-pad1_
- net_c5-pad1_
- net_c6-pad1_
- net_c7-pad1_
- net_c8-pad1_
- net_c9-pad1_
- net_r10-pad1_

List of Branches:

- all

Plot


Multimeter

Function:

Clear

Plot Function

Standard functions:

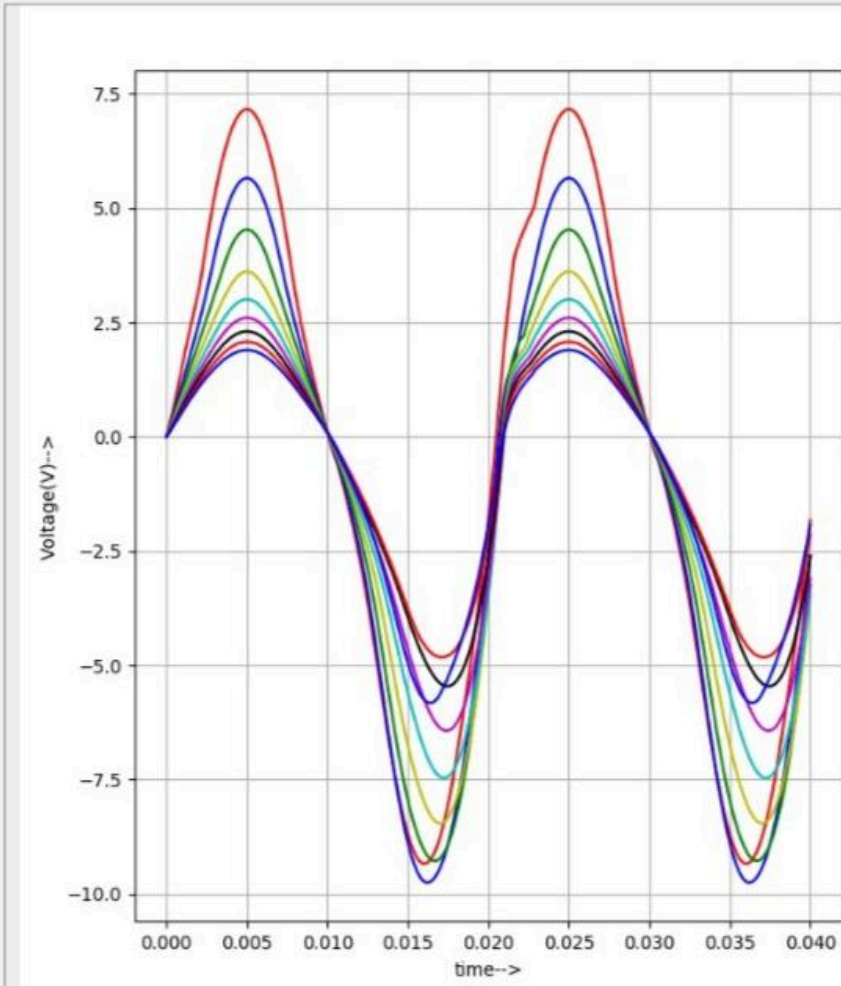

- V(3) —
- V(4) —
- V(5) —
- V(6) —
- V(7) —
- V(8) —
- V(9) —
- net_c1-pad1_ —
- net_c2-pad1_ —
- net_c3-pad1_ —
- net_c4-pad1_ —
- net_c5-pad1_ —
- net_c6-pad1_ —
- net_c7-pad1_ —
- net_c8-pad1_ —
- net_c9-pad1_ —
- net_r10-pad1_ —

List of Branches:

- all —

Plot

Multimeter

Function:

Clear Plot Function

Standard functions

- Addition: Node1 + Node2
- Subtraction: Node1 - Node2
- Multiplication: Node1 * Node2
- Division: Node1 / Node2
- Comparison: Node1 vs Node2

(a) Combined waveform of all the nine waves



(b) Legend

Conclusion:

Hence, three sine waves were generated and an appropriate waveform was obtained.

References:

<https://www.homemade-circuits.com/3-phase-signal-generator-using/>

<https://microcontrollerslab.com/three-phase-sine-wave-generator/>

<https://circuitdigest.com/electronic-circuits/sine-wave-generator-circuit>