

# Bidirectional shift registers using flip flops and basic gates using eSim

**THEORY:** Bidirectional Shift registers are the storage devices which are capable of shifting the data either right or left depending on the mode selected.

**Design:**


Eg: SET=0, RESET=0

v1(mode)=5(right shift operation)

v2(datainforright shift)=5

v5(datainforleft shift)=5

**SCHEMATIC DIAGRAM:**

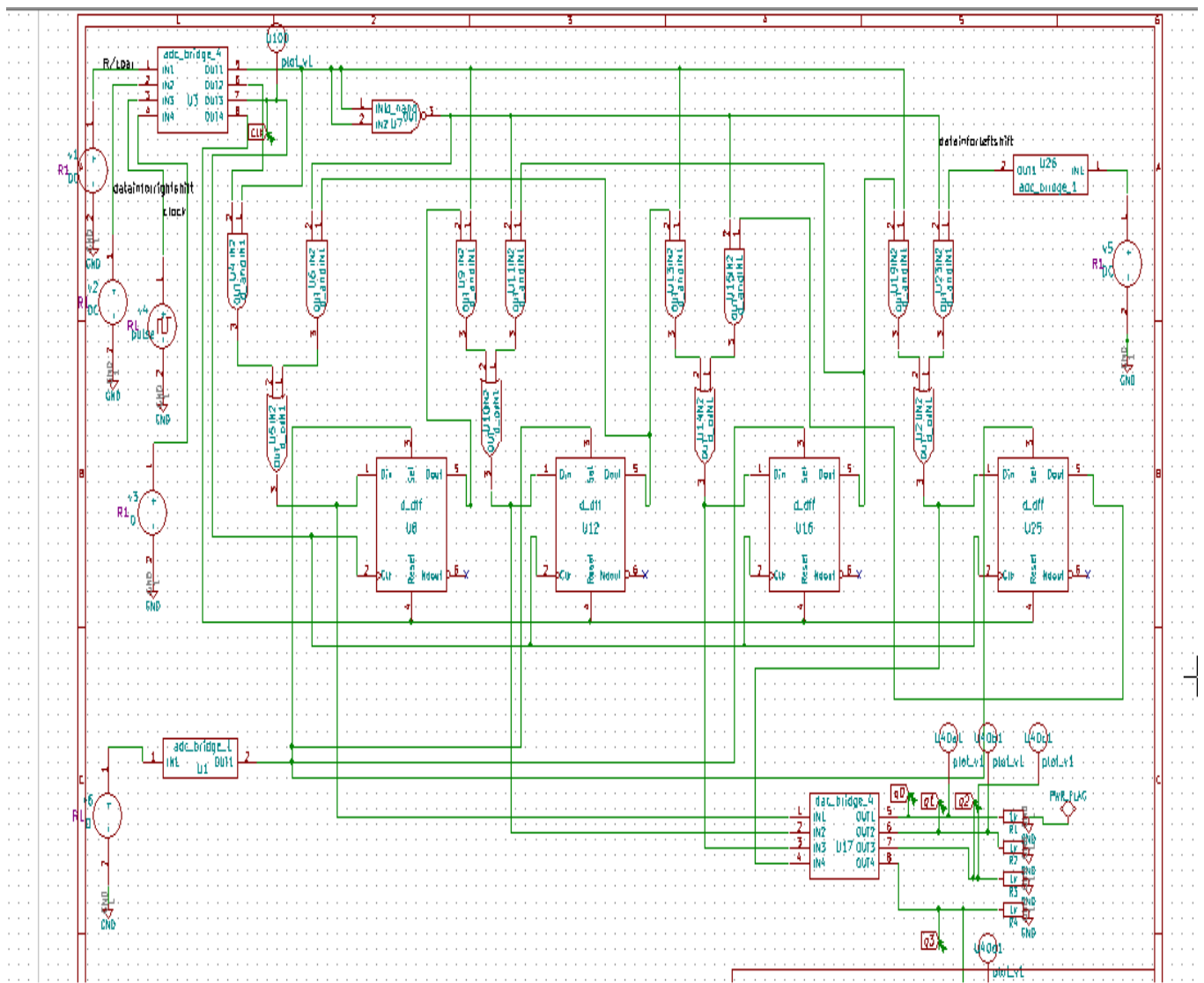

## NgSpice plots

### LEFT SHIFT OPERATION:

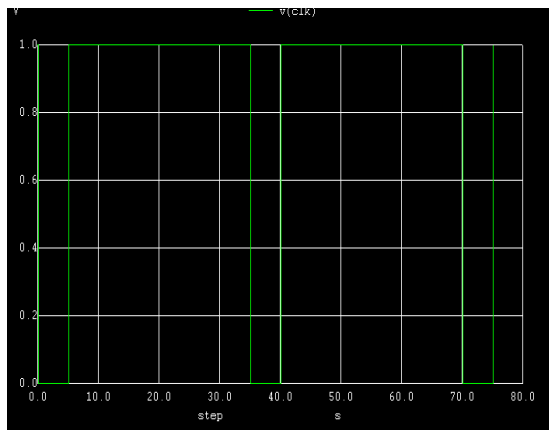


Fig1:clock

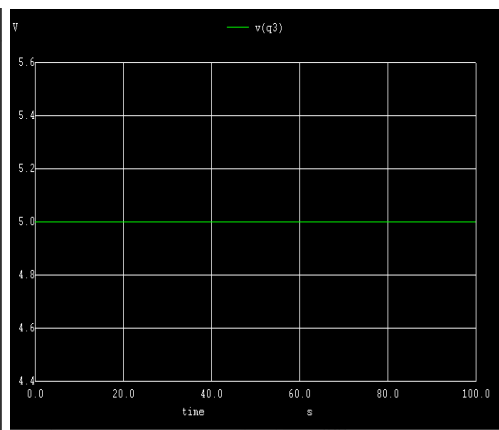


Fig2:q3 output plot

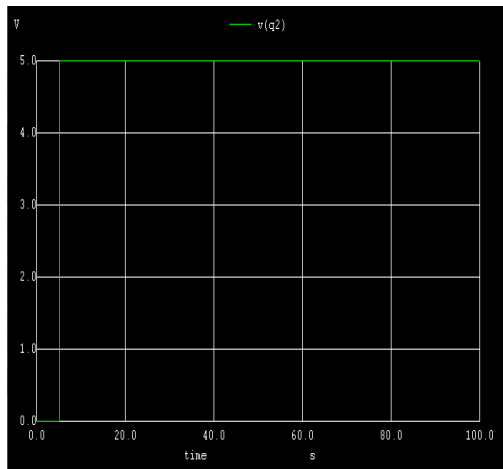


Fig3:q2 output plot

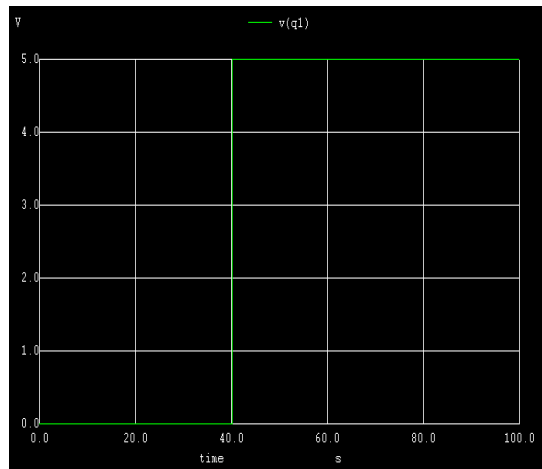


Fig4:q1 output plot

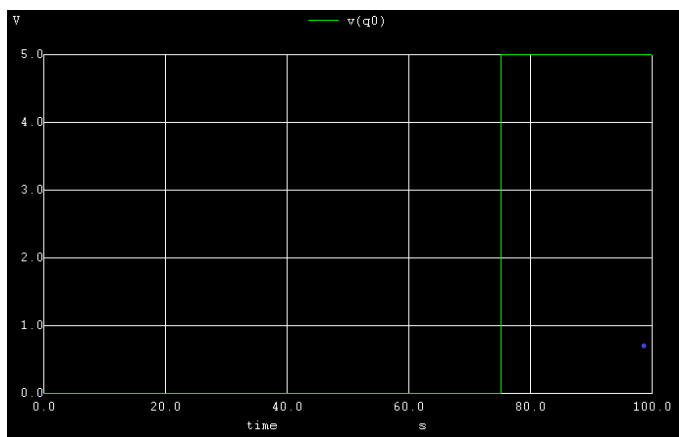


Fig5:q0 output plot

## RIGHT SHIFT OPERATION

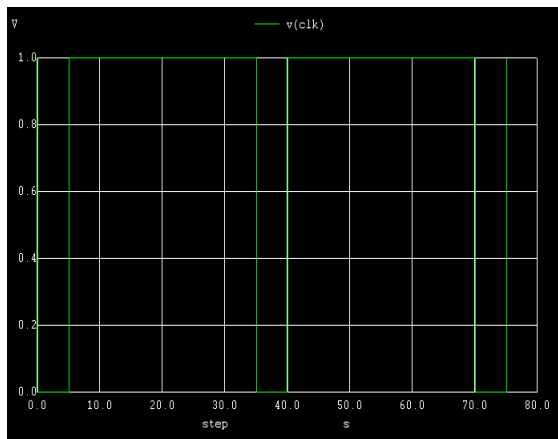


Fig6:clock

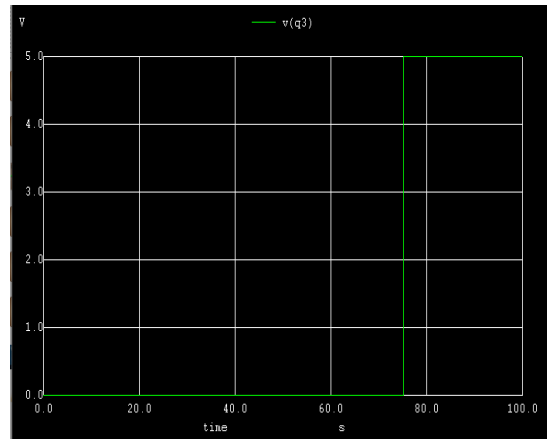


Fig7:q3 output plot

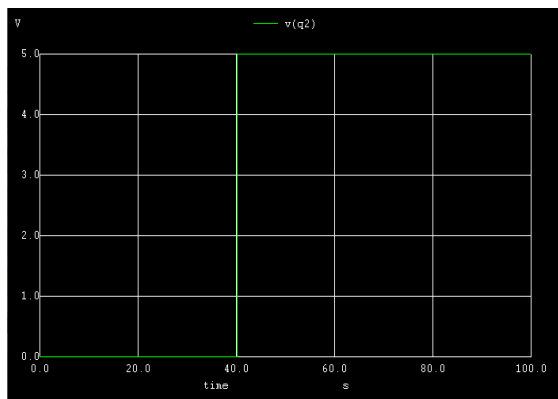


Fig7:q2 output plot

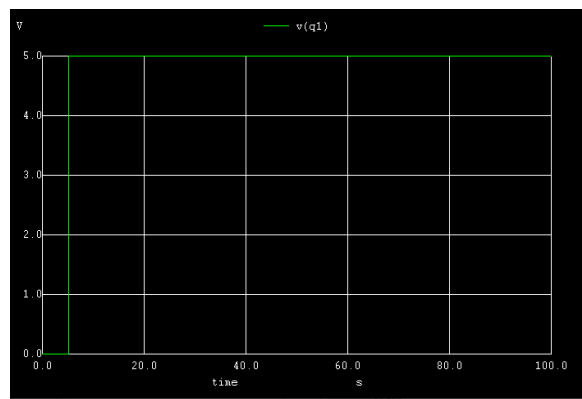


Fig8:q1 output plot

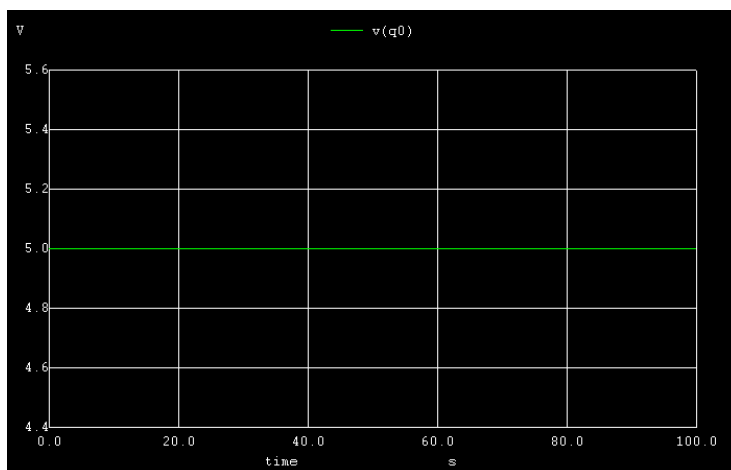


Fig9:q0 output plot

## PYTHON PLOTS:

### LEFT SHIFT OPERATION

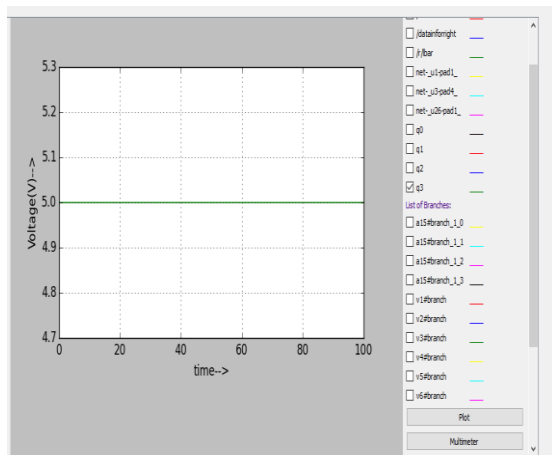


Fig1:q3 output plot

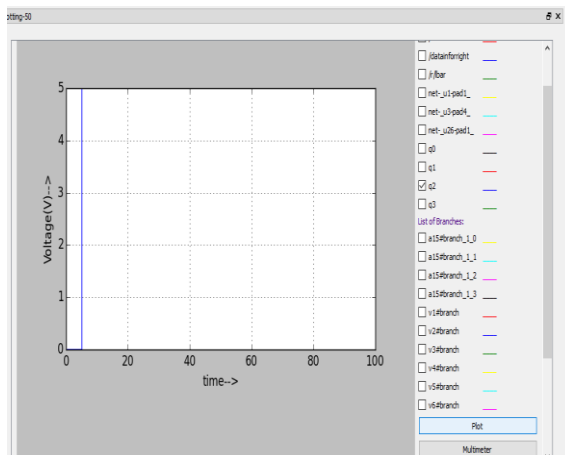


Fig2:q2 output plot

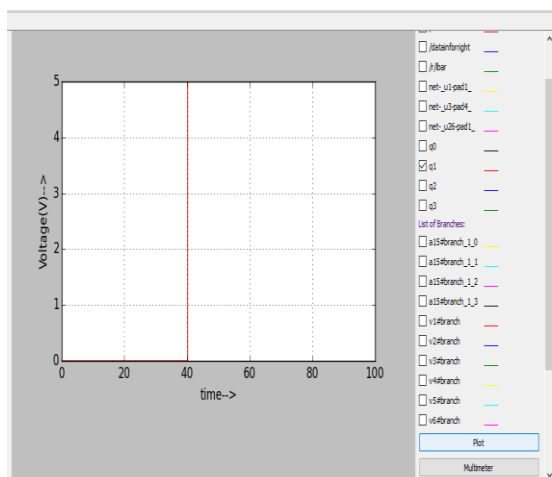


Fig3:q1 output plot

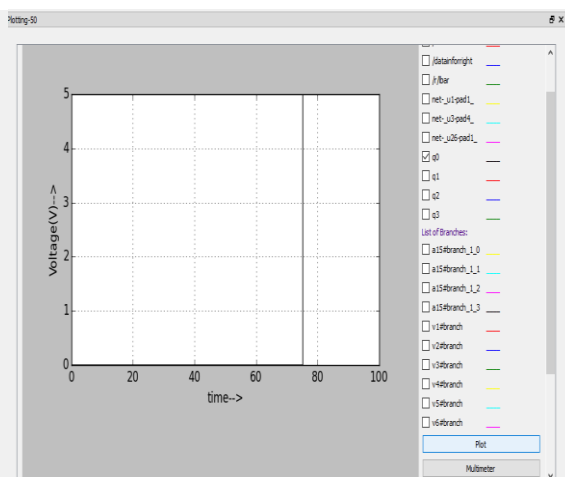


Fig4:q0 output plot

### RIGHT SHIFT OPERATION

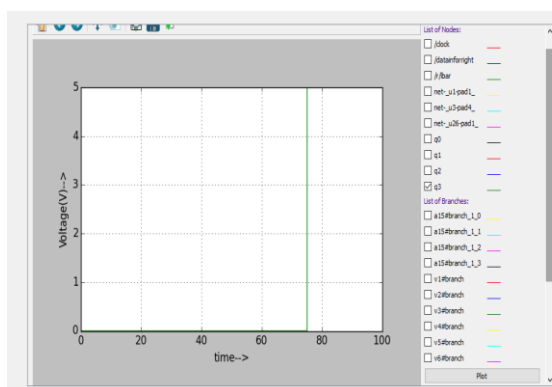


Fig5:q3 output plot

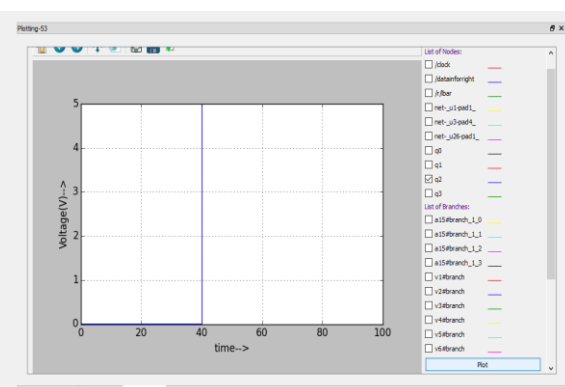


Fig6:q2 output plot

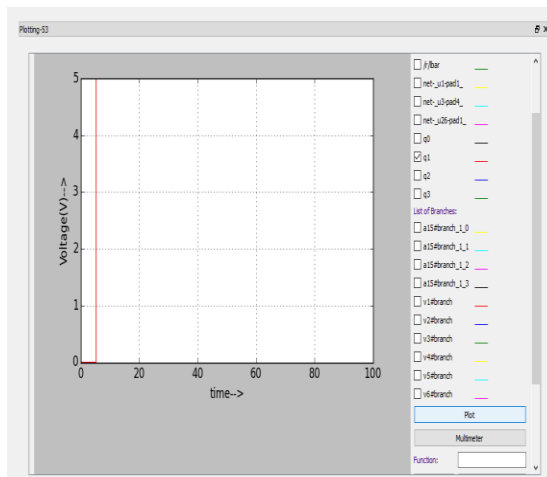


Fig7:q1 output plot

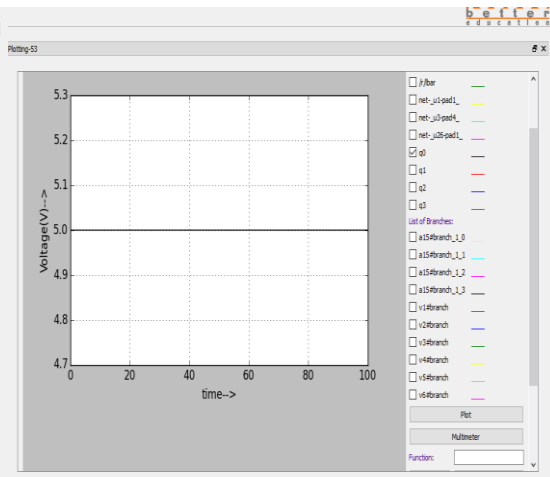


Fig8:q0 output plot

REFERENCES: <https://www.electrical4u.com/bidirectional-shift-register/>