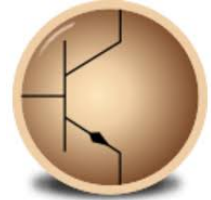




VIT[®]
Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)



Circuit Simulation Project

<https://esim.fossee.in/circuit-simulation-project>

NON-INVERTING SUMMER USING OP-AMP

by

Karthick Srivatsa R


under the guidance of **Dr.Subhashini N**,SENSE,VIT Chennai

THEORY/DESCRIPTION:

The Non-Inverting summer also known as the adder is an Op-Amp based circuit where multiple input signals of different voltages are added. This is an extended version / example of the Non-Inverting amplifier but with multiple inputs. Here the input voltages are applied the inverting terminal of the Op-Amp and a part of the output is fed back to the inverting input terminal, through voltage-divider-bias feedback. Here the output is in the same phase as the input(i.e) there is no phase shift.

DESIGN:

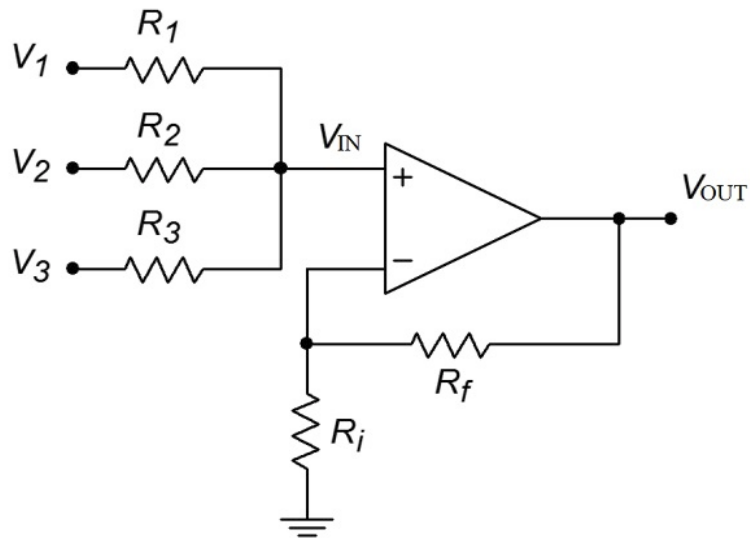The circuit of a Non-Inverting Summer is shown in the following image. For the sake of convenience, the following circuit consists of only three inputs, but more inputs can be added.




$$V_{OUT} = V_{IN} (1 + (R_f / R_i)) , V_{IN} = V_{IN1} + V_{IN2} + V_{IN3}$$

Here the $R_f/R_i=1$ and hence the equation becomes

$$V_{OUT} = V_{IN1} + V_{IN2} + V_{IN3}$$



SCHEMATIC DIAGRAM:

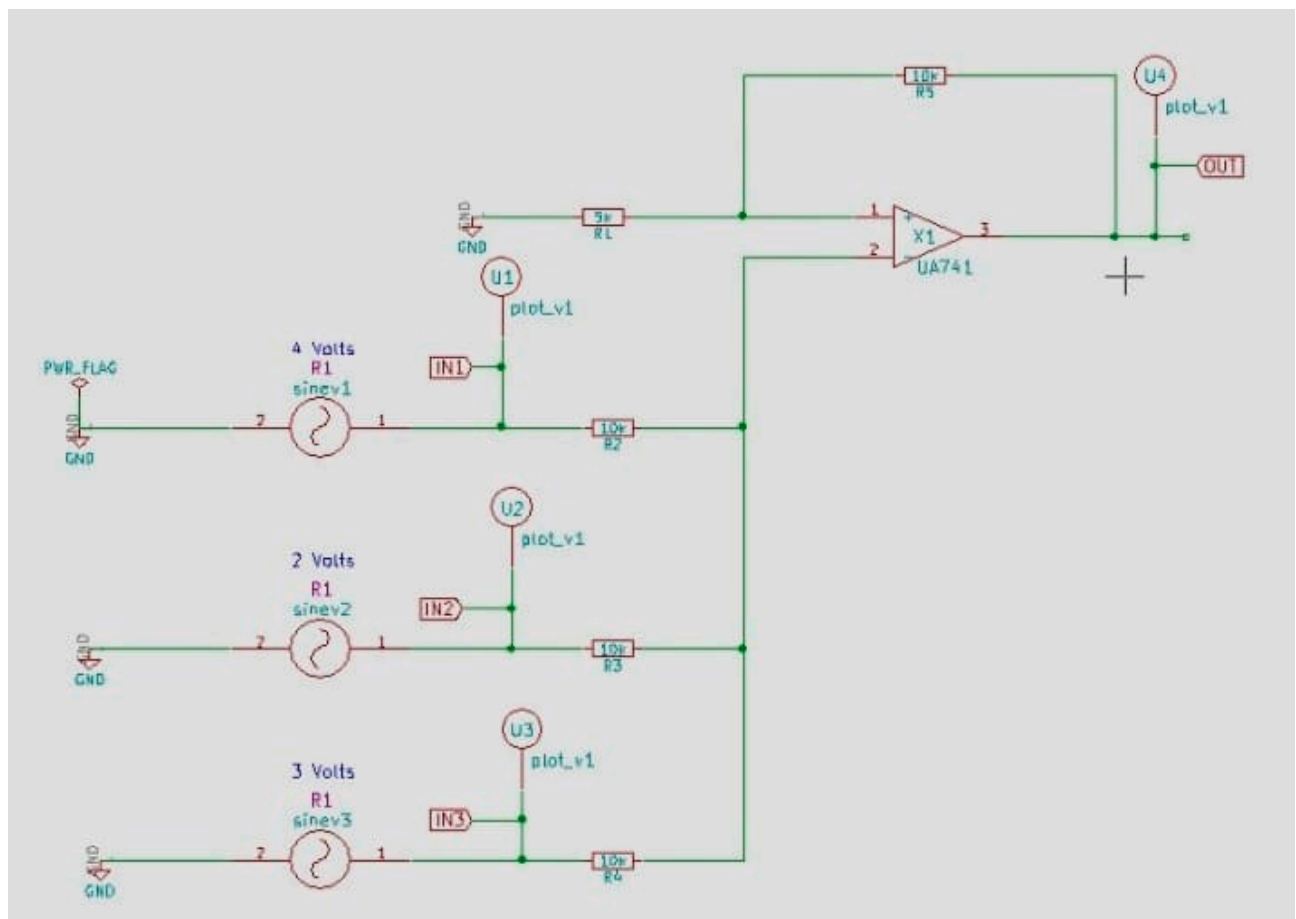


SIMULATION RESULTS:


Ngspice Plots-

Input Voltages

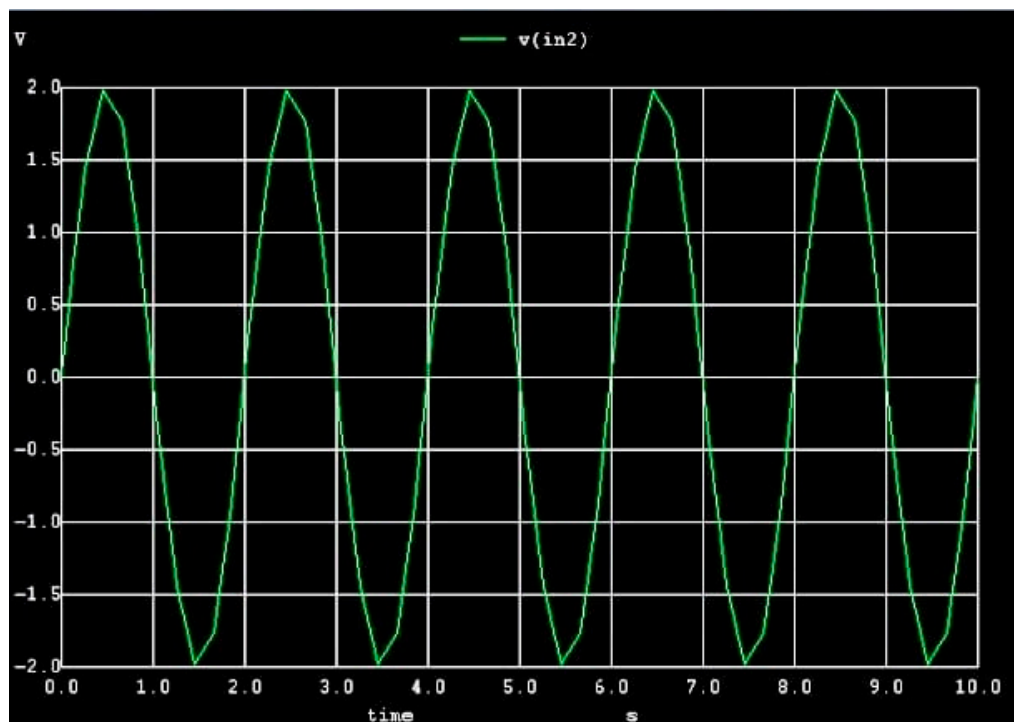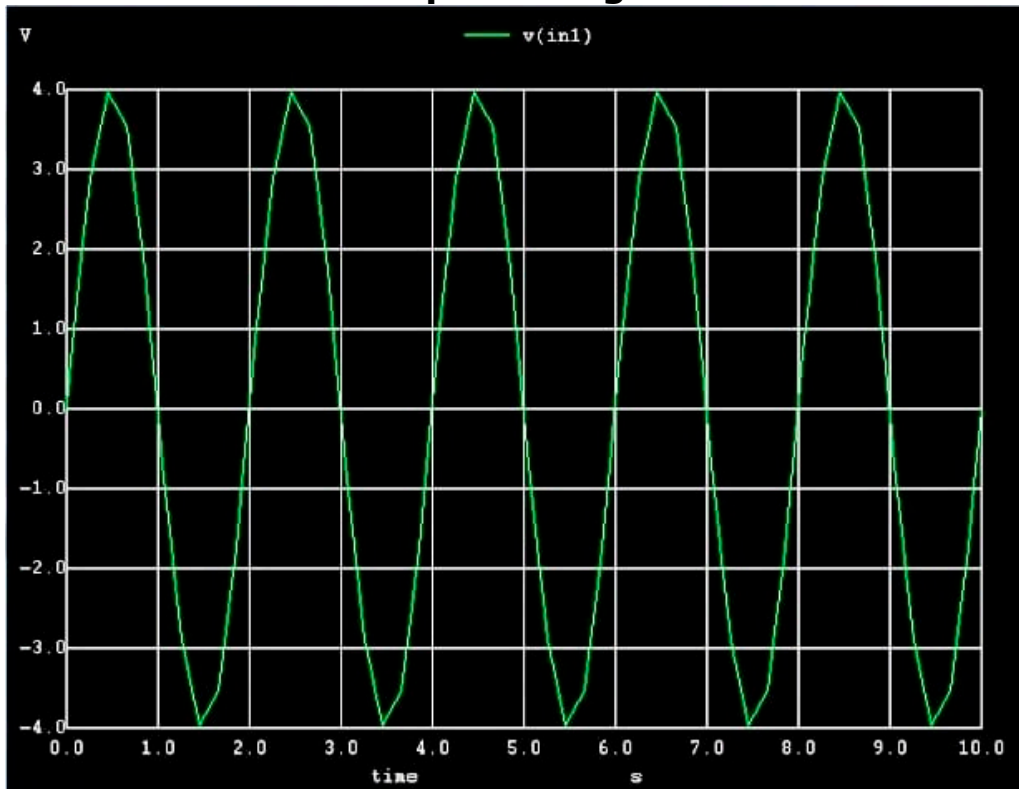


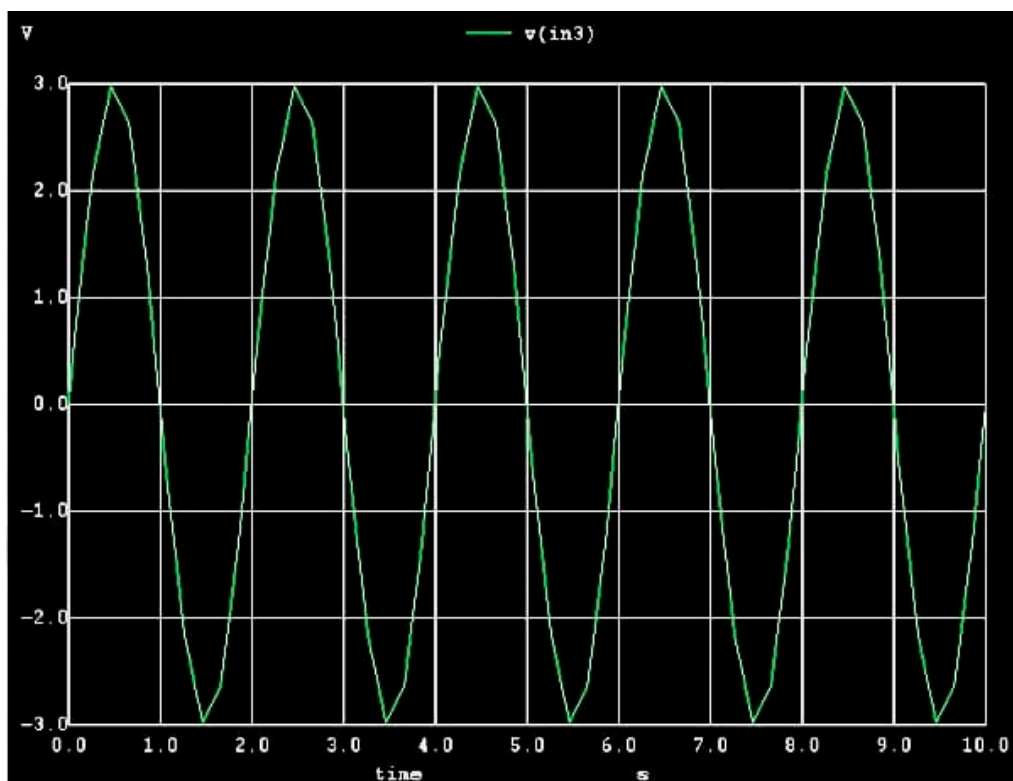



Output Voltage

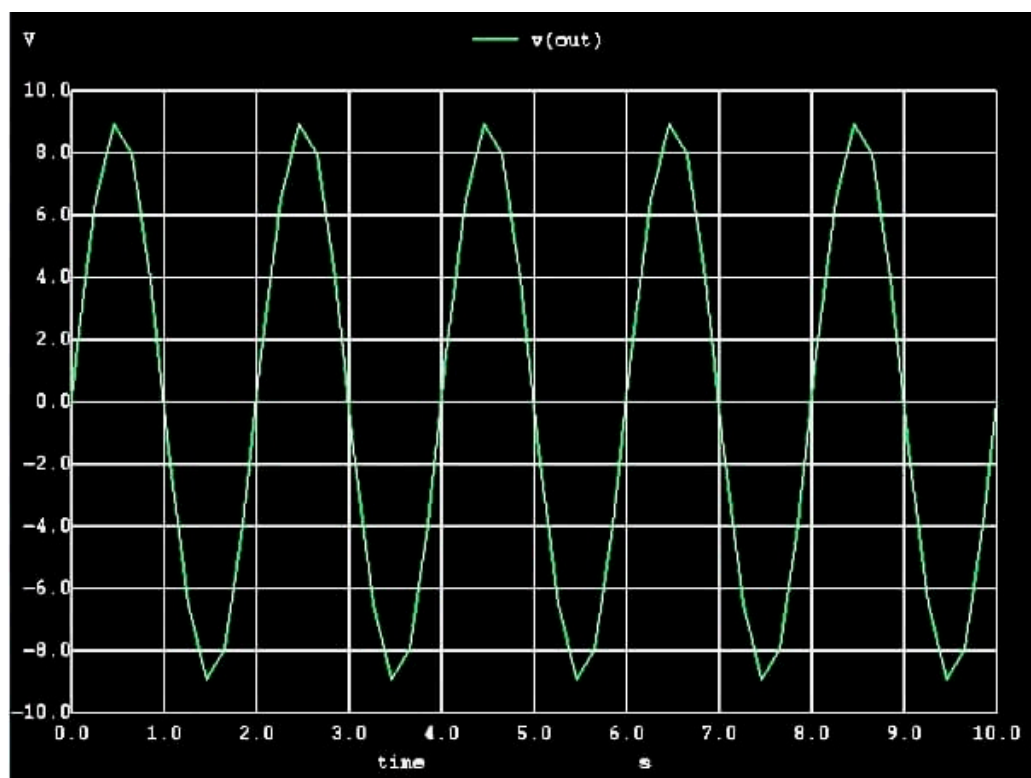


Python plots:

Input plots

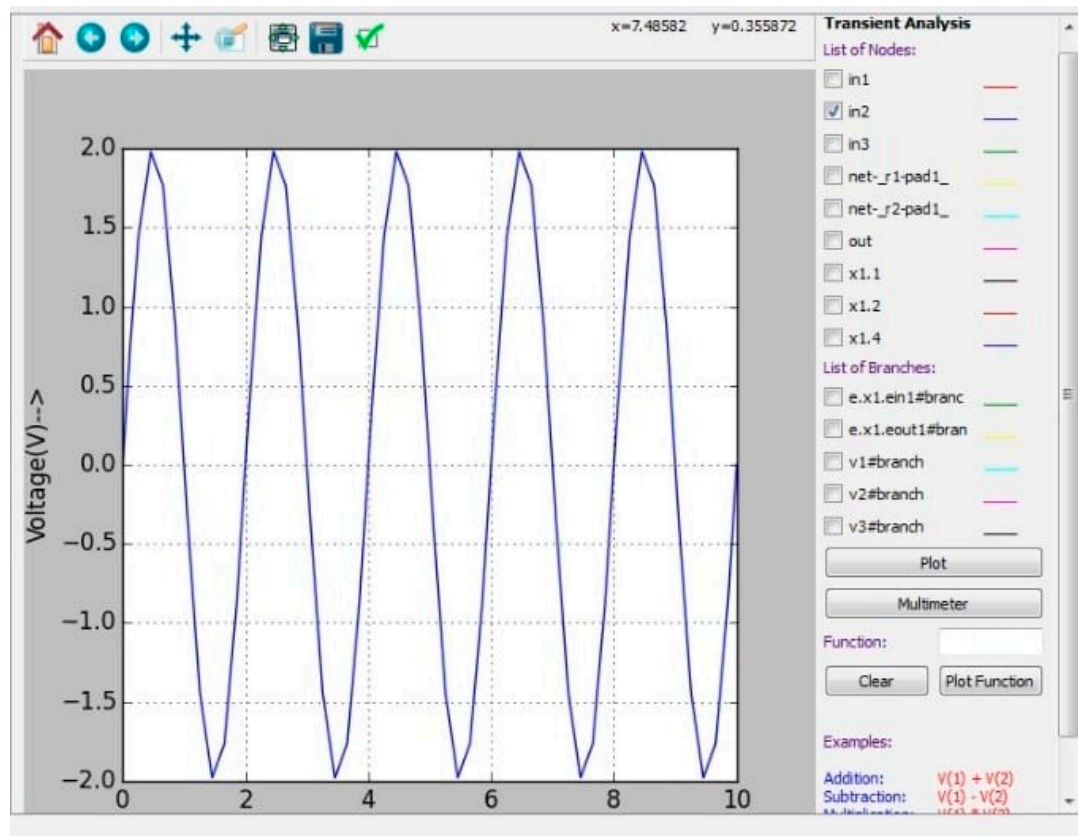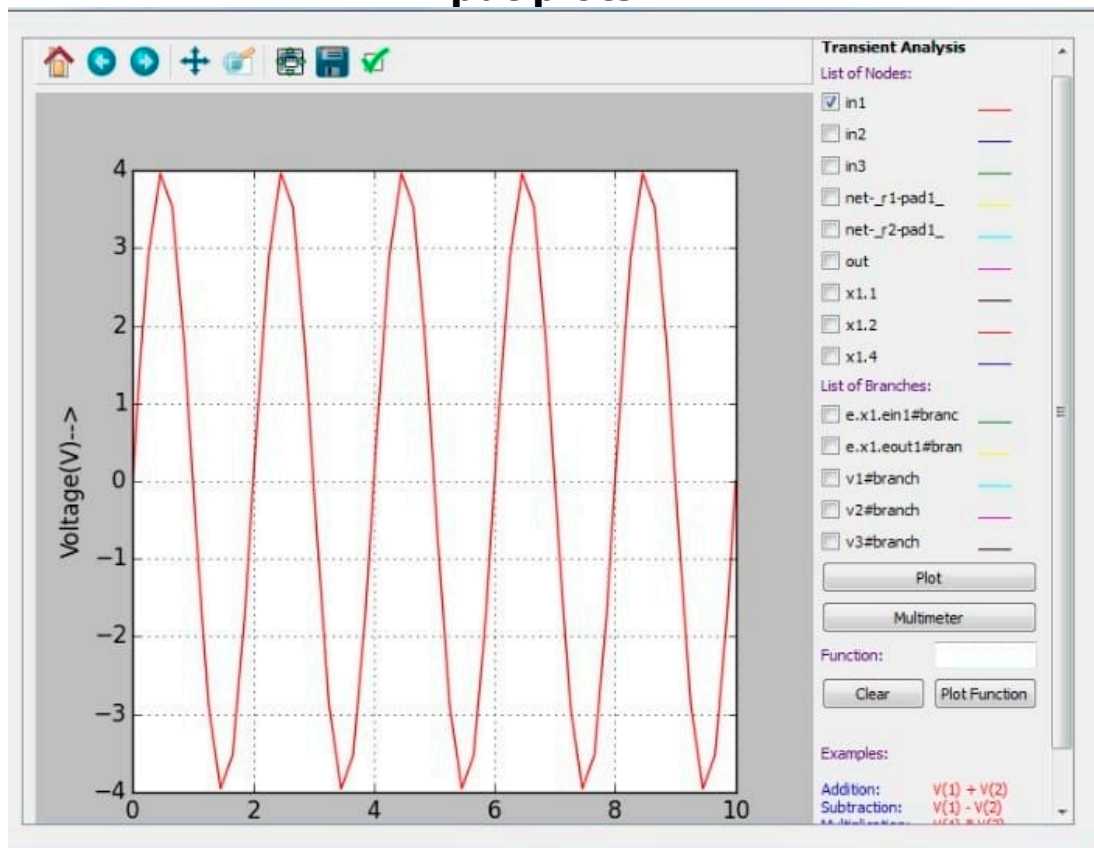


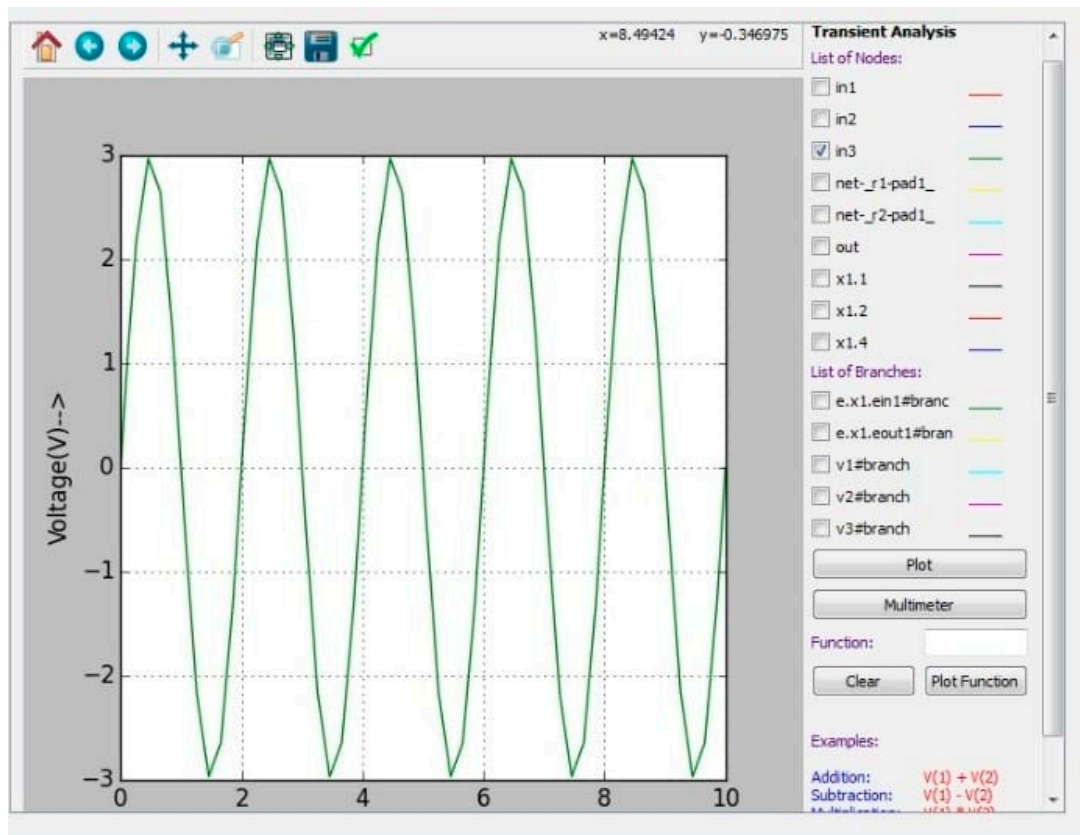

Output plot

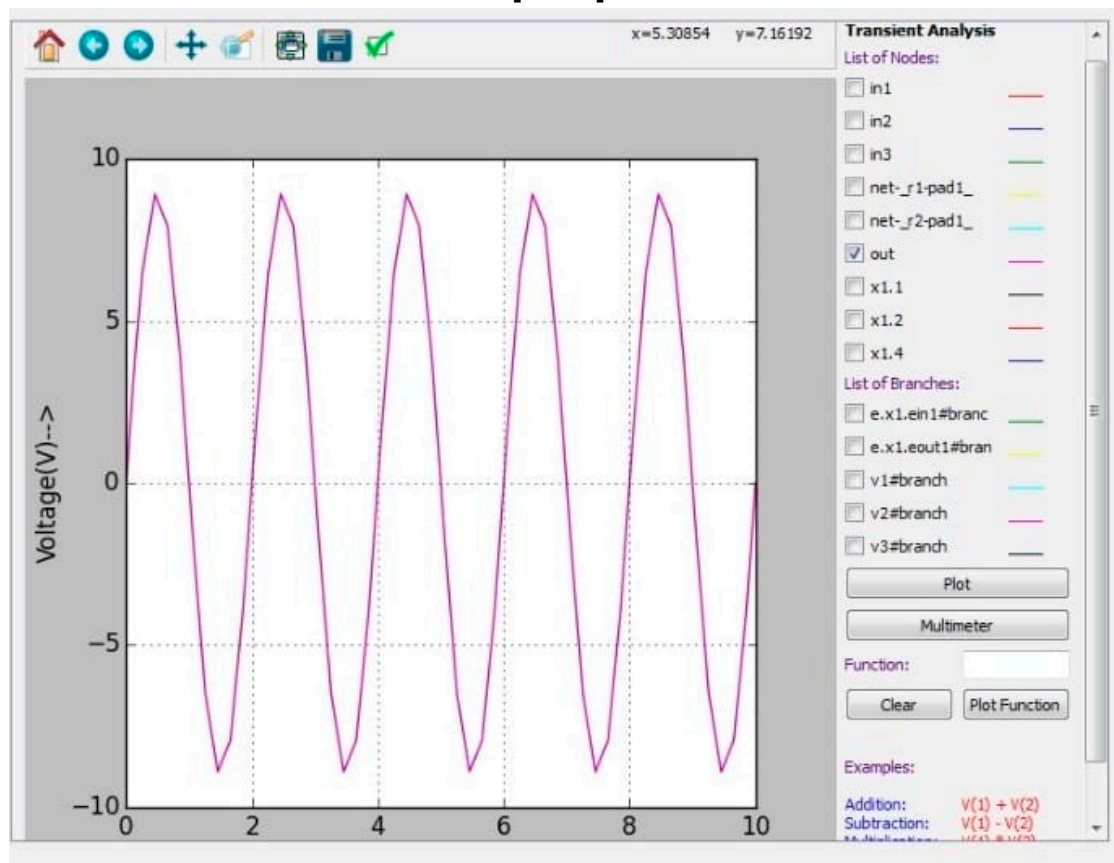

Input and Output voltage Plot

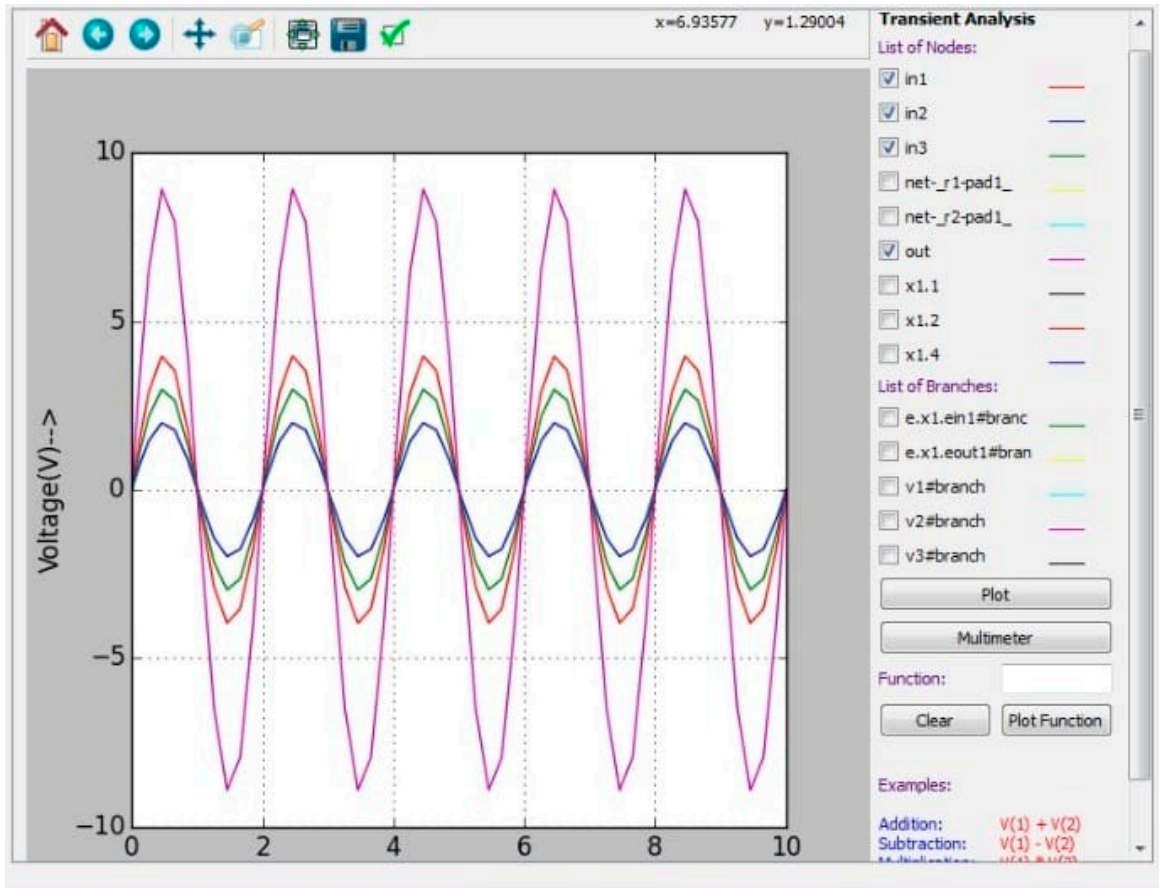

CONCLUSION:

Hence, we have designed a Non-Inverting Summer and plotted the input and output waveforms using esim.

REFERENCES:

<https://www.electronicshub.org/summing-amplifier/>