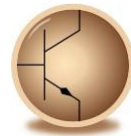




# VIT<sup>®</sup>

**Vellore Institute of Technology**

(Deemed to be University under section 3 of UGC Act, 1956)



## Circuit Simulation

### Project

<https://esim.fossee.in/circuit-simulation-project>

Name of the participant :- Krishna Kumar

Project Guide :- Dr. Maheswari.R


Institute :- Vellore Institute of Technology, Chennai

### **Topic :- 1X4 DEMULTIPLEXER**

**Theory :- De-Multiplexer** is a combinational circuit that performs the reverse operation of Multiplexer. It has single input, 'n' selection lines and maximum of  $2^n$  outputs. The input will be connected to one of these outputs based on the values of selection lines.

Since there are 'n' selection lines, there will be  $2^n$  possible combinations of zeros and ones. So, each combination can select only one output. De-Multiplexer is also called as **De-Mux**.

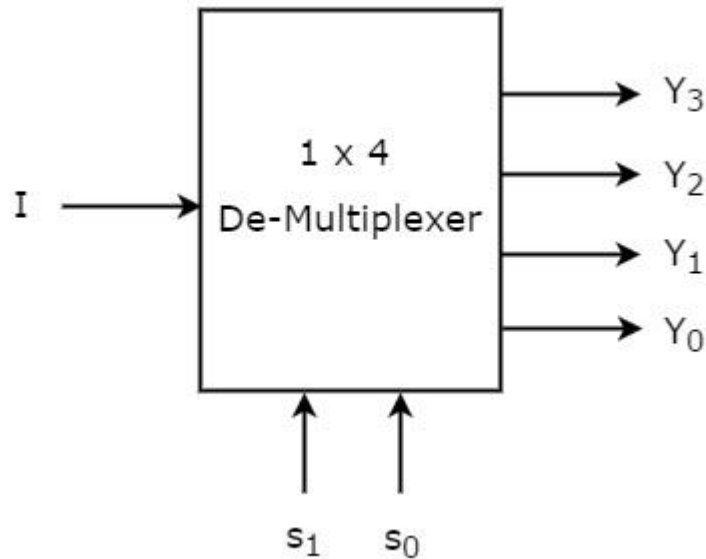1x4 De-Multiplexer has one input I, two selection lines, s1 & s0 and four outputs Y3, Y2, Y1 & Y0. The **block diagram** of 1x4 De-Multiplexer is shown in the following figure.



The single input 'I' will be connected to one of the four outputs, Y3 to Y0 based on the values of selection lines s1 & s0. The **Truth table** of 1x4 De-Multiplexer is shown below.

Selection Inputs		Outputs			
S <sub>1</sub>	S <sub>0</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

From the above Truth table, we can directly write the **Boolean functions** for each output as


$$Y_3 = s_1 s_0 I$$

$$Y_2 = s_1 s_0' I$$


$$Y_1 = s_1' s_0 I$$

$$Y_0 = s_1' s_0' I$$

**Circuit Diagram**

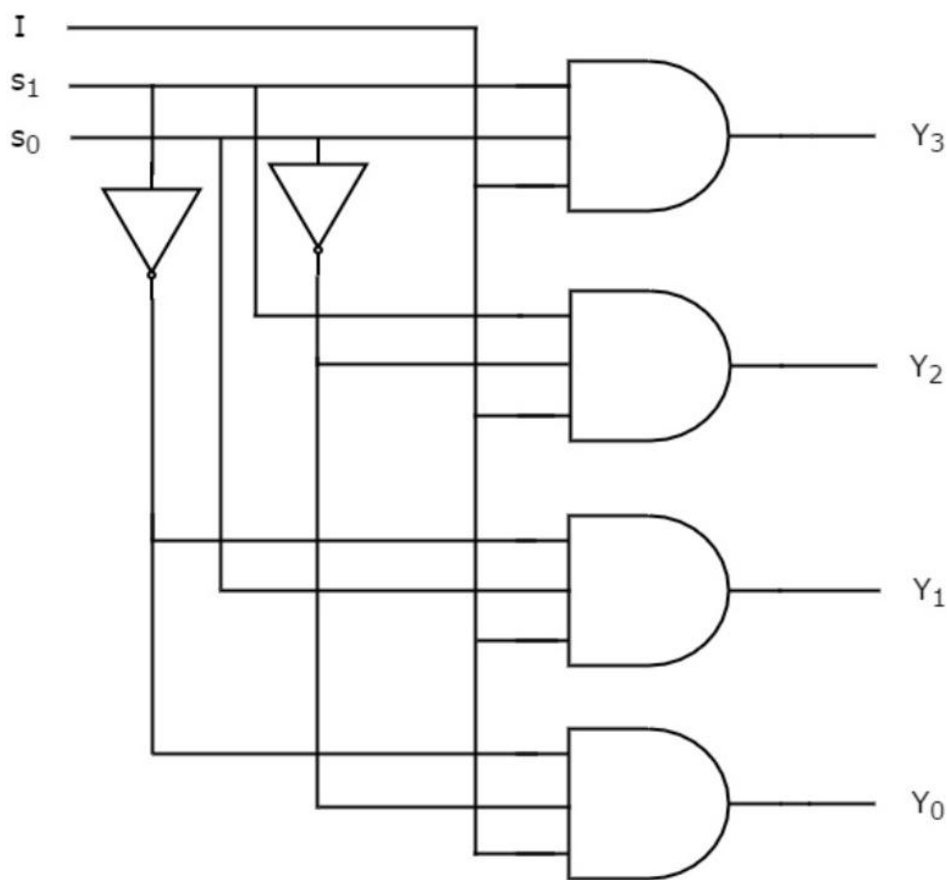


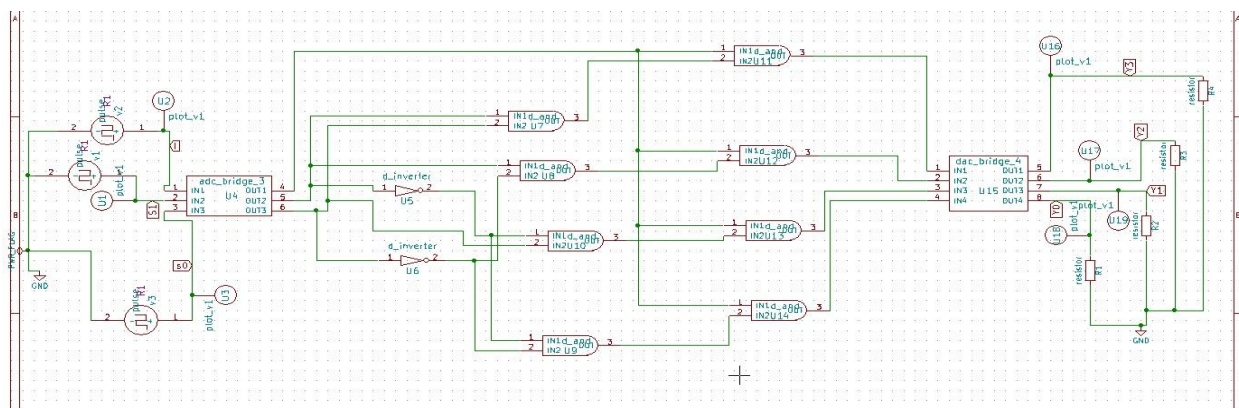**Schematic Diagram (ESim Implementation)**




## Simulation Plots :-


1) I

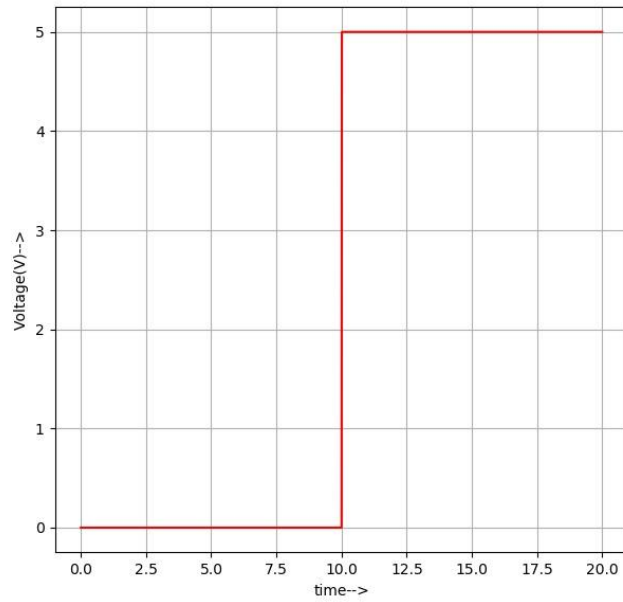


2) So

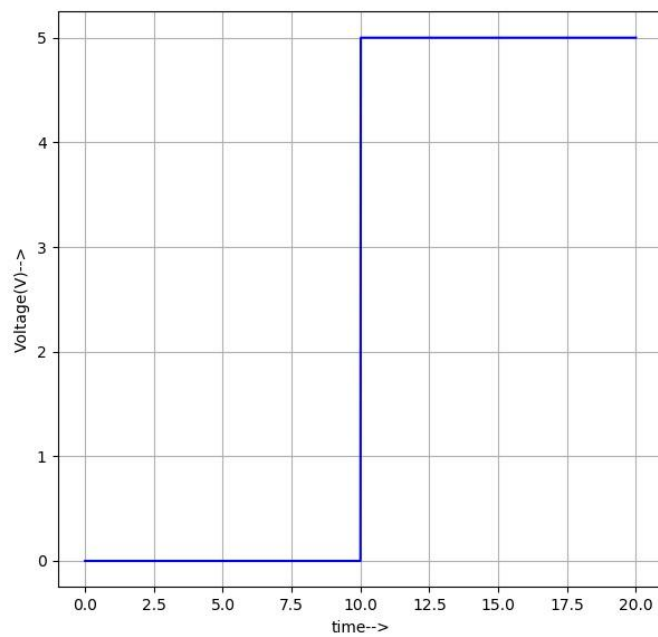


3) S1

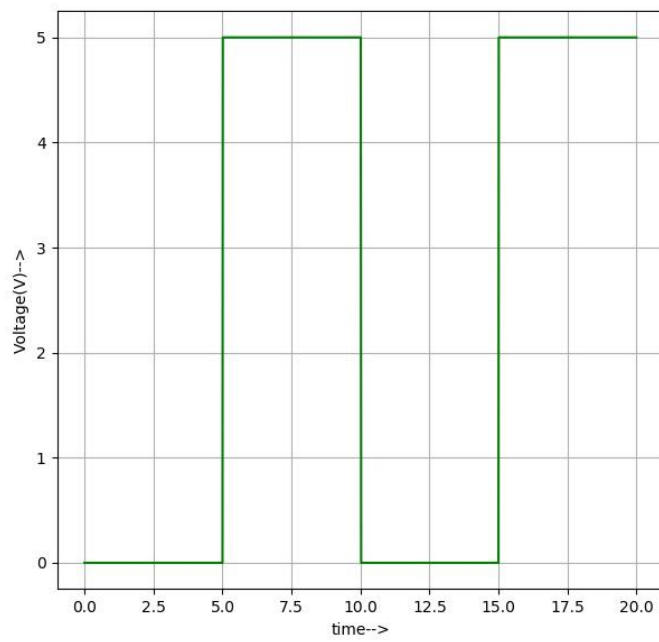


4) Y0

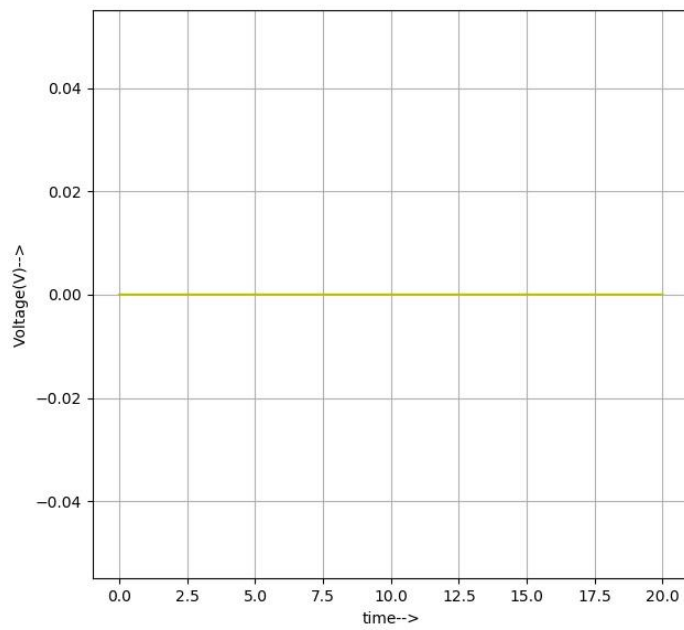


5) Y1

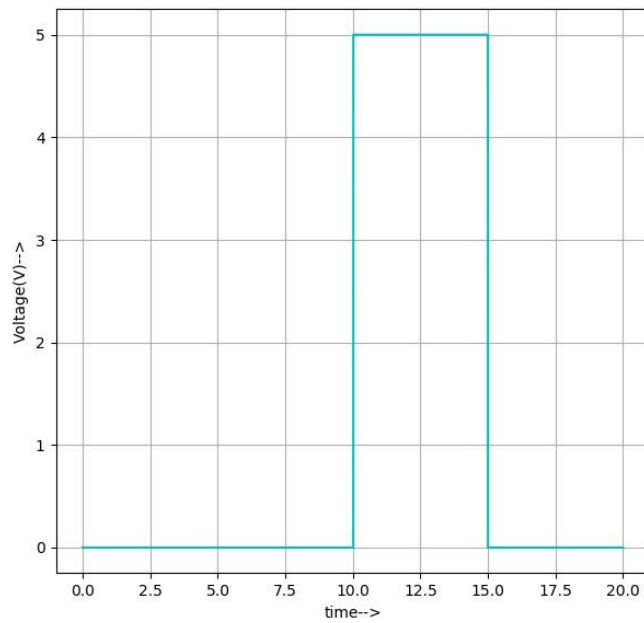

6) Y2

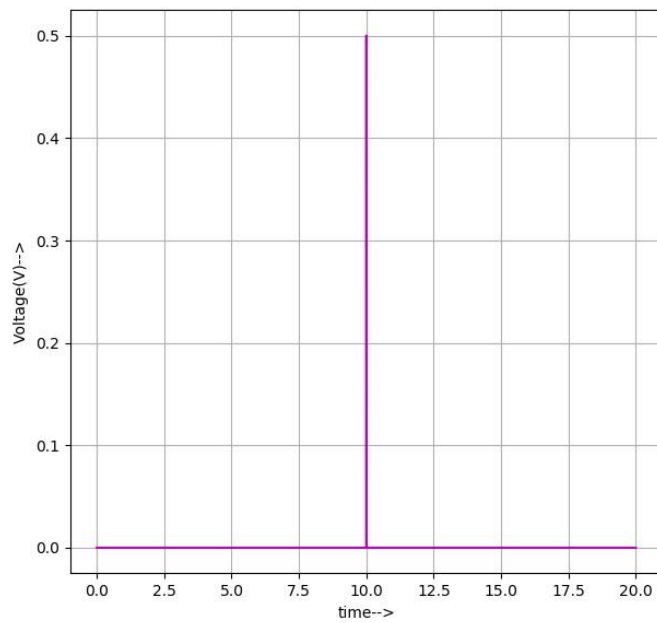

## 7) Y3

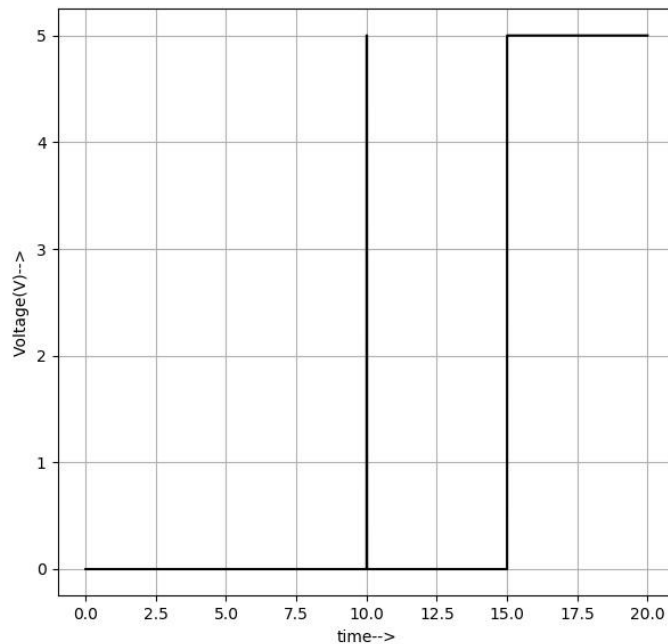

**Conclusion:** Using the circuit simulated, we have studied the logic and output of 1X4 Demultiplexer circuit. The results simulated follow the truth table, thus validating the correctness of the circuit simulated.

## **References:**

[https://www.tutorialspoint.com/digital\\_circuits/digital\\_circuits\\_demultiplexers.htm](https://www.tutorialspoint.com/digital_circuits/digital_circuits_demultiplexers.htm)