

Title of the Experiment:

Construction and working of a Full Adder using 3x8 decoder.

Theory:

A full adder circuit takes three inputs and gives two outputs. It provides the sum and carry and is implemented using a 3x8 decoder in our circuit.

We give our 3 pulse inputs to the 3x8 decoder. We came to the conclusion that


$$\text{Sum} = \Sigma m(1, 2, 4, 7)$$

$$\text{Carry} = \Sigma m(3, 5, 6, 7)$$


Our final sum will be the OR operation of 2nd, 3rd, 5th and 8th output of our decoder and final carry will be the OR operation of 4th, 6th, 7th and 8th output of the decoder.

Schematic Diagram:




3x8 decoder schematic:


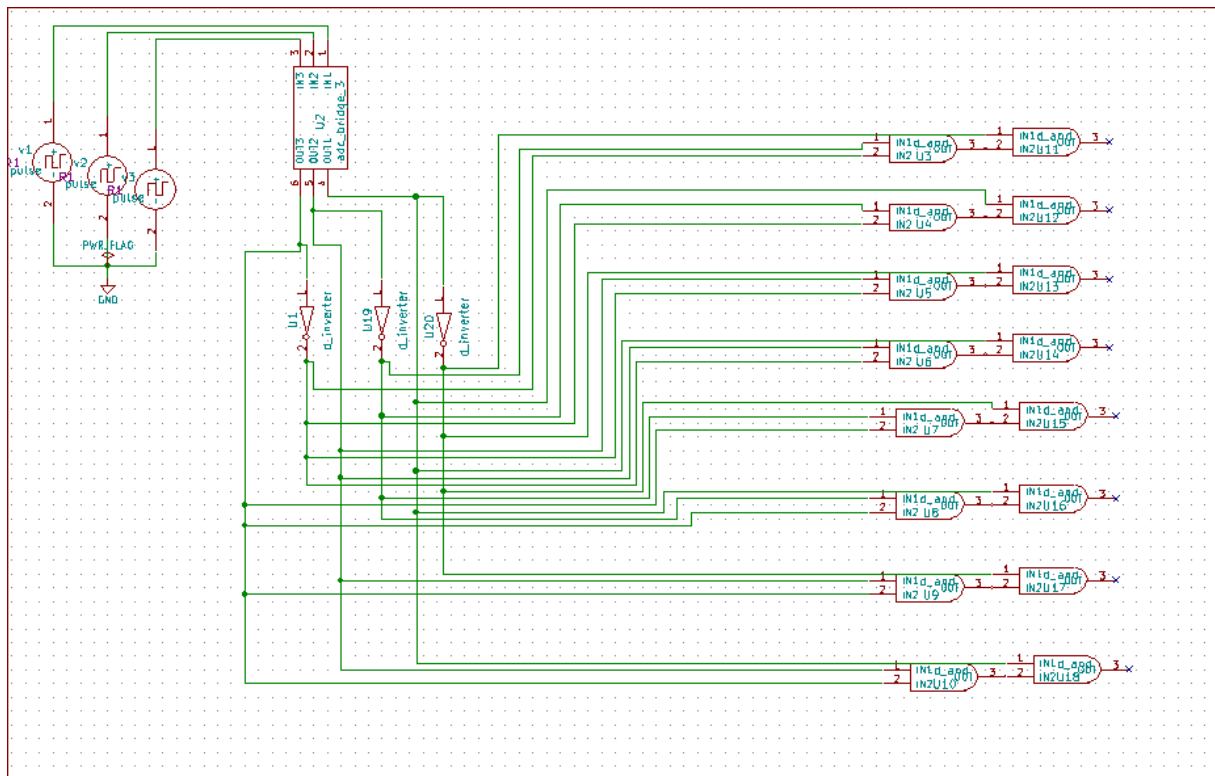


Full adder using 3x8 decoder:

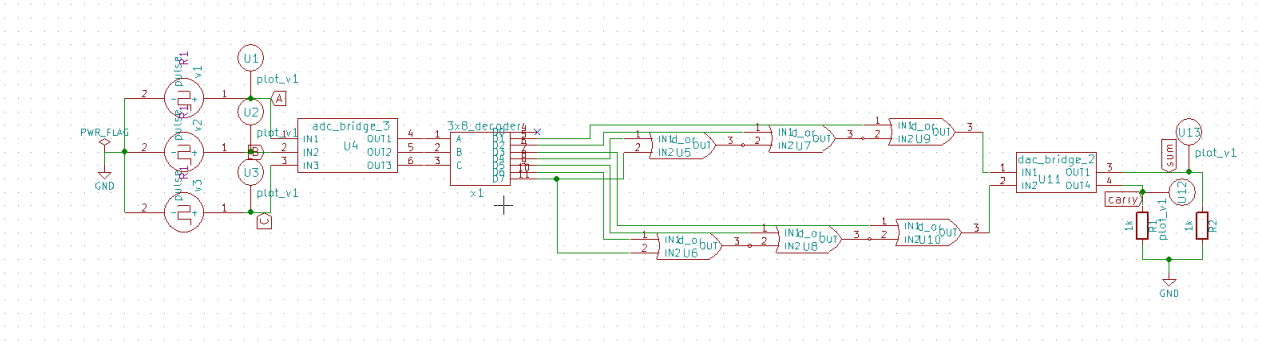

Python plots:

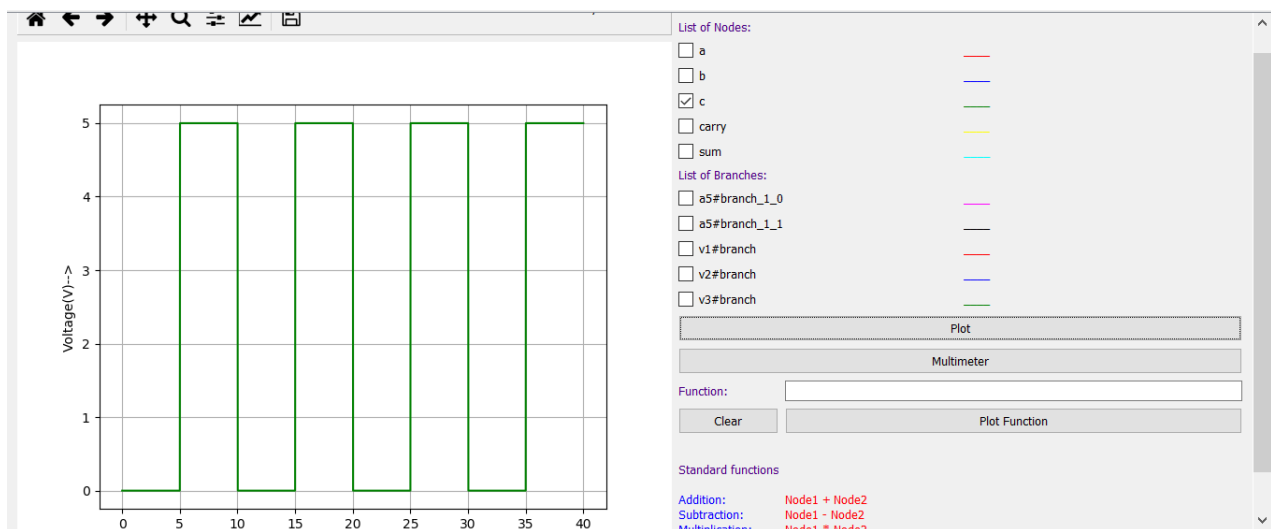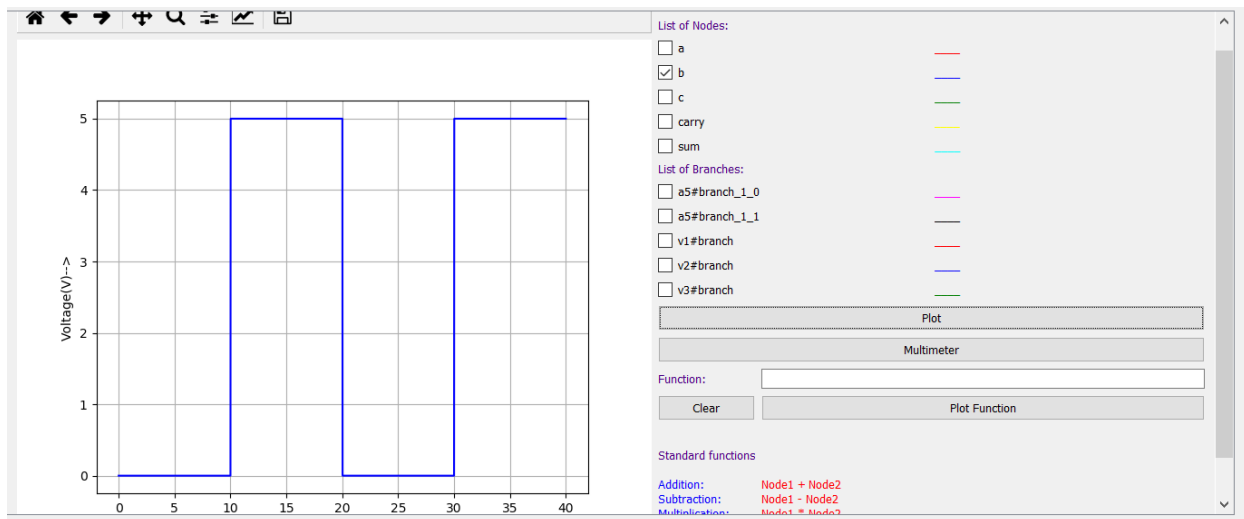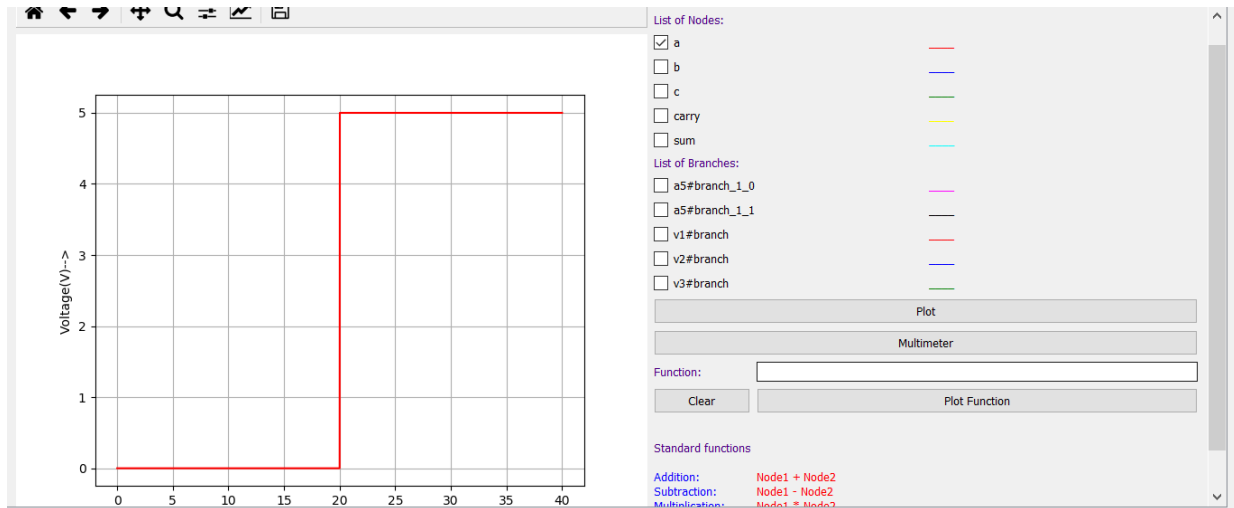

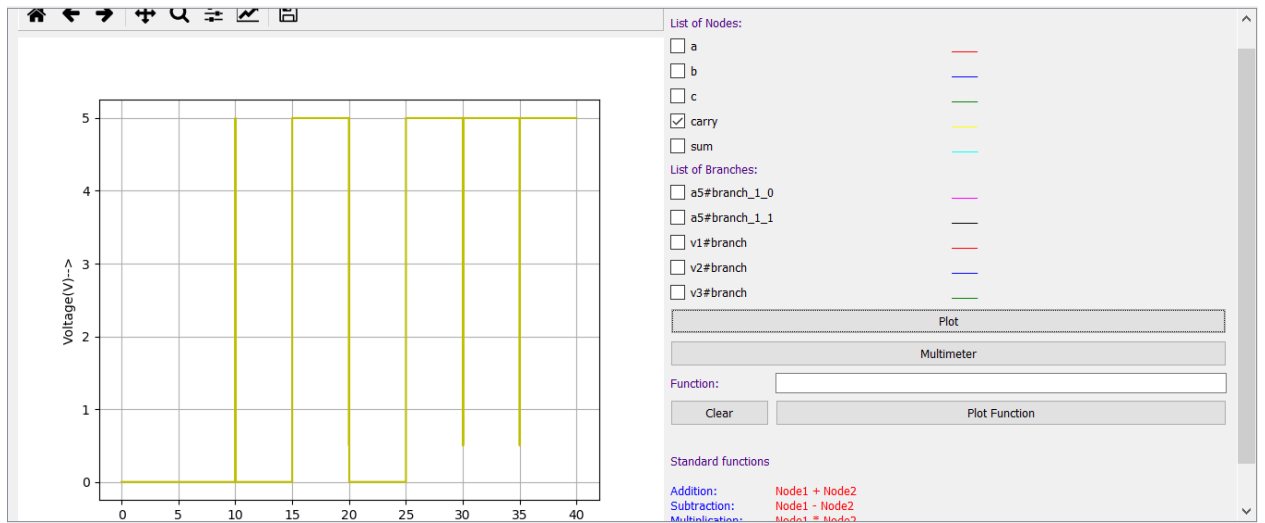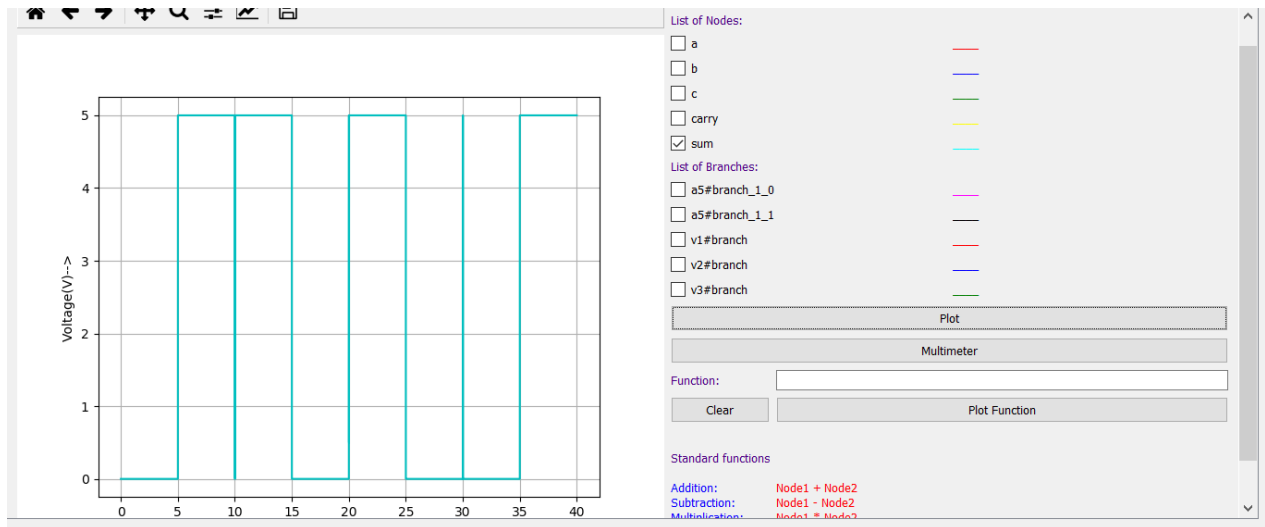

References:

<https://www.deldsim.com/study/material/51/full-adder-function-using-38-decoder/>