



Circuit Simulation Project

<https://esim.fossee.in/circuit-simulation-project>

Name of the Participant: Shubhangi Agrawal (20BCE1161)

Project Guide: Dr R. Maheshwari

Title of the Circuit: Implementation of AND gate using NOR gates

Theory:

An AND gate gives a 1 output when both inputs are 1. Therefore, an AND gate is made by inverting the inputs of a NOR gate. Again, note that a NOT gate is equivalent to a NOR with its inputs joined.

From De Morgan's theorems: $(A+B)' = A'B' \Rightarrow (A'+B')' = A''B'' = AB$

So, give the inverted inputs to a NOR gate, obtain AND operation at output


CIRCUIT DIAGRAM:

Desired AND Gate



$$Q = A \text{ AND } B$$

NOR Construction

 


$$= (A \text{ NOR } A) \text{ NOR } (B \text{ NOR } B)$$

Truth Table:

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	0
1	0	0
1	1	1


e-Sim Schematic:

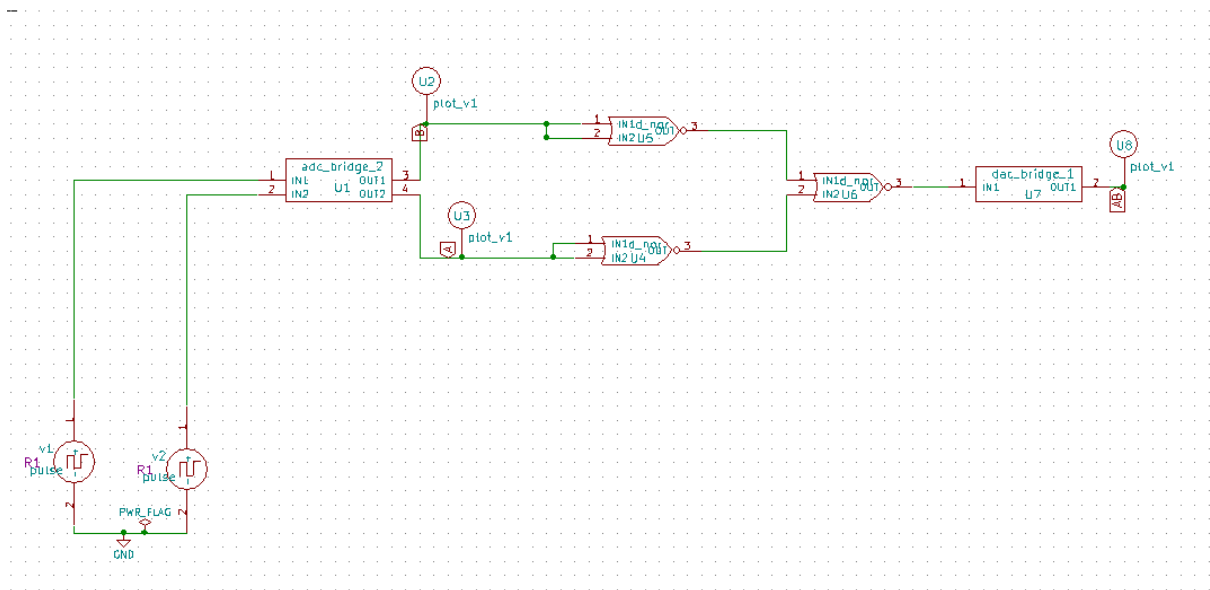


Simulation Results:

1. Python Waveforms:


A

 

B

 


A.B

 


NG Spice Waveforms:


A

 

B

 

A.B

 

Transient Analysis:

Select Analysis Type

☐ AC☐ DC☒ TRANSIENT

Transient Analysis

Start Time

0

Sec

Step Time

20

ms

Stop Time

20

Sec

Analysis	Source Details	Ngspice Model	Device Modeling	Subcircuits
Enter delay time (seconds):				10
Enter rise time (seconds):				0
Enter fall time (seconds):				0
Enter pulse width (seconds):				20
Enter period (seconds):				40
Add parameters for pulse source v2				
Enter initial value(Volts/Amps):				0
Enter pulsed value(Volts/Amps):				5
Enter delay time (seconds):				5
Enter rise time (seconds):				0
Enter fall time (seconds):				0
Enter pulse width (seconds):				10
Enter period (seconds):				20

Conclusion:

Thus, the circuit has been designed and verified.

References:

<https://www.iitr.ac.in/departments/PH/uploads/Teaching%20Laboratory/Electronics/5.Interconversion%20of%20Universal%20Gates%20and%20De%20Morgans%20Theorem.pdf>

https://en.wikipedia.org/wiki/NOR_logic