

SAFETY BUZZER IN A CAR

(WITH THE HELP OF 3 FACTORS DOOR, SEAT BELT AND KEY)

THEORY/DESCRIPTION :

The following is a review of the design and operation of a combinational logic circuit using AOI logic. This design controls the safety buzzer in a car and is designed to the following specifications:

The buzzer is ON whenever the door is open OR the key is in the ignition AND the seat belt is NOT buckled.

TRUTH TABLE :

Car Buzzer – Truth Table			
Seat Belt	Key	Door	Buzzer
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Seat Belt	{	0 : Seat Belt is NOT Buckled 1 : Seat Belt is Buckled
Key	{	0 : Key is NOT in the Ignition 1 : Key is in the Ignition
Door	{	0 : Door is NOT Open 1 : Door is Open
Buzzer	{	0 : Buzzer is OFF 1 : Buzzer is ON

Now according to the truth table our logical equation for buzzer becomes,
(A= seat belt, B= key, c= door)

$$\overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}C + ABC$$

We will try to minimize it,

Start

$$\overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}C + ABC$$

Apply the Distributive Law: $AB+AC = A(B+C)$

$$\overline{A}C(\overline{B}+B) + \overline{A}B\overline{C} + A\overline{B}C + ABC$$

Apply the Complement Law: $A+\overline{A} = 1$

$$\overline{A}C1 + \overline{A}B\overline{C} + A\overline{B}C + ABC$$

Apply the Identity Law: $A1 = A$

$$\overline{A}C + \overline{A}B\overline{C} + A\overline{B}C + ABC$$

Apply the Distributive Law: $AB+AC = A(B+C)$

$$\overline{A}(B\overline{C}+C) + A\overline{B}C + ABC$$

Apply the Distributive Law: $AB+AC = A(B+C)$

$$\overline{A}(B+C)+AC(\overline{B}+B)$$

Apply the Complement Law: $A+\overline{A} = 1$

$$\overline{A}(B+C)+AC1$$

Apply the Identity Law: $A1 = A$

$$\overline{A}(B+C)+AC$$

Apply: Distribution

$$\overline{A}B+\overline{A}C+AC$$

Apply the Distributive Law: $AB+AC = A(B+C)$

$$\overline{A}B+C(\overline{A}+A)$$

Apply the Complement Law: $A+\overline{A} = 1$

$$\overline{A}B+C1$$


Apply the Identity Law: $A1 = A$

$$\overline{A}B+C$$

Hence ,

Buzzer= seat_belt.key + door

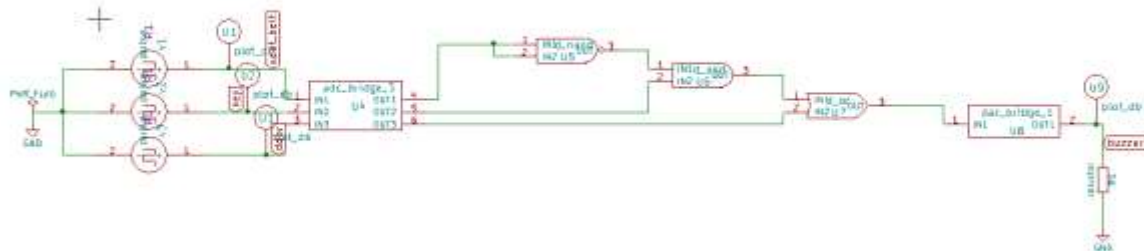
E-SIM CIRCUIT DIAGRAM WITH APPROPRIATE RESULT :




****instead of not gate nand is used as not.**

1.for seat_belt

a.ngspice

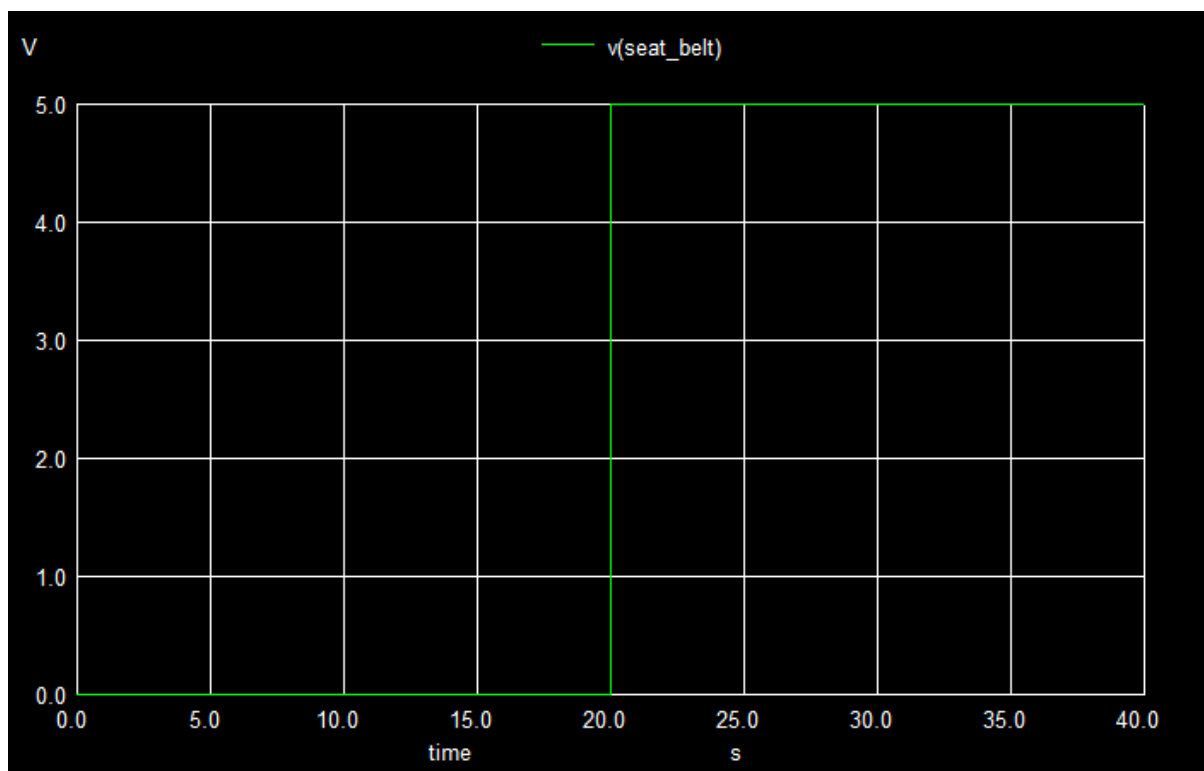


b.python plot

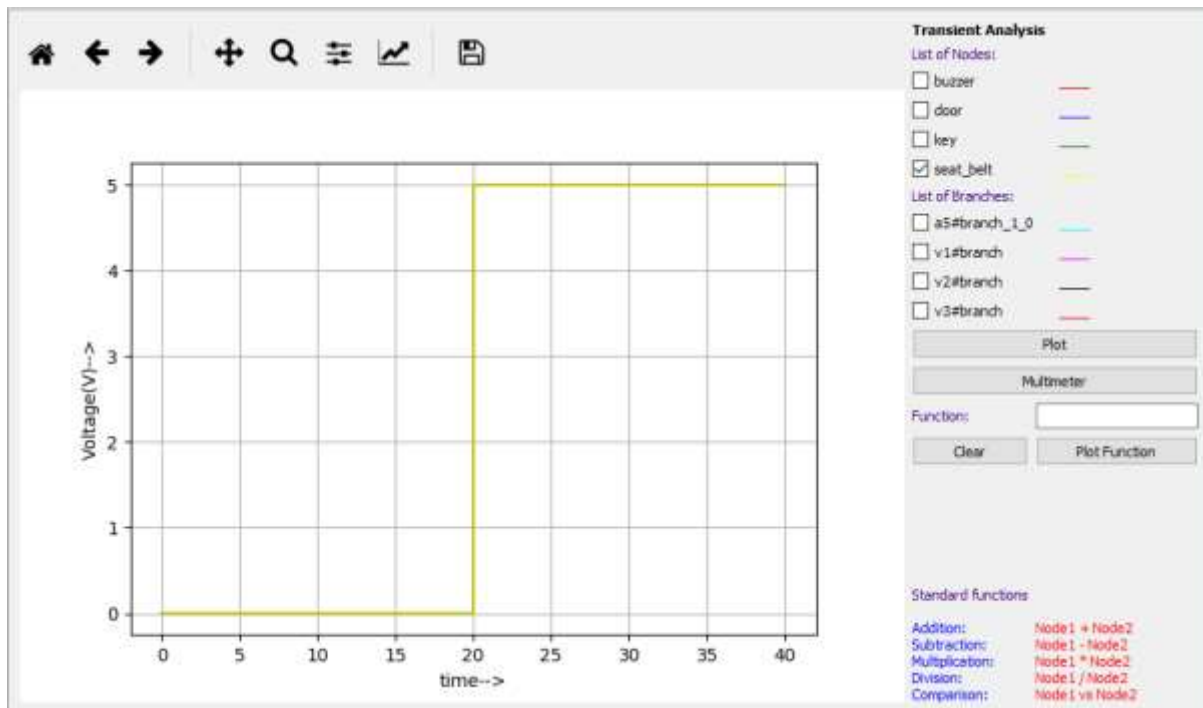


2.for key ignition

a.ngspice

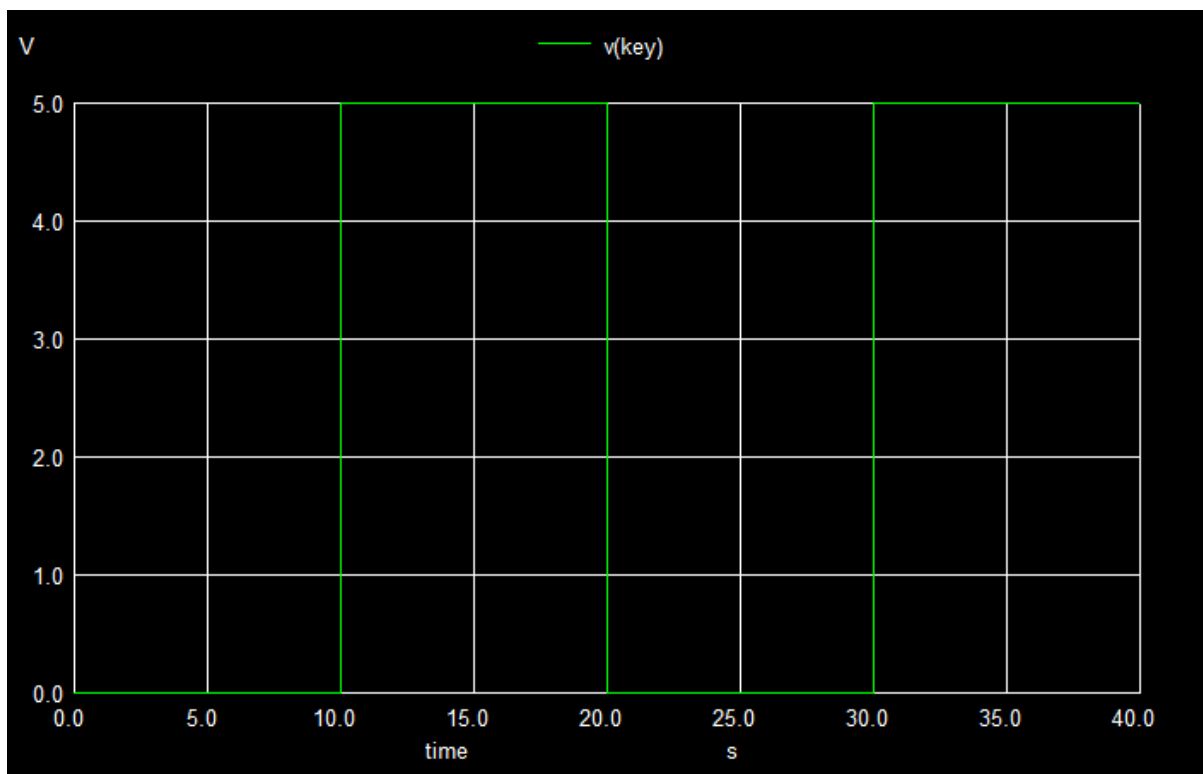


b.python plot

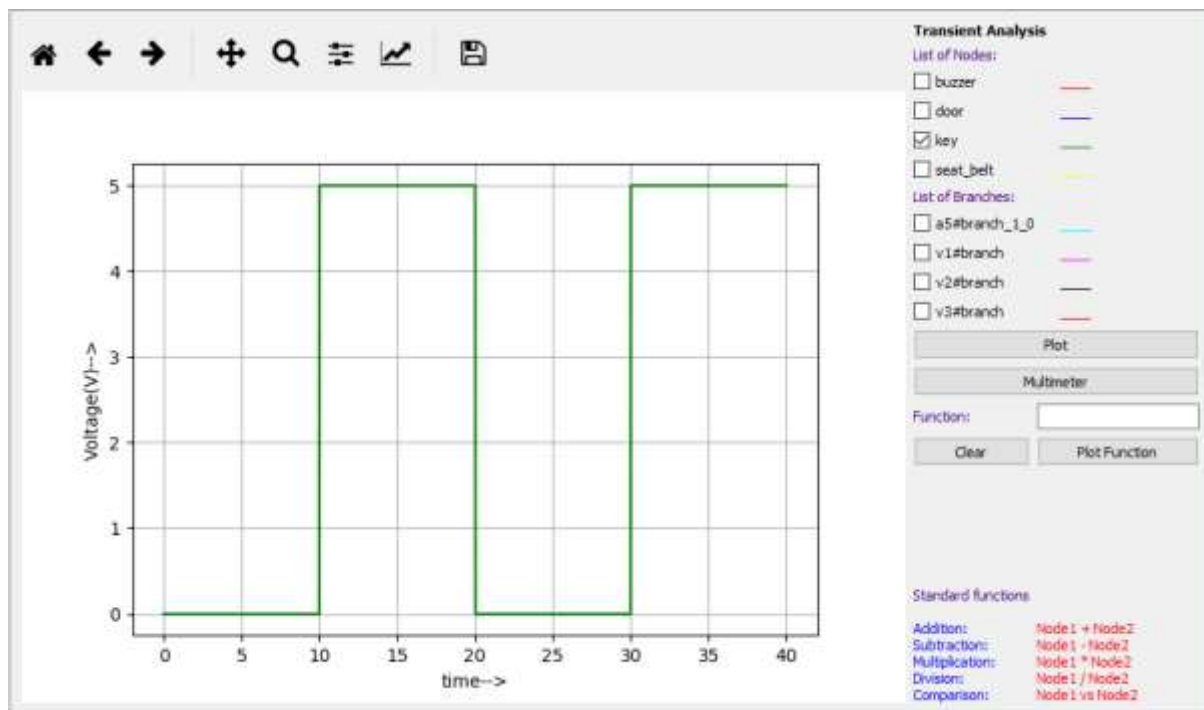


3.for door

a.ngspice

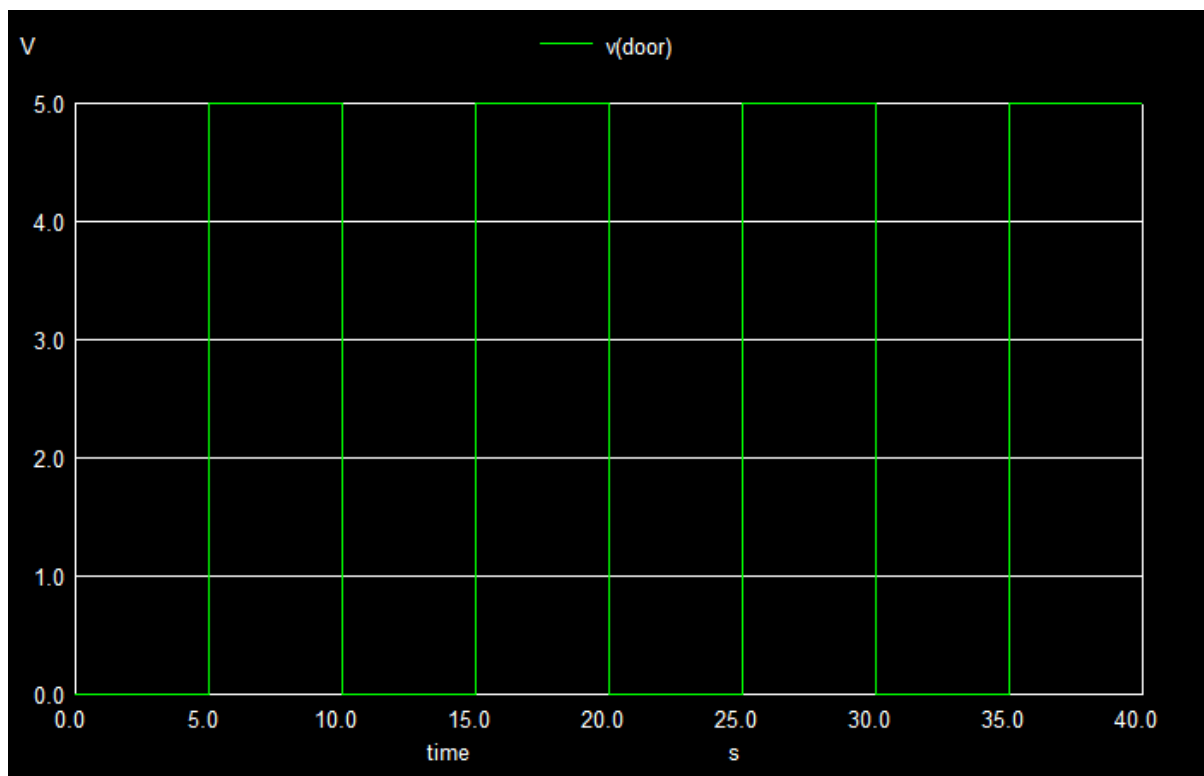


b.python plot

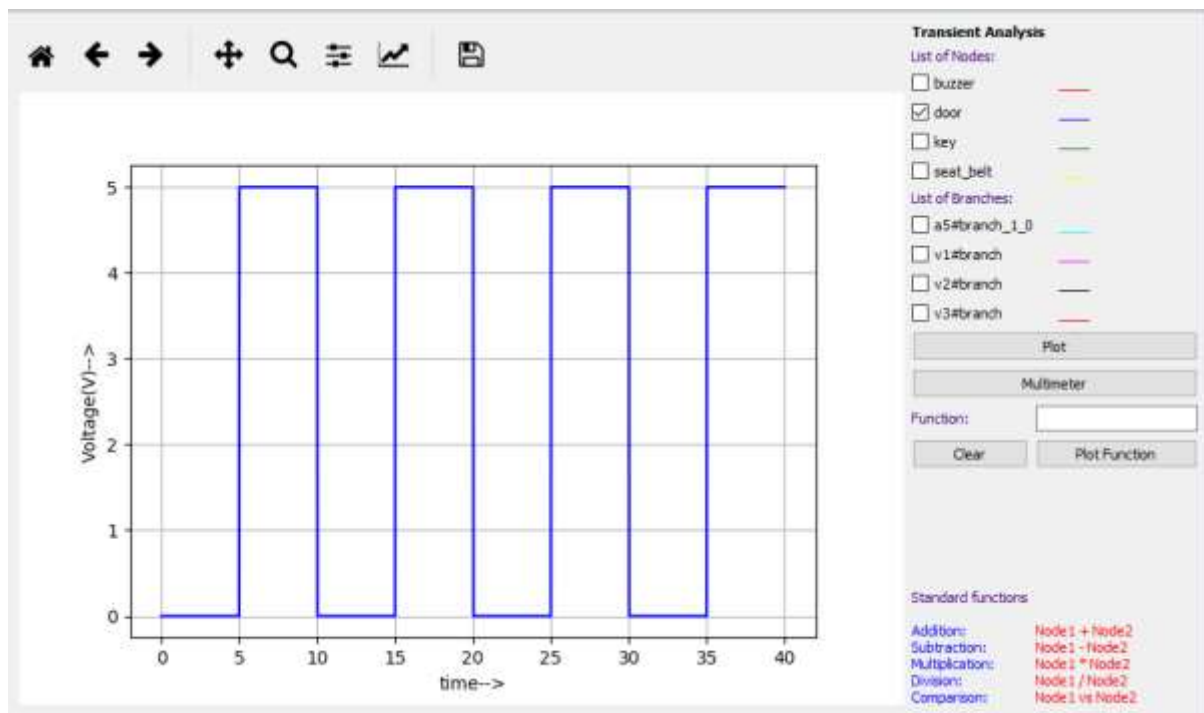


4.for buzzer

a.ngspice

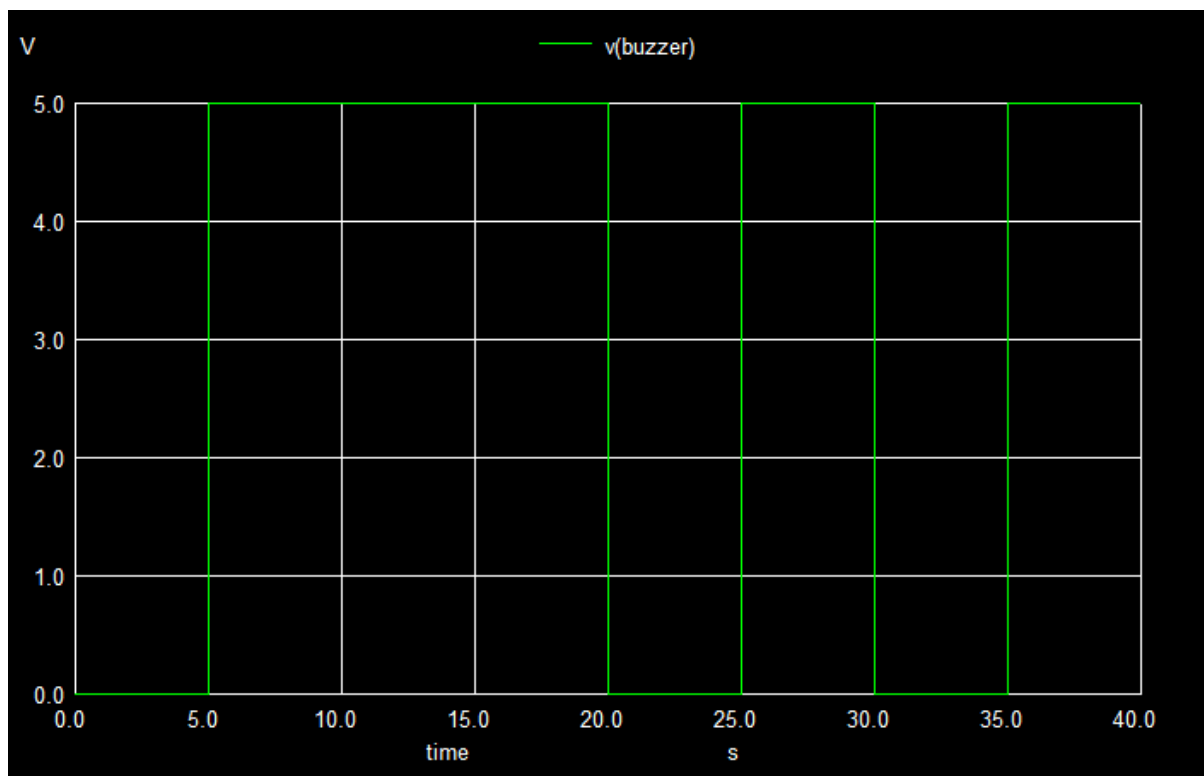

b.python plot

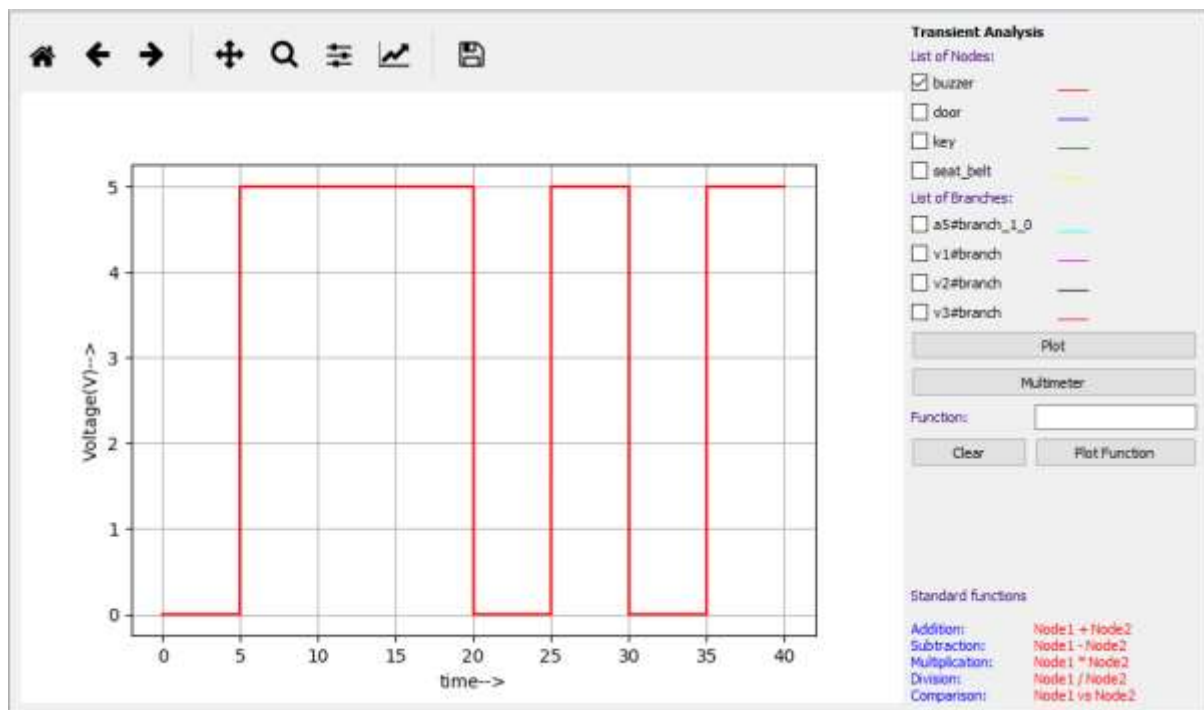

CONCLUSION :

With the help of only one and and or gate along with not gate we can logically implement such safety buzzer circuit.

REFERENCES :

<https://www.lancasterschools.org/cms/lib/NY19000266/Centricity/Domain/1055/CombinationalLogicOverview.pdf>

