



Sri Eshwar
College of Engineering
An Autonomous Institution



TITLE OF EXPERIMENT - AC VOLTAGE FOLLOWER

STUDENT NAME - MS. SREE VISHNU VARTHINI S

MENTOR - DR. MAHESWARI RAJA

COLLEGE - SRI ESHWAR COLLEGE OF ENGINEERING


ABSTRACT

An AC voltage follower, also known as a unity-gain buffer or voltage buffer, is a fundamental electronic circuit used to isolate input and output impedances while maintaining the same voltage level as the input. It essentially mimics the input voltage at its output without amplifying or attenuating it. This circuit consists of an operational amplifier (op-amp) with its non-inverting input connected directly to the input voltage source and its output connected to its inverting input through a feedback resistor.

The primary function of an AC voltage follower is impedance matching, which ensures minimal signal loss and distortion when interfacing different electronic components. It presents a high input impedance to the source and a low output impedance to the load, effectively preventing signal degradation due to impedance mismatch.

In practical applications, AC voltage followers are commonly employed in audio equipment, instrumentation, and signal conditioning circuits. They facilitate signal transmission between stages with varying impedance characteristics, ensuring fidelity and integrity of the signal throughout the system. Additionally, they serve as impedance buffers, preventing loading effects that could affect the performance of preceding stages.


CIRCUIT DIAGRAM

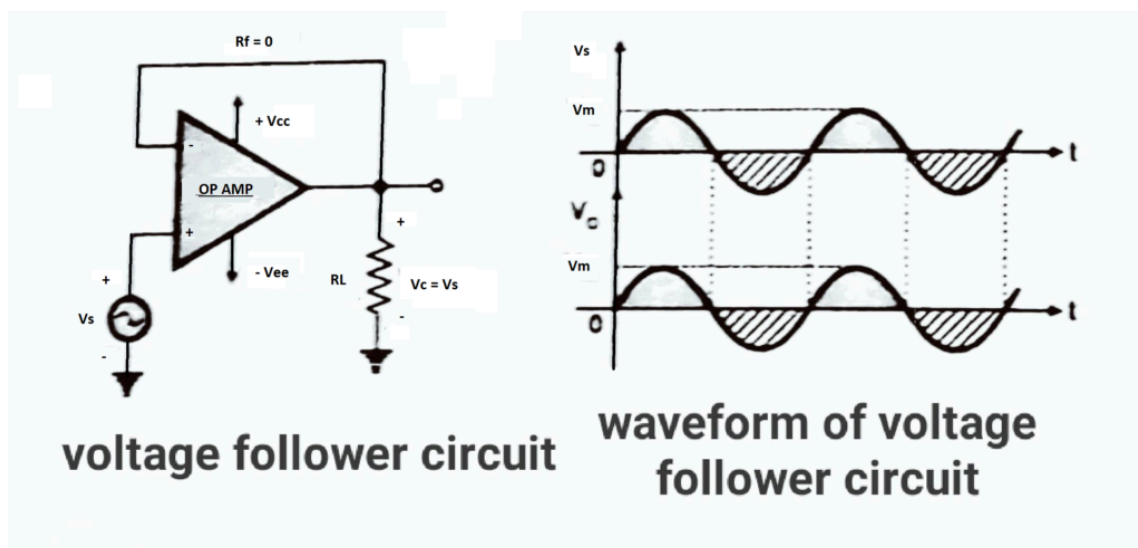

eSIM REQUIRED COMPONENTS:


COMPONENT	TYPE
LM 741	OP-AMP
V1 (VOLTAGE SOURCE 1)	AC SOURCE
V2 (VOLTAGE SOURCE 2)	DC SOURCE
RESISTOR	100k OHM
CAPACITOR	0.1uF, 0.5uF

eSIM CIRCUIT:

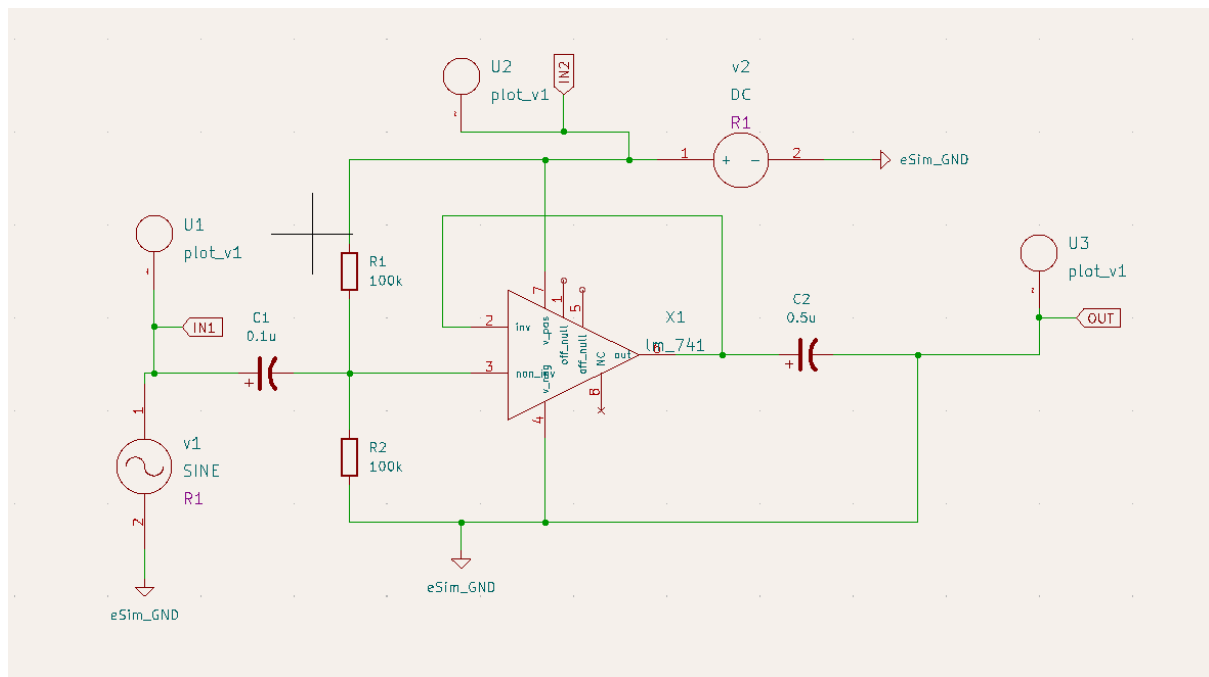


OUTPUT

INPUT WAVEFORM:

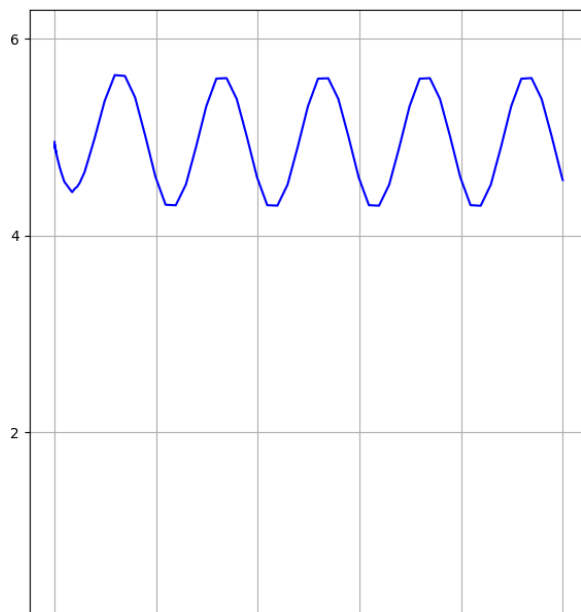

OUTPUT WAVEFORM:

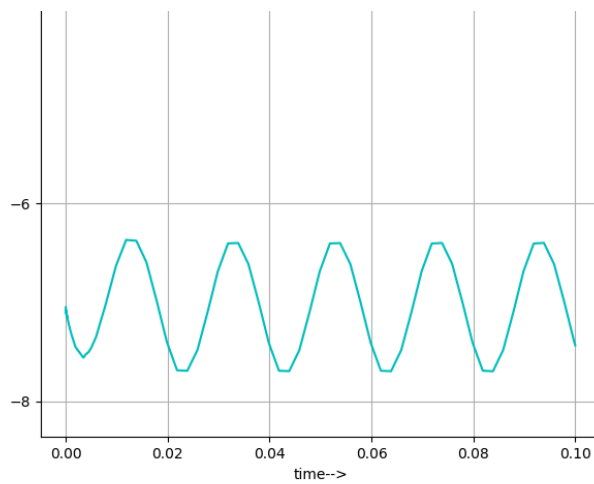

REFERENCES:

<https://hackatronic.com/opamp-voltage-follower-or-buffer-amplifier/>