

Title of the experiment:

## VOLTAGE CONVERTER TO A STABLE +5V OUTPUT USING ESIM .

### Theory:

This circuit is a Fixed Linear Voltage Regulator designed to convert a high DC input voltage into a stable +5V output. It utilizes the LM7805 IC, which employs internal current limiting, thermal shutdown, and safe-area compensation. The input capacitors (C1, C2) filter high-frequency noise and stabilize the input, while the output capacitors (C3, C4) improve the transient response and ensure a ripple-free DC output. A Schottky diode (D1) is included for reverse-polarity protection.

### Schematic Diagram:

The circuit schematic of the Fixed linear voltage Regulator in eSim is as shown below:

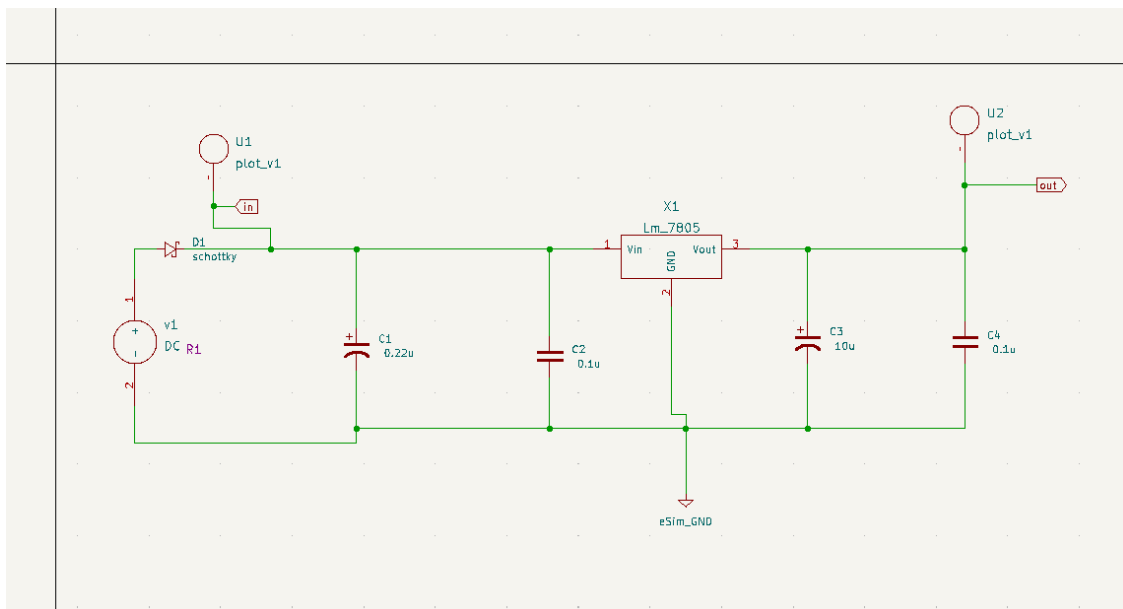


Figure 1: schematic capture of classical voltage converter

### Simulation Results :

1. Ngspice Plots (NOTE: I have zoomed enough like decimal in the ngspice so the graph makes the circuit looks screaming of noise, but it's working. For a very stable output, we can increase the value of frequency, high filter capacitance C4)

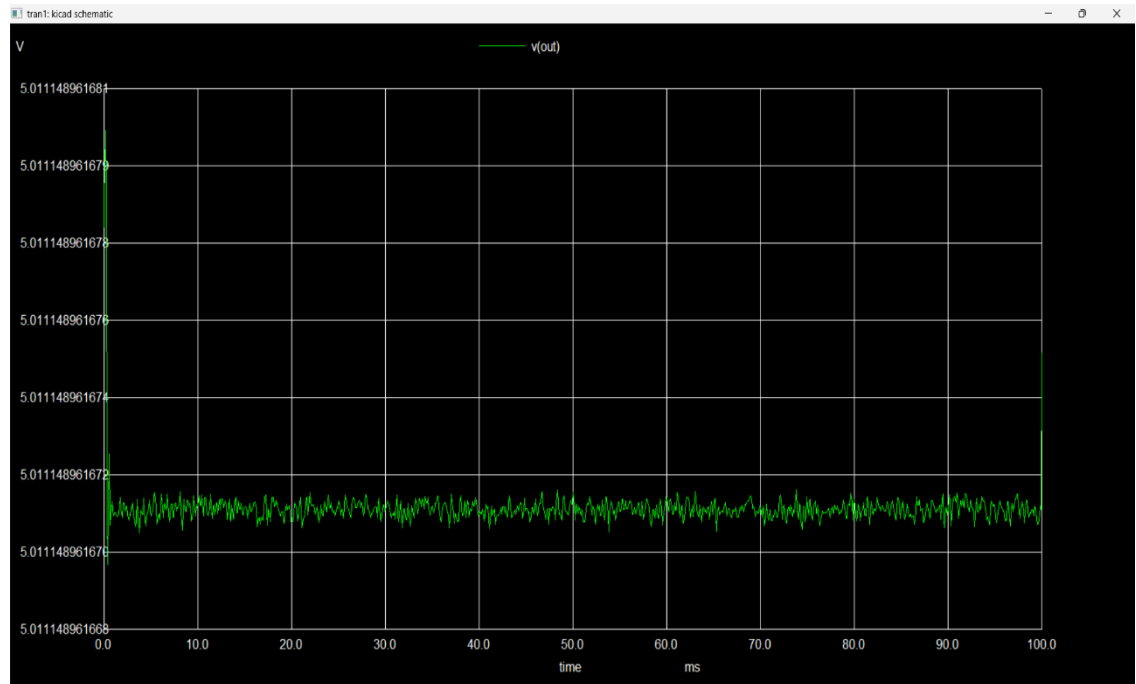


Figure 2: Ngspice Input Plot

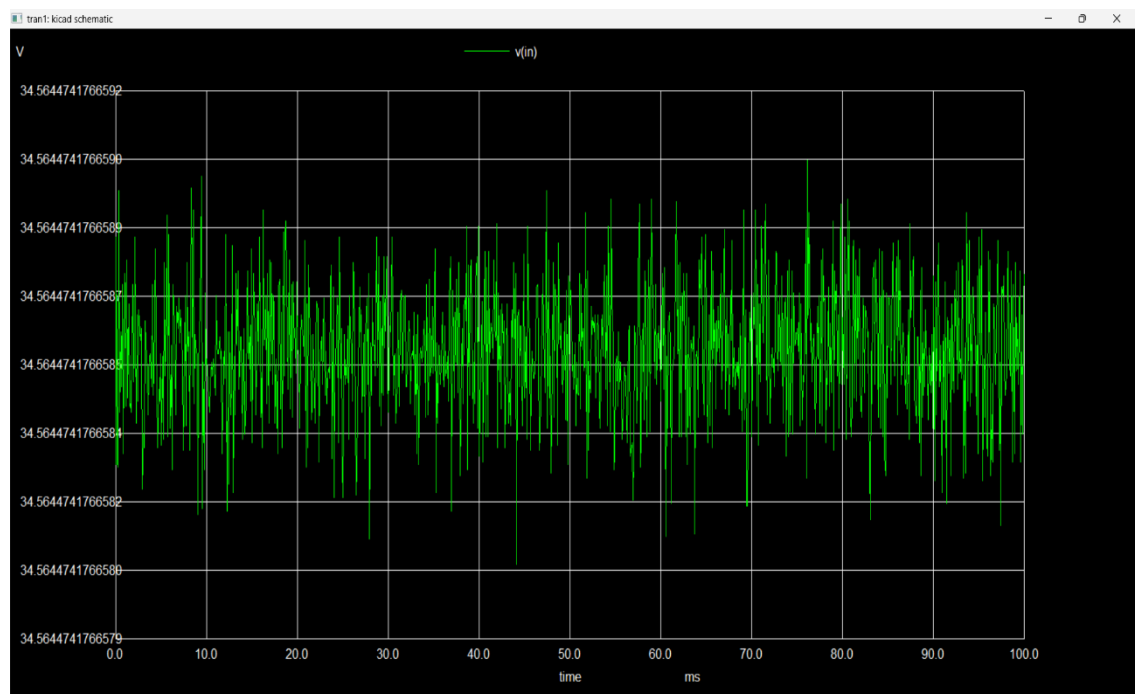


Figure 3: Ngspice Output

## 2. Python Plots:

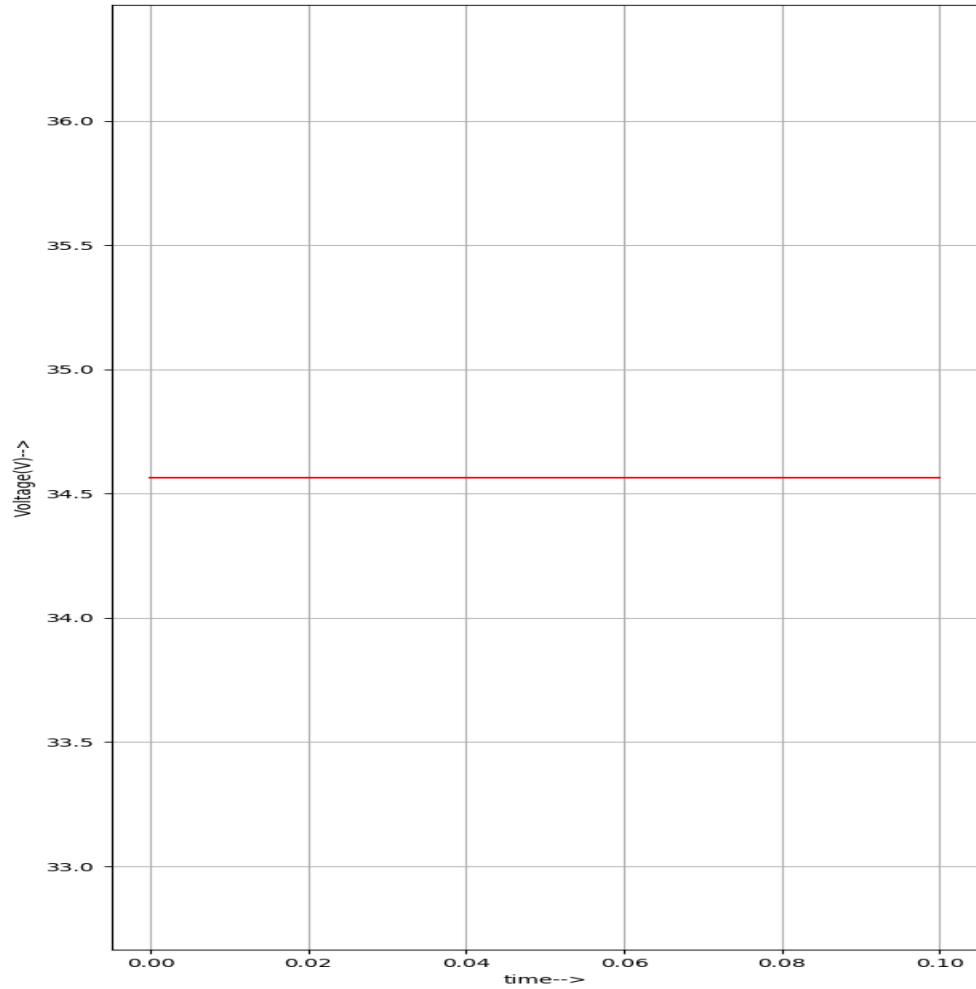


Figure 4: Python Plot Input +35V but explanation in the figure 5 below.

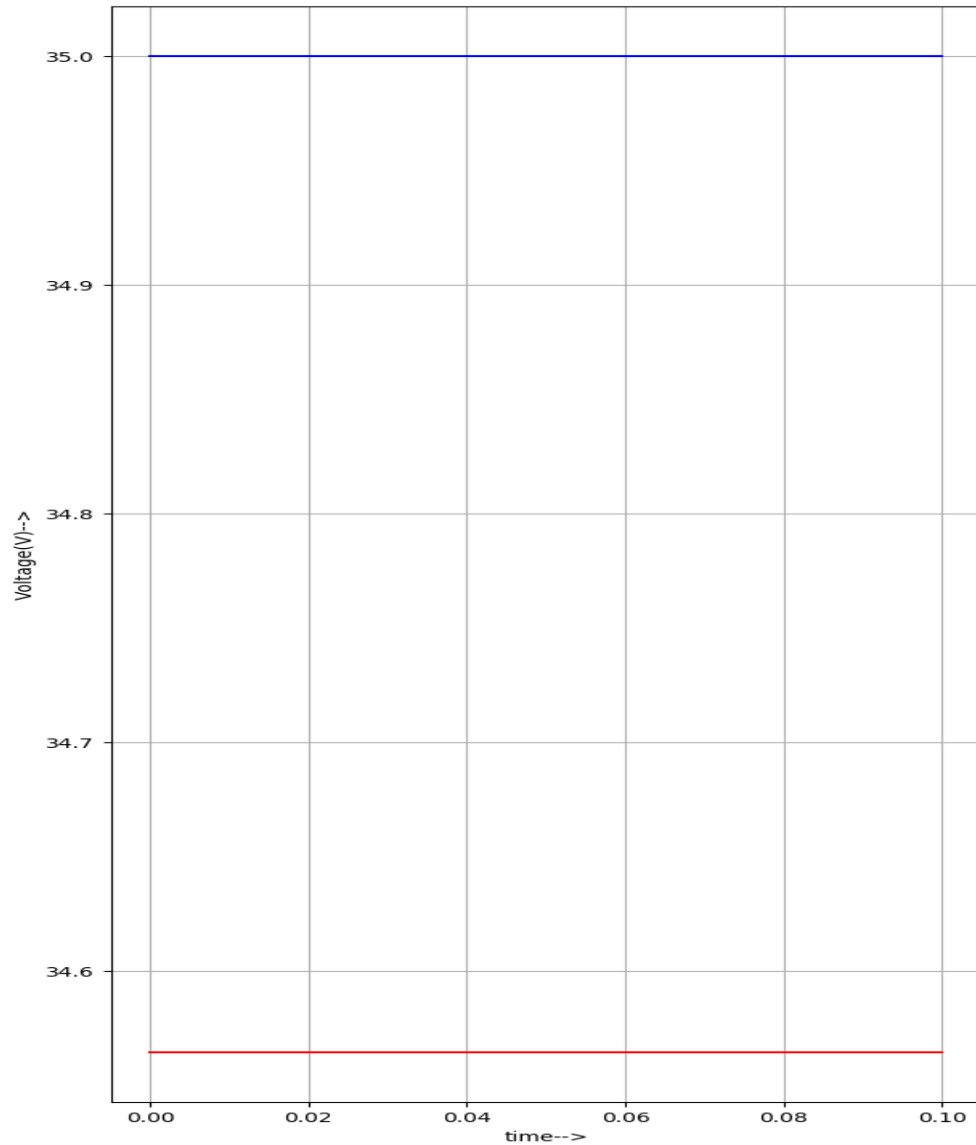


Figure 5: output at node (NOTE: WE CAN SEE HERE THE INPUT VOLTAGE IS +35V BUT IN THE INPUT IS SHOWS APROXX~34.7 V THIS IS DUE TO THE DIODE(D1). YOU CAN SEE THAT I PLACED THE PLOT\_V1 AFTER THE DIODE TO SHOW THE VOLTAGE DROP)

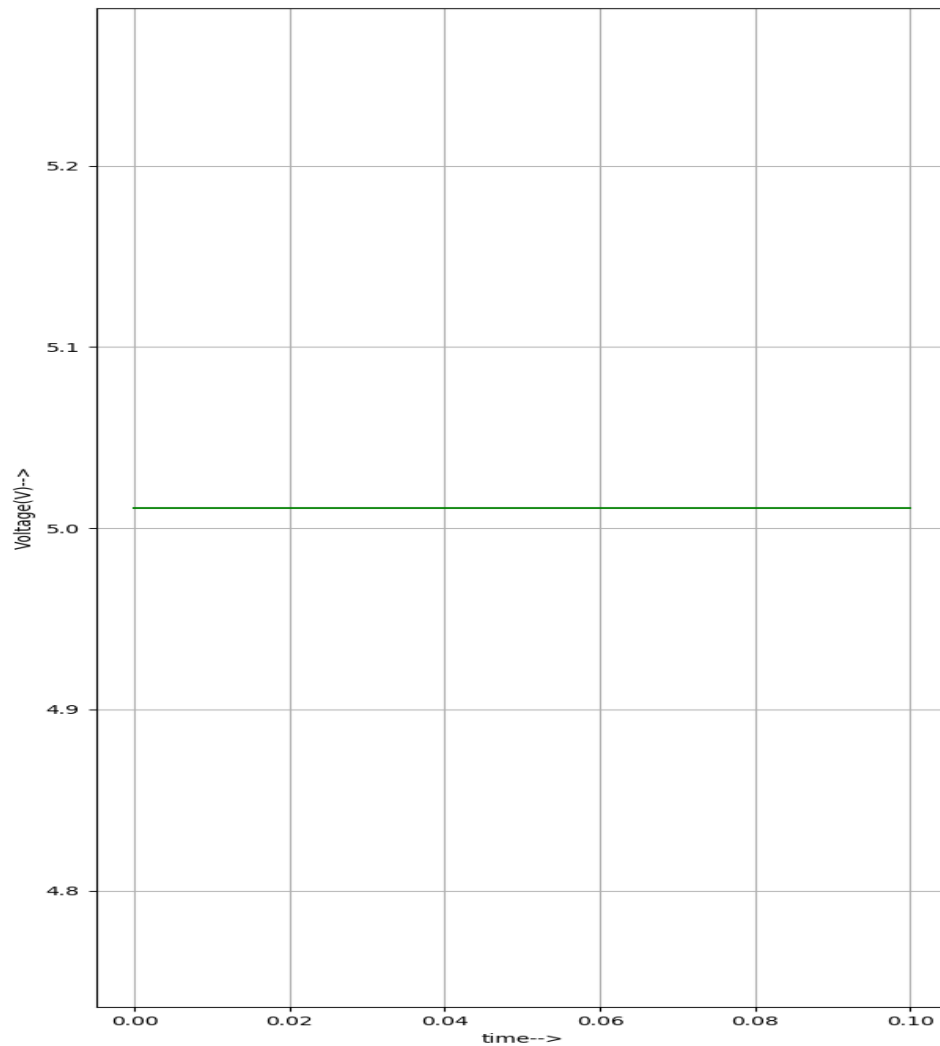


FIGURE 6: python plot output +5V

## Conclusion :

Thus, we have studied the a Fixed Linear Voltage Regulator designed to convert a high DC input voltage into a stable +5V output circuit

## References :

<https://www.circuits-diy.com/12v-to-5v-converter-using-lm7805-ic-power-supply/>