

EXPERIMENT NO: 13

Author: Gaurav Supal, Vineeta Parmar

Date: March 16, 2016

Aim of the Experiment:

Analysis of Binary to Gray converter using eSim.

Theory:

An interesting application for the exclusive - OR gate is a logic gate to change a binary number to its equivalent in gray code. The logic circuit in Figure - 1 can be used to convert a 4-bit binary number into its gray code equivalent, G0, G1, G2 and G3. As an example, the binary number 0011 will be converted into its gray-code equivalent of 0010 by the circuit. Following are the steps involved:

1. The M.S.B. of the gray code will be exactly equal to the first bit of the given binary number.
2. Now the second bit of the code will be exclusive-or of the first and second bit of the given binary number, i.e if both the bits are same the result will be 0 and if they are different the result will be 1.
3. The third bit of gray code will be equal to the exclusive-or of the second and third bit of the given binary number.

Thus the binary to gray code conversion goes on.

Procedure:

1. Create the schematic of the Binary to Gray Converter as shown in Figure-1.
2. Annotate the schematic.
3. Test Electric rules.
4. Generate the netlist.
5. Insert analysis for transient analysis from 0 to 100 ms with a step time of 10 μ s.

6. Insert Source Details.
7. Insert values for Ngspice Models.
8. Convert KiCad netlist to Ngspice netlist.
9. Simulate the Ngspice netlist using Ngspice simulator.

Source Parameters:

Following are the Pulse input parameters for V1:

1. Enter Initial Value - 0
2. Enter Pulsed Value - 5
3. Enter Delay Time - 0
4. Enter Rise Time - 0
5. Enter Fall Time - 0
6. Enter Pulse Width - 40m
7. Enter Period - 80m

Following are the Pulse input parameters for V2:

1. Enter Initial Value - 0
2. Enter Pulsed Value - 5
3. Enter Delay Time - 0
4. Enter Rise Time - 0
5. Enter Fall Time - 0
6. Enter Pulse Width - 20m
7. Enter Period - 40m

Following are the Pulse input parameters for V3:

1. Enter Initial Value - 0
2. Enter Pulsed Value - 5
3. Enter Delay Time - 0

Simulation Results:

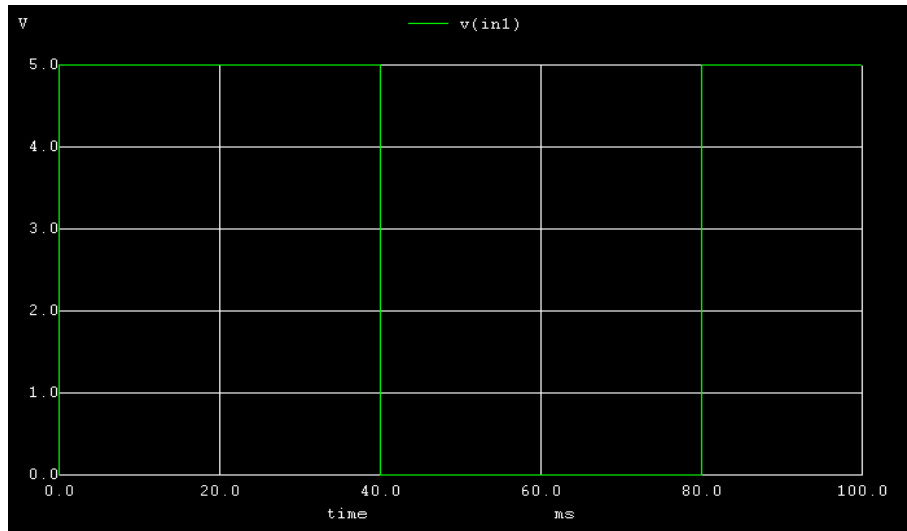


Figure 2: Ngspice Input-1 Plot

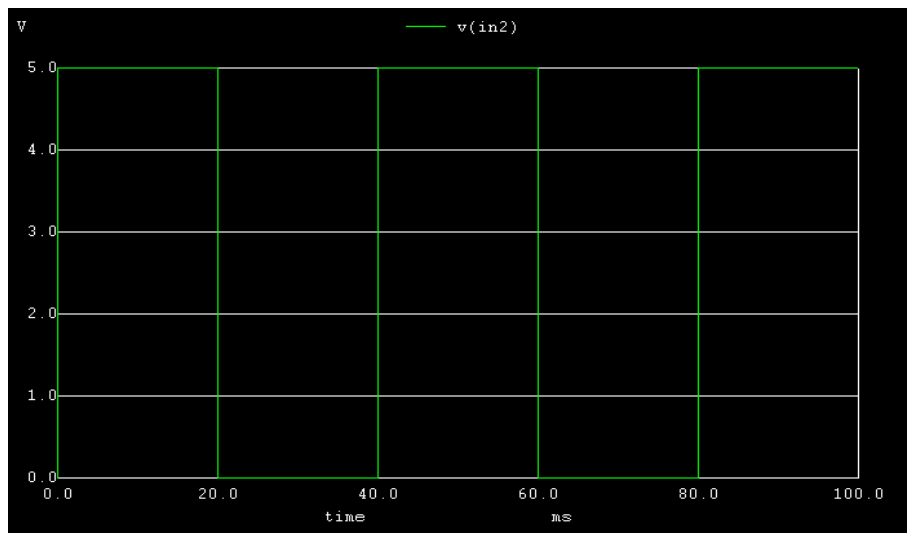


Figure 3: Ngspice Input-2 Plot

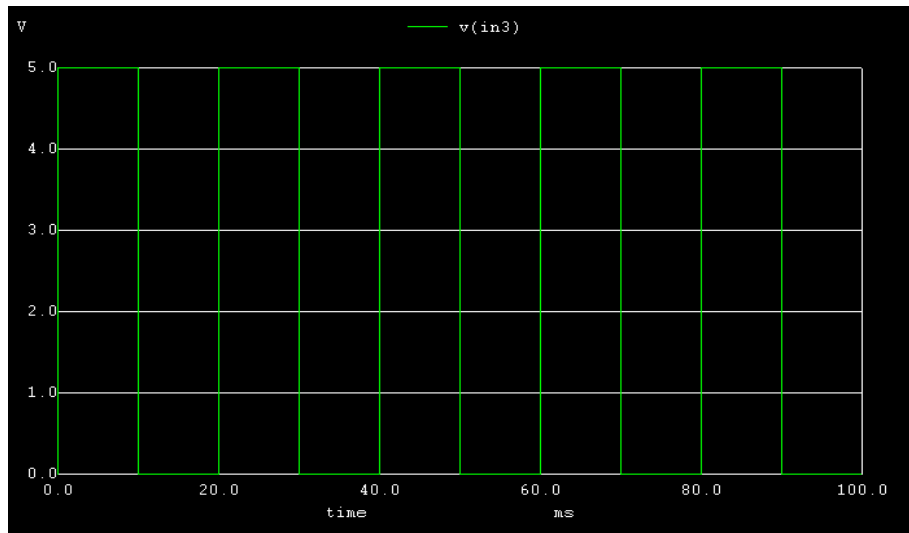


Figure 4: Ngspice Input-3 Plot

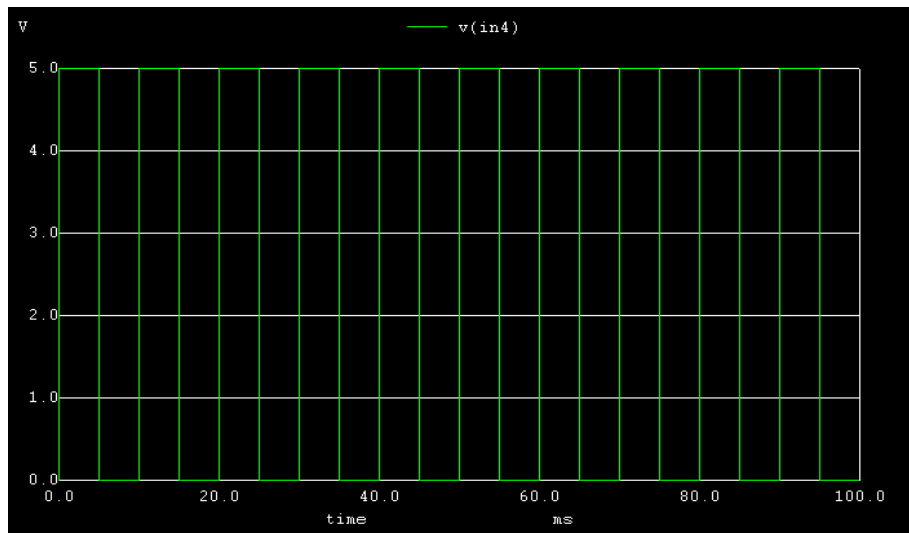


Figure 5: Ngspice Input-4 Plot

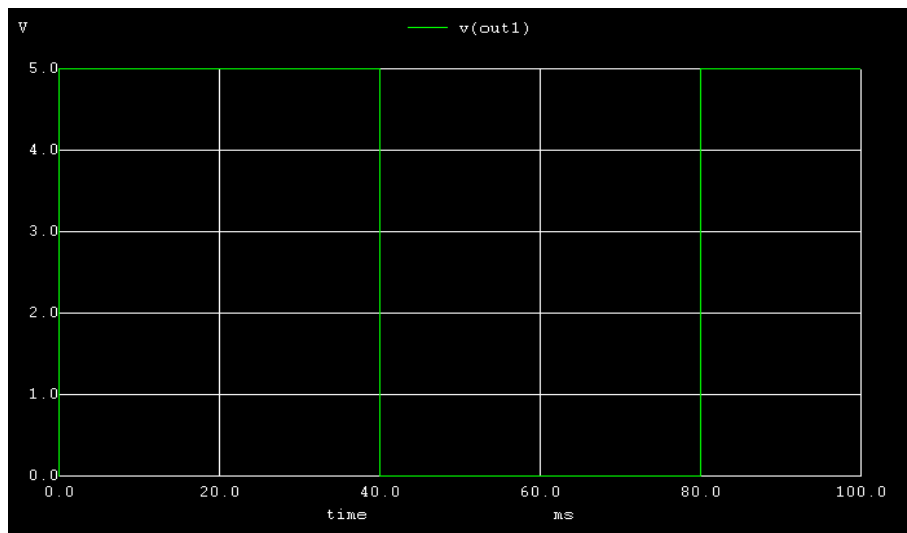


Figure 6: Ngspice Output-1 Plot

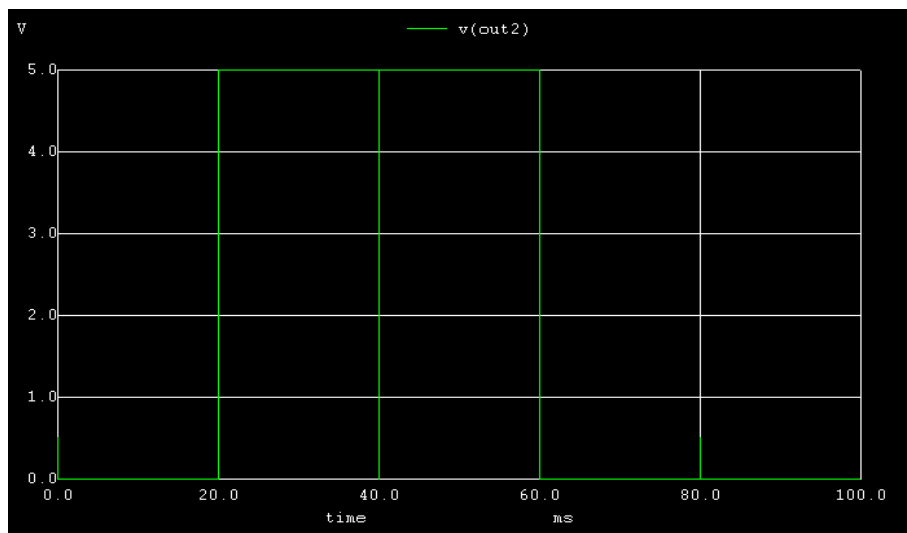


Figure 7: Ngspice Output-2 Plot

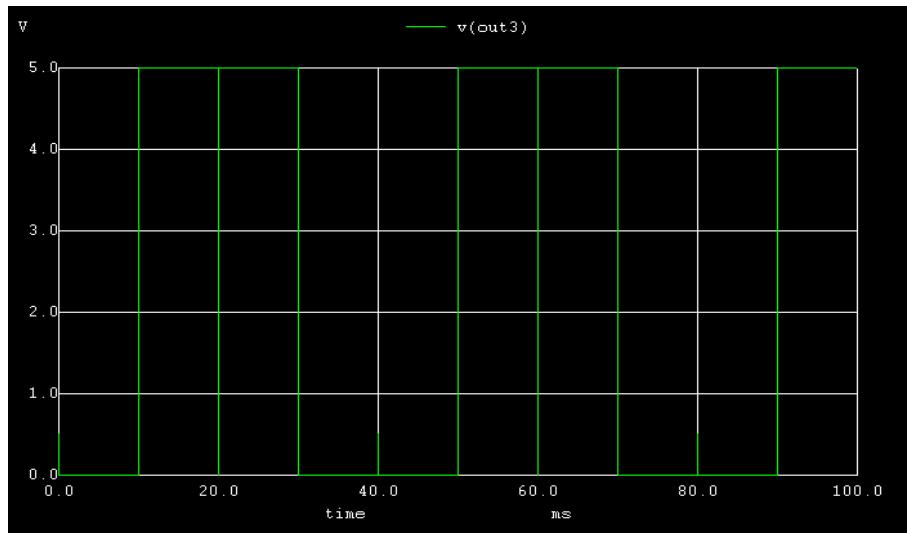


Figure 8: Ngspice Output-3 Plot

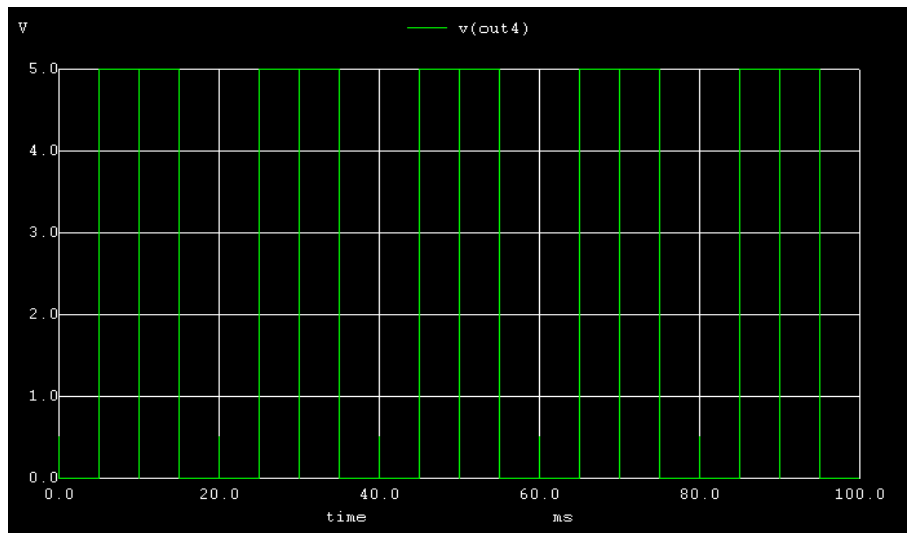


Figure 9: Ngspice Output-4 Plot

Conclusion:

Thus, we have studied the binary to gray converter using eSim and we get the appropriate waveforms.

References:

<http://www.electrical4u.com/gray-code-binary-to-gray-code-and-that-to-binary-conversion/>