


## Experiment 8

Aim: To Verify truth table of SR Latch

Theory:


In this circuit when Set S as active the output Q would be high and Q' will be Low. This is irrespective of anything else. (This is an active-low circuit so active here means low, but for an active high circuit active would mean high)

Circuit Diagram:

 


| S | R | Q | Q' |
|---|---|---|----|
| 0 | 0 | 0 | 1  |
| 0 | 1 | 0 | 1  |
| 1 | 0 | 1 | 0  |


Circuit diagram:

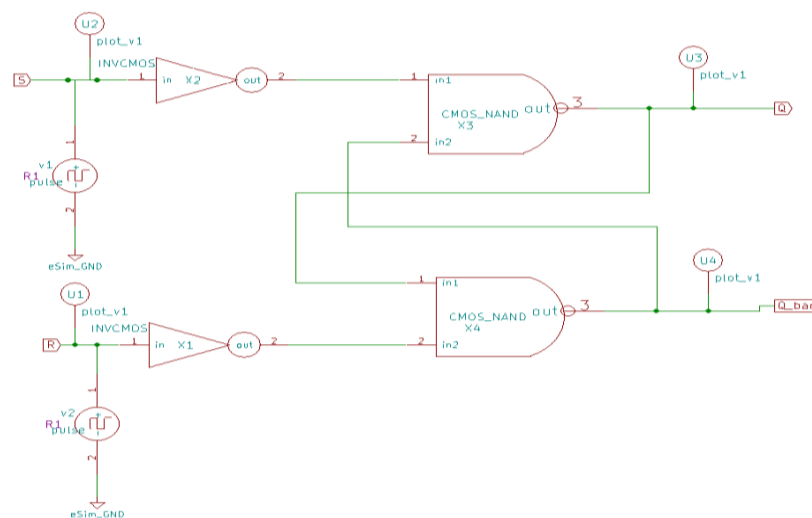


NGSPICE Plot of input s:

 


NGSPICE Plot of input R:

 


NGSPICE plot of q:

 


NGSPICE plot of  $q\_bar$ :

 


Python Plot of input s:

 


Python Plot of input r:

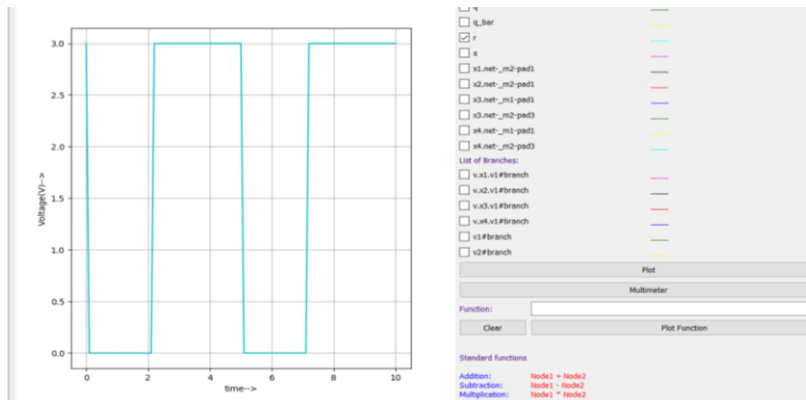

Python Plot of output q:

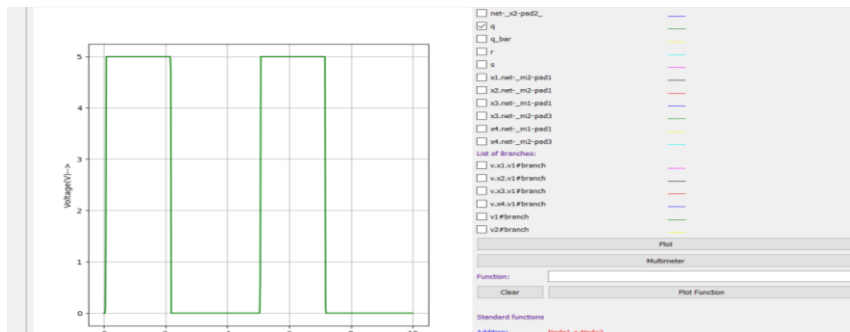

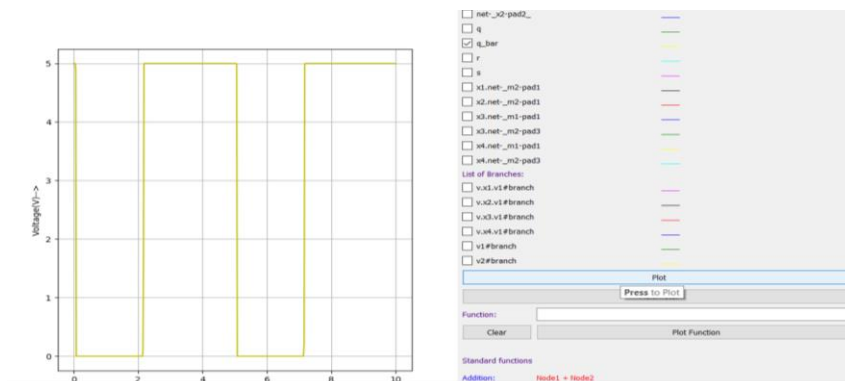Python Plot of output  $q_{\text{bar}}$ :



Source/Reference(s) :

1) CMOS VLSI Design A circuit and systems perspective by Neil H.E. Weste, David M. Harris. fourth edition.\

2) Digital logic and computer Design by Morris Mano

3) <https://www.electronicsforu.com/technology-trends/learn-electronics/flip-flop-rs-jk-t-d>