

# Multiplexer Design and simulation

B. S. Abdur Rahman Crescent Institute Of Science And Technology

**Abstract**—At the start a brief and concise introduction to multiplexer specifically a simplest 2 to 1 multiplexer is provided with the explanation of the output they will show. A multiplexer can also be referred as a mux in short form and 2 to 1 mux is the simpler of its kind

## I. REFERENCE CIRCUIT DETAILS

A simple multiplexer is used to display a number of input signals on a single output line with the help of a select switch. A total of  $2^n$  input signals can be displayed on a single output line with the help of  $n$  select switch. A simple multiplexer diagram and functionality is shown in the figure 1

Depending on the value of the select switch one out of all the inputs will be displayed at the output as is obvious from the figure 1

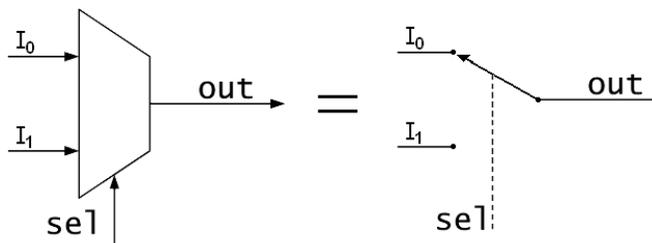


Fig. 1.

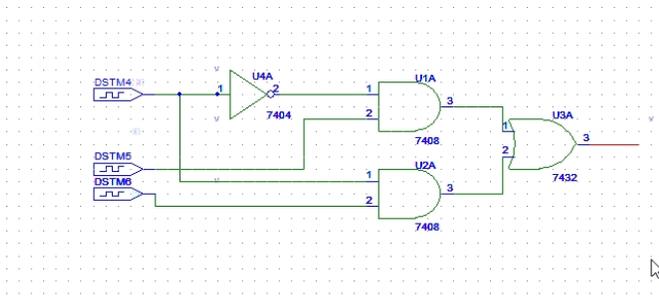


Fig. 2. Complete circuit diagram

## II. OUTPUT

The output of the circuit shows that when the select switch is 0, the value at the input  $I_0$  will be displayed at the output  $V_{out}$ . Similarly, when the select switch is 1 then the value at the input line  $I_1$  will be mirrored on the output  $V_{out}$ . The select switch will select which out of all the inputs which of the input will be displayed on the single line output.

## REFERENCE

<https://microcontrollerslab.com/multiplexer-design-simulation-bspice/>

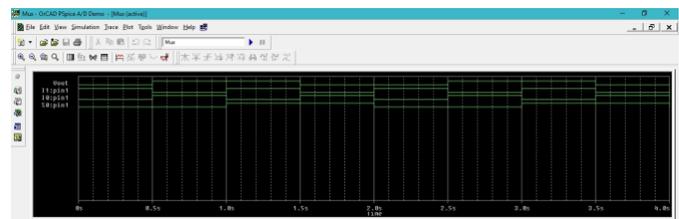


Fig. 3.