

Clk_Generator-RVMYTH-DAC mixed-signal circuit Design & Simulations with eSim


khadija Fahr : Khadija.fahr@googlemail.com

Abstract

This paper presents a result of implementation and simulations of a mixed signal circuit with the open-source EDA tools eSim. First I design and simulate 2 analog circuits *Fahr_clk-gen* and *Fahr_10bitDac* after I simulate the tlv code of my digital circuit *Fahr_rvmyth* by Makerchip and create it s model by Ngveri .Finally I implement my reference mixed signal circuit and simulate it with eSim.


Keywords: RVMyth, DAC, Clk-Gen, eSim, , makerchip,Ngveri,NgSpice

I. REFERENCE CIRCUIT

 

1 *Fahr clk gen* Circuit

 I design a circuit to generate the clk signal by using the subchip clk_pulse_generator from eSim component, I generate a verilog module for *Fahr_clk-Gen* and obtain the analog v(clk) for R1=R2=20K,Vdd=10V ,v(c_out) the plot at the out of capacitor C=0.1u




Design

v(c_out) ,

v(clk)

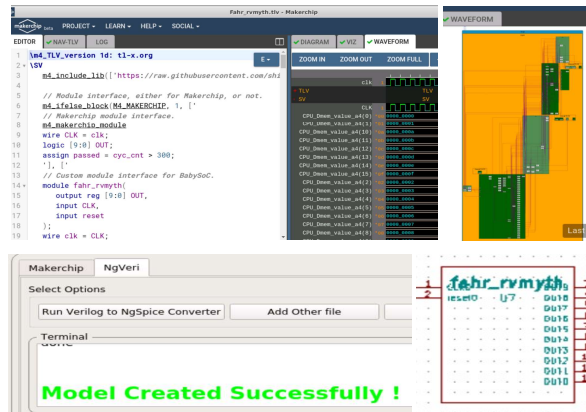
2) *Fahr rvmyth* circuit

I used the tlv code for rvmyth and create it sucessefly by makerchip and run verilog to NgSpice Converter to create the model *fahr_rvmyth*



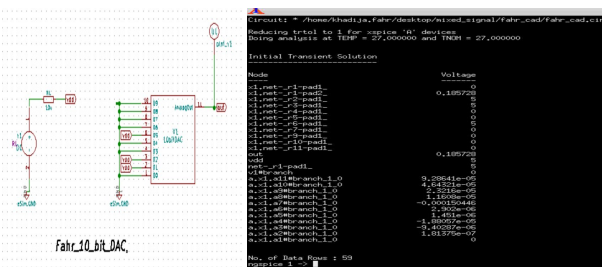3) *Fahr 10bit DAC* Circuit

I used the subship 10bit_DAC from library to generate a Netlist verilog module of DAC and obtain the analog v(out) for digital inputs to test it.




Design of DAC

NgSpice


calcul of V(out)

 *Simulation of the v(out) ,Vdd 5V, DC mode




II. DESIGN & SIMULATION OF REFERENCE CIRCUIT


* Implementation with eSim

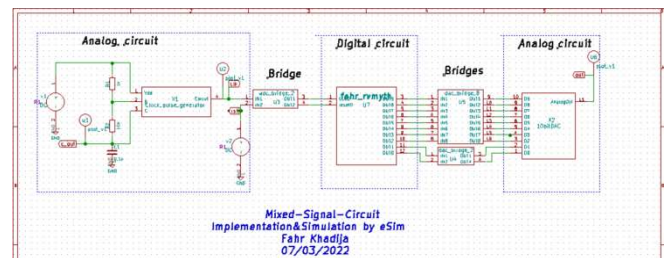

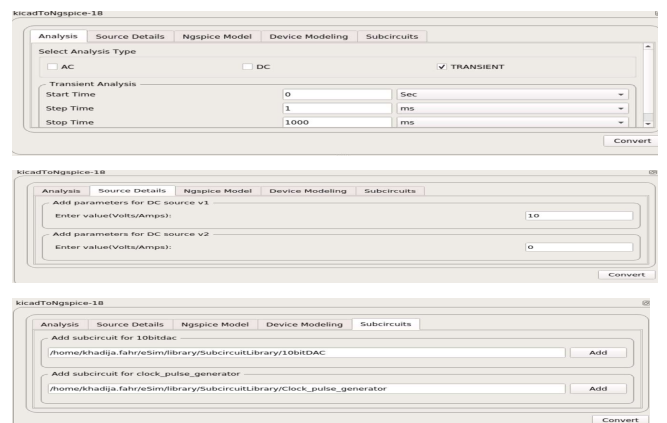* Setting of Analysis type –source detail—add Subchips



 *Simulation of the reference mixed circuit



REFERENCES

- [1] https://github.com/vsdip/rvmyth_avsddac_interface
- [2] https://github.com/vsdip/rvmyth_avsdp11_interface
- [3] <https://esim.fossee.in/circuit-simulation-project/esim-circuit-simulation-run>
- [4] <https://hackathon.fossee.in/esim/>

