


MIXED CIRCUIT IN 4:1 MULTIPLEXER USING ESIM

Susmitha T – Bannari Amman Institute of Technology, Erode

Abstract- A multiplexer is a unidirectional device that is utilized in any application where data must be switched from numerous sources to a destination. Modern VLSI design now places a high premium on low power circuits. Here we are implementing the 4:1 multiplexer using eSim simulator. Digital and Analog circuits of a certain circuit are both included in mixed signal circuits. A data selector called MUX produces a single output from several data inputs. Here, we've put into practice a two-input MUX that will produce a single output depending on a single line of input.

 1. DESCRIPTION:

A multiplexer is a combinational circuit that has a single output line, n selection lines, and up to $2n$ data inputs. On the basis of the values of the selection lines, one of these data inputs will be connected to the output. There will be 2^n potential combinations of zeros and ones as there are ' n ' selection lines. Thus, just one data input will be chosen for each combination. Another name for a multiplexer is a Mux. A 4-to-1 multiplexer has a single output line (Y), two select lines (S_0 and S_1), and four data input lines (D_0 to D_3). The four input lines are chosen by the select lines S_0 and S_1 to link to the output line.




The input line that will be chosen to pass from the multiplexer will be D_0 when selection lines A and B both have values of 0. As a result, for input line D_0 , MUX will short circuit, and for all other input lines, it will be open circuited.

The input line that will be chosen is D_1 if selection line A represents 0 and selection line B represents 1. In this scenario, MUX will act as an open circuit for all other input lines while acting as a short circuit for input line D_1 .

The output will produce the input line D_2 if the selection line A is 1 and the selection line B is 0. In this case, the MUX will only let D_2 travel through it and will block all other input.

The last input line, D_3 , will be chosen if both selection lines have the value 1. In this scenario, the MUX will only permit the D_3 to flow through it, preventing the passage of other input lines.

2. IMPLEMENTED DIAGRAM

 

3. REFERENCE

- (1) Performance Evaluation of 4:1 multiplexer - https://iaeme.com/MasterAdmin/Journal_uploads/IJECE/T/VOLUME 7 ISSUE 4/IJECET 07 04 003.pdf
- (2) High performance, low power 200 Gb/s 4:1 MUX with TGL in 45 nm technology - <https://link.springer.com/article/10.1007/s13204-013-0206-0>