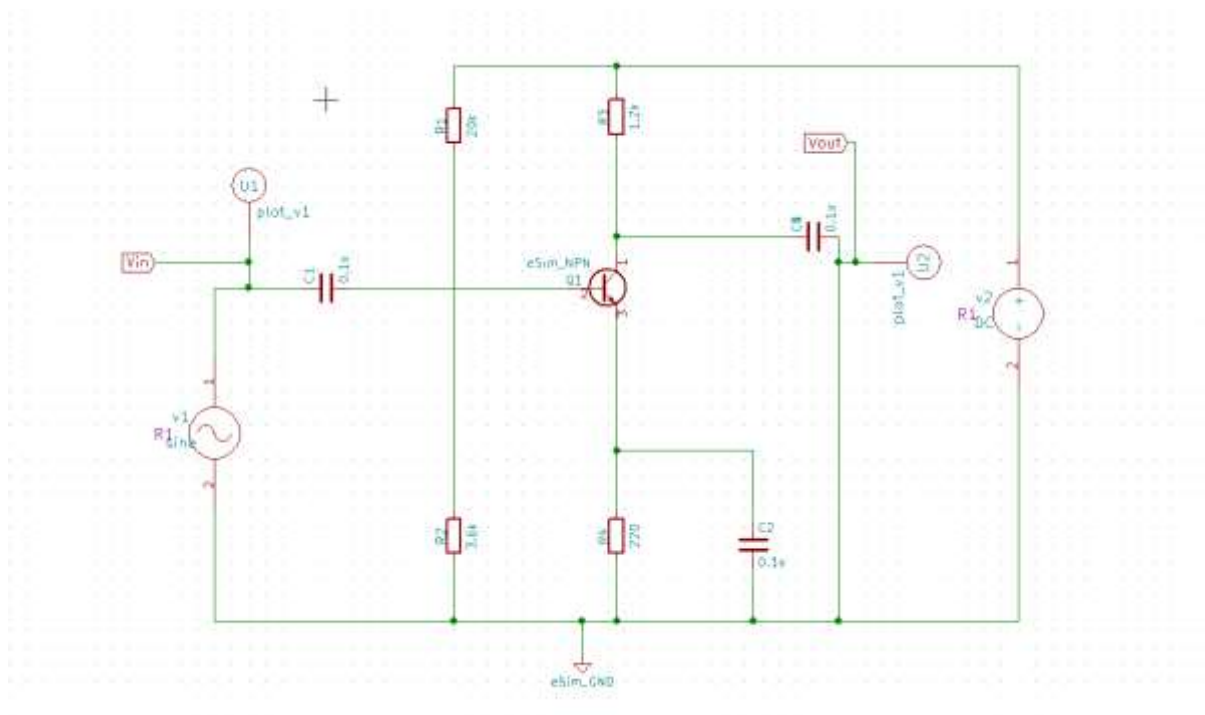


Title: Amplification of weak electrical signals using a common emitter amplifier and verification of current and voltage gain

Name: J.A Jenie Shalin

College Name: Easwari Engineering College

Circuit Diagram: CE amplifier



Reference

1. https://www.electronics-tutorials.ws/amplifier/amp_2.html
2. <https://www.elprocus.com/common-emitter-amplifier-circuit-working/>

