

# Circuit Simulation Project


<https://esim.fossee.in/circuit-simulation-project>

**Name of the participant :** Jovin P John

**Title of the circuit :** 4-bit Baugh-Wooley Multiplier

**Theory/Description :** A 4-bit Baugh-Wooley multiplier is a circuit that directly multiplies two 4-bit signed numbers without separate sign handling. It uses a grid of logic gates and adders arranged systematically to generate the 8-bit product result. This design efficiently handles negative numbers using two's complement arithmetic in hardware.

**Circuit Diagram(s) :**

 

**Results (Input, Output waveforms and/or Multimeter readings) :**

| a    | b    | Output (Product) |
|------|------|------------------|
| 1111 | 1111 | 11100001         |
| 1110 | 1110 | 11000100         |
| 1101 | 1101 | 10101001         |
| 1100 | 1100 | 10010000         |
| 1011 | 1011 | 01111001         |
| 1010 | 1010 | 01100100         |
| 1001 | 1001 | 01001001         |
| 1000 | 1000 | 01000000         |
| 0111 | 0111 | 00110001         |
| 0110 | 0110 | 00100100         |
| 0101 | 0101 | 00011001         |
| 0100 | 0100 | 00010000         |
| 0011 | 0011 | 00001001         |
| 0010 | 0010 | 00000100         |
| 0001 | 0001 | 00000001         |
| 0000 | 0000 | 00000000         |

**Source/Reference(s) :** Puttaswamy, M., Premananda, B. S., & Kamat, N. (2024). Area and energy optimized Hamming encoder and decoder for nano-communication. Journal of Electrical Engineering