

# Simulation and Analysis of Diode Clippers and Clampers Using eSIM

Submitted by:

Abdullah Najam

Indian Institute of Engineering Science and Technology, Shibpur

---

## 1. Introduction

Wave shaping circuits such as **clippers** and **clampers** play a crucial role in signal processing applications. Clippers (also known as limiters) are designed to remove portions of the waveform beyond a certain voltage level, altering its shape. Clampers, on the other hand, shift the entire waveform to introduce a DC bias without changing its form. These circuits are widely used in **communication systems, television receivers, and signal conditioning applications**.

This project focuses on simulating diode-based clipper and clamper circuits using **eSIM**, an open-source electronic simulation tool. The objective is to analyze the behavior of these circuits under different configurations and observe their impact on waveform transformation.

---

## 2. Circuit Theory and Description

### 2.1 Clipper Circuits

- **Series Positive Clipper:** Removes the positive half-cycle of the input waveform.
- **Series Negative Clipper:** Removes the negative half-cycle of the input waveform.
- **Biased Clippers:** Allows clipping at a voltage level other than zero by introducing a bias voltage.


### 2.2 Clamper Circuits

- **Positive Clamper:** Shifts the waveform upward by adding a positive DC level.
- **Negative Clamper:** Shifts the waveform downward by adding a negative DC level.


These circuits employ **diodes, resistors, capacitors, and function generators** to shape the signal.

---


## 3. Circuit Diagram(s)

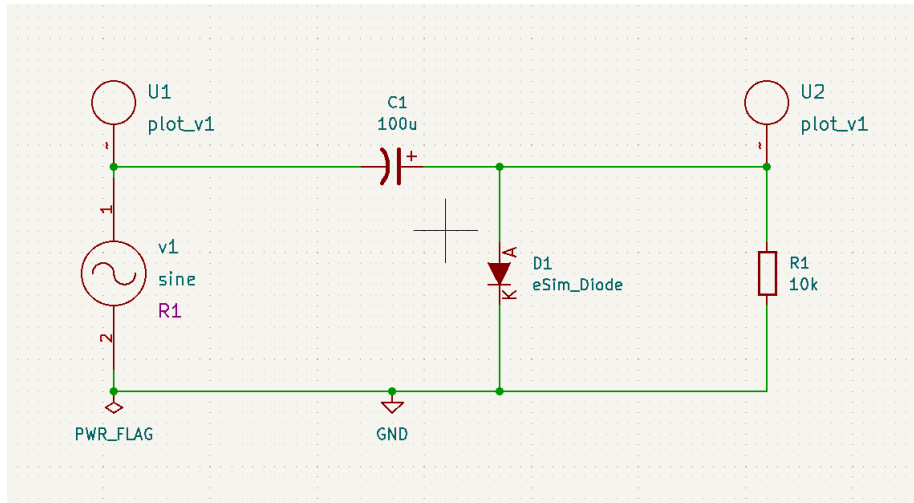


**Negative Clamper Circuit**

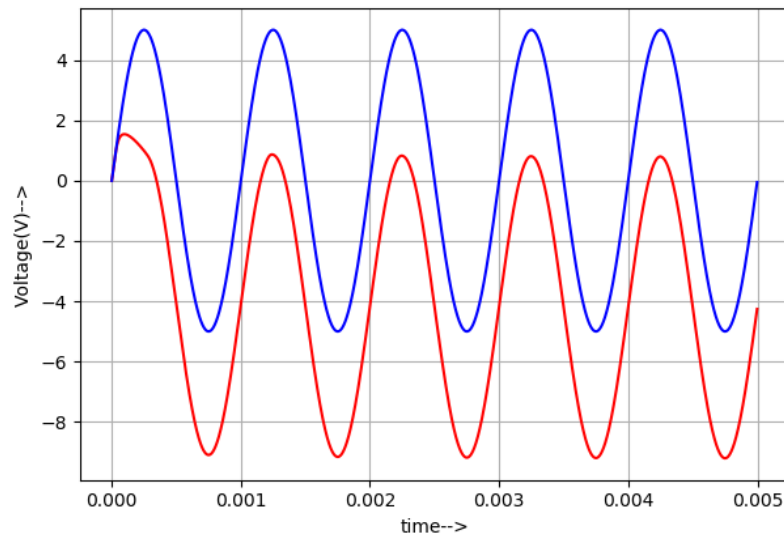


**Negative Clamper Output Waveform**

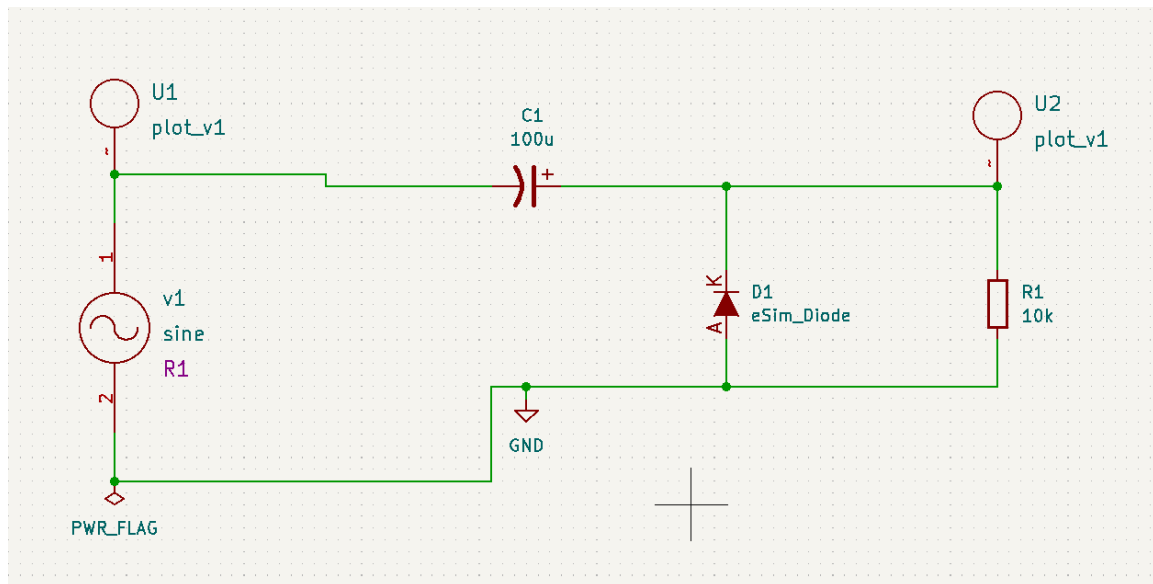


**Positive Clamper Circuit**

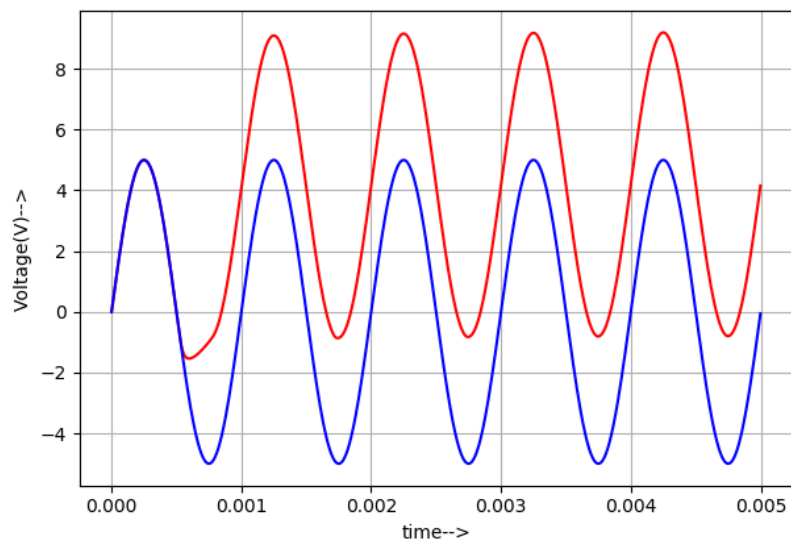


**Positive Clamper Output Waveform**

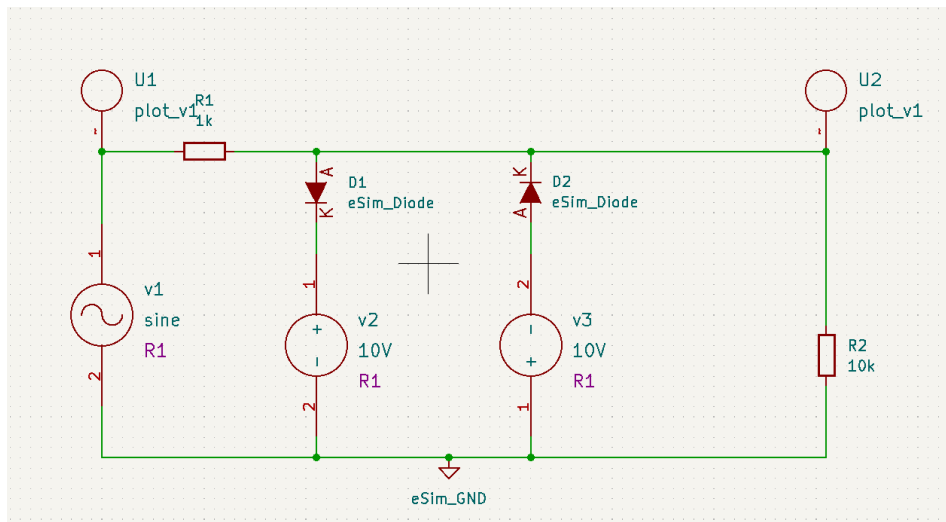


**Biased Clipper with diode Circuit**

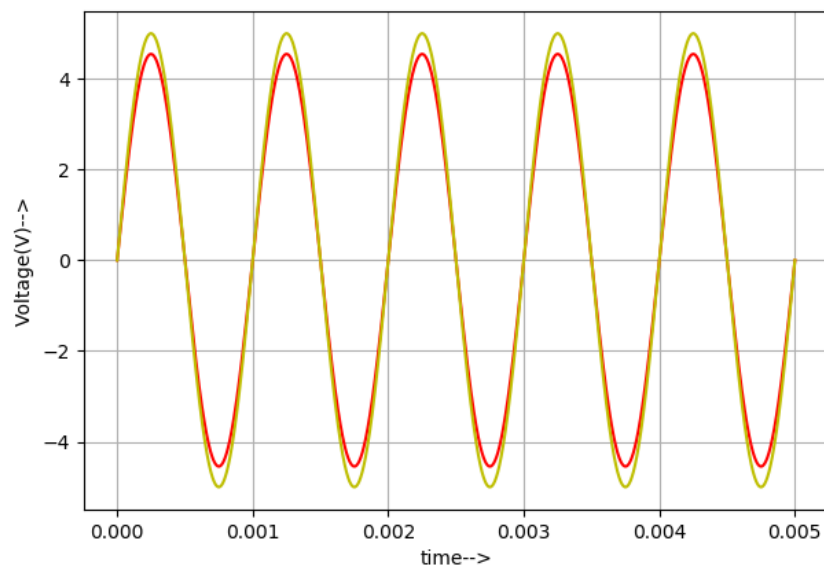

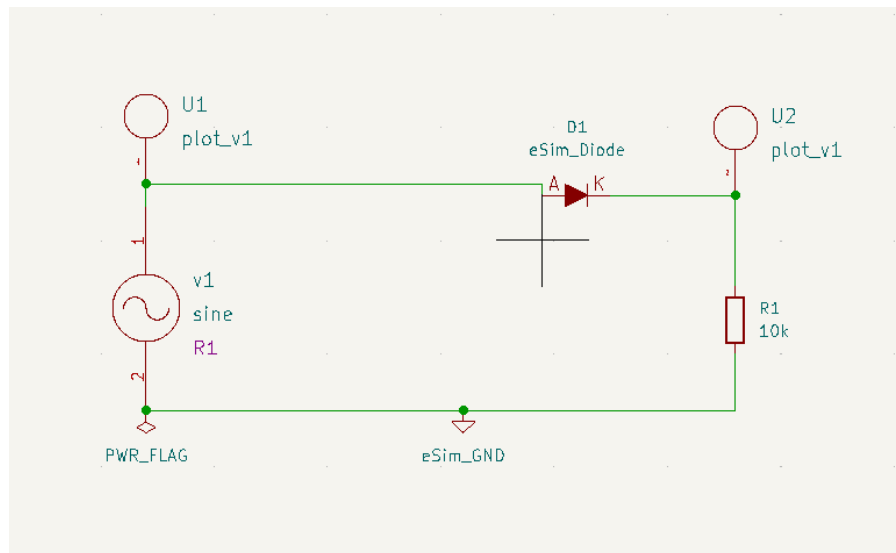
**Biased Clipper with diode Circuit Output Waveform**




**Negative Clipper Circuit**

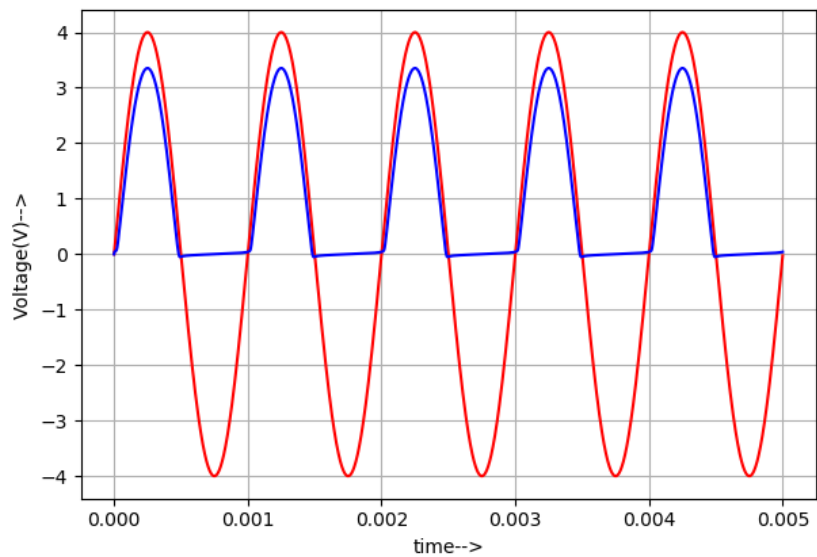

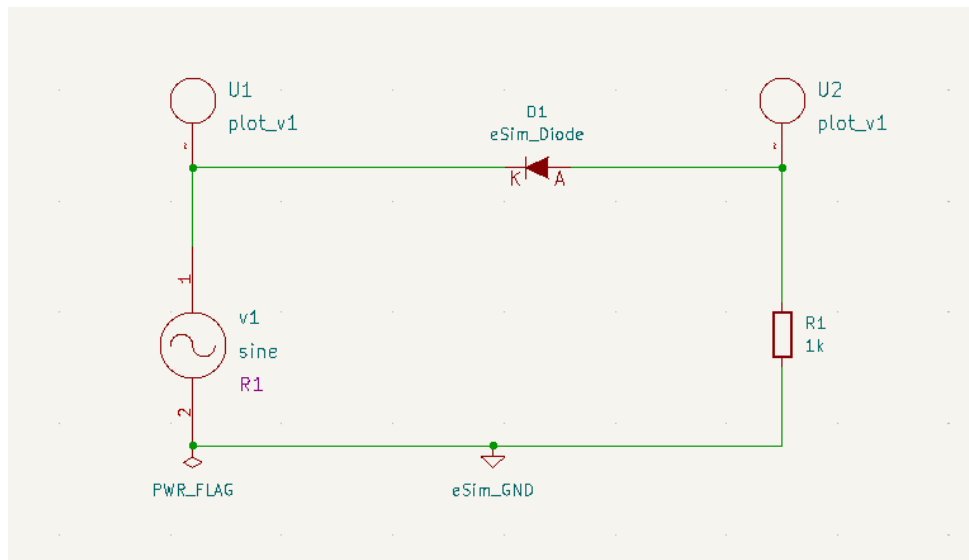**Negative Clipper Circuit Output Waveform**



**Positive Clipper Circuit**

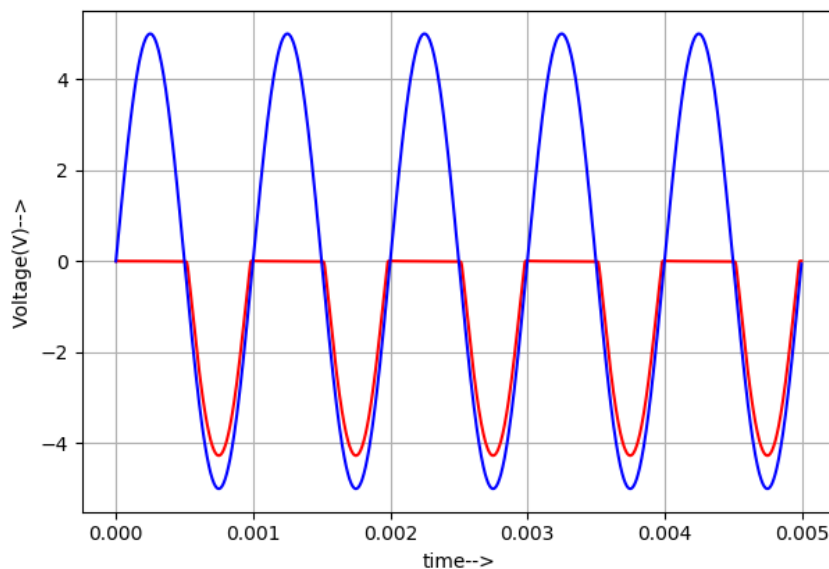

**Positive Clipper Circuit Output Waveform**

#### 4. Simulation Setup and Procedure

1. **Launching eSIM:** Open the eSIM software and create a new project.
2. **Circuit Construction:** Place the required components (**diodes, resistors, capacitors, and function generators**) in the circuit editor.
3. **Input Signal Configuration:** Apply a sinusoidal input signal of **1 kHz frequency and 5V amplitude**.
4. **Simulation Execution:** Run the simulation and analyze the output waveform using a virtual oscilloscope.

5. **Observations:** Compare the input and output waveforms to examine the clipping and clamping effects.
- 

## 6. Conclusion

This project successfully **simulated diode-based clippers and clampers** using eSIM. The results validate the expected modifications in the waveform caused by clipping and clamping circuits. The study highlights the significance of these circuits in practical applications, such as **signal modulation, wave shaping, and noise reduction** in electronic systems.

---

## 7. References

1. **IRE Journals - Study and Analysis of Clipper and Clamper Circuits**  
<https://www.irejournals.com/paper-details/1701522>
  2. **CircuitBread - Using Diodes as Clippers or Clampers**  
<https://www.circuitbread.com/tutorials/using-diodes-as-clippers-or-clampers>
  3. **IEEE Xplore - Diode Applications in Nonlinear Wave Shaping Circuits**  
<https://ieeexplore.ieee.org/document/793507>
-