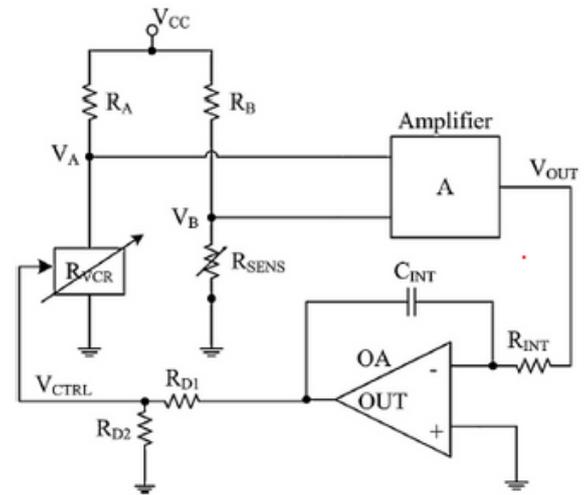


Analog Wheatstone bridge-based automatic interface for grounded wide-range resistive sensors

Ayaz Mumtaz Ansari
Jamia Millia Islamia
26/06/2024

Abstract

Presenting an analog Wheatstone bridge-based architecture for a resistive sensor circuit. In this circuit, the change in external stimulus is measured with a highly sensitive change in resistance. The change in resistance is then converted into output voltage, which holds a direct relation with the reciprocal of the sensor resistance. The circuit operates in autonulling mode, meaning the bridge remains balanced automatically for a wide range of sensor resistance.




proposed uncalibrated Wheatstone bridge.

Circuit Design

The proposed circuit works properly for the range of resistive sensor 10kohm to 200kohm in the autonulling mode. In the auto nulling mode the change in the sensor resistance is automatically calibrated across the parallel arm of the bridge and the overall bridge remains balanced, outside the auto-nulling region the bridge is unbalanced as the integrator saturates and in this case output of the amplifier ($V_A - V_B$) is the measure of sensor resistance. A **voltage controlled resistance** has been employed using a Analog Multiplier by which we can control the resistance value with the help of integrator output voltage.

- In this Circuit R_{Sens} is the sensor resistance and it will vary according to external stimulus.
- If the Sensor resistance is in the range of 10kohm to 200kohm . The circuit properly operates in the autonulling mode and the bridge is automatically balanced.
- In the auto-nulling mode the measure of the sensor resistance is given by the output of the integrator (V_{ctrl}).
- In the autonulling mode the differential output of amplifier should be ideally zero.
- Outside the autonulling mode , the measure of the sensor resistance is given by the differential output of the INA.
- We will analyse the resistance of the VCR by ohms law formula and verify if the bridge is balanced or not.
- **For the balanced bridge condition to satisfy we must get ($R_{vcr} = R_{sens}/10$) .**
- **(Taking $R_A/R_B = 0.1$)**


Multisim Schematic-

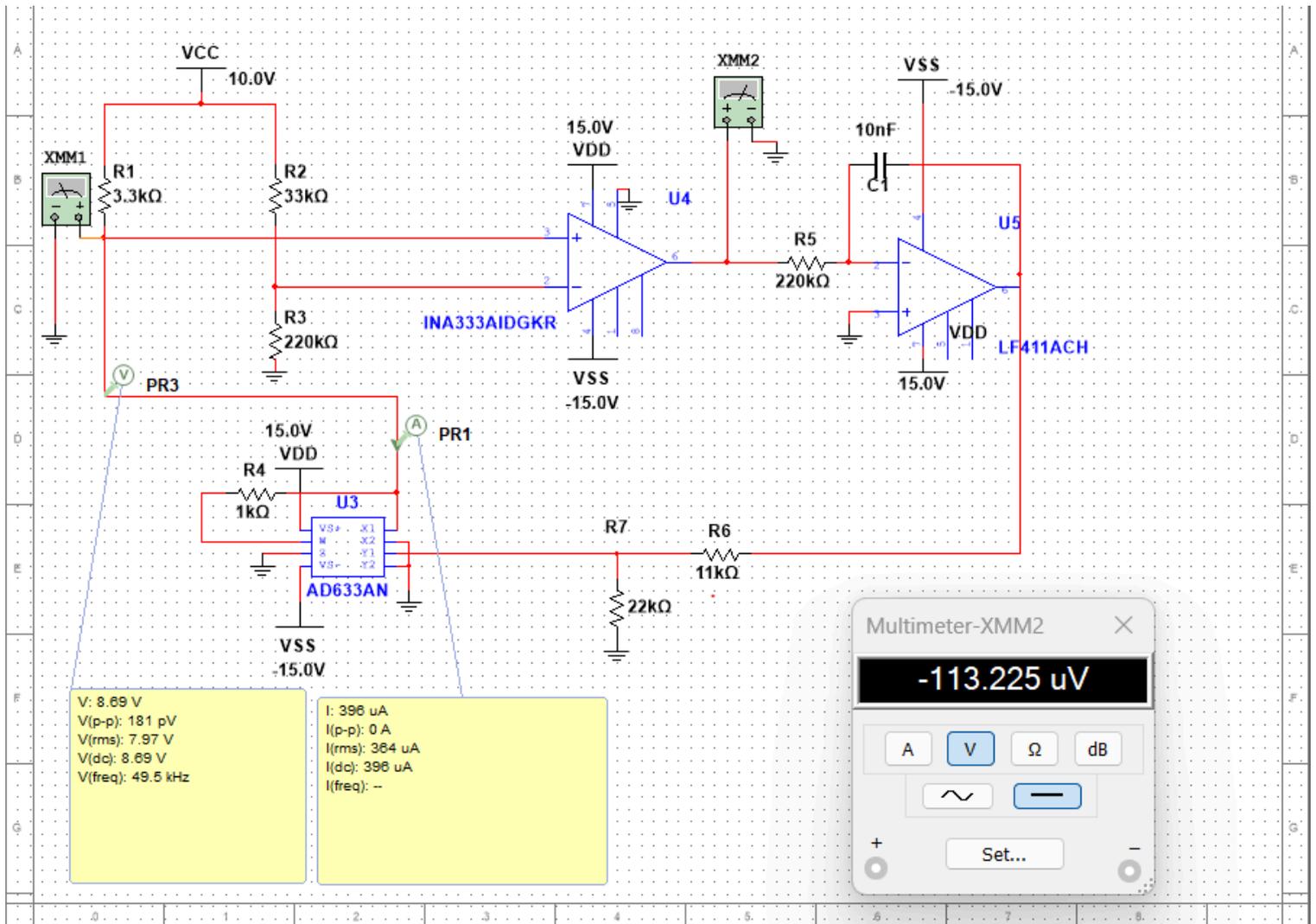

Circuit Simulated in Multisim



Note: Here R3 is the grounded sensor resistance.

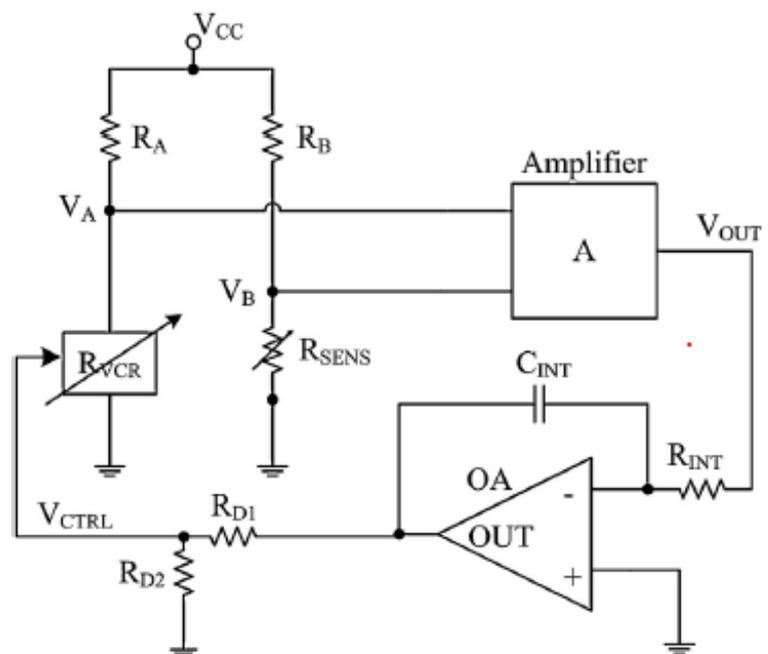- We can see for $R_{sens} = 200\text{kohms}$, we get $V_a = 8.69\text{ V}$ and $I = 0.396\text{ mA}$. So we get $R_{vcr} = V_a/I = 21.944\text{ kohm}$.
- Similarly the circuit works for the range of 10 kohm to 220 kohm



EESchema Schematic-

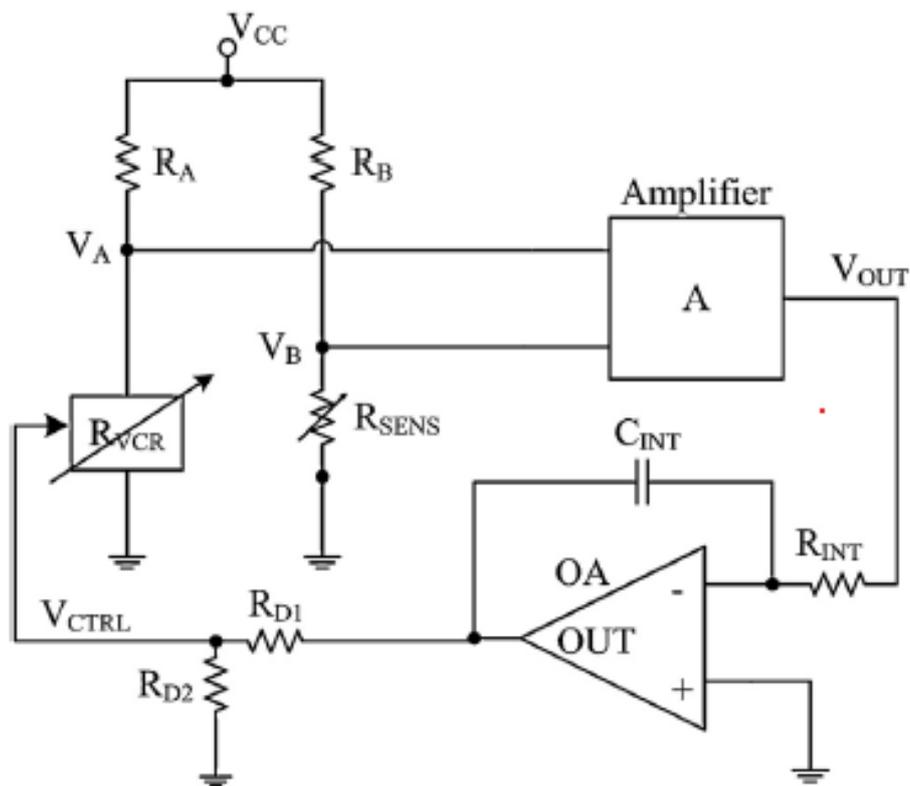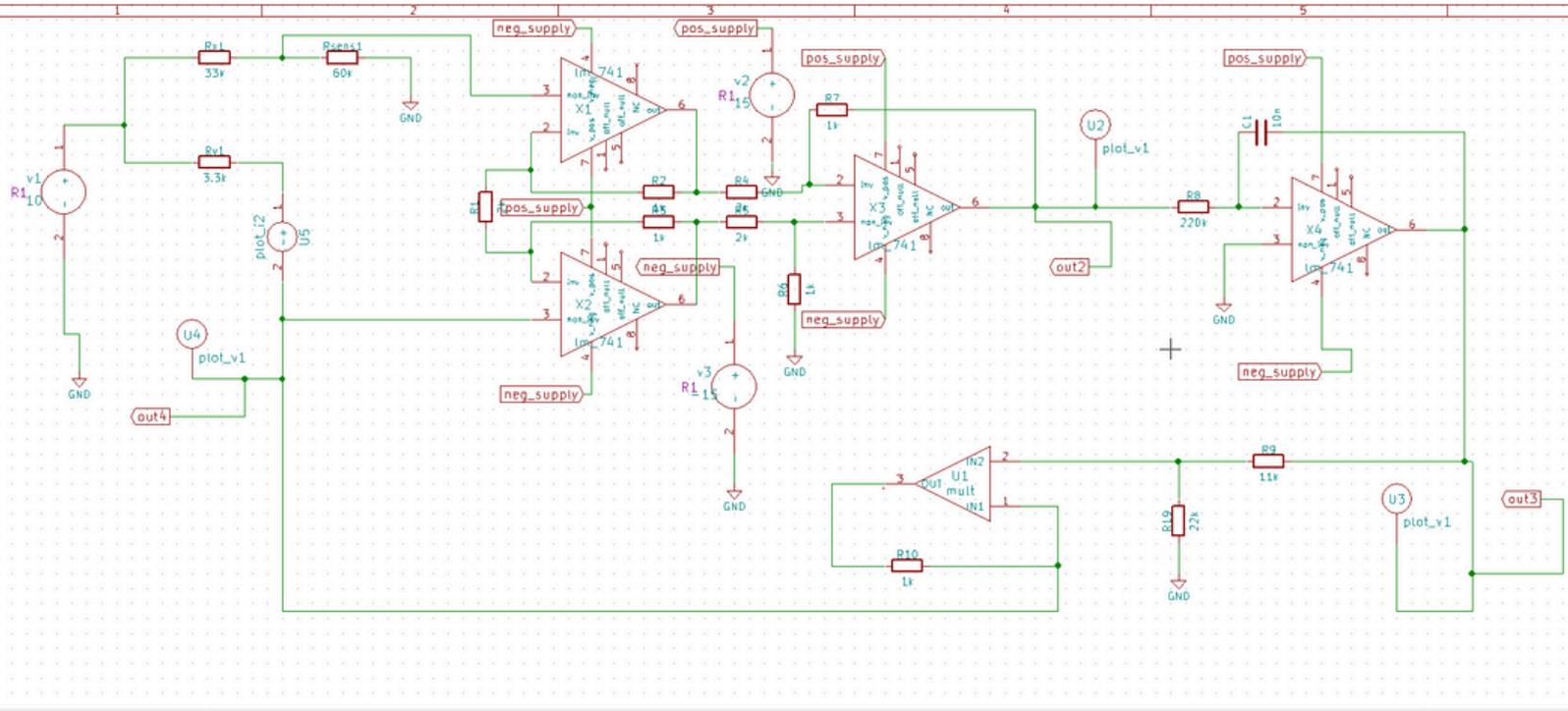- Here i have made INA using 3 lm-741 op amps.
- The working of the schematic will be verified similarly as done in multsim simulation that is by calculating R_{vcr} .
- In the auto nulling mode , the bridge to be balanced the valur of R_{vcr} should be $R_{sens}/10$.



NGspice result-

- Here $R_{sens} = 60k$, therefore R_{vcr} should be $6k\Omega$.
- We Measure R_{vcr} in simulation by value of U4 (Voltage in branch of VCR) and U5(Current in branch of VCR)

```
ngspice 35
x1.net_q15-pad2_ -14.3309
x1.net_q15-pad3_ -14.9645
x1.net_q18-pad3_ 6.48925
net_r2-pad2_ 6.43617
x1.net_q19-pad3_ 6.43617
x2.net_q1-pad1_ 14.4587
out4 6.47515
x2.net_q1-pad3_ 5.95242
net_r1-pad1_ 6.47589
x2.net_q2-pad3_ 5.95281
x2.net_q3-pad2_ -13.9466
x2.net_q13-pad1_ 5.43364
x2.net_c1-pad2_ -13.7933
```

• $V_a / U4 = 6.47515$ volts

```
D:\ayaz\newproject\newproject.cir.out
ngspice 35
x4.net_q18-pad3_ 12.5354
x4.net_q19-pad3_ 12.5259
net_r19-pad2_ 8.35063
net_r10-pad1_ 5.40716
v_u5#branch 0.00106814
v3#branch 0.00821387
v2#branch -0.0107561
v1#branch -0.00117576
a1#branch_1_0 0.00106799
No. of Data Rows : 108
ngspice 1 ->
```

• $I / U5 = 1.06799$ mA

- Hence we get $R_{vcr} = V_a / I = 6.063$ K ohms which is close to $6k\Omega$ and thus the bridge is balanced

```
x3.net_q14-pad2_ -0.116332
x3.net_q14-pad3_ -0.757231
x3.net_q15-pad2_ -14.3151
x3.net_q15-pad3_ -14.9567
x3.net_q18-pad3_ 0.0281473
out2 0.0281473
x3.net_q19-pad3_ -0.0786426
net_c1-pad1_ 0.000677512
out3 12.5259
x4.net_q1-pad1_ 14.4611
x4.net_q1-pad3_ -0.518449
x4.net_q2-pad3_ -0.518089
x4.net_q3-pad2_ -13.9492
```



Differential output voltage
 $V_a - V_b$

(ideally should be zero in auto-nulling but there is a minute error)


V_{ctrl} (Output of integrator, this is the measure of R_{sens} in auto-nulling mode)

```
D:\ayaz\newproject\newproject.cir.out
```


NGspice Plot-

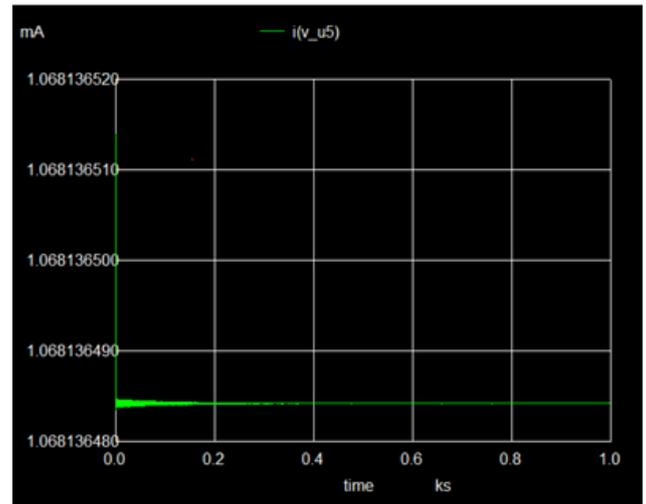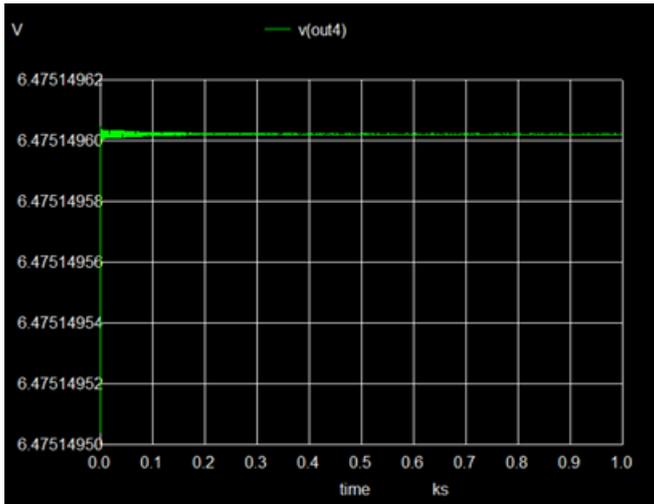
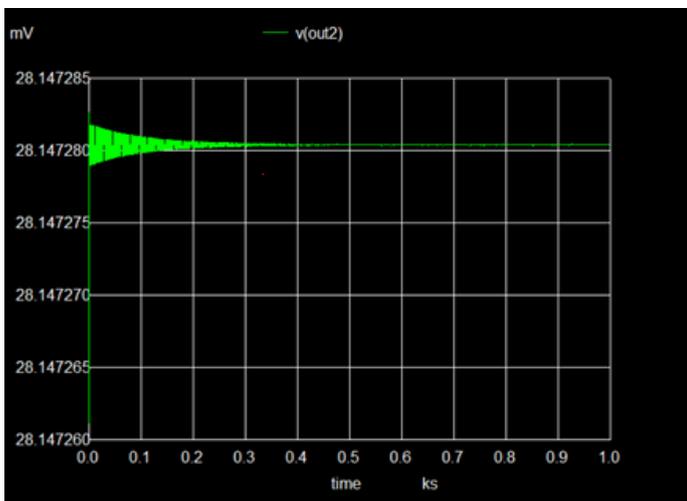
$$R_{vcr} = V_{ou4} / I = 6.063 \text{ kohm}$$



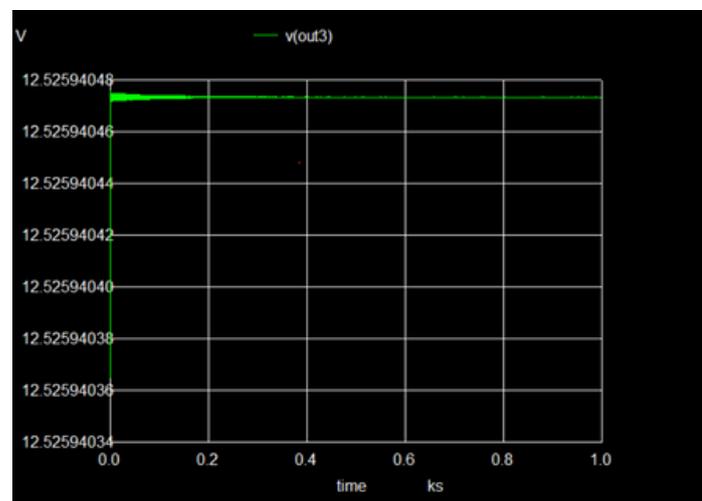**V_a-V_b = Differential
Output of the Balanced
Bridge**



**V_{ctrl} = Output of the
Integerator**

Observation-

- The Circuit Works Properly for a range of 10kohm to 200kohm with max error of _____ in the autonulling mode (Automatic Bridge Balancing).
- The Simulation have been performed in Multisim and EeSchema both , the result is then verified.

Future Work Scope -

- I am working on the same circuit for AC Excitation.

Reference -

- Analog Wheatstone bridge-based automatic interface for grounded and floating wide-range resistive sensors - DOI: [10.1016/j.snb.2012.12.044](https://doi.org/10.1016/j.snb.2012.12.044)