

## Type-II - 3rd Order Phase-Locked Loop (PLL) Design

**Introduction :** A Phase-Locked Loop (PLL) synchronizes the phase and frequency of a generated signal with a reference signal. A Type-II, 3rd order PLL consists of a Phase Frequency Detector (PFD), Charge Pump, Loop Filter, Voltage-Controlled Oscillator (VCO), and a Frequency Divider. The PFD, designed using a NOR latch, compares the phase and frequency of the input and feedback signals, generating UP and DOWN signals. The charge pump then converts these signals into an analog current, which is further smoothed by the loop filter consisting of  $R_1$ ,  $C_1$ , and  $C_2$ . This control voltage drives a current-starved VCO, generating a corresponding output frequency. The output is divided by a factor of 48 using a divider circuit, and the feedback is compared with the reference to achieve phase lock. The Type-II, 3rd order PLL is preferred for its improved noise performance and stability. By using a third-order loop filter, the system effectively suppresses high-frequency noise. Careful design considerations, such as optimizing the loop filter components and ensuring proper biasing of the VCO, contribute to minimizing phase noise. Additionally, selecting an appropriate charge pump current and divider ratio ensures faster lock time and reliable frequency synthesis. This design is widely used in applications like clock generation, frequency synthesis, and communication systems.

### Circuit Diagram :

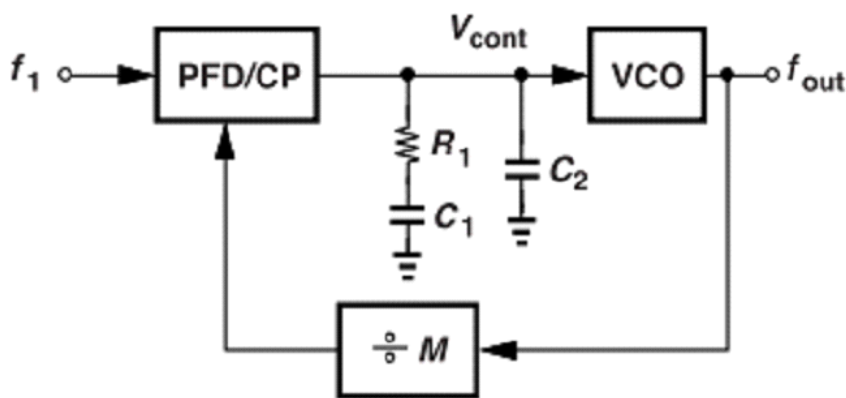


Fig - 1 : A Complete PLL (Phase Locked Loop)

## Schematic :

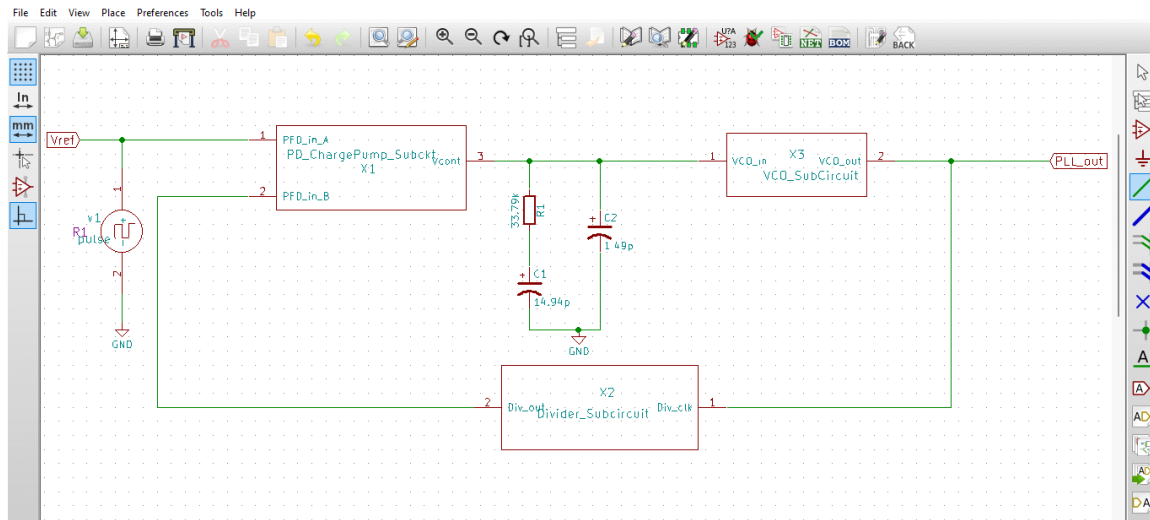


Fig - 2 : Schematic of PLL

## Sub-Blocks :

### 1. Phase / Frequency Detector & Charge Pump

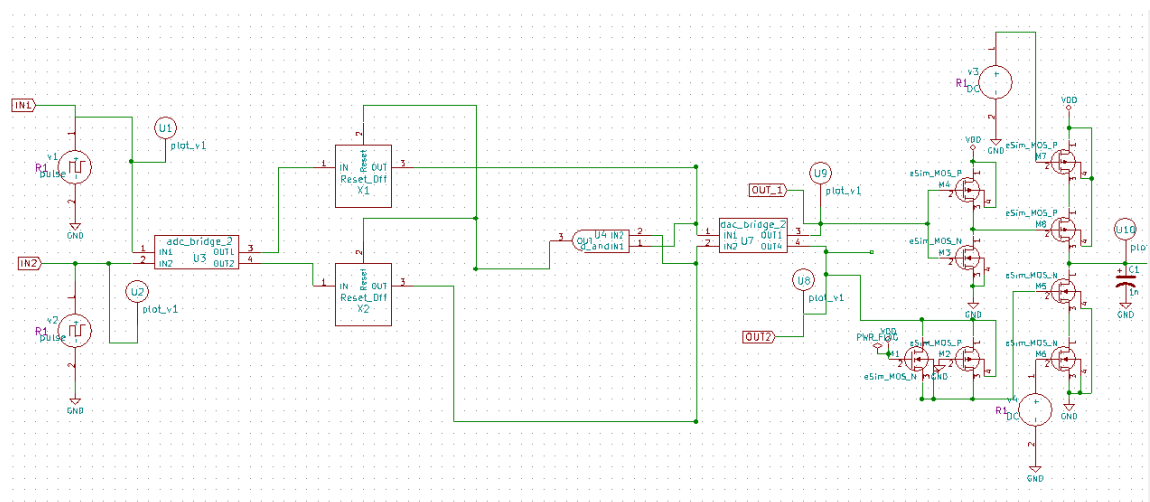


Fig-3 : Schematic of Phase Detector & Charge Pump Circuit

## Output & Waveforms

 


Fig-4 : Frequencies of input1 & input are equal



 


Fig-5 : Frequencies of input1 is less than input2

 

**Fig-6 : Frequencies of input1 is greater than input2**

## 2. Charge Pump

 

**Fig-7 : Output waveform of Charge Pump**

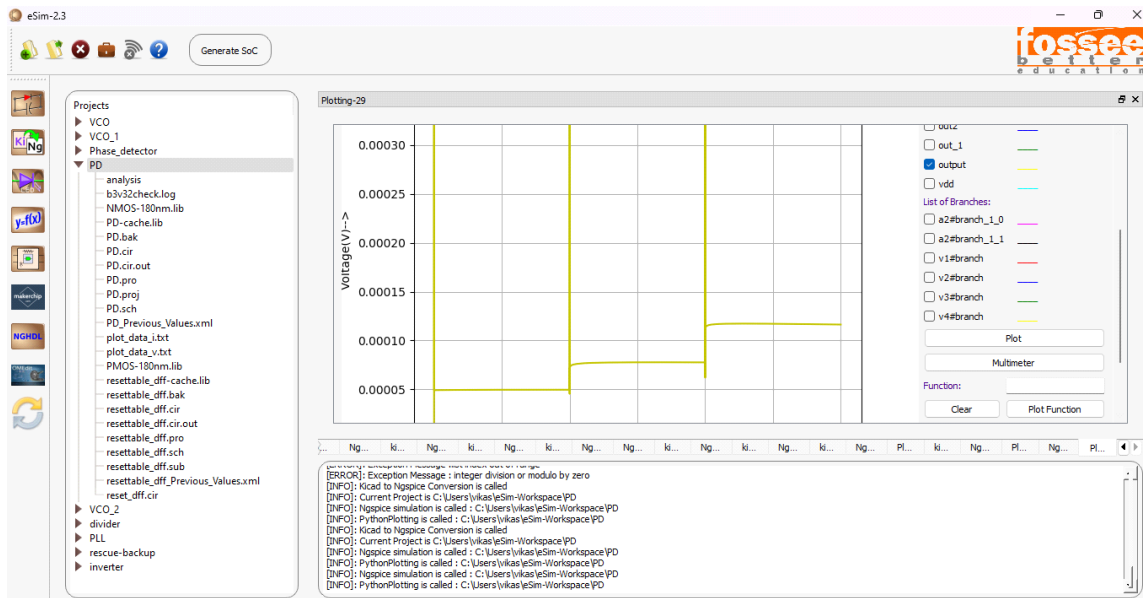
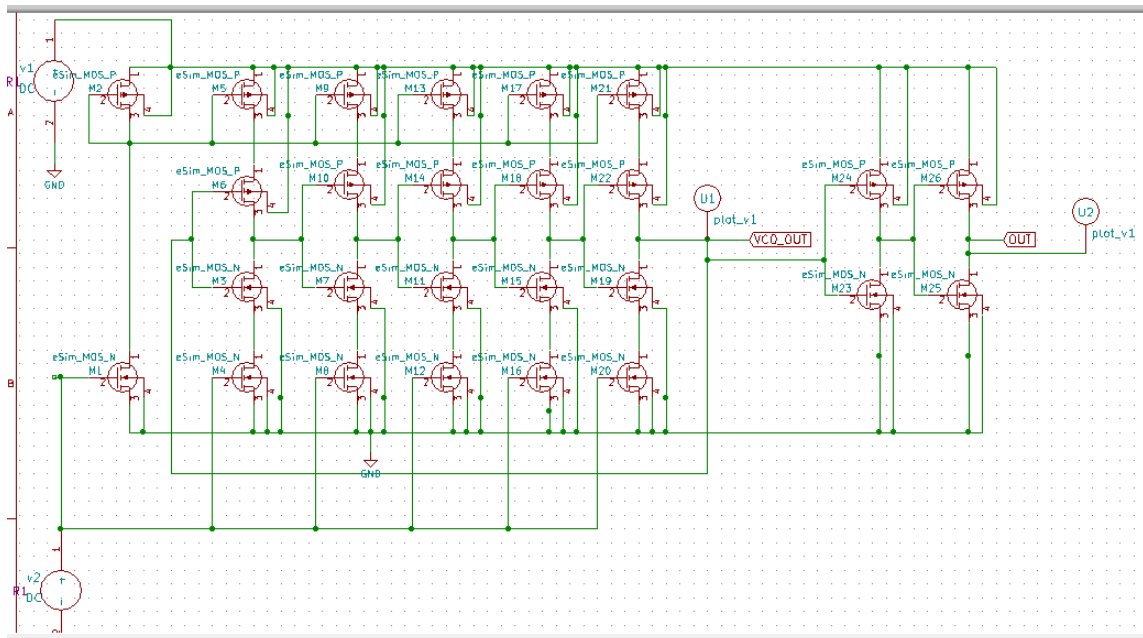



Fig-8 : Python plot of Charge Pump
 
### 3. Voltage Controlled Oscillator

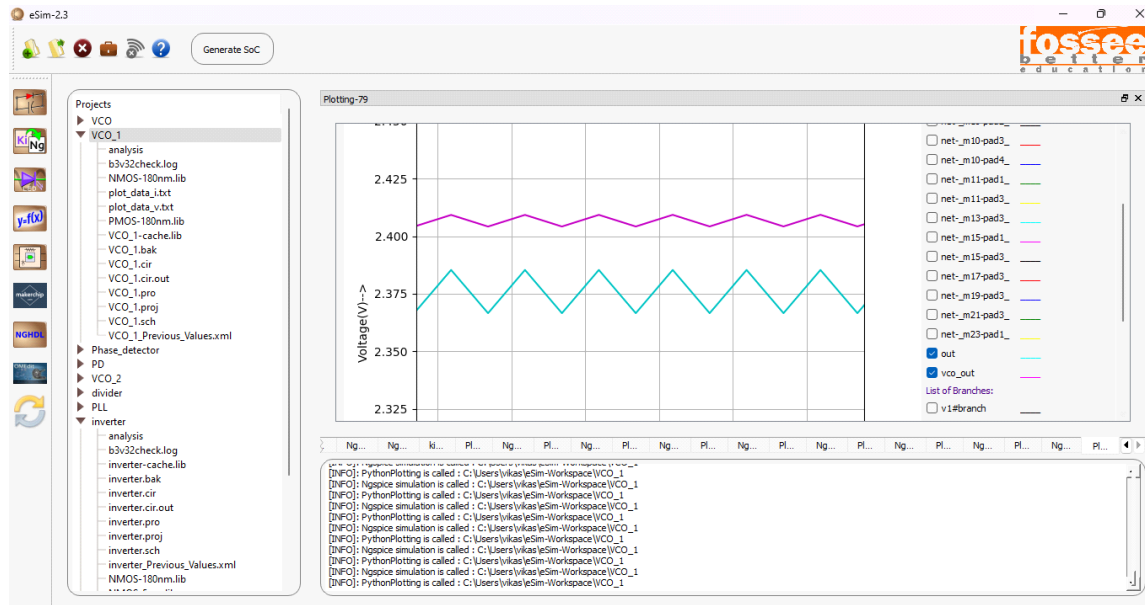


**Fig - 9 : Schematic of Voltage Controlled Oscillator**


## Output & Waveforms



**Fig-10 : Output of Voltage Controlled Oscillator**



### 3. Divider

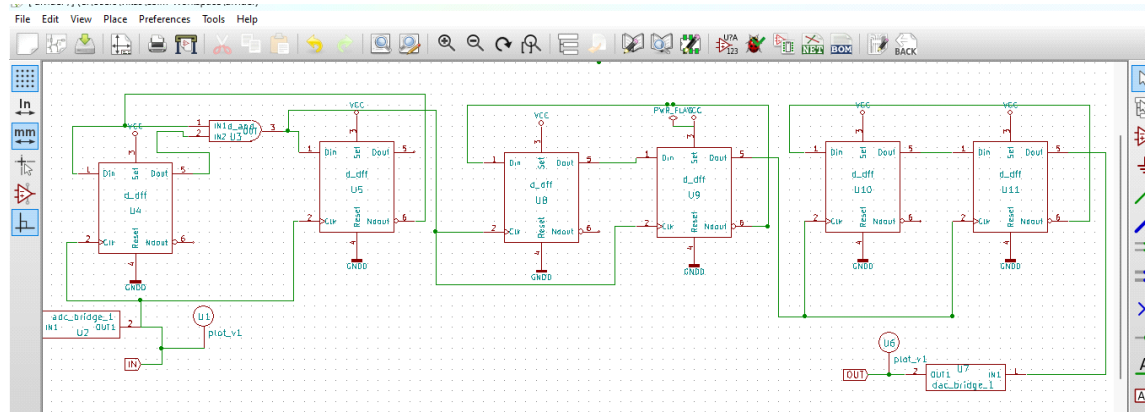

### Design the PLL : Finding R1, C1, C2, N to get $f_0=1.846$ GHz

**Given:** (i) Reference frequency,  $f_{ref} = 38.45 \text{ MHz}$ , (ii)  $f_o = 1.846 \text{ GHz}$  (iii)  $\zeta = 1$

**Use** Charge pump current  $I_p = 100 \text{ uA}$ , VCO Gain,  $K_{VCO} = 949 \text{ MHz/V}$  ( Experimently get from VCO experiment )

$$\zeta = \frac{R_1}{2} \sqrt{\frac{I_p K_{VCO} C_1}{2\pi M}}, \quad \omega_n = \sqrt{\frac{I_p K_{VCO}}{2\pi M C_1}}, \quad \omega_u = 2.1 \omega_n = \frac{\omega_{REF}}{10}.$$

$C_2 = 0.1 C_1$ .

## Result


From calculation, I get

$C_1 = 14.94 \text{ pF}$

$C_2 = 1.494 \text{ pf}$ ,

$R_1 = 33.79 \text{ Kohm}$ ,

$K_{vco} = 949 \text{ MHz /V}$

 

**Fig-X: Output Waveform of PLL**

**Conclusion :** Locking Achieved at = 900mv

## References / Sources :

1. <https://github.com/madane20340-droid/Type-II-3rd-Order-Classical-PLL/blob/main/COMPLETE%20PLL.docx>
2. [https://onlinecourses.nptel.ac.in/noc22\\_ee92/preview](https://onlinecourses.nptel.ac.in/noc22_ee92/preview)



3. <https://ieeexplore.ieee.org/abstract/document/10129815>

4. Design of CMOS Phase-Locked Loops: From Circuit Level to Architecture Level -  
Behzad Razavi

**Project Submitted By :**

Karri Pavan

Rajiv Gandhi University Of Knowledge Technologies,

IIIT Nuzvid,

Eluru, 521202