

Title (proposal) : (Design and Analysis) Waveform Generator using IC741 (OP-AMP)

PRESENTED BY

ANISH R. KHAPARE

BE/ EXTC (3rd year)

1) THEORY : This project presents the design and simulation of a waveform generator circuit using a Schmitt trigger and an integrator, implemented in eSim. The objective of this circuit is to generate two fundamental waveforms a square wave and a triangular wave which are widely used in signal processing, communication systems, and control applications.



The circuit operates by combining two basic building blocks: an operational amplifier (op-amp) configured as a Schmitt trigger and another op-amp configured as an integrator. The Schmitt trigger provides regenerative feedback, ensuring a stable square-wave output. This output is then fed into the integrator, which produces a corresponding triangular waveform by integrating the square wave.

2) WORKING PRINCIPLE :

The given circuit generates square wave and triangular wave outputs using operational amplifiers configured as a Schmitt Trigger and an Integrator.

- **Schmitt Trigger (Op-Amp U1):**
 - The first op-amp is configured as a Schmitt trigger with positive feedback.
 - It converts the continuously varying input signal from the integrator into a bistable square wave.
 - The output of the Schmitt trigger switches between $+V_{sat}$ and $-V_{sat}$, depending on whether the input voltage crosses the upper or lower threshold set by the resistors.
 - This square wave is available at OUT1.
- **Integrator (Op-Amp U2):**
 - The square wave output of the Schmitt trigger is applied to the integrator circuit made using the second op-amp, resistor, and capacitor.
 - The integrator continuously integrates the square wave, producing a triangular waveform at its output.
 - The slope of the triangular wave depends on the amplitude of the square wave and the RC time constant of the integrator.
 - This triangular wave is available at OUT2.

3) DESIGN OF WAVEFORM GENERATOR

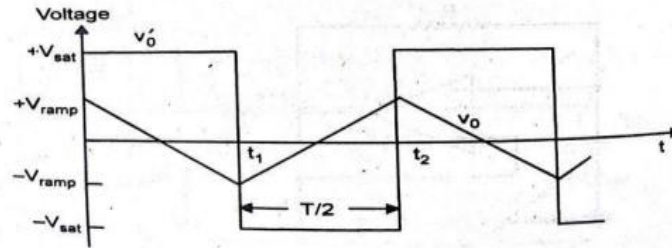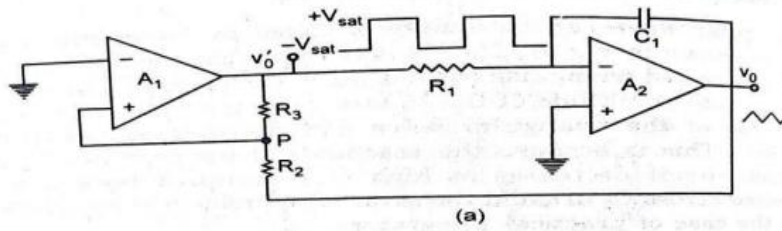

ASSUME: $f_o = 2\text{KHz}$ $V_{OUT2} = 7\text{Vp-p}$ (Triangular Wave) $+V_{sat} = -V_{sat} = 14\text{v}$ (V_{OUT1})

$$1) V_{OUT1} \text{ or } V_o = (2 \cdot R_2 / R_3) \cdot V_{sat}$$

$$\text{Therefore, } 7 = (2 \cdot R_2 / R_3) \cdot 14$$

Assume $R_3 = 10\text{K ohm}$

After calculation we get $R_2 = 2.5\text{K ohm}$

$$2) f_o = R_3 / 4 \cdot R_1 \cdot C_1 \cdot R_2$$

Assume $C_1 = 0.1\mu\text{F}$

$$2\text{ KHz} = 10\text{ K ohm} / 4 \cdot R_1 \cdot 0.1\mu\text{F} \cdot 2.5\text{K ohm}$$

After calculation we get $R_1 = 5\text{K ohm}$

4) PROPOSED CIRCUIT IN eSIM SOFTWARE

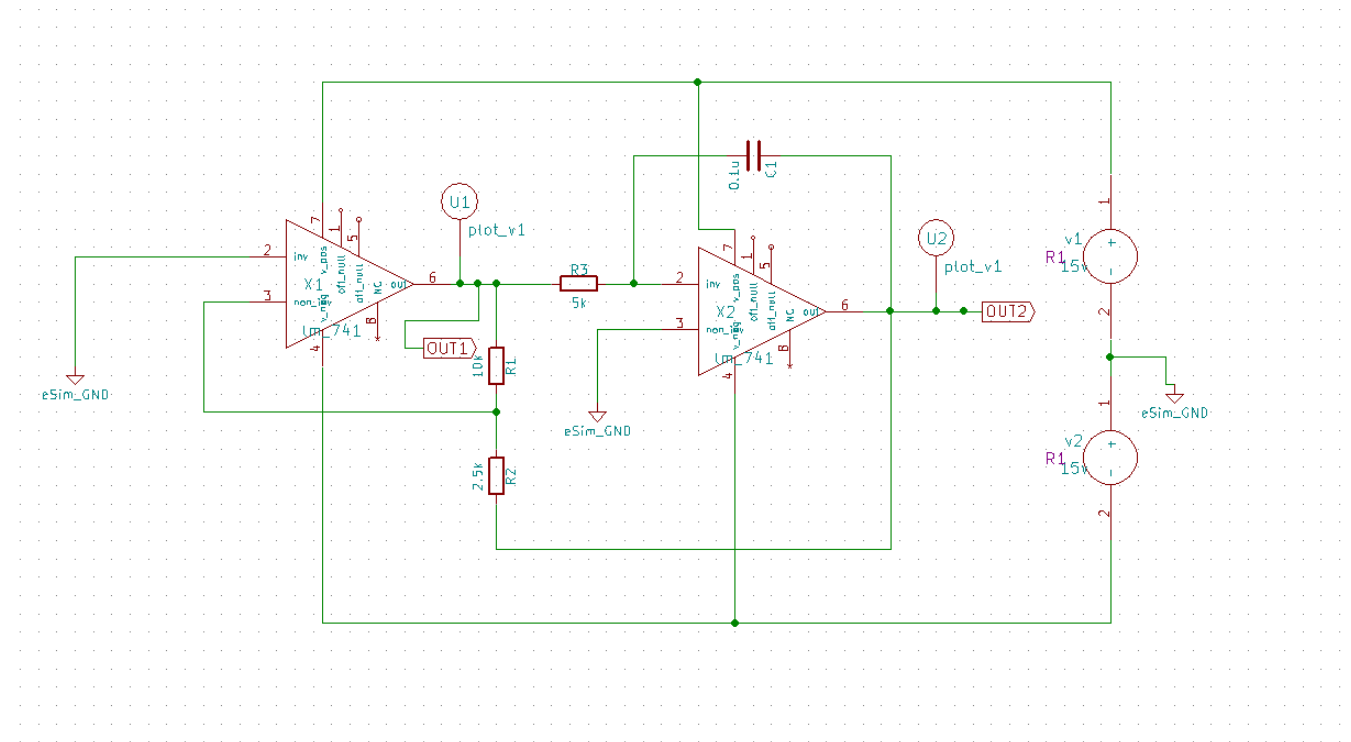


Fig 1 : Waveform generator circuit in eSim software

5) SIMULATION RESULTS

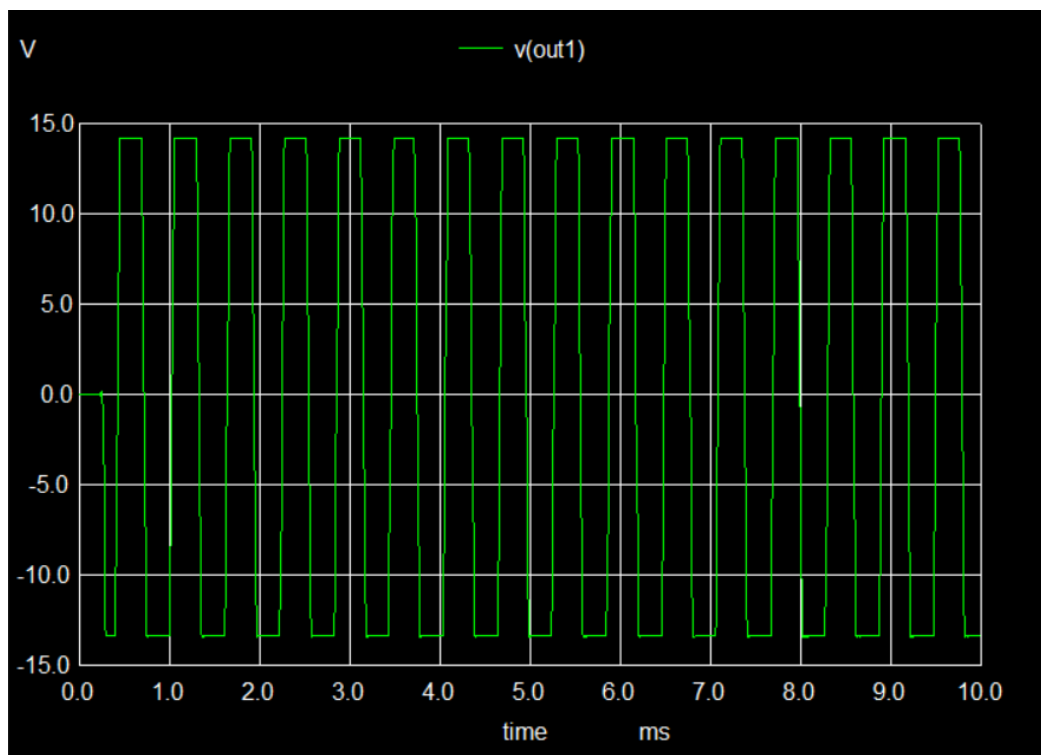


Fig 2 : Square waveform through Vout1 (asper calculations/assumptions)

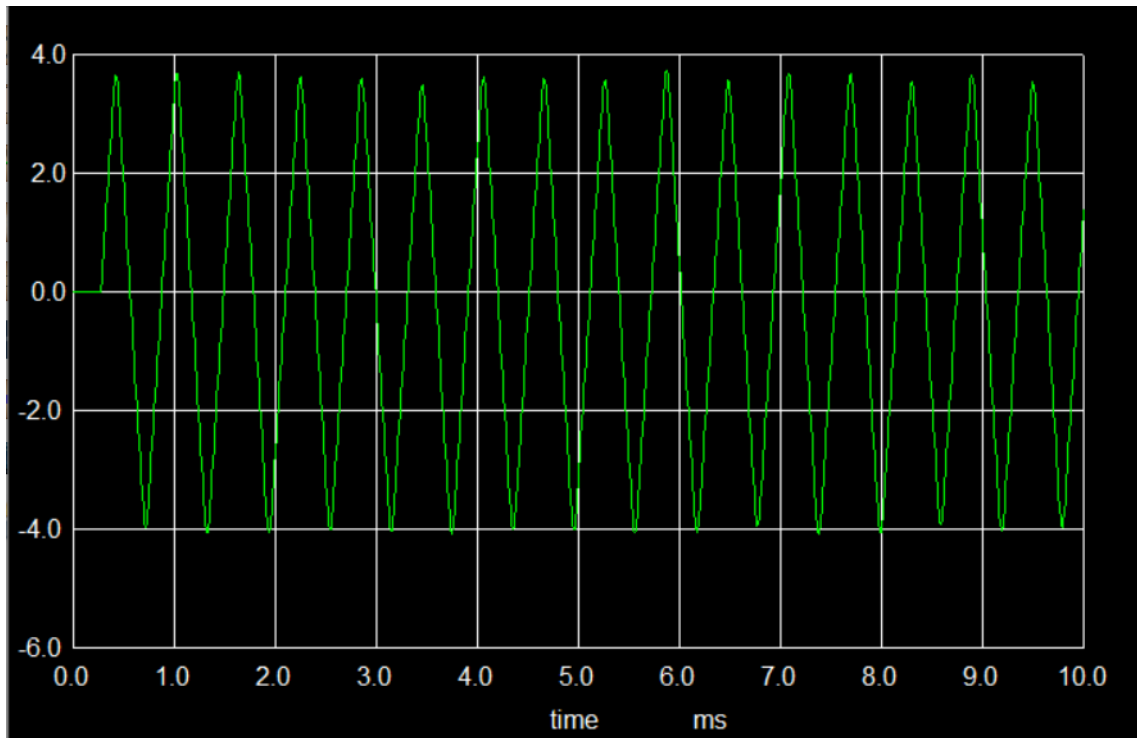


Fig 3 : Triangular Waveform through Vout2

6) CONCLUSION :

The designed waveform generator circuit successfully produces both square and triangular waveforms using two operational amplifiers configured as a Schmitt trigger and an integrator. The Schmitt trigger provides a stable square wave with well-defined switching thresholds, while the integrator converts this square wave into a triangular waveform. The simulation results confirm that the frequency and amplitude of the generated waveforms can be controlled by selecting appropriate resistor and capacitor values.

7) REFERENCE :

Textbook :Ramakant A. Gayakwad, “Op-Amps and Linear Integrated Circuits”, Pearson Prentice Hall, 4th Edition.