

# Circuit Simulation Project


<https://esim.fossee.in/circuit-simulation-project>

**Name of the participant :** Jovin P John

**Title of the circuit :** 4 Bit Carry Bypass Adder

**Theory/Description :** A 4-bit Carry Bypass Adder is a circuit that adds two 4-bit binary numbers using full adders to produce the sum outputs and the final carry. Unlike a simple ripple-carry adder, it also checks whether the carry can skip all four stages through a shortcut path. This decision is controlled by the block propagate signal  $p$ , defined as  $p = p_0 \cdot p_1 \cdot p_2 \cdot p_3$ , where each  $p_i = a_i \text{ XOR } b_i$ . If  $p = 1$ , a multiplexer forwards the input carry directly to the output carry for faster operation, while if  $p = 0$ , the carry ripples through the adders in the normal way.

**Circuit Diagram(s) :**

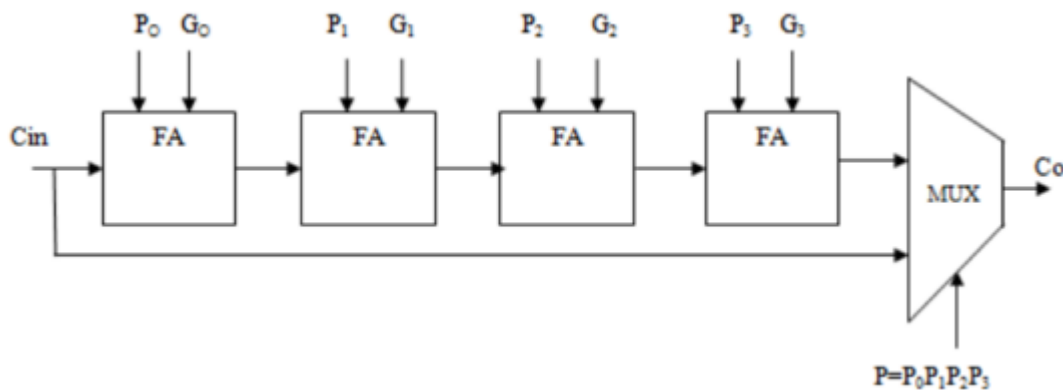

**Results (Input, Output waveforms and/or Multimeter readings) :**

a3a2a1a0 | b3b2b1b0 | c0 | s3s2s1s0 | c4 | p

0000 | 0000 | 0 | 0000 | 0 | 0

0000	0000	1   0001	0   0
0001	0001	0   0010	0   0
0001	0001	1   0011	0   0
0010	0010	0   0100	0   0
0010	0010	1   0101	0   0
0011	0011	0   0110	0   0
0011	0011	1   0111	0   0
0100	0100	0   1000	0   0
0100	0100	1   1001	0   0
0101	0101	0   1010	0   0
0101	0101	1   1011	0   0
0110	0110	0   1100	0   0
0110	0110	1   1101	0   0
0111	0111	0   1110	0   0
0111	0111	1   1111	0   0
1000	1000	0   0000	1   0
1000	1000	1   0001	1   0
1001	1001	0   0010	1   0
1001	1001	1   0011	1   0
1010	1010	0   0100	1   0
1010	1010	1   0101	1   0
1011	1011	0   0110	1   0
1011	1011	1   0111	1   0
1100	1100	0   1000	1   0
1100	1100	1   1001	1   0
1101	1101	0   1010	1   0
1101	1101	1   1011	1   0
1110	1110	0   1100	1   0
1110	1110	1   1101	1   0

1111 | 1111 | 0 | 1110 | 1 | 0

1111 | 1111 | 1 | 1111 | 1 | 0

**Source/Reference(s)** : Sunitha, G. S., & Rakesh, H. M. (2017). Design and implementation of adder architectures and analysis of performance metrics. *International Journal of Electronics and Communication Engineering and Technology (IJCET)*