

Project – Three Op-Amp Instrumentation Amplifier (IA) Design & Simulation


Report:

- **Theory:**

- An **Instrumentation Amplifier (IA)** is an electronic circuit designed to **amplify very small signals accurately**. It is called an “instrumentation” amplifier because it behaves like an **instrument that amplifies** tiny input signals and converts **low-level signals into high-level outputs**.
- In this project, we use a **three op-amp instrumentation amplifier**, which means the circuit is built using **three operational amplifiers**. We simulate this circuit in eSim. The core working principle is based on a **differential amplifier**, which amplifies the **difference between two input signals** while rejecting anything common to both.

- Three Op-Amp Instrumentation Amplifier (IA) amplifier is preferred because it offers important characteristics:
- **High Common-Mode Rejection Ratio (CMRR)** – it rejects noise and interference.
- **High input impedance** – it does not load or disturb the sensor.
- **Low output impedance** – it can easily drive the next stage of a circuit.
- Because of these properties, instrumentation amplifiers are widely used in **temperature measurement, humidity sensing, biomedical instruments, and precision sensor applications**, where small and sensitive signals must be measured cleanly.

- **Gain:**

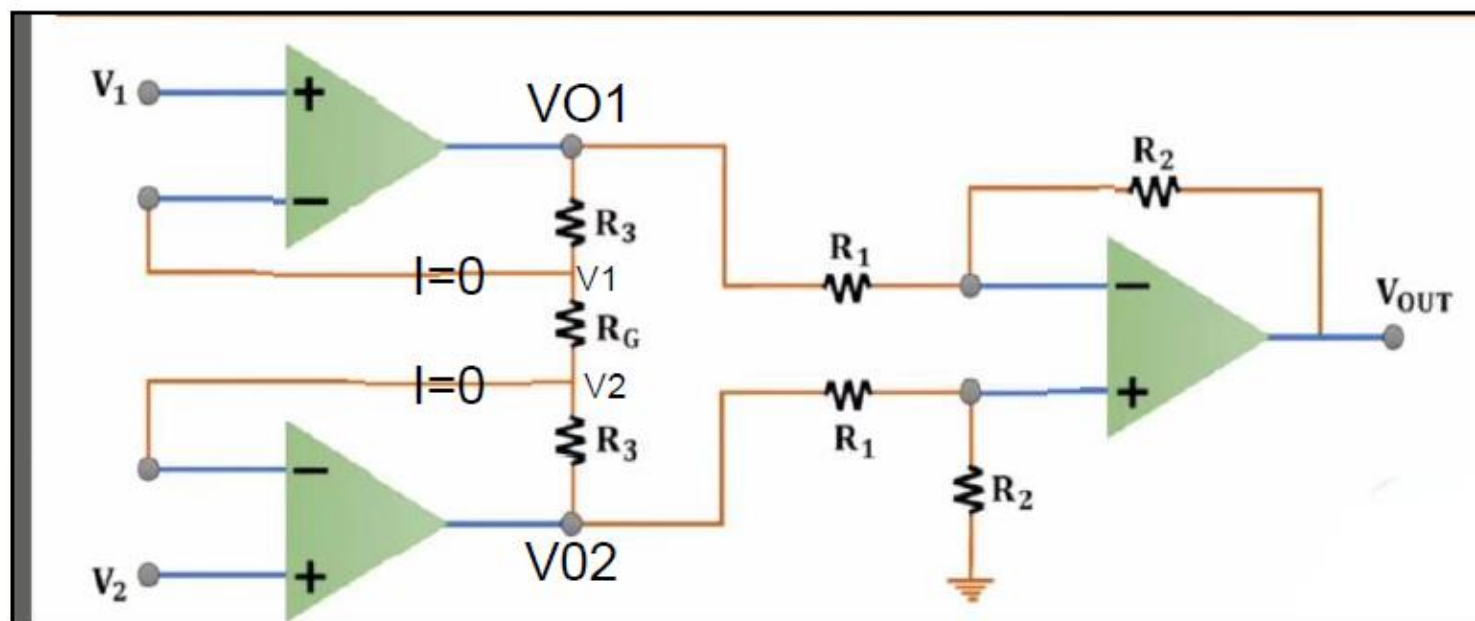


As shown in image,

- Current passing through $I_G = (V_2 - V_1) / R_G \longrightarrow \boxed{1}$
- Current in inverting terminal for both op-amps $I=0$
- So current passing between V_{01} to V_{02} is also $I_G = (V_{02} - V_{01}) / (2R_3 + R_G) \longrightarrow \boxed{2}$
- So from the Equation 1 & 2,

$$V_{02} - V_{01} = (2R_3 + R_G) \cdot (V_2 - V_1) / R_G$$
- Final Output $V_o = (R_2 / R_1) \cdot (V_{02} - V_{01})$
- Final Output $V_o = (R_2 / R_1) \cdot (2R_3 + R_G) \cdot [(V_2 - V_1) / R_G]$
- Gain $V_o / (V_2 - V_1) = (R_2 / R_1) \cdot (2R_3 + R_G) / R_G$

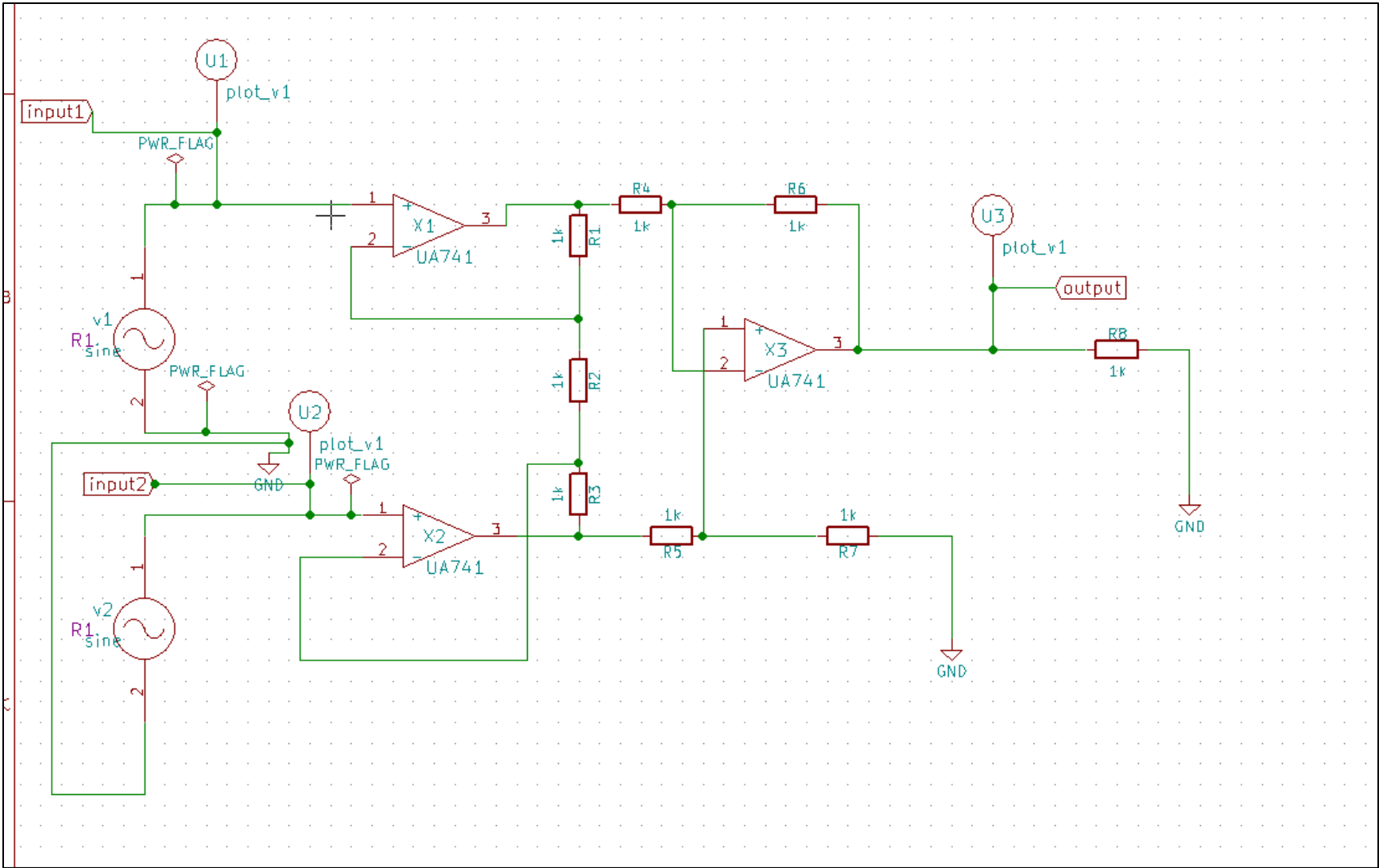• Schematic Diagram & It’s explanation & Result:



- Upper input source $\rightarrow V_1$
 - Lower input source $\rightarrow V_2$
 - Upper op-amp output $\rightarrow V_{O1}$
 - Lower op-amp output $\rightarrow V_{O2}$
 - Last (right side) op-amp output $\rightarrow V_{out}$
-
- Transient Parameters:
 - All the resistors used in the circuit have a value = $1k\Omega$.
 - The input (voltage signal) V_1 is set at 10mV at 100Hz.
 - The input (voltage signal) V_2 is set at 20mV at 100Hz.
 - The output signal is observed across the load R_8 ($1k\Omega$).
 - The output (voltage signal) V_0 is given by the,



$$V_o = \left(\frac{R_2}{R_1}\right) \cdot (2R_3 + R_G) \cdot ((V_2 - V_1) / R_G)$$

So $\left(\frac{R_2}{R_1}\right) \cdot (2R_3 + R_G) / R_G = 3$


$$V_{out} = 3(V_2 - V_1)$$

$$V_{out} = 3 \times (20 \text{ mV} - 10 \text{ mV}) = 30 \text{ mV}.$$


• Source details & Analysis:

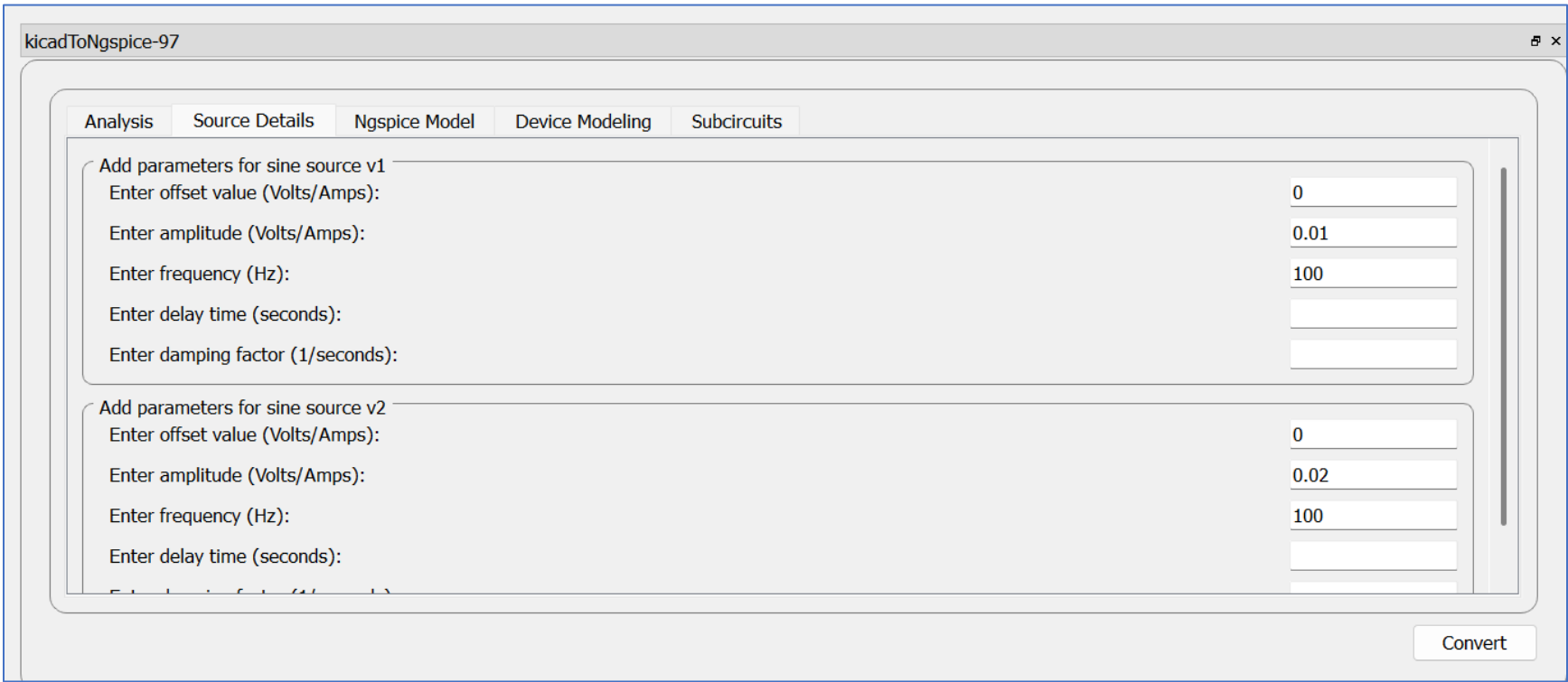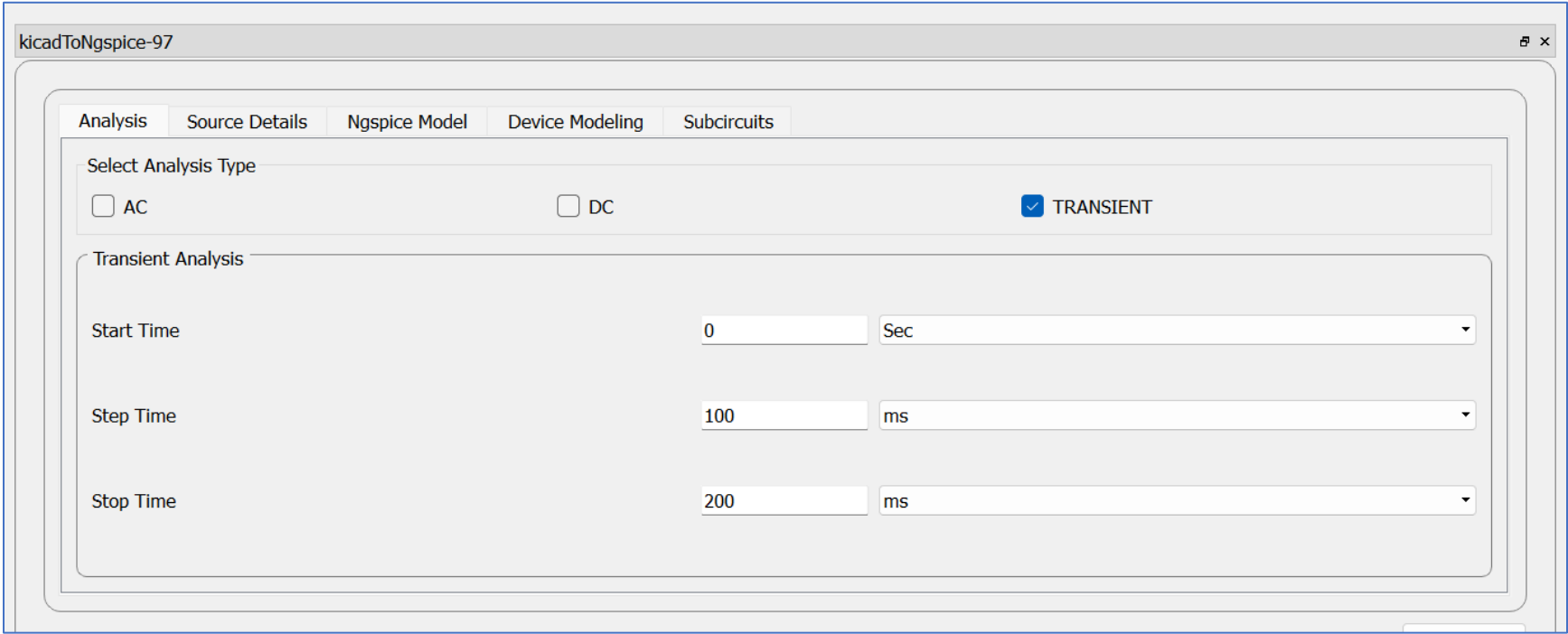


• Block Diagram:

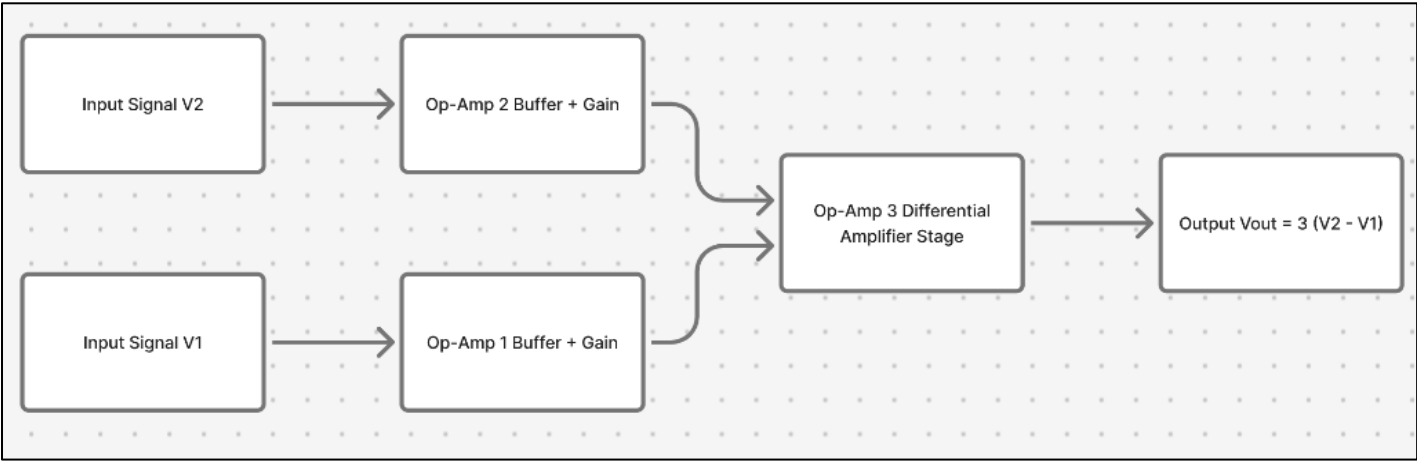


• **Result:**

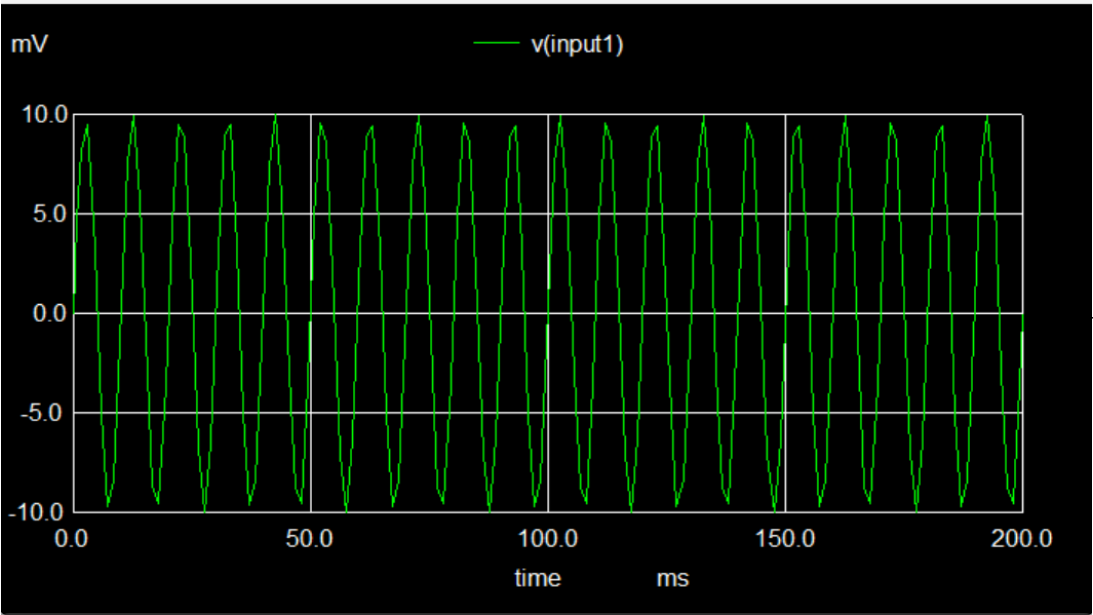

[Fig-3 input-1 10mv at 100Hz]

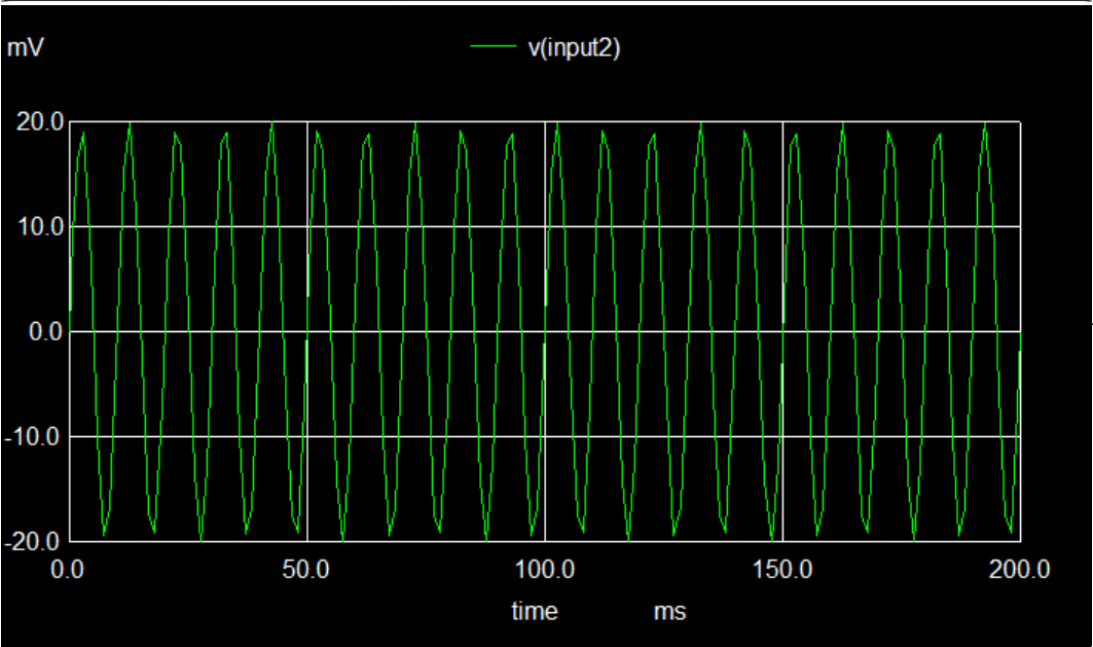


[Fig-4 input-2 20mv at 100Hz]

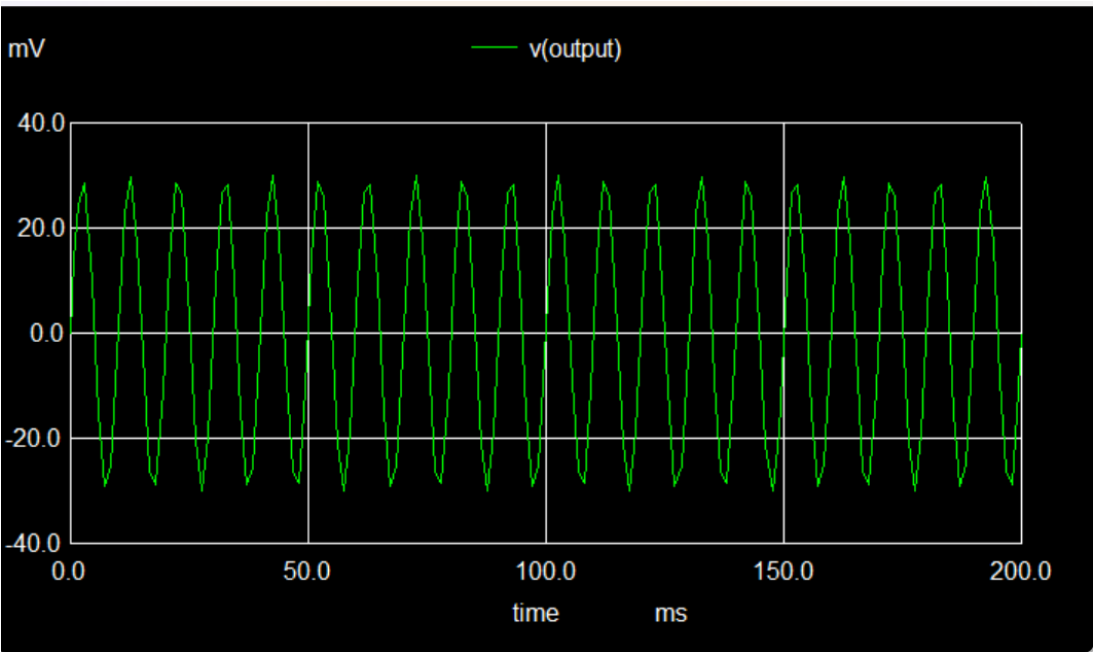


[Fig-5 output 30mv at 100Hz]


• Python plot:

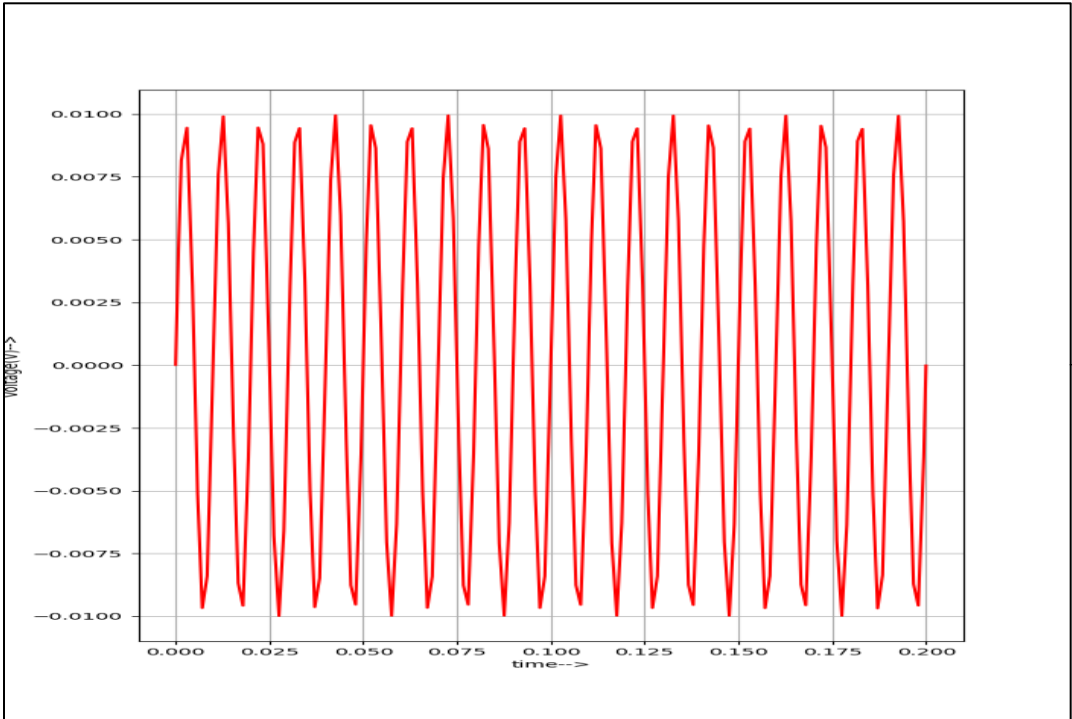


[Fig-6 input-1 10mv at 100Hz]

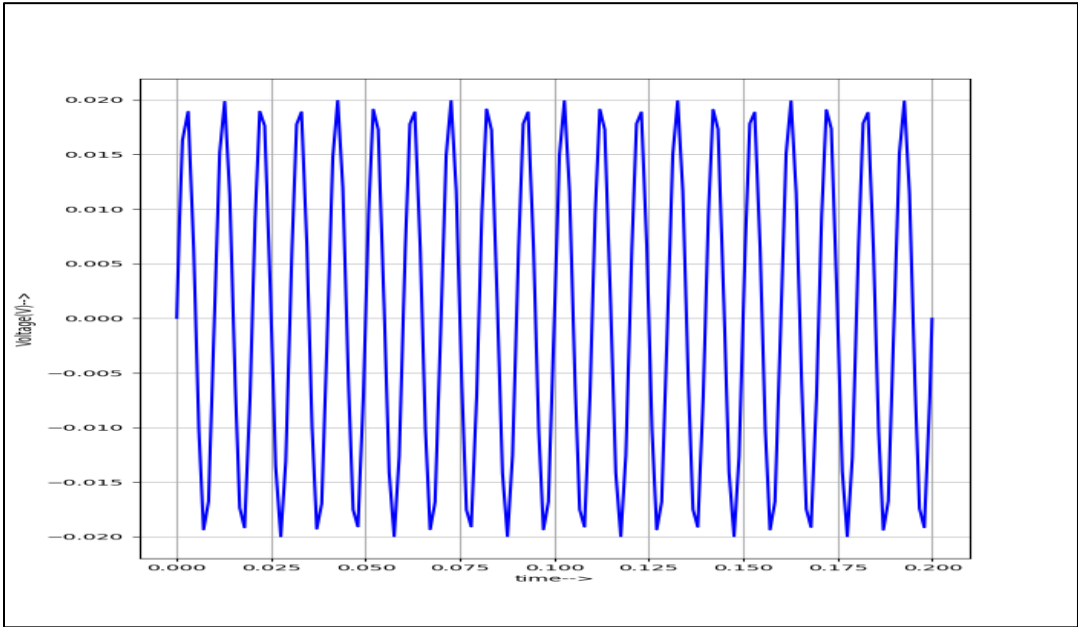

[Fig-7 input-2 20mv at 100Hz]

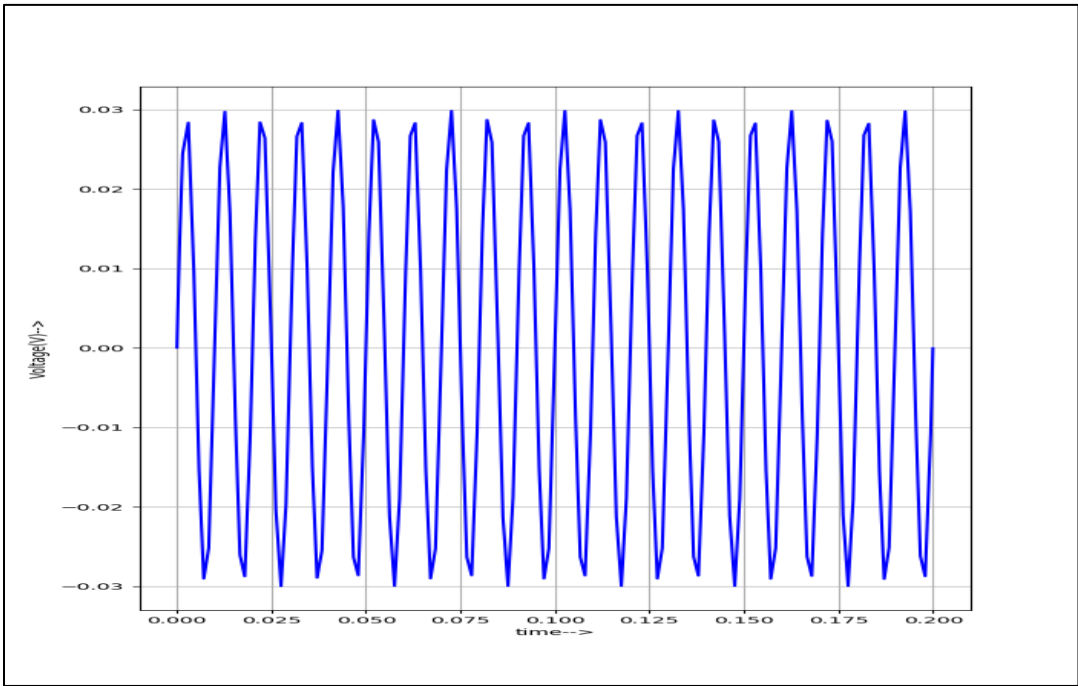

[Fig-8 output 30mv at 100Hz]

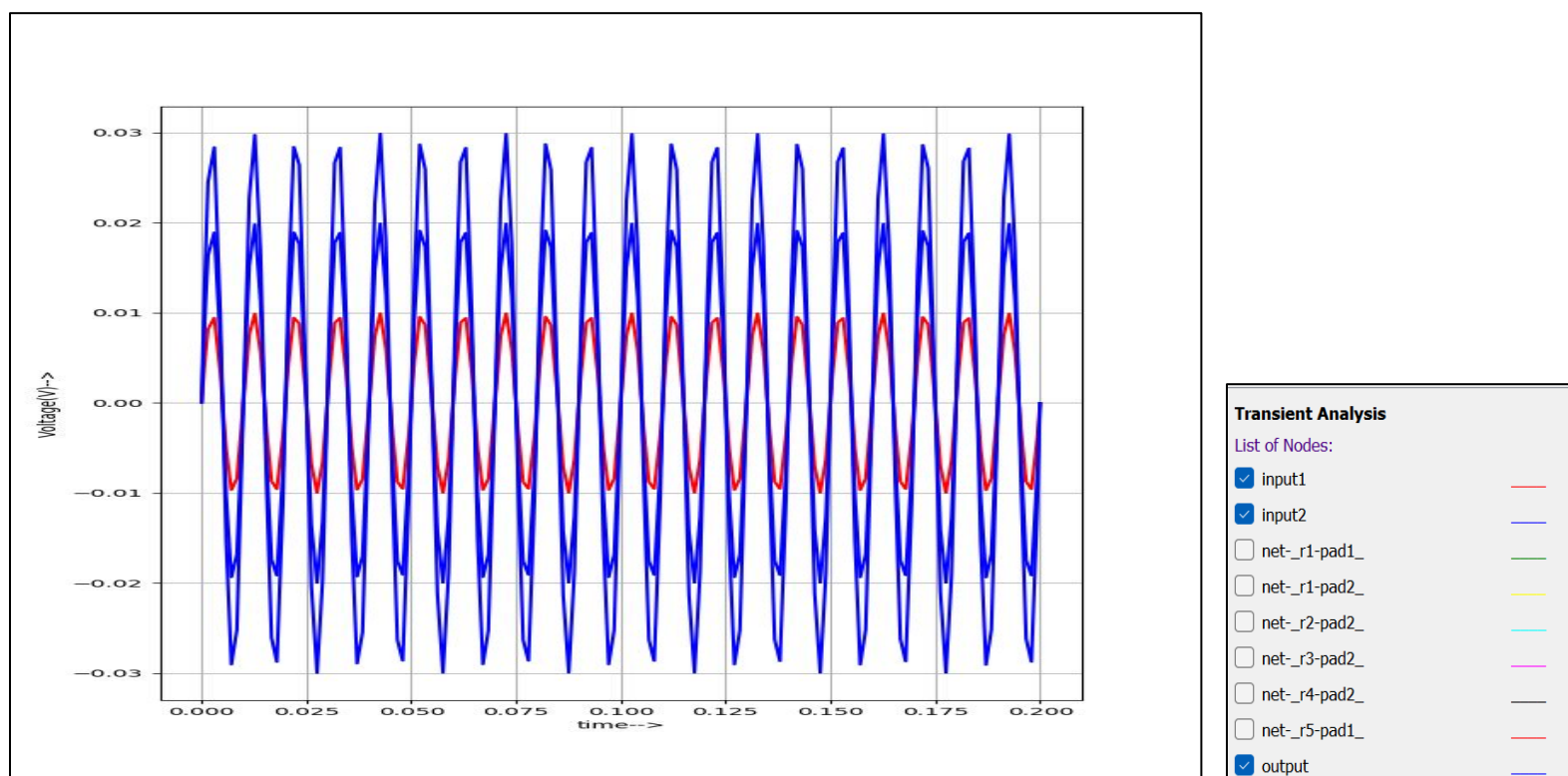

- The **input difference** is **10 mV**(because **20 mV – 10 mV**), and the overall gain of the three-op-amp system is **3**. So when this gain is applied to the 10 mV difference, the **final output** becomes **30 mV**, matching the practical value.

- **Conclusion:**

- The three-op-amp instrumentation amplifier was successfully designed and simulated. The circuit accurately amplified the differential input while rejecting common-mode noise, and the final output matched the theoretical gain expression.

[Reference]

- R. D. White, “Phase Compensation of the Three Op-Amp Instrumentation Amplifier,” IEEE Transactions on Instrumentation and Measurement, 1987.
- **Direct PDF Link (Accessible):**
- https://www.researchgate.net/profile/David-White-74/publication/258422382_Phase_Compensation_of_the_Three-Op-Amp-Instrumentation-Amplifier/links/5524eecd0cf22e181e73b30c/Phase-Compensation-of-the-Three-Op-Amp-Instrumentation-Amplifier.pdf
- [Note: This paper is originally published in IEEE Transactions (IEEE Journal), but the free-access version is available via ResearchGate.
- Link for esim- <https://esim.fossee.in/>