

Two Stage Operational Transconductance Amplifier

Yash Kiran Ekhande, *Student, Electronics And Computer Engineering , K.J.Somaiya College of Engineering, Vidyavihar, Mumbai*

Abstract—Operational Transconductance Amplifiers (OTAs) play a critical role in analog and mixed-signal circuits, where high gain, stability, and load-driving capability are essential. However, single-stage OTAs often fail to meet the demands of modern communication and signal processing systems due to limited gain and poor stability. This report addresses these challenges by designing a two-stage OTA, integrating a differential amplifier for initial voltage amplification and a common-source amplifier for enhanced gain and load-driving performance.

I. INTRODUCTION

Operational Transconductance Amplifiers (OTAs) are fundamental building blocks in analog and mixed-signal design, widely used in filters, oscillators, and signal processing circuits. A two-stage OTA configuration is often employed to overcome the limitations of single-stage OTAs, such as inadequate voltage gain and insufficient load-driving capability. By combining a differential amplifier as the first stage and a common-source amplifier as the second stage, the two-stage OTA provides higher gain and stability, making it suitable for high-performance applications. This report outlines the design and simulation of a two-stage OTA, emphasizing its key performance metrics, including voltage gain, phase margin, and bandwidth, and showcasing its suitability for advanced analog circuit applications.

December 10, 2024


II. CIRCUIT IMPLEMENTATION

The two-stage operational Transconductance amplifier[Fig.A].

A) The first stage consists of a differential amplifier with an active load, which amplifies the input differential signal while maintaining a high input impedance. This stage ensures accurate signal amplification with minimal distortion.

B) The second stage is a common-source amplifier, which further boosts the gain and provides sufficient output drive for the load. To ensure stability, a compensation capacitor is incorporated between the two stages, effectively enhancing the phase margin and preventing unwanted oscillations.

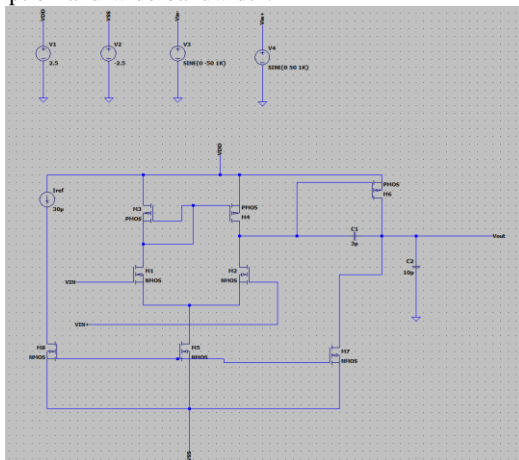C) The circuit design also considers the appropriate biasing of transistors to achieve optimal operating points, ensuring low power consumption and wide bandwidth.



Fig,A - Stage Two OTA

SIMULATIONS AND RESULTS

The simulation (Fig.B) results demonstrate a phase difference in the output voltage, with the output leading the input voltage due to the characteristics of the differential amplifier stage. The observed voltage gain is approximately 5216, which translates to 74.34 dB. The bandwidth of the amplifier, determined by the frequency at which the gain drops by 3 dB (to 71.34 dB), meeting the design requirement where the gain of a two-stage OTA is typically expected to be 5000 or higher. The bandwidth of the amplifier determined and identified through the frequency response analysis. These results confirm that the designed two-stage OTA achieves high gain and maintains stability across a wide bandwidth, validating its suitability for high-performance analog circuit applications.

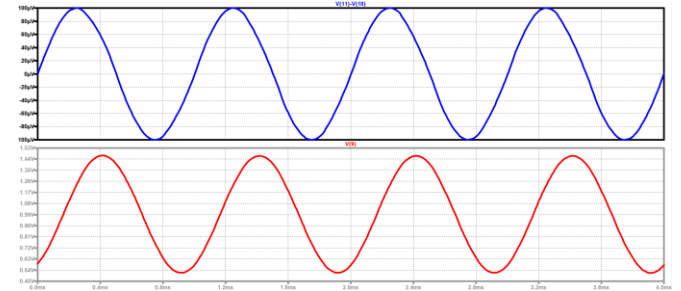


Fig.B- Simulation results

III. APPLICATION

Two-stage operational transconductance amplifiers (OTAs) are widely used in practical applications such as active filters, analog-to-digital converters (ADCs), signal conditioning circuits, and voltage-controlled oscillators. Their high gain and stability make them essential in communication systems, biomedical devices, and sensor interfaces.

CONCLUSION

The two-stage operational transconductance amplifier achieves a high gain of approximately 5216 and stable operation, demonstrating its effectiveness for applications such as filtering, ADCs, and signal processing. While addressing power consumption and stability challenges, the design validates its suitability for high-performance analog system

REFERENCES

- Sedra, A. S., & Smith, K. C. *Microelectronic Circuits*. Oxford University Press.
- Razavi, B. *Design of Analog CMOS Integrated Circuits*. McGraw-Hill Education.
- I. S. Dhanjal, "Two-Stage Operational Transconductance Amplifier," Lecture Notes, [KJSCE,SVU], [Mumbai, Maharashtra],